

CH. 1 – PROBLEM SOLUTIONS (UPDATED NOVEMBER 12, 2013)

© 2015 McGraw-Hill Education. All rights reserved.

1.1

$[V, k\Omega, mA]$. By the superposition principle,

$$V_{oc} = \frac{R_2}{R_1 + R_2} V_S - R_3 I_S = \frac{3}{2+3} V_S - 1 I_S = 0.6 V_S - I_S.$$

By inspection, $R_{eq} = (R_1 \parallel R_2) + R_3 = (2 \parallel 3) + 1 = 2.2 k\Omega$.

(a) $V_{oc} = 0.6 \times 25 - 4 = 11 V > 0 \Rightarrow$ Diode is on with $v = 0$
and $i = 11 / 2.2 = 5 mA$

(b) $V_{oc} = 0.6 \times 10 - 10 = -4 V \Rightarrow$ Diode is off; $i = 0, v = -4 V$.


(c) $V_{oc} = 0 \Rightarrow$ Diode is off; $i = 0, v = 0$

(d) No difference in (a) and (c), as $v = 0$ in both cases.

In (b) the diode voltage changes from $v = -4 V$ to

$$v = \frac{1.8}{2.2 + 1.8} (-4) = -1.8 V < 0 \Rightarrow i = 0 \text{ still.}$$


1.2

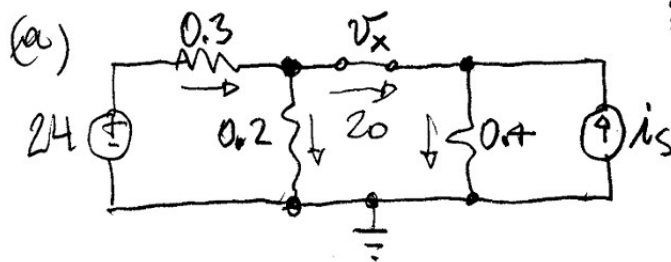[V, mA, k Ω].

$$\frac{24 - V_x}{0.3} = \frac{V_x}{0.2} + 20 \Rightarrow V_x = 7.2 \text{ V};$$

$$20 + i_S = \frac{7.2}{0.4} \Rightarrow i_S = -2 \text{ mA},$$


or $i_S = 2 \text{ mA}$ (↓).

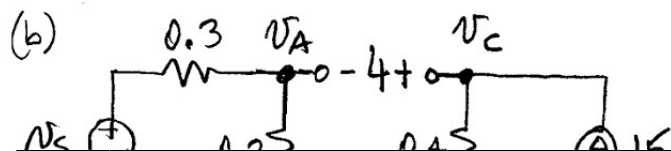

$$V_C = 0.4 \times 15 = 6 \text{ V};$$


$$V_A = V_C - 4 = 6 - 4 = 2 \text{ V};$$

1.3

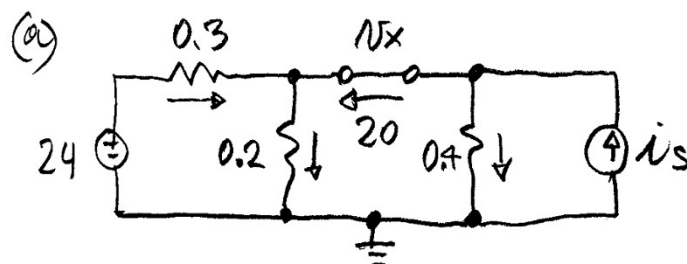[V, mA, k Ω].

$$\frac{24 - V_x}{0.3} + 20 = \frac{V_x}{0.2} \Rightarrow V_x = 12 \text{ V};$$
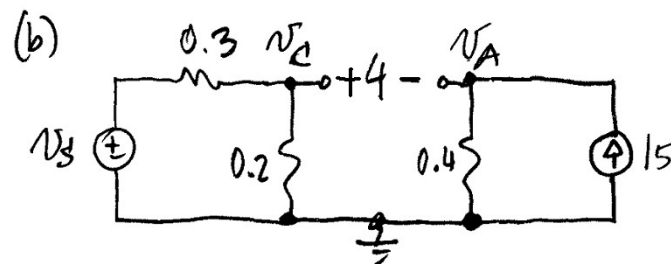
$$i_S = 20 + \frac{12}{0.4} = 50 \text{ mA}.$$




$$V_A = 0.4 \times 15 = 6 \text{ V};$$

$$V_C = V_A + 4 = 10 \text{ V};$$

$$10 = \frac{0.2}{0.3 + 0.2} V_S \Rightarrow V_S = 25 \text{ V}.$$

(c) $V_A = 10 \times 0.4 = 4 \text{ V} = V_C = \frac{0.2}{0.3 + 0.2} V_S \Rightarrow V_S = 10 \text{ V}.$

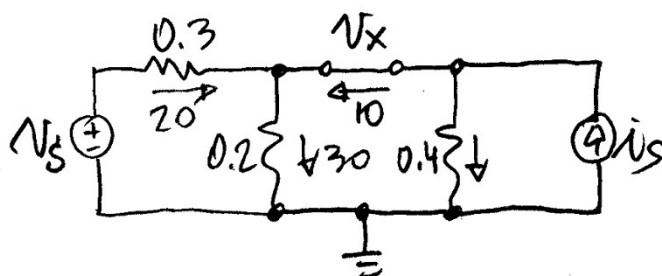(d) Solution is not unique, depending on the choice of the directions for i_{300} and i_{200} . One possibility:



$$V_x = 0.2 \times 30 = 6 \text{ V};$$

$$\frac{V_S - V_x}{0.3} = 20 \Rightarrow V_S = 12 \text{ V}$$

$$i_S = 10 + \frac{V_x}{0.4} = 10 + \frac{6}{0.4} = 25 \text{ V}.$$



If i_{300} is assumed to flow to the left, then we need $V_S = 0$ and $i_S = 65 \text{ mA}.$

1.4

$[V, mA, k\Omega]$. (a) The open-circuit voltage seen by the diode is

$$V_{OC} = \frac{R_2}{R_1 + R_2} V_S - R_3 i_S = \frac{0.3}{0.2 + 0.3} V_S - 0.1 \times 30 = 0.6 V_S - 3V.$$



$$V_S < 5V \Rightarrow \text{diode} = \text{off} \Rightarrow i = \frac{V_S}{0.2 + 0.3} = \frac{V_S}{0.5k\Omega} = 2V_S; V = 3V.$$

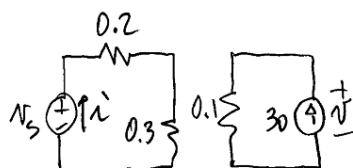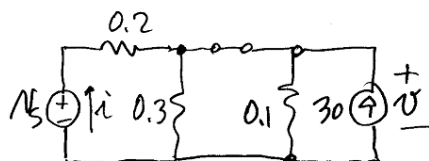
 $V_S < 5V$

 $V_S > 5V$

$$V_S > 5V \Rightarrow \text{diode} = \text{on} \Rightarrow i = \frac{V_S}{0.2 + (0.3 // 0.1)} - \frac{V}{0.2};$$

$$V = \frac{0.3 // 0.1}{0.2 + (0.3 // 0.1)} V_S + (0.2 // 0.3 // 0.1) 30 = \frac{3V_S + 18}{11} V.$$
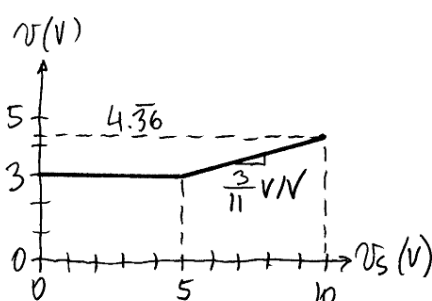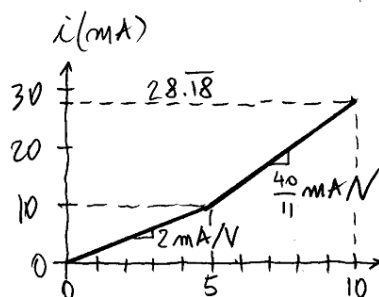
$$\text{Substituting, } i = \frac{40V_S - 90}{11} V.$$





(b) $V_{OC} = 0.6 \times 5 - 0.1 i_S = 3 - 0.1 i_S.$

$$i_S > 30mA \Rightarrow \text{diode} = \text{off} \Rightarrow i = \frac{5}{0.2 + 0.3} = 10mA, V = 0.1 i_S.$$

$$i_S < 30mA \Rightarrow \text{diode} = \text{on} \Rightarrow$$

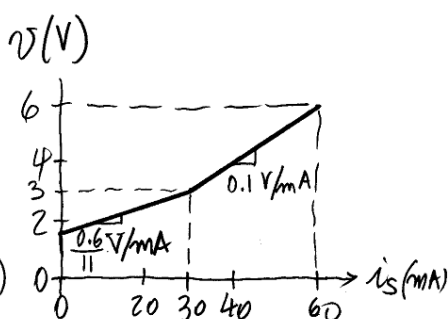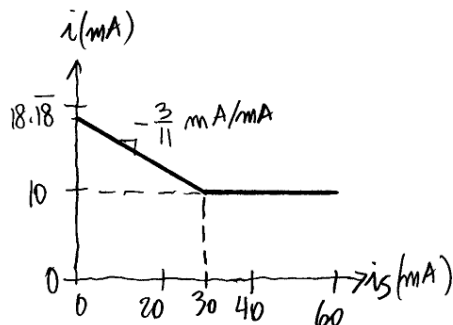
$$V = \frac{15 + 0.6 i_S}{11}, i = \frac{200 - 3 i_S}{11}.$$




1.5

$[V, k\Omega, mA]$. By the superposition principle, D_1 's anode sees $V_{oc} = \frac{15}{30+15} 15 + \frac{30}{30+15} (-15) = -5V$ and $R_{eq} = 15//30 = 10 k\Omega$. Redraw the circuit in simplified form:

(a) $D_1 = OFF$
 $D_2 = D_3 = ON$

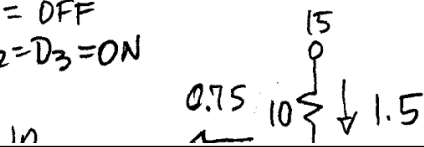


(b) $D_1 = D_3 = OFF$
 $D_2 = ON$

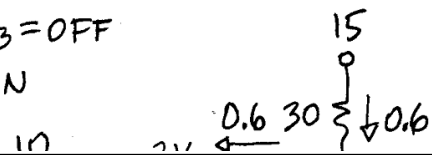

1.6


$[V, mA, k\Omega]$. The network seen by D_1 's anode admits a Thévenin equivalent with $R_{eq} = 30//15 = 10 k\Omega$ and $V_{oc} = 15 \times [15/(30+15)] - 15 \times [30/(30+15)] = -5V$.

(a) $D_1 = D_2 = D_3 = ON$

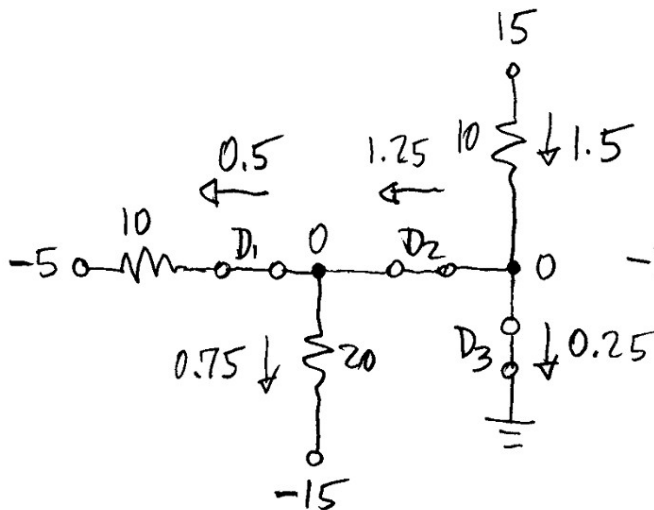

(b) $D_1 = D_3 = ON, D_2 = OFF$


$$V_{D_2} = -8.3 V.$$

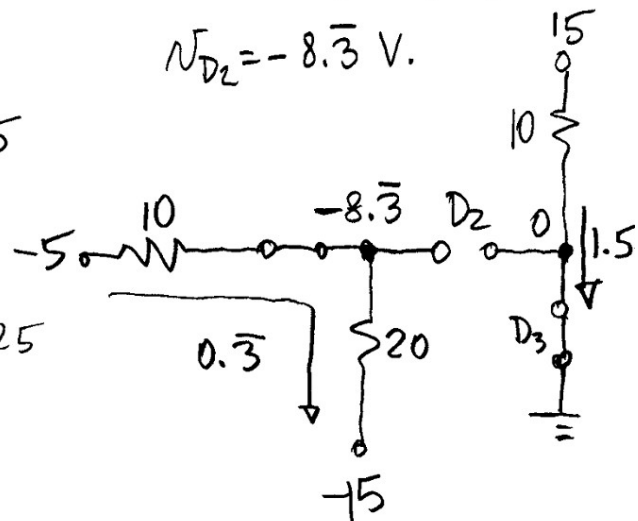

(c) $D_2 = ON, D_1 = D_3 = OFF$

$$V_{D_1} = -10V$$

$$V_{D_3} = -5V$$

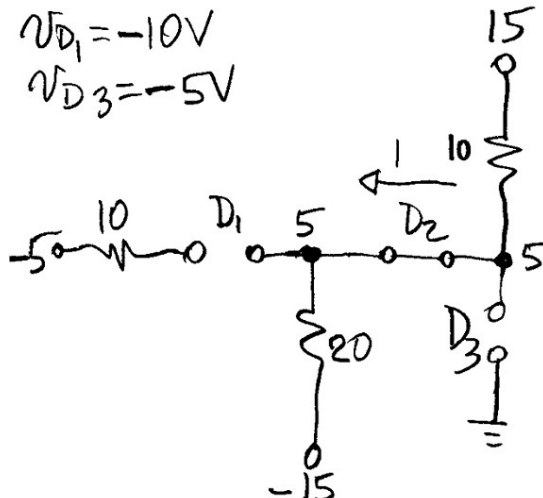


(d) $D_1 = D_2 = D_3 = OFF$


$$V_{D_1} = -10V$$

$$V_{D_2} = -30V$$

$$V_{D_3} = -15V$$

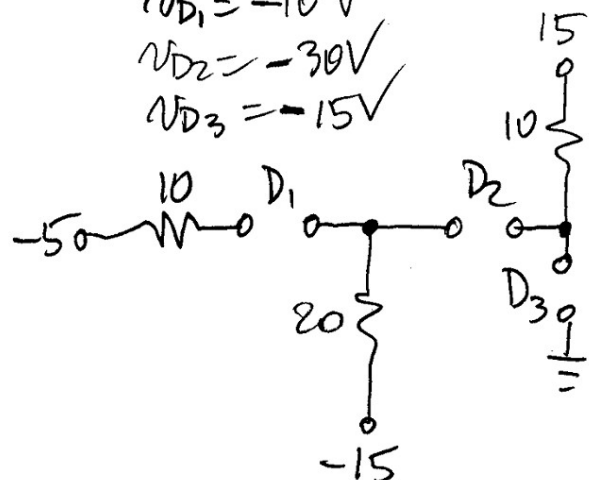


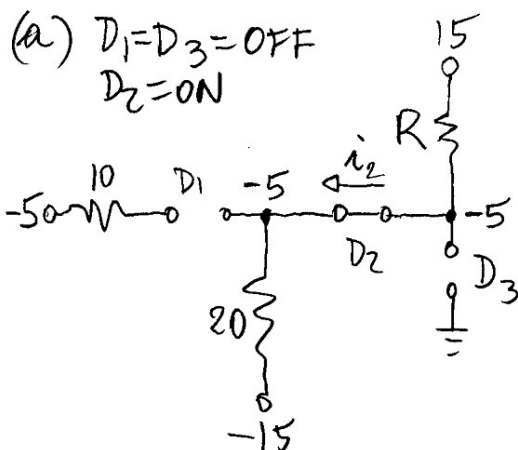1.7 [V, mA, kΩ]. D_1 's anode sees a Thévenin equivalent consisting of $R_{eq} = 30 // 15 = 10 \text{ k}\Omega$ and $V_{oc} = 15 \left[\frac{15 - 30}{30 + 15} \right] = -5 \text{ V}$.



$$i_2 = \frac{-5 - (-15)}{20} = 0.5 \text{ mA};$$
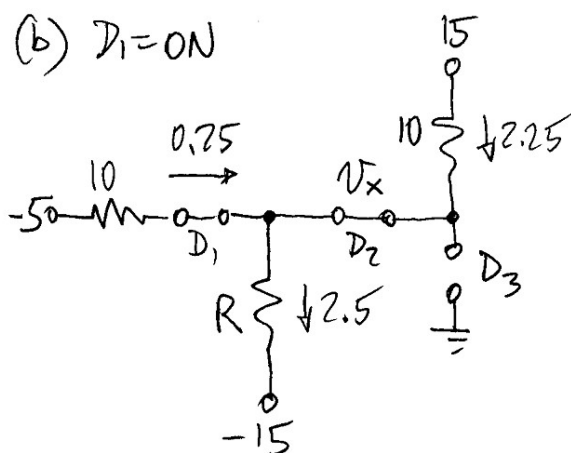
$$R = \frac{15 - (-5)}{0.5} = 40 \text{ k}\Omega$$




$$\frac{-5 - V_x}{10} = 0.75 \Rightarrow V_x = -7.5 \text{ V};$$

$$\Rightarrow D_2 = \text{ON} \Rightarrow D_3 = \text{OFF};$$

$$0.75 + \frac{15 - V_x}{10} = \frac{V_x - (-15)}{R}$$

$$\Rightarrow R = 3 \text{ k}\Omega.$$

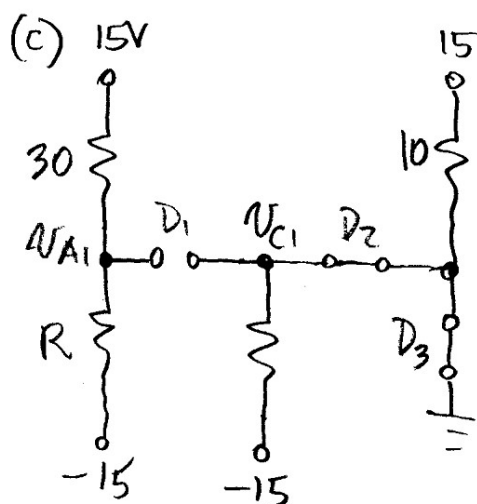

$$i_{D1} = 0 \Rightarrow D_2 = D_3 = \text{ON}, D_1 = \text{OFF}$$

$$\Rightarrow V_{C1} = 0 \text{ V}$$

$$V_{D1} = 0 \Rightarrow V_{A1} = 0.$$

$$i_{D1} = 0 \Rightarrow i_{30} = i_R \Rightarrow$$

$$\frac{15 - 0}{30} = \frac{0 - (-15)}{R} \Rightarrow R = 30 \text{ k}\Omega.$$

1.8

(a) For $V_I = 0$ all diodes are on, so $V_O = V_I = 0$. Ditto for $V_I = \pm 3$ V, when we also have $V_O = \pm 3$ V. For $V_I = 6$ V, D_1 and D_4 are off, D_2 and D_3 are on. So, $V_O = [10/(10+10)]10 = 5$ V. By symmetry, when $V_I = -6$ V, $V_O = -5$ V.


(b) With $R_3 = 30$ k Ω , V_I would have to exceed $\pm \frac{30}{10+30}10 = \pm 7.5$ V for any diode to go off. Consequently all diodes are on, and $V_O = 0, \pm 3$ V, ± 6 V.

(c) With $R_1 = 30$ k Ω , it takes $V_I > \frac{10}{30+10}10 = 2.5$ V to turn D_1 off. Consequently, $V_I = 0, +3, +6$ V yields $V_O = 0, +2.5, +2.5$ V. For $V_I \leq 0$, the situation remains as in (a), so $V_I = 0, -3, -6$ V gives $V_O = 0, -3, -5$ V.


(d) $D_3 = D_4 = \text{OFF}$. For $V_I \geq 0$, the situation is as in (a), so $V_I = 0, +3, +6$ V gives $V_O = 0, +3, +5$ V. For $V_I \leq 0$, $D_2 = \text{OFF}$ and $V_O = 0$ regardless of V_I . So, $V_I = 0, -3, -6$ V gives $V_O = 0, 0, 0$ V.

1.9


(a) For $V_I = 0$ V, all diodes are on, in effect shorting V_O to V_I to give $V_O = V_I$. If we raise V_I above 0 V, the diodes will continue to remain on till V_I reaches $\frac{R_3}{R_1 + R_3} 10 = \frac{10}{10+10} 10 = 5$ V. Raising V_I above 5 V will cause D_1 and D_4 to go off, thus giving $V_O = 5$ V. By symmetry, lowering V_I below -5 V will cause D_2 and D_3 to go off, thus giving $V_O = -5$ V. In summary, $V_O = V_I$ for $|V_I| < 5$ V, $V_O = +5$ V for $V_I > 5$ V, $V_O = -5$ V for $V_I < -5$ V.

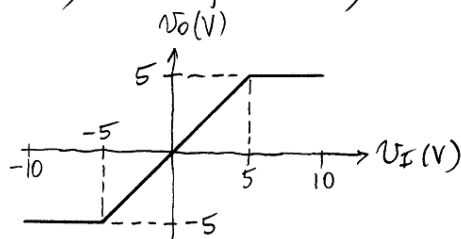

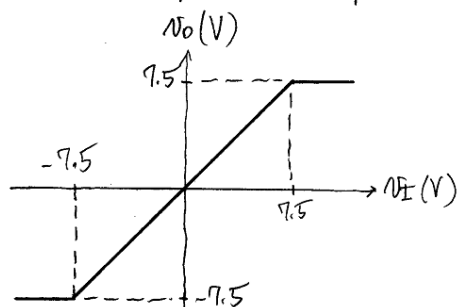(b) Now the breakpoints occur for $V_I = \pm \frac{30}{10+30} 10 = \pm 7.5$ V.




(c) No change for $|V_I| < 5$. For $V_I > 5$ V, D_1 and D_4 go off, D_3 and D_2 are on, and $(V_I - V_O)/10 + (10 - V_O)/10 = V_O/10$, or $V_O = (V_I + 10)/3$. Slope is now $(1/3) V/V$, and V_O peaks at $V_O = 20/3 = 6.\bar{6}$ V. By symmetry, for $V_I < 0$, V_O peaks at $-6.\bar{6}$ V.

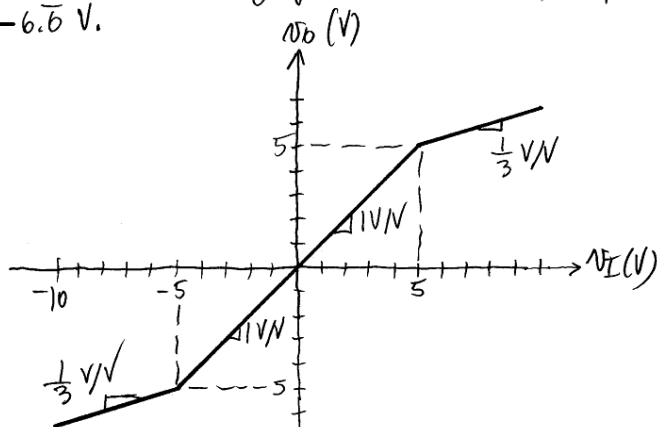

1.10

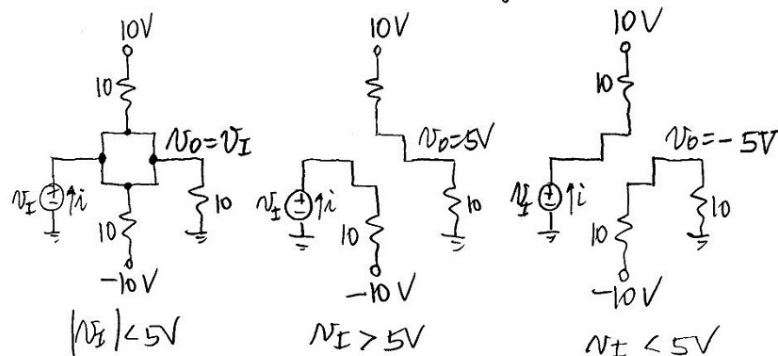(a) Shown below are three significant cases:



For $|v_I| < 5V$ all diodes are on. Applying KCL to the diode supernode gives $i + \frac{10 - v_I}{10} = \frac{v_I}{10} + \frac{v_I - (-10)}{10}$, or $i = 0.3v_I$.


At the extremes, $i = 0.3(\pm 5) = \pm 1.5 \text{ mA}$.

For $v_I > 5V$, D_1 and D_4 go off, and $i = \frac{v_I - (-10)}{10} = 0.1v_I + 1$.


At the extreme, $i = 0.1(10) + 1 = 2 \text{ mA}$.

For $v_I < -5V$, D_2 and D_3 go off, and $i = -\frac{10 - v_I}{10} = 0.1v_I - 1$.

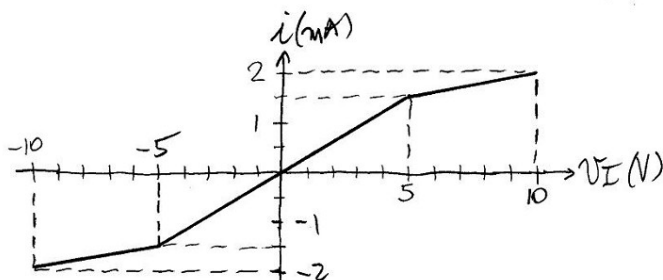At the extreme, $i = 0.1(-10) - 1 = -2 \text{ mA}$.




(b) As long as $|v_I| < 5V$, R_4 has no effect as it is shorted out by the diodes, so $i = 0.3v_I$. For $|v_I| > 5V$, the source v_I sees a resistance $R_{eq} = 10 // [5 + (10/10)] = 5k\Omega$, so the slope of i versus v_I is now $1/R_{eq} = 1/5 = 0.2 \text{ mA/V}$. At the extremes, we have $i = \pm(1.5 + 0.2 \times 5) = \pm 2.5 \text{ mA}$.

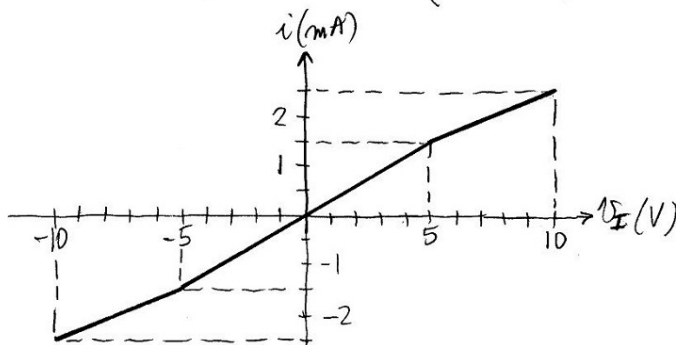


1.11


(a) Y grounded:

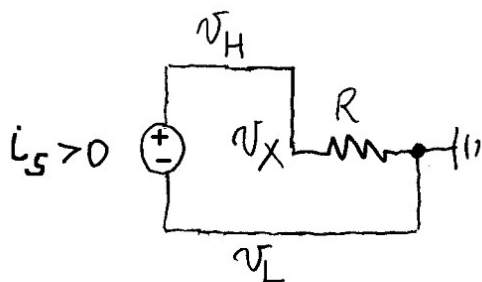


$$v_L = 0, v_X = v_H = v_I$$

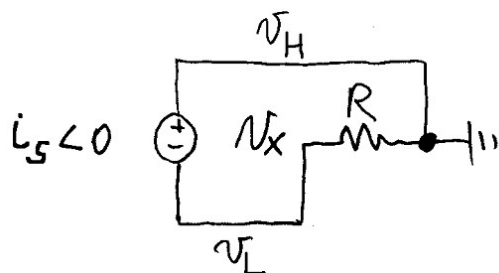

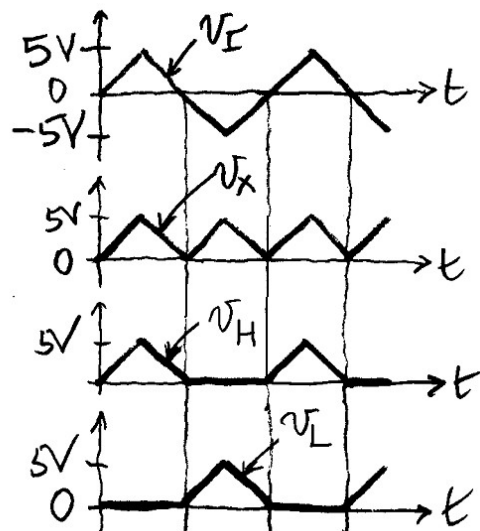
$$v_H = 0, v_X = v_L = v_H - v_I = -v_I$$




(b) X grounded:

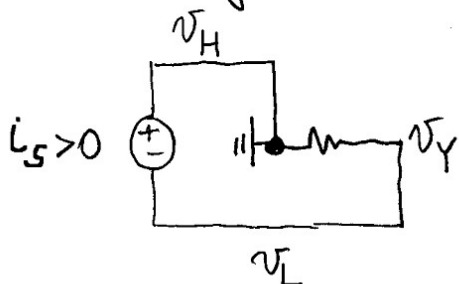
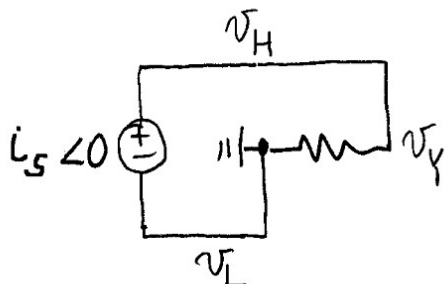
$$v_H = 0, v_Y = v_L = v_H - v_I = -v_I$$



$$v_L = 0, v_Y = v_H = v_I$$

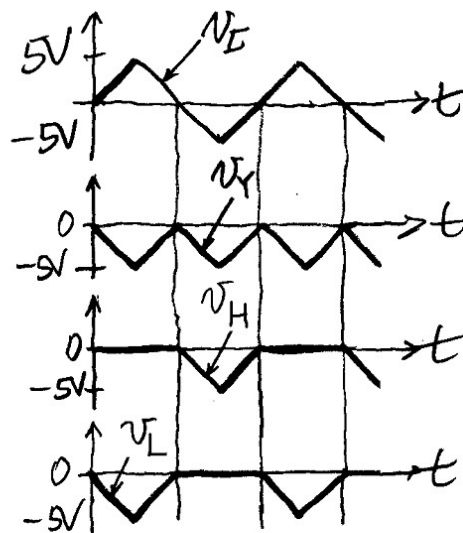


1.12

(a) As long as $-R_L I_S < v_I < +R_L I_S$, all diodes are on, in effect shorting the output node to the input node, and forcing $v_O = v_I$. If v_I is raised above $+R_L I_S$, D_1 and D_4 go off, giving $v_O = +R_L I_S$. Conversely, lowering v_I below $-R_L I_S$ causes D_3 and

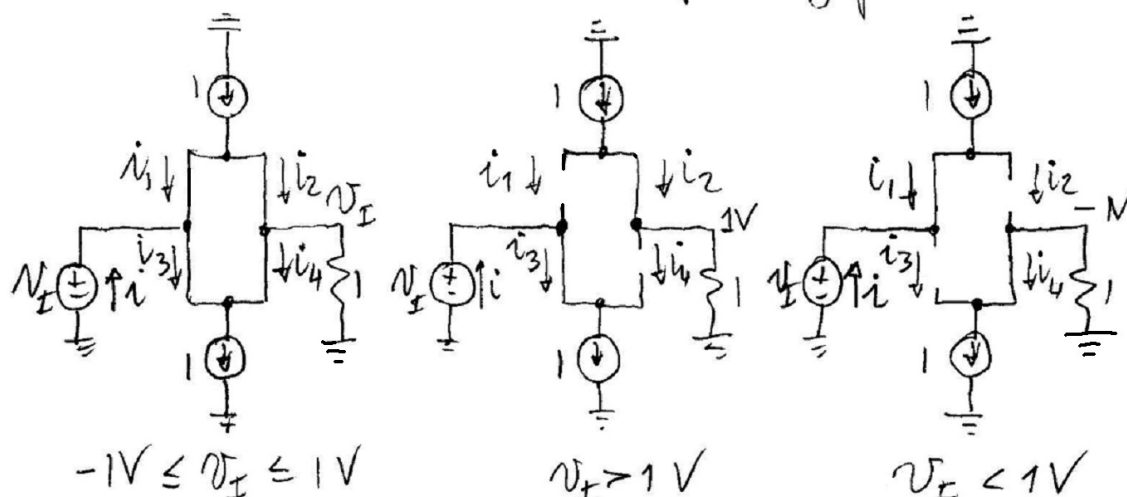1.13



$[V, \text{mA}]$. We have the following possibilities:



(a) For $-1V \leq v_I \leq +1V$, we apply KCL at the supernode, $i+1 = 1 + \frac{v_I}{1}$, or $i = v_I$. Applying KCL further, $i_1 + i_2 = 1$, $i_3 + i_4 = 1$, $i_3 = i_1 - i = i_1 - v_I$; $i_4 = i_2 - \frac{v_I}{1} = i_2 - v_I$. Combining, $i_1 + i_4 = 1 - v_I$, and $i_2 + i_3 = 1 + v_I$. But, by symmetry, $i_1 = i_4 = (1 - v_I)/2$, and $i_2 = i_3 = (1 + v_I)/2$.


(b) For $v_I > 1V$, $i = 1$, $i_1 = i_4 = 0$, $i_2 = i_3 = 1$.

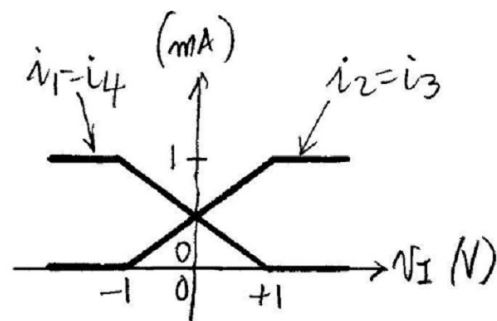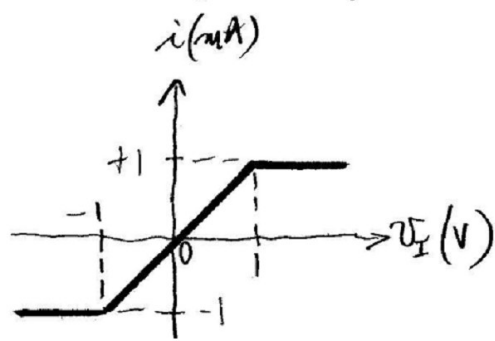(c) For $v_I < -1V$, $i = -1$, $i_1 = i_4 = 1$, $i_2 = i_3 = 0$.



1.14

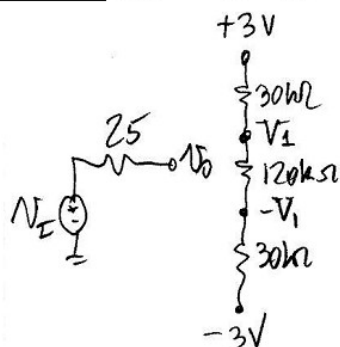(a) For $v_I = 0$ all diodes are off and we have $v_O = v_I$. The




voltages at the extremes of R_3 are $\pm V_1$, where V_1 is such that

$$\frac{3 - V_1}{30} = \frac{V_1 - (-3)}{120 + 30}, \text{ or } V_1 = 2 \text{ V.}$$

As v_I increases to 2 V, D_1 goes on, in effect shorting v_O to node V_1 .


We now have $(v_I - v_O)/25 + (3 - v_O)/30 = [v_O - (-3)]/(120 + 30)$, or $v_O = 0.5v_I + 1 \text{ V}$. Once v_I is raised to the point of making $v_O = 3 \text{ V}$, D_2 goes on, shorting v_O to the +3V source. This occurs when $0.5v_I + 1 = 3$, or $v_I = 4 \text{ V}$.

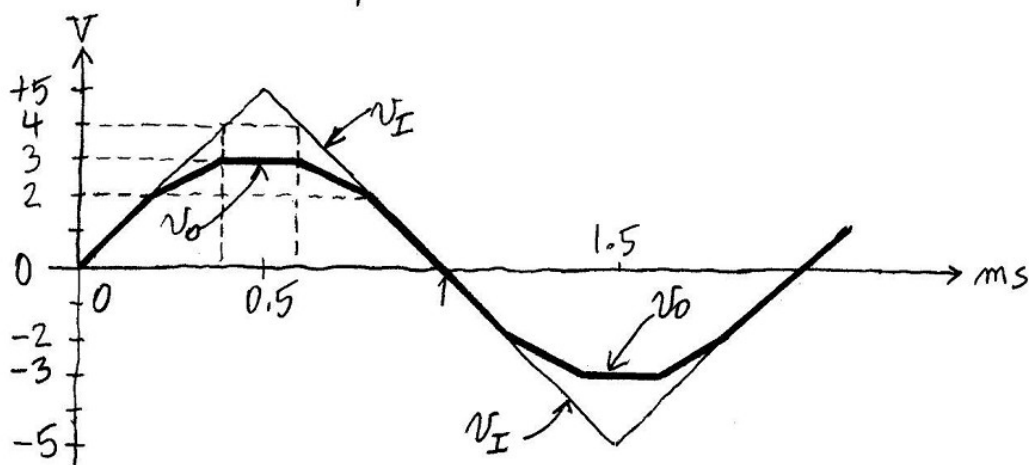The case $v_I \geq 0$ can be summarized by saying that $v_O = 0.5v_I$ for $0 < v_I < 2 \text{ V}$, $v_O = 0.5v_I + 1 \text{ V}$ for $2 \text{ V} < v_I < 4 \text{ V}$, and $v_O = 3 \text{ V}$ for $v_I > 4 \text{ V}$. Circuit behavior for $v_I < 0$ is symmetric to that for $v_I > 0$. This circuit can be used as a waveshaper.



(b) Removing D_2 and D_4 will eliminate the flat segments at the top and bottom; v_O will peak out at $\pm (0.5 \times 5 + 1) = \pm 3.5 \text{ V}$.

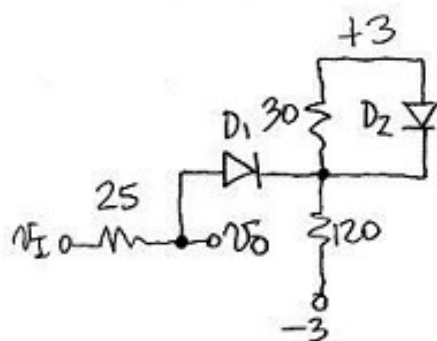
1.15 [V, mA, k Ω]. (a) Since circuit is symmetric, consider only the case $V_I > 0$. As long as




only the case $V_I > 0$. As long as $0 < V_I < 3V$, $D_1 = \text{OFF}$ and $D_2 = \text{ON}$, so $V_O = V_I$. D_1 turns on when V_I reaches $3V$, and stays on for $V_I > 3V$. As long as it still on, D_2 clamps V_O at $3V$. D_2 goes

off when V_I is raised to a value such that

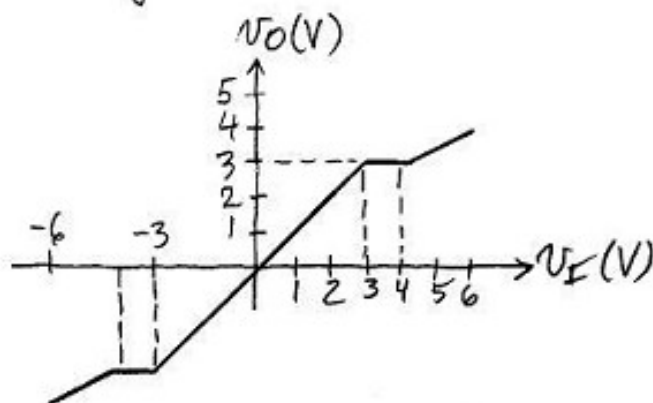$\frac{V_I - 3}{25} = \frac{3 - (-3)}{120}$, or $V_I = 4.25V$. For $V_I > 4.25V$, the slope of the VTC becomes $\frac{30 \parallel 120}{25 + (30 \parallel 120)} = \frac{24}{49} (\approx 0.5) V/V$. The case $V_I < 0$ is symmetric to the case $V_I > 0$.



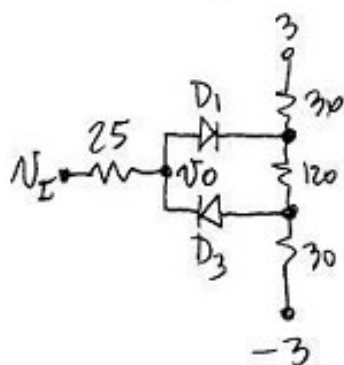(b) We now have the situation below. For $V_I = 0$, both




diodes are off. The voltage at D_1 's cathode is $3 - 30 \frac{3 - (-3)}{30 + 120 + 30} = 2V$, and that at D_3 's anode is $-2V$. So, for $0 \leq V_I \leq 2V$ we have $V_O = V_I$, and for $V_I > 2V$ we have


(Continued)

(1.15 continued) $\frac{v_I - v_O}{25} + \frac{3 - v_O}{30} = \frac{v_O - (-3)}{150} \Rightarrow v_O = 0.5v_I + 1V$

By symmetry,

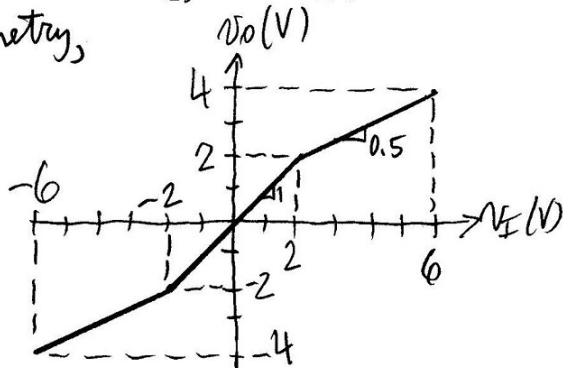

(c) The circuit is now as shown:

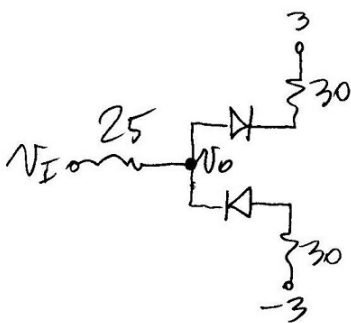


$$0 \leq v_I \leq 3V \Rightarrow v_O = v_I$$


$$v_I > 3V \Rightarrow$$

$$v_O = \frac{30v_I + 25 \times 3}{25 + 30} = \frac{6v_I + 15}{11}$$

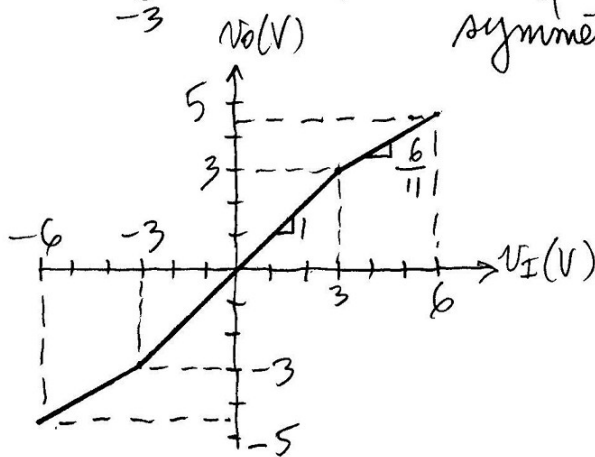The curve for $v_I < 0$ is symmetric of that for $v_I > 0$.




1.16 (a) $[V, mA, k\Omega]$.

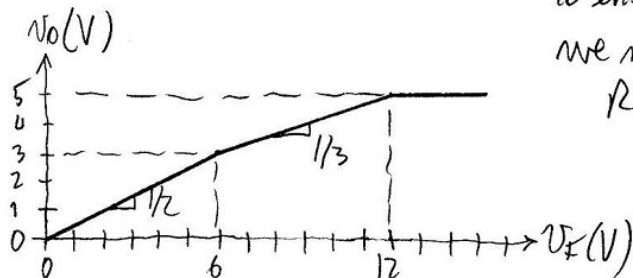


To ensure symmetry,
we must have
 $R_3 = R_2$.

$0 < v_i < 6V$:

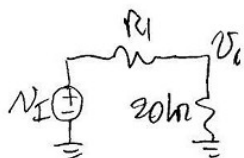


$$v_o = 0.5 v_i \Rightarrow R_1 = 20k\Omega$$

$v_i > 6V$:

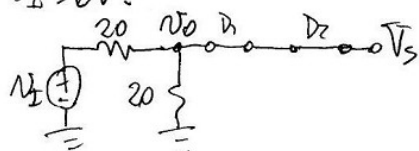

$$v_o = 5V \Rightarrow v_s = 5V$$

$6V < v_i < 12V$

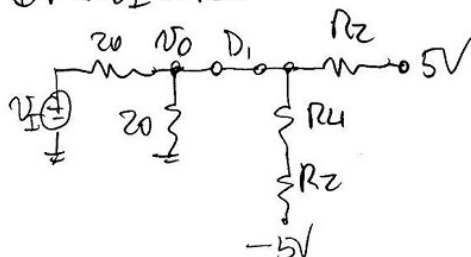

D_1 goes on for $v_i = 6V$,
or $v_o = 3V$. So,

$$\frac{5-3}{R_2} = \frac{3-(-5)}{R_4 + R_2}$$

$$\Rightarrow R_4 = 3R_2$$

To ensure a slope of $1/3$ V/V, we need

$$\frac{1}{3} = \frac{[20 // R_2 // (R_4 + R_2)]}{20 + [20 // R_2 // (R_4 + R_2)]} = \frac{20 // R_2 // 3R_2}{20 + [20 // R_2 // 4R_2]}$$


$$\Rightarrow 3 = \frac{20}{20 // R_2 // 4R_2} + 1 \Rightarrow 2 = 20 \left(\frac{1}{20} + \frac{1}{R_2} + \frac{1}{4R_2} \right) \Rightarrow R_2 = 25k\Omega$$

$$\therefore R_1 = 20k\Omega, R_2 = R_3 = 25k\Omega, R_4 = 75k\Omega, v_s = 5V.$$

(b) If D_2 and D_4 are omitted, slope will be $1/3$ V/V
also for $|v_i| > 12V$.




(c) If v_s is doubled, the coordinates of the breakpoints
will double, while the slopes will remain the
same.

1.17

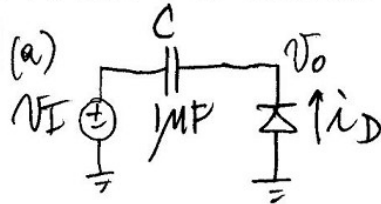

During conduction,
 $i_D = C \frac{d(v_O - v_I)}{dt}$
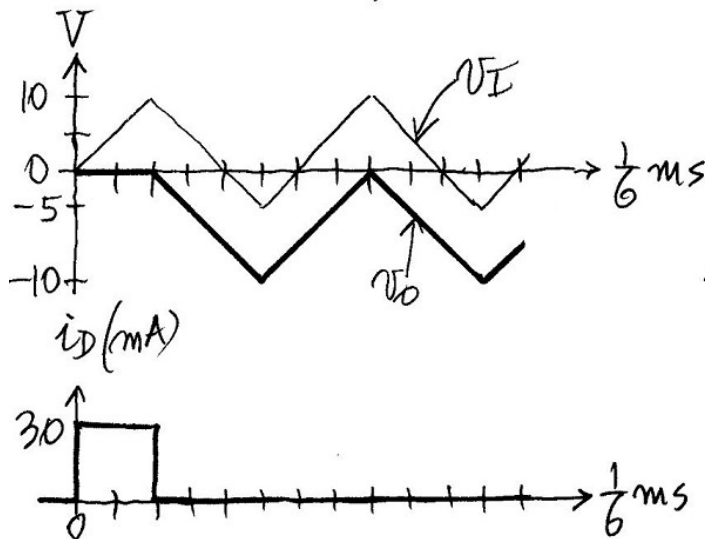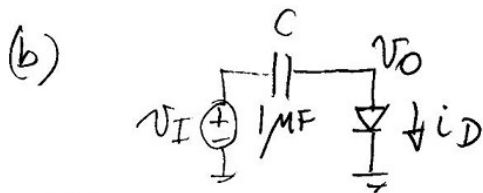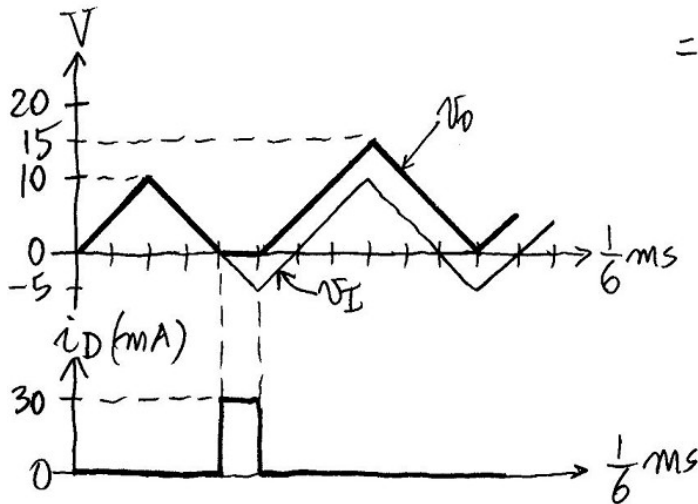
$$= 10^{-6} \frac{5}{(1/6)10^{-3}} = 30 \text{ mA}$$







$$i_D = C \frac{\Delta V}{\Delta t}$$



$$= 10^{-6} \frac{10}{(2/6)10^{-3}} = 30 \text{ mA}$$

(c) Doubling (halving) the frequency will yield similar waveforms, but with half (twice) the period, and i_D twice (half) as large, or 60 mA (15 mA).

1.18

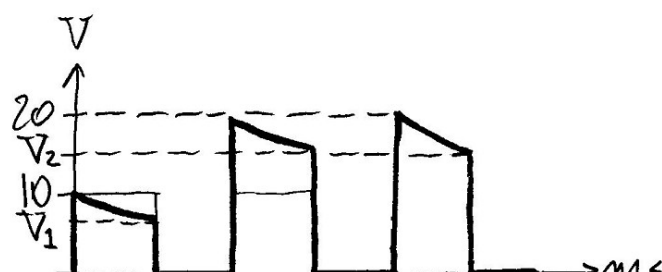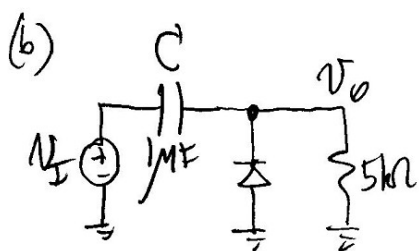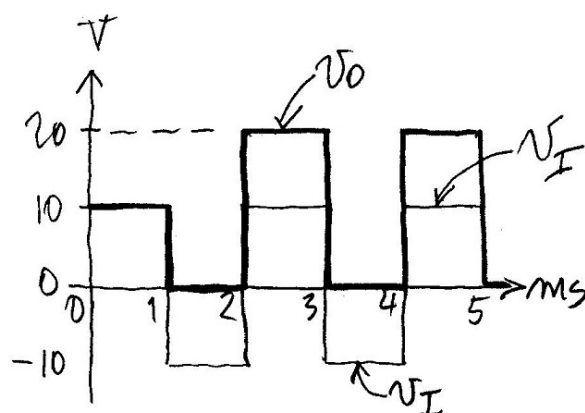
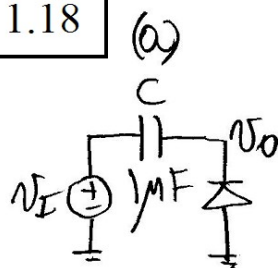


1.19

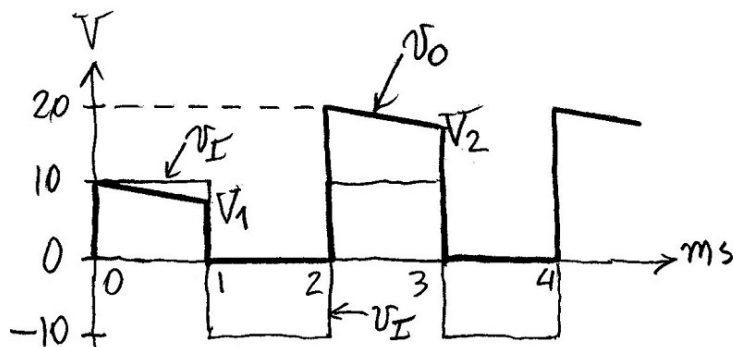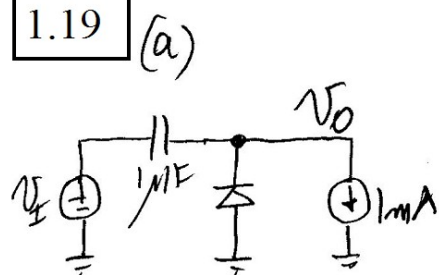

$C\Delta V = I\Delta t \Rightarrow \Delta V = I\Delta t/C = (10^{-3} \times 10^{-3})/10^{-6} = 1 \text{ V}$. So, $V_1 = 9 \text{ V}$, and $V_2 = 19 \text{ V}$.

(b)

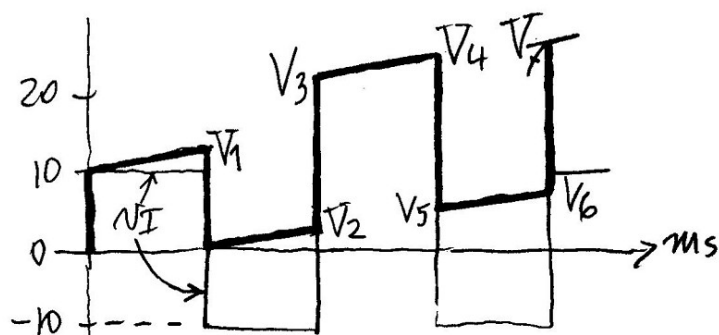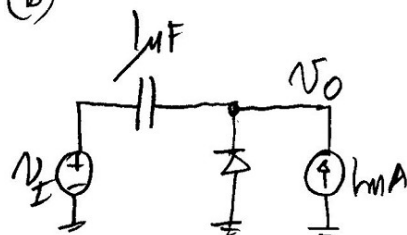

$V_1 = 10 + 1 = 11 \text{ V}$; $V_2 = 0 + 1 = 1 \text{ V}$; $V_3 = V_2 + 20 = 21 \text{ V}$; $V_4 = V_3 + 1 = 22 \text{ V}$; $V_5 = 22 - 10 = 12 \text{ V}$; $V_6 = V_5 + 1 = 13 \text{ V}$; $V_7 = V_6 + 20 = 33 \text{ V}$, and so on.

1.20

Op amp rule $\Rightarrow v_N = v_P = 0\text{ V}$ (virtual ground).

(a) $v_I > 0 \Rightarrow i_{R1}$ flows to the right $\Rightarrow D_1 = \text{ON} \ \& \ D_2 = \text{OFF}$, so $v_O = v_N = 0$. $v_I < 0 \Rightarrow i_{R1}$ flows to the left $\Rightarrow D_1 = \text{OFF} \Rightarrow D_2 = \text{ON} \Rightarrow v_O = -(R_2/R_1)v_I = -v_I$; $v_I < 0 \Rightarrow v_O > 0$.

(b) $v_O = 0$ for $v_I > 0$, $v_O = -2v_I$ for $v_I < 0$.

(c) $v_O = -4v_I$ for $v_I > 0$, $v_O = 0$ for $v_I < 0$.

1.21

Op amp rule: $v_N = v_P = 1.0\text{ V}$.

(a) $v_I > 1.0\text{ V} \Rightarrow i_{R1}$ flows to the right $\Rightarrow D_1 = \text{ON} \Rightarrow D_2 = \text{OFF} \Rightarrow i_{R2} = 0 \Rightarrow v_O = v_N = 1.0\text{ V}$. $v_I < 1.0\text{ V} \Rightarrow i_{R1}$ flows to the left $\Rightarrow D_1 = \text{OFF} \ \& \ D_2 = \text{ON}$. KCL $\Rightarrow (v_O - v_N)/R_2 = (v_N - v_I)/R_1 \Rightarrow v_O - 1 = 2(1 - v_I) \Rightarrow v_O = 3 - 2v_I$. Summarizing, $v_O = 1\text{ V}$ for $v_I > 1\text{ V}$, $v_O = 3 - 2v_I$ for $v_I < 1\text{ V}$.


(b) $v_I > 1\text{ V} \Rightarrow D_1 = \text{OFF} \ \text{and} \ D_2 = \text{ON}$, so $(v_I - 1)/R_1 = (1 - v_O)/R_2 \Rightarrow v_O = 4 - 3v_I$. $v_I < 1\text{ V} \Rightarrow D_1 = \text{ON} \ \& \ D_2 = \text{OFF} \Rightarrow v_O = 1.0\text{ V}$

1.22

$v_N = 0$ (virtual ground); $i_{R3} = 3/R_3 = 0.1\text{ mA}$ (\rightarrow). The onset of conduction for D_1 occurs when $i_{R1} = i_{R3}$, or $(v_N - v_I)R_1 = 0.1\text{ mA} \Rightarrow (0 - v_I)/10 = 0.1 \Rightarrow v_I = -1\text{ V}$. Two cases:

$v_I < -1\text{ V} \Rightarrow D_1 = \text{ON} \ \text{and} \ D_2 = \text{OFF} \Rightarrow i_{R2} = 0 \Rightarrow v_O = v_N = 0$.

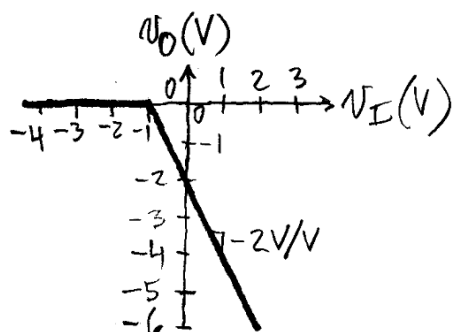$v_I > -1\text{ V} \Rightarrow D_1 = \text{OFF} \ \text{and} \ D_2 = \text{ON} \Rightarrow i_{R1} + i_{R3} = i_{R2} \Rightarrow v_I/R_1 + 0.1 = (0 - v_O)/R_2 \Rightarrow v_I/10 + 0.1 = -v_O/20 \Rightarrow v_O = -2 - 2v_I$.



1.23


Consider the case $V_I > 0$ first. This results in $V_O < 0$, so D_2 's anode is negative and we can ignore the

1.24

Consider first the case $V_I > 0$. This implies $V_O < 0$, indicating that D_2 will be off, and the entire circuit made up of D_2 , R_5 , and R_6 can be ignored. Now, D_1 's anode is at virtual ground, and D_1 will go on when V_O is sufficiently negative to result in $(V_5 - 0)/R_3 = (0 - V_O)/R_4$, or when V_O reaches $-(R_4/R_3)V_5 = -(10/20)12 = -6V$. Given that with D_1 still off we have $V_O = -(R_2/R_1)V_I = -2V_I$, D_1 will start conducting when $V_I = -(-6)/2 = +3V$.

So, for $V_I > 3V$, D_1 goes on, placing R_4 in parallel with R_2 , and causing the op amp to act as a summing amp, $V_O = -\left(\frac{R_4 \parallel R_2}{R_1} V_I - \frac{R_4 \parallel R_2}{R_3} V_5\right) = -\left(\frac{10/20}{10} V_I - \frac{10/20}{20} 12\right) = -\frac{2}{3} V_I - 4V$.

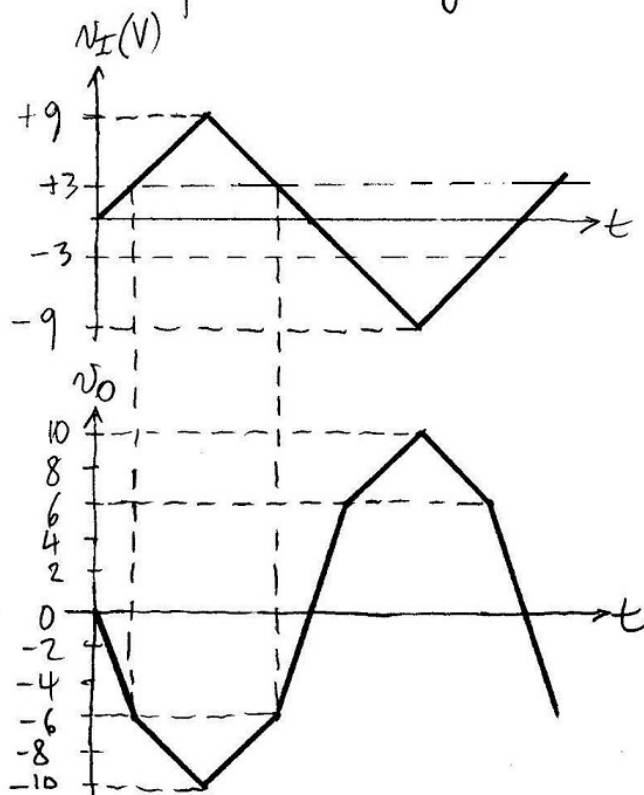Circuit behavior for $V_I < 0$ is symmetric to that for $V_I > 0$.




1.25

Consider first the case $V_I > 0$. Since D_1 's anode is at virtual ground and D_1 's cathode is positive, D_1 will be off, and we can ignore the circuit made up of D_1 , R_3 , and R_4 . As long as D_2 is also off, we have $V_O = -(R_2/R_1)V_I = -V_I$. D_2 will go on when V_I is sufficiently positive to yield $(V_I - 0)/R_5 = [0 - (-V_S)]/R_6$, or $V_I/10 = 10/20$, or $V_I = +5V$. For $V_I > 5V$, D_2 is on, in effect placing R_5 in parallel with R_1 , and causing the op amp to work as a summing amplifier,


$$V_O = -\left(\frac{R_2}{R_1/R_5} V_I - \frac{R_2}{R_4} (-V_S)\right) = -\left(\frac{10}{10/10} V_I - \frac{10}{20} (-10)\right) = -2V_I + 5V.$$

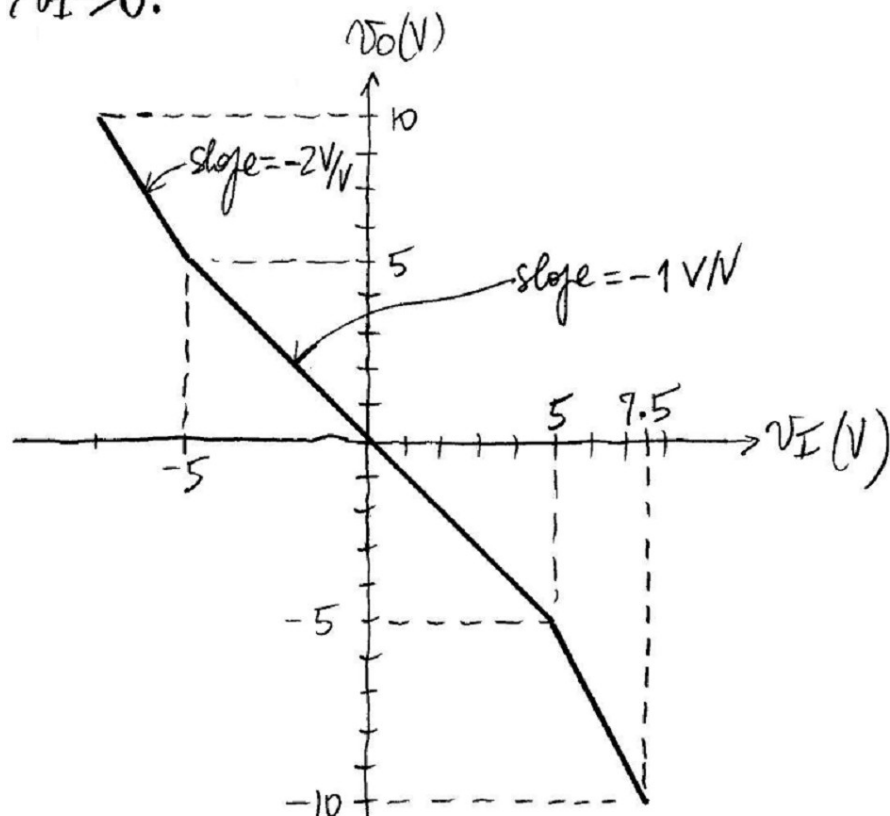Circuit behavior for $V_I < 0$ is symmetric to that for $V_I > 0$.



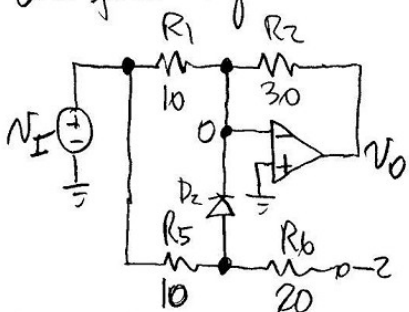
1.26

For $V_I > 0$ we have $V_O < 0$, indicating that the op amp output will sink current out of the inverting input node. This node is at virtual ground, so D_1 will be off for $V_I > 0$, and we only need to examine the following subcircuit:



For $V_I > 0$ & V_I sufficiently small, $D_2 = \text{OFF}$, and $V_O = -(30/10)V_I = -3V_I$. D_2 goes on when V_I is such that

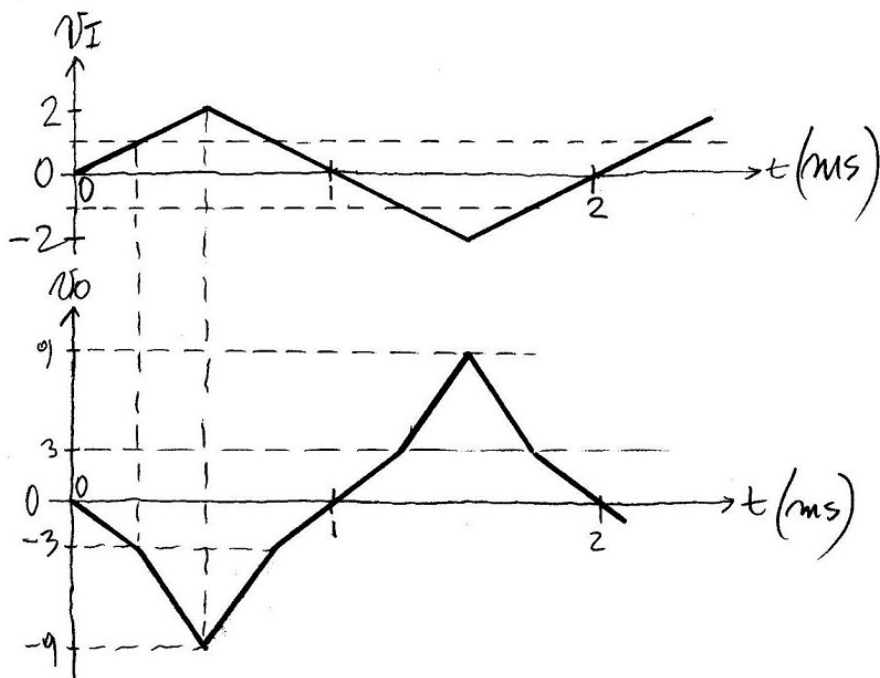$(V_I - 0)/10 = [0 - (-2)]/20$, or $V_I = +1\text{ V}$. Once on, D_2 in effect places R_5 in parallel with R_1 , giving a slope of $-30/(10 \parallel 10) = -6\text{ V/V}$. In fact, using the superposition principle, we have $V_O = -6V_I - (30/20)(-2) = 3 - 6V_I$. Circuit behavior for $V_I < 0$ is symmetric to that for $V_I > 0$.



1.27

(a) n -type slab, with $n \approx N_D - N_A = 10^{15} - 4 \times 10^{14} = 6 \times 10^{14} / \text{cm}^3$; $p = (2 \times 10^{20}) / (6 \times 10^{14}) = 0.33 \times 10^5 / \text{cm}^3$.

(b) $n_i^2(400\text{K}) = 1.5 \times 10^{33} \lambda 400 \exp(-14028/400) = 5.6 \times 10^{25} / \text{cm}^6$. So, $n \approx 6 \times 10^{14} / \text{cm}^3$, $p = (5.6 \times 10^{25}) / (6 \times 10^{14}) = 0.93 \times 10^{10} / \text{cm}^3$.

(c) $p \approx N_A - N_D \Rightarrow N_A \approx p + N_D = 5 \times 10^{15} + 10^{16} = 1.5 \times 10^{16} / \text{cm}^3$.

(d) $\mu_n = 68 + \frac{1346}{1 + \left(\frac{1.5 \times 10^{16} + 10^{16}}{9.2 \times 10^{16}} \right)^{0.71}} = 1031 \text{ cm}^2/\text{Vs}$

$\mu_p = 45 + \frac{427}{1 + \left(\frac{2.5 \times 10^{16}}{2.2 \times 10^{17}} \right)^{0.72}} = 398 \text{ cm}^2/\text{Vs}$

1.28

$R = \rho \frac{L}{A} = \rho \frac{10 \times 10^{-4}}{1 \times 10^{-4} \times 2 \times 10^{-4}} = 5 \times 10^4 \rho$

(a) $\rho = \frac{1}{q n_i (\mu_p + \mu_n)} = \frac{1}{1.6 \times 10^{-19} \times 1.4 \times 10^{10} (45 + 427 + 68 + 1346)}$
 $= 2.4 \times 10^5 \Omega \text{ cm} \Rightarrow R = 5 \times 10^4 \times 2.4 \times 10^5 = 12 \text{ G}\Omega$.

(b) $n \gg p \Rightarrow \rho \approx \frac{1}{q N_D \mu_n} = \frac{1}{1.6 \times 10^{-19} \times 10^{16} \times 1183} = 0.53 \Omega \text{ cm}$
 $\Rightarrow R = 26 \text{ k}\Omega$

(c) $\rho \approx \frac{1}{q N_A \mu_p} = \frac{1}{1.6 \times 10^{-19} \times 10^{18} \times 152} = 41 \text{ m}\Omega \text{ cm} \Rightarrow R = 2 \text{ k}\Omega$

(d) $\rho \approx \frac{1}{1.6 \times 10^{-19} \times 10^{20} \times 77} = 811 \mu\Omega \text{ cm} \Rightarrow R = 41 \Omega$

(e) $\rho \approx \frac{1}{1.6 \times 10^{-19} \times 10^{20} \times 50} = 41.4 \mu\Omega \text{ cm} \Rightarrow R = 62.5 \Omega$

(f) $R = 5 \times 10^4 \times 2.7 \times 10^{-6} = 0.14 \Omega$.

1.29

$$(a) E = V/L = (1V)/(20\mu m) = 1/(20 \times 10^{-4}) = 500 V/cm$$

$$(b) n \approx 10^{14}/cm^3, p \approx 2 \times 10^{20}/10^{14} = 2 \times 10^6/cm^3.$$

$$\mu_n \approx 1400 cm^2/Vs; \mu_p \approx 470 cm^2/Vs.$$

$$v_n = \mu_n E = 1400 \times 500 = 700 \times 10^3 cm/s$$

$$v_p = \mu_p E = 235 \times 10^3 cm/s$$

$$(c) |J_n| = q n v_n = 1.602 \times 10^{-19} \times 10^{14} \times 700 \times 10^3 = 11.2 A/cm^2$$

$$|J_p| = q p v_p = 1.602 \times 10^{-19} \times 2 \times 10^6 \times 235 \times 10^3 = 75 mA/cm^2$$

$\Rightarrow |J_p| \ll |J_n| \Rightarrow$ can ignore drift minority current.

$$(e) R = V/i = V/[(J_p + J_n)A] \approx V/(J_n A) = \frac{1}{11.2 \times 2 \times 5 \times (10^{-4})^2}$$

$$= 893 \Omega$$


$$(d) t_m = \frac{L}{v_n} = \frac{20 \times 10^{-4}}{700 \times 10^3} = 2.86 ns; t_p = 8.5 ns.$$

1.30

$$n(L) = 2 \times 10^{14}$$

$$\mu_n = 68 + \frac{1}{1 + [10^{16}/]}$$

$$D_n = \mu_n V_T = 1183 \times 1$$

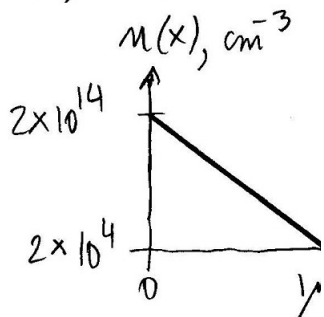


$$i = JA = -9.9 (20 \times 10^{-4})$$


(or 98.6 μA flow)

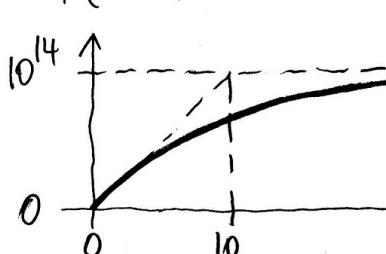1.32

$$(a) \mu_p = 45 + \frac{427}{1 + [10^{16}/(2.2 \times 10^{17})]^{0.72}} \approx 430 cm^2/Vs$$



$$J_p (A/cm^2)$$

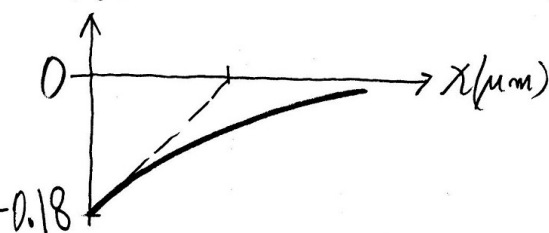

$$D_p = 430 \times 0.026 \approx 11.2 cm^2/s$$

$$\frac{dp}{dx} = -10^{14} e^{-x/(10\mu m)} \frac{-1}{10\mu m}$$

$$= +10^{17} e^{-x/(10\mu m)} cm^{-4}$$

$$J_p = -q D_p \frac{dp}{dx} = -1.6 \times 10^{-19} \times 11.2 \times 10^{17} e^{-x/(10\mu m)}$$

$$\approx 0.18 e^{-x/(10\mu m)} A/cm^2$$

(b) J_p depends on dp/dx , regardless of whether p is large or small. In our example, slope is highest where p is small, and vice-versa.


1.33


$$\phi_p = 26 \ln \frac{1.4 \times 10^{10}}{10^{16}} = -350 \text{ mV}; \quad \phi_n = 26 \text{ mV} \ln \frac{N_D}{1.4 \times 10^{10}};$$

$$\phi_0 = \phi_n + 0.35 \text{ V}; \quad x_{p0} = \sqrt{\frac{2\epsilon_s \epsilon_0 \phi_0}{q N_A} \frac{N_D}{N_A + N_D}}; \quad x_{n0} = \sqrt{\frac{2\epsilon_s \epsilon_0 \phi_0}{q N_D} \frac{N_A}{N_A + N_D}};$$

$$E_{mo} = \sqrt{\frac{2q \phi_0}{\epsilon_s \epsilon_0} \frac{N_A N_D}{N_A + N_D}}. \quad \text{Use the above to create the table:}$$

$N_D (\text{cm}^{-3})$	10^{16}	4×10^{16}	10^{17}
$\phi_p (\text{V})$	-0.35	-0.35	-0.35
$\phi_n (\text{V})$	0.35	0.386	0.410
$\phi_0 (\text{V})$	0.700	0.736	0.760
$x_{p0} (\text{mm})$	213	277	300
$x_{n0} (\text{mm})$	213	69	30
$\rho_p (\text{mC/cm}^3)$	-1.6	-1.6	-1.6
$\rho_n (\text{mC/cm}^3)$	1.6	6.4	16
$E_{mo} (\text{kV/cm})$	33	43	47

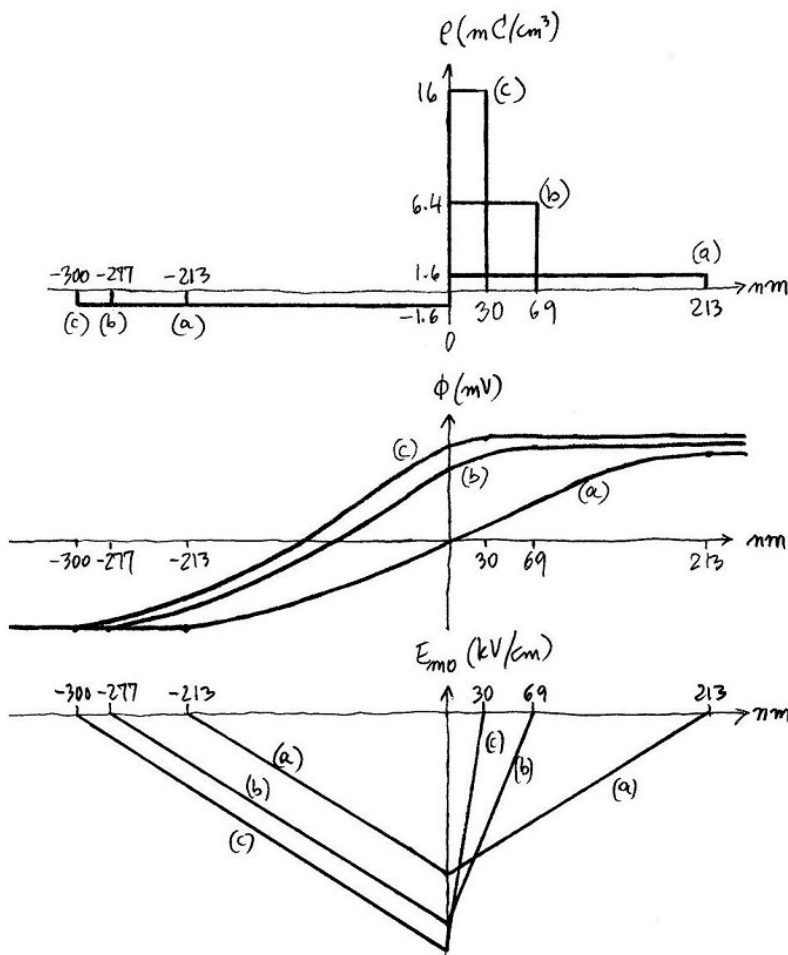

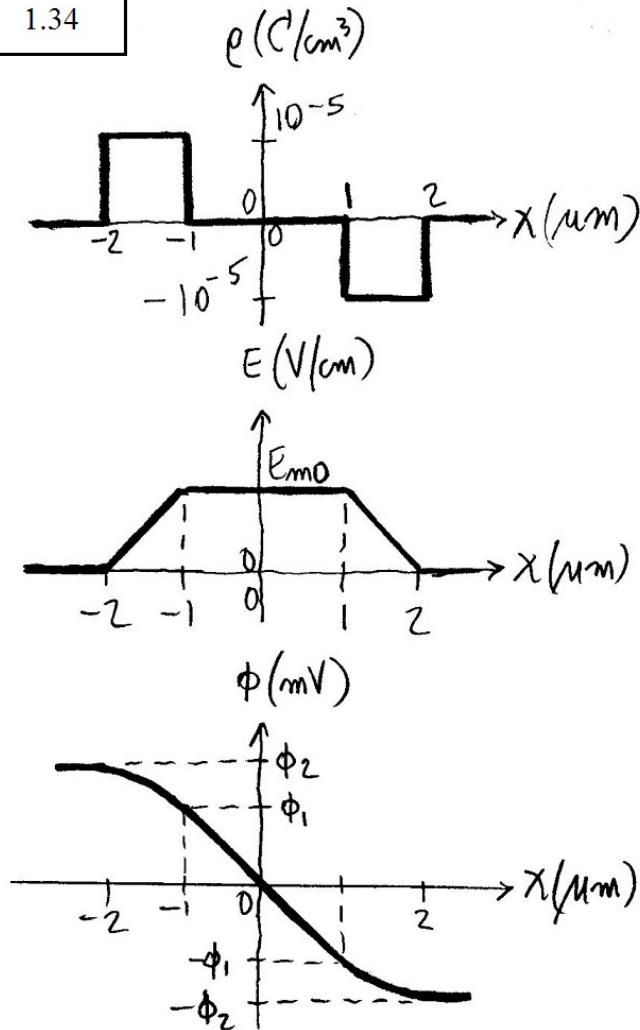

$$\frac{dE(x)}{dx} = \frac{e}{\epsilon_{si}} \Rightarrow$$

$E = \text{constant}$ for $|x| < 1 \mu\text{m}$
and $|x| > 2 \mu\text{m}$, and
 $E = \text{linear}$ for
 $1 \mu\text{m} < |x| < 2 \mu\text{m}$.

$$\frac{E_{m0}}{(2-1)10^{-4}} = \frac{10^{-5}}{1.04 \times 10^{-12}} \Rightarrow$$

$$E_{m0} = 962 \text{ V/cm}.$$

$$E = -\frac{d\phi}{dx} \Rightarrow$$

$\phi = \text{linear}$ for $|x| < 1 \mu\text{m}$
and $\phi = \text{quadratic}$ for
 $1 \mu\text{m} < |x| < 2 \mu\text{m}$.

$$\phi(1 \mu\text{m}) = -E_m \times 1 \mu\text{m} = -962 \times 10^{-4} = -96.2 \text{ mV} = -\phi_1; \quad \phi(-1 \mu\text{m}) = \phi_1.$$

For $1 \mu\text{m} < x < 2 \mu\text{m}$ we have

$$\phi(x) = -\phi_1 - \int_{1 \mu\text{m}}^{2 \mu\text{m}} E(x) dx$$

$$\begin{aligned} \phi(2 \mu\text{m}) &= -\phi_1 - (\text{area under } E \text{ from } 1 \mu\text{m} \text{ to } 2 \mu\text{m}) \\ &= -96.2 \text{ mV} - \frac{962 \times 10^{-4}}{2} = -144.3 \text{ mV} = -\phi_2; \end{aligned}$$

$$\phi(-2 \mu\text{m}) = \phi_2.$$

1.35

(a) Let $N = N_A = N_D$. Then, $0.7 = 0.026 \ln [N^2 / (2 \times 10^{20})]$
 $\Rightarrow N = 9.9 \times 10^{15} / \text{cm}^3$.

$$E_{mo} = -\sqrt{\frac{2 \times 1.6 \times 10^{-19} \times 0.7}{10^{-12}} \times \frac{9.9}{2} \times 10^{15}} = 33.3 \text{ kV/cm},$$

$$x_{po} = x_{no} = \frac{10^{-12} \times 33.3 \times 10^3}{1.6 \times 10^{-19} \times 9.9 \times 10^{15}} = 0.21 \mu\text{m}.$$

$$Q_{jo} = (10 \times 20) 10^{-8} \sqrt{2 \times 10^{-12} \times 1.6 \times 10^{-19} \times 0.7 \times \frac{9.9}{2} \times 10^{15}} = 66.6 \text{ fC}.$$

(b) $0.7 = 0.026 \ln [10 N_A \times N_A / (2 \times 10^{20})] \Rightarrow N_A = 3.14 \times 10^{15} / \text{cm}^3$.

1.36


$$\phi_m = 26 \ln \frac{10^{18}}{1.4 \times 10^{10}} = 470 \text{ mV}; \quad \phi_p = -350 \text{ mV}; \quad \phi_o = 0.82 \text{ V}.$$

$$x_{d0} = -\sqrt{\frac{2 \times 10^{-12} (0.47 + 0.35)}{1.6 \times 10^{-19}} \frac{10^{16} + 10^{18}}{10^{16} \times 10^{18}}} = 346 \text{ nm}$$

$$(a) 1 = 0.346 \sqrt{1 - V / 0.82} \Rightarrow V = -6.86 \text{ V}$$

$$(b) \frac{x_p}{x_n} = \frac{N_D}{N_A} \Rightarrow x_p = 100 x_n. \text{ But, } x_p + x_n = 1 \mu\text{m}. \text{ So,}$$
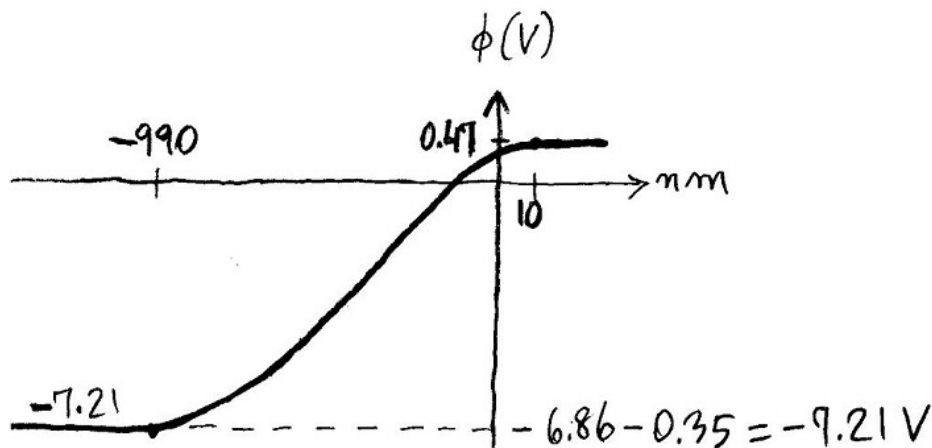
$$x_p \approx 1 \mu\text{m}, \quad x_n \approx 10 \text{ nm}.$$



$$(c) C = \epsilon_0 \frac{A}{x_d} \Rightarrow 10^{-12} = 1.04 \times 10^{-12} \frac{A}{10^{-4}} \Rightarrow A = 10^{-4} = (100 \mu\text{m} \times 100 \mu\text{m}).$$

1.37

$$C_{j0} = C_j(0) = 10 \text{ pF} = 10^{-11} \text{ F}$$

$$C_j = \frac{10}{(1 - v/\phi_0)^m} \Rightarrow m \log(1 - v/\phi_0) = \log \frac{10^{-11}}{C_j}$$

$$m \log(1 + 2/\phi_0) = \log \frac{10}{6.87}$$

$$m \log(1 + 8/\phi_0) = \log \frac{10}{4.87} \quad \text{Let } x = 2/\phi_0. \text{ Then,}$$

$$\frac{m \log(1+x)}{m \log(1+4x)} = \frac{\log(10/6.87)}{\log(10/4.87)} = 0.5218 \Rightarrow$$

$$\log(1+x) = 0.5218 \log(1+4x) \Rightarrow$$

$$1+x = (1+4x)^{0.5218} \Rightarrow x = (1+4x)^{0.5218} - 1.$$

$$\text{Solve by iteration to find } x = 2.483 \Rightarrow$$

$$\phi_0 = 805 \text{ mV}.$$

$$m = [\log(10/6.87)] / \log(1+2.483) = 0.3 \Rightarrow \text{graded.}$$

1.38

$$\phi_0 = 0.026 \ln \frac{10^{17} \times 10^{19}}{2 \times 10^{20}} = 0.94 \text{ V.}$$

$$Q_{j0} \cong (25 \times 10^{-4})(50 \times 10^{-4}) \sqrt{2 \times 10^{-12} \times 1.6 \times 10^{-19} \times 0.94 \times 10^{17}} = 2.17 \text{ pC.}$$

$$(a) Q_j(0 \text{ V}) = 2.17 \text{ pC}; Q_j(-1 \text{ V}) = 2.17 \sqrt{1 + \frac{1}{0.94}} = 3.12 \text{ pC}$$

$$\Delta Q_j = 3.12 - 2.17 = 0.95 \text{ pC from source to junction.}$$

$$C_{eq} = \frac{\Delta Q}{\Delta V} = \frac{0.95}{1} = 0.95 \text{ pF.}$$

$$(b) Q(-2 \text{ V}) = 2.17 \sqrt{1 + \frac{2}{0.94}} = 3.84 \text{ pC}$$

$$\Delta Q_j = 3.84 - 3.12 = 0.72 \text{ pC from source to junction.}$$

$$C_{eq} = 0.72 \text{ pF.}$$

$$(c) Q_j(-3 \text{ V}) = 2.17 \sqrt{1 + \frac{3}{0.94}} = 4.44 \text{ pF}$$

$$\Delta Q_j = 0.6 \text{ pC from junction to source; } C_{eq} = 0.6 \text{ pF.}$$

1.39

$I_p + I_m = 1 \text{ mA}$. By the diode equation,

$$\frac{I_p}{I_m} = \frac{D_p}{L_p N_D} \times \frac{L_n N_A}{D_n} = \frac{D_p}{D_n} \frac{L_n}{L_p} \frac{N_A}{N_D} = \frac{D_p}{D_n} \sqrt{\frac{D_p \tau_p}{D_n \tau_n}} \frac{N_A}{N_D}$$

$$= \left(\frac{D_p}{D_n} \right)^{3/2} \sqrt{\frac{\tau_p}{\tau_n}} \frac{N_A}{N_D} \cong \left(\frac{\mu_p}{\mu_n} \right)^{3/2} \times 1 \times \frac{N_A}{N_D}$$

$$(a) N_D = 10^{18} / \text{cm}^3, N_A = 10^{16} / \text{cm}^3 \Rightarrow n\text{-region } \mu_p \cong 152 \text{ cm}^2/\text{Vs}, \\ p\text{-region } \mu_n \cong 1183 \text{ cm}^2/\text{Vs}. I_p/I_m = (10^{16}/10^{18})(152/1183)^{3/2} = \\ 1/2171 \Rightarrow I_m \cong 1 \text{ mA}, I_p \cong 10^{-3}/2171 = 0.46 \mu\text{A}.$$


$$(b) N_D = 10^{16} / \text{cm}^3, N_A = 10^{18} / \text{cm}^3 \Rightarrow \mu_p \cong 430 \text{ cm}^2/\text{Vs}, \mu_n \cong \\ 280 \text{ cm}^2/\text{Vs}, I_p/I_m = (10^{18}/10^{16})(430/280)^{3/2} = 190 \Rightarrow$$

$$I_p \cong 1 \text{ mA}, I_m \cong 10^{-3}/190 = 5.3 \mu\text{A}.$$

$$(c) I_p/I_m = 1 \Rightarrow (10^{17}/N_D)(1/1.6)^{3/2} = 1 \Rightarrow N_D \cong 0.5 \times 10^{17} / \text{cm}^3.$$

1.40

(a)

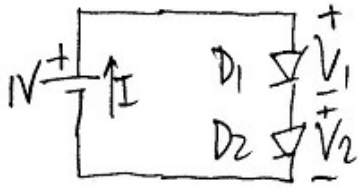


$$V_1 + V_2 = 1 \text{ V} = 1000 \text{ mV}$$

$$I = I_{S1} e^{V_1/V_T} = I_{S2} e^{V_2/V_T}$$

$$\frac{I_{S2}}{I_{S1}} = e^{(V_1 - V_2)/V_T} \Rightarrow V_1 - V_2 = V_T \ln \frac{I_{S2}}{I_{S1}}$$

$$\Rightarrow V_1 - V_2 = 0.026 \ln 5 = 41.8 \text{ mV} \Rightarrow V_1 = 521 \text{ mV}, V_2 = 479 \text{ mV}, I = 10^{-15} \times e^{521/26} = 503 \text{ nA}.$$

(b)

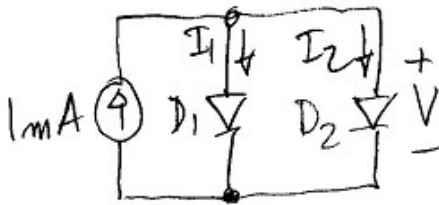

$$I_1 + I_2 = 1 \text{ mA}$$

$$I_1/I_2 = I_{S1}/I_{S2} = 1/5 = 0.2$$

$$\Rightarrow I_1 = 0.16 \text{ mA}, I_2 = 0.83 \text{ mA},$$

$$V = 26 \times \ln \frac{0.16 \times 10^{-3}}{10^{-15}} = 672 \text{ mV}.$$

1.41

(a) $N_D = 10^{17}/\text{cm}^3 \Rightarrow \mu_n = 1414 \text{ cm}^2/\text{Vs}$; $N_A = 10^{16}/\text{cm}^3 \Rightarrow \mu_p = 430 \text{ cm}^2/\text{Vs}$. $D_n = 1414 \times 0.026 = 36.8 \text{ cm}^2/\text{s}$, $D_p = 430 \times 0.026 = 11.2 \text{ cm}^2/\text{s}$.

$$I_s = (25 \times 50) 10^{-8} \times 2 \times 10^{20} \times 1.6 \times 10^{-19} \left(\frac{11.2}{10^{-4} \times 10^{17}} + \frac{36.8}{10^{-4} \times 10^{16}} \right)$$

$$= 0.45 + 14.7 = 15.2 \text{ fA}$$

$$\bar{i} = (15.2 \times 10^{-15}) \times e^{650/26} = 1.092 \text{ nA}$$

(b) $\phi_0 = 0.026 \ln \frac{10^{16} \times 10^{17}}{2 \times 10^{20}} = 0.760 \text{ V}$

$$\chi_p \approx \sqrt{\frac{2 \times 10^{-12} \times 0.76}{1.6 \times 10^{-19} \times 10^{16}}} \sqrt{\frac{10^{17}}{10^{16} + 10^{17}}} \sqrt{1 - \frac{650}{760}} = 0.112 \text{ } \mu\text{m},$$

$$\chi_n = \chi_p (N_A/N_D) = 0.011 \text{ } \mu\text{m}. \text{ Applying the corrections,}$$

$$I_s = 0.45 \frac{1}{1 - 0.011} + 14.7 \frac{1}{1 - 0.112} \approx 17 \text{ fA},$$

$$\bar{i} = 1.092 \times \frac{17}{15.2} = 1.22 \text{ nA}. \text{ Ignoring } \chi_p \text{ and } \chi_n \text{ we commit an error of about } -11.7\%.$$

1.42

(a) In the example it was found that $\phi_0 = 0.82 \text{ V}$ and $E_{m0} \approx 5 \times 10^4 \text{ V/cm}$. Impose

$$300 \times 10^3 = 5 \times 10^4 \sqrt{1 - v/0.82} \text{ and get } v \approx -28.3 \text{ V.}$$

$$(b) \phi_0 = 820 + 18 = 838 \text{ mV.}$$

$$E_{m0} = \sqrt{\frac{2 \times 1.6 \times 10^{-19} \times 0.838}{10^{-12}} \frac{2 \times 10^{16} \times 10^{18}}{2 \times 10^{16} \times 10^{18}}} = 7.25 \times 10^4 \text{ V/cm}$$

$$300 \times 10^3 = 7.25 \times 10^4 \sqrt{1 - v/0.838} \Rightarrow v = -13.5 \text{ V.}$$

1.43

Since $N_D \ll N_A$, $N_A N_D / (N_A + N_D) \approx N_D$. Also,


$$\phi_0 - v \approx -v, \text{ so}$$


$$E_{m0} \approx \sqrt{\frac{2q}{\epsilon_{sc}} N_D (-v)}$$

$$(a) 300 \times 10^3 \approx \sqrt{\frac{2 \times 1.6 \times 10^{-19}}{10^{-12}} N_D (100)} \Rightarrow N_D = 2.9 \times 10^{15} / \text{cm}^3$$

1.45


(a)
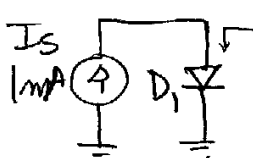
$$R = r_{d1} = \frac{nV_T}{I_D} = \frac{nV_T}{I_S} = \frac{50}{1} = 50 \Omega.$$

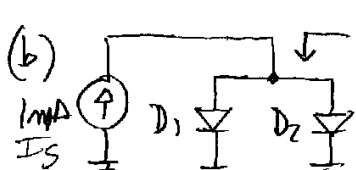
$$(b) R = r_{d1} \parallel r_{d2} = \frac{1}{2} r_{d1} = \frac{1}{2} \frac{nV_T}{I_S R} = \frac{1}{2} \frac{50}{0.5} = 50 \Omega.$$


Two diodes in \parallel act as a single diode with twice the area. The dynamic resistance of a diode is independent of its area.

(c)
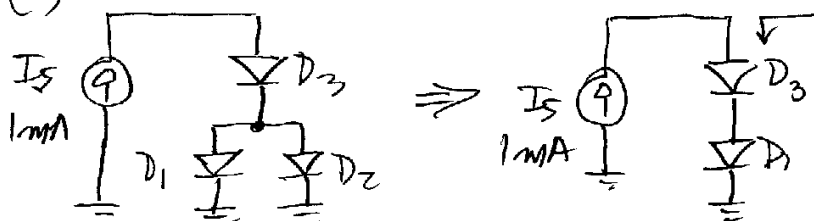
$$R_{eq} = r_{d3} + r_{d1} = 2 \frac{nV_T}{I_S} = 100 \Omega.$$


Now dynamic resistances add up and the result is twice as large.

1.46

(a) $900 - 750 = 150 \text{ mV}$. T increases by $150/2 = 75^\circ\text{C}$.

(b) $P = V_D I_D = 0.75 \times 10 = 7.5 \text{ W}$. Thermal res $= 75/7.5 = 10^\circ\text{C/W}$.

(c) If connected in series, both diodes experience the same situation of (a), so T increases by 75°C , and $P = 7.5 \text{ W}$ for each device.

(d) If connected in parallel, each diode carries $1/2$ the current, or 5 A . So, initially, $V_D(0) = (900 - 2 \times 18) \text{ mV} = 0.864 \text{ V}$, and $P(0) = 0.864 \times 5 = 4.32 \text{ W}$. Thus, T increases by $(4.32 \text{ W}) \times (10^\circ\text{C/W}) = 43.2^\circ\text{C}$, so $V_D(\infty) = 864 - 2 \times 43.2 = 0.778 \text{ V}$. Iterate:

$P(\infty) = 0.778 \times 5 = 3.9 \text{ W}$, $\Delta T = 39^\circ\text{C}$, $V_D(\infty) = 864 - 2 \times 39 = 0.786 \text{ V}$. Iterate once more, and get $P(\infty) = 0.786 \times 5 = 3.93 \text{ W}$, $V_D(\infty) = 0.785 \text{ V}$.

1.47


(a) With $I_S = 2 \text{ fA}$ and $nV_T = 26 \text{ mV}$, D_2 gives 1 nA @ 700 mV . $(700 - 340) \text{ mV} = 360 \text{ mV} = 6 \times 60 \text{ mV}$
 $\Rightarrow I_R = (1 \text{ nA})/10^6 = 1 \text{ nA}$.

(b) $340 + 18 = 358 \text{ mV}$. (c) $340 - 18 = 322 \text{ mV}$.

(d) $I_R = (1 \text{ nA}) \times 2^{50/10} = 32 \text{ nA}$. Because of the increase in I_R , V would increase by $5 \times 18 = 90 \text{ mV}$. However, because of the increase in T , V would decrease by $2 \times 50 = 100 \text{ mV}$. The final value is $V = 340 + 90 - 100 = 330 \text{ mV}$.

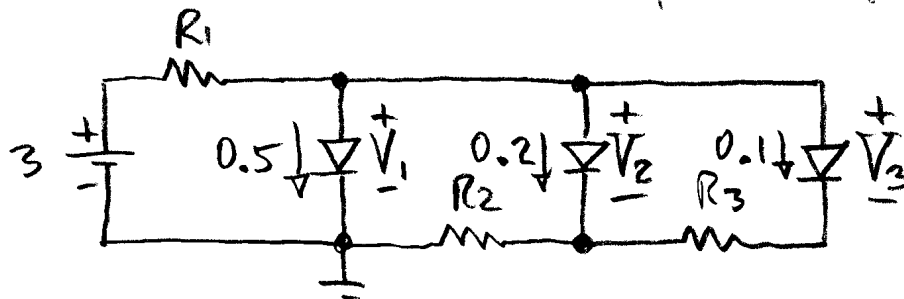1.48

[mA, V, k Ω]: Use rules of thumb (18 mV , 60 mV):



$$V_1 = 700 - 18 = 682 \text{ mV}$$

$$V_2 = 700 - 60 + 18 = 658 \text{ mV}$$


$$V_3 = 700 - 60 = 640 \text{ mV}$$

$$R_3 = (V_2 - V_3)/0.1 = 18/0.1 = 180 \Omega$$

$$R_2 = (V_1 - V_2)/(0.2 + 0.1) = 24/0.3 = 80 \Omega$$

$$R_3 = (3 - 0.682)/(0.5 + 0.2 + 0.1) = 2.9 \text{ k}\Omega$$

1.49 [mV, mA, Ω]

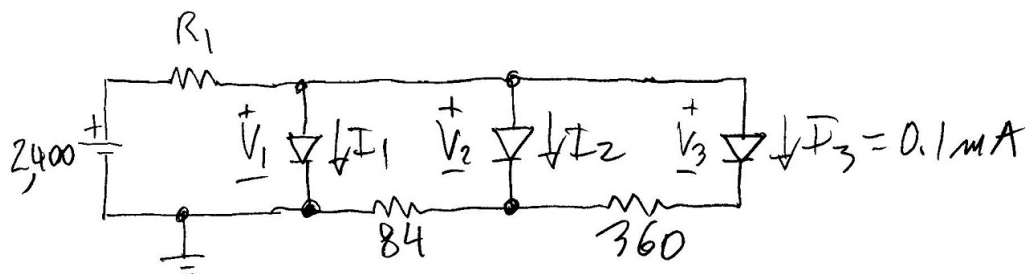

$$I_3 = 0.1 \text{ mA} = (1 \text{ mA})/10 \Rightarrow V_3 = 700 - 60 = 640 \text{ mV}.$$

$$V_2 = V_3 + R_3 I_3 = 540 + 360 \times 0.1 = 640 + 36 = 640 + 18 + 18$$

$$\Rightarrow I_2 = 0.1 \times 2 \times 2 = 0.4 \text{ mA}.$$

$$V_1 = V_2 + R_2 (I_2 + I_3) = 676 + 84(0.4 + 0.1) = 676 + 42 =$$

$$718 = 700 + 18 \Rightarrow I_1 = 1 \times 2 = 2 \text{ mA}.$$

$$R_1 = (V_s - V_1) / (I_1 + I_2 + I_3) = (2400 - 718) / (2 + 0.4 + 0.1) = 672.8 \Omega.$$

1.50 $I_{D2} = 0.1 \text{ mA} \Rightarrow V_{D2} = 700 - 60 = 640 \text{ mV}.$

$$V_{D3} = V_T \ln \frac{0.640 - V_{D3}}{1440 \times 2 \times 10^{-15}} = 0.026 \ln \frac{0.640 - V_{D3}}{2.88 \times 10^{-12}}.$$

Start out with $V_{D3} = 0.62 \text{ V}$, and iterate till you get $V_{D3} = 604 \text{ mV}$. Then, $I_{D3} = (0.64 - 0.604) / 1440 = 25 \mu\text{A}$. KCL: $I_{D2} + I_{D3} = 100 + 25 = 125 \mu\text{A}$.

$$V_{D1} = 336 \times 0.125 \times 10^{-3} + V_{D2} = 682 \text{ mV}. \text{ But, } 700 - 682 = 18 \text{ mV, so } I_{D1} = (1 \text{ mA})/2 = 0.5 \text{ mA. KCL: } I_{R1} =$$

$$I_{D1} + I_{D2} + I_{D3} = 0.5 + 0.125 = 0.625 \text{ mA. KVL:}$$

$$V_s = V_{D1} + 2 \times 0.625 = 1.932 \text{ V}.$$

1.51

$$(a) V_{D1AT} = V_{D1} - V_{D2} = V_T \left(\ln \frac{I_1}{I_{S1}} - \ln \frac{I_2}{I_{S2}} \right) =$$

$$\frac{kT}{q} \ln \frac{I_1 I_{S2}}{I_2 I_{S1}} = KT, \quad K = \frac{k}{q} \ln \frac{I_1 I_{S2}}{I_2 I_{S1}}.$$

$$(b) K = \frac{1.381 \times 10^{-23}}{1.602 \times 10^{-19}} \ln 10 = 198.5 \mu\text{V}/^\circ\text{C}.$$

(c) Nothing changes, as the ratio I_2/I_1 remains constant.

$$(d) 10 \times 10^{-3} = A \times 198.5 \times 10^{-6} \Rightarrow A = 50.4 \text{ V/V}.$$

1.52


$$(a) V_{PTAT} = V_{D1} - V_{D2} = V_T \left(\ln \frac{I_1 - I_2}{I_{S1}} - \ln \frac{I_2}{I_{S2}} \right) =$$

$$\frac{kT}{q} \ln \left[\left(\frac{I_1}{I_2} - 1 \right) \frac{I_{S2}}{I_{S1}} \right] = KT, \quad K = \frac{k}{q} \ln \left[\left(\frac{I_1}{I_2} - 1 \right) \frac{I_{S2}}{I_{S1}} \right].$$

$$(b) K = \frac{1.381 \times 10^{-23}}{1.602 \times 10^{-19}} \ln \left(\frac{100}{20} - 1 \right) = 119.5 \mu\text{V}/^\circ\text{C}.$$

$$(c) K = (86.2 \mu\text{V}/^\circ\text{C}) \ln \left[\left(\frac{100}{50} - 1 \right) 2 \right] = 59.75 \mu\text{V}/^\circ\text{C}.$$

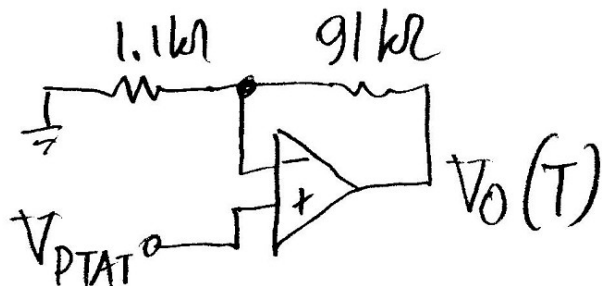(d) Use the setup of (b). Then $A = (10 \times 10^{-3}) / (119.5 \times 10^{-6}) = 83.7 \text{ V/V}$. Use a noninverting amp:



$$A = 1 + \frac{91}{1.1} \cong 83 \text{ V/V}.$$


1.53

[V, mA, k Ω]:

$$V_{OC} = \frac{3}{2+3} 5 - 2 \times 1 = 1 \text{ V}, \quad R_{eq} = 2//3 + 1 = 2.2 \text{ k}\Omega.$$

$$V_D = V_T \ln \frac{I_D}{I_S} = V_T \ln \frac{(V_{OC} - V_D) R_{eq}}{I_S} = 0.026 \ln \frac{1 - V_D}{2.2 \times 10^3 \times 5 \times 10^{-15}}$$

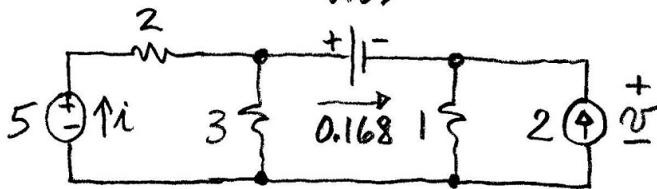Iterate and find $V_D = 0.630 \text{ V}$ and $I_D = 0.168 \text{ mA}$.



$$V = 1(2 + 0.168) = 2.168 \text{ V}; \quad i = \frac{5 - (2.168 + 0.63)}{2} = 1.1 \text{ mA}.$$

Using the 0.7-V model we get

$V_D = 0.7 \text{ V}$, $I_D = (1 - 0.7)/2.2 = 0.136 \text{ mA}$; a current error of about 20%, a voltage error of about 10%.

1.54


[V, mA, k Ω]:

$$V_{oc} = 1 \times 4 - [3/(2+3)] 4 = 1.6 \text{ V}, R_{eq} = 2 // 3 + 1 = 2.2 \text{ k}\Omega.$$

$$V_D = m V_T \ln \frac{V_{oc} - V_D}{R_{eq} I_s} = 0.035 \ln \frac{1.6 - V_D}{2.2 \times 10^3 \times 20 \times 10^{-15}} \quad | \quad 82$$

$$V_D = 0.035 \ln \frac{1.6 - V_D}{4.4 \times 10^{-11}}. \text{ Iterate } \Rightarrow V_D = 0.825 \text{ V} \Rightarrow$$
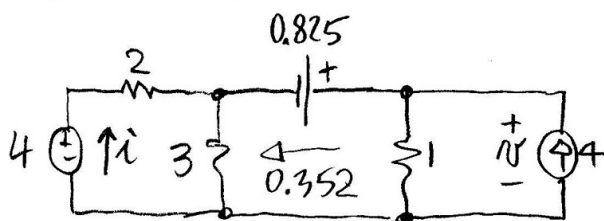
$$I_D = (1.6 - 0.825) / 2.2 = 0.352 \text{ mA}.$$



$$V = 1 \times (4 - 0.352) = 3.648 \text{ V}$$

$$i = \frac{4 - (3.648 - 0.825)}{2} = 0.588 \text{ mA}.$$


Using the 0.7-V diode model, we get

$$I_D = \frac{1.6 - 0.7}{2.2} = 0.409 \text{ mA (16% overestimate)}$$

$$V = 1 (4 - 0.409) = 3.591 \text{ V (1.6% underestimate)}$$

$$i = \frac{4 - (3.591 - 0.7)}{2} = 0.555 \text{ mA (5.6% underestimate)}.$$

1.55

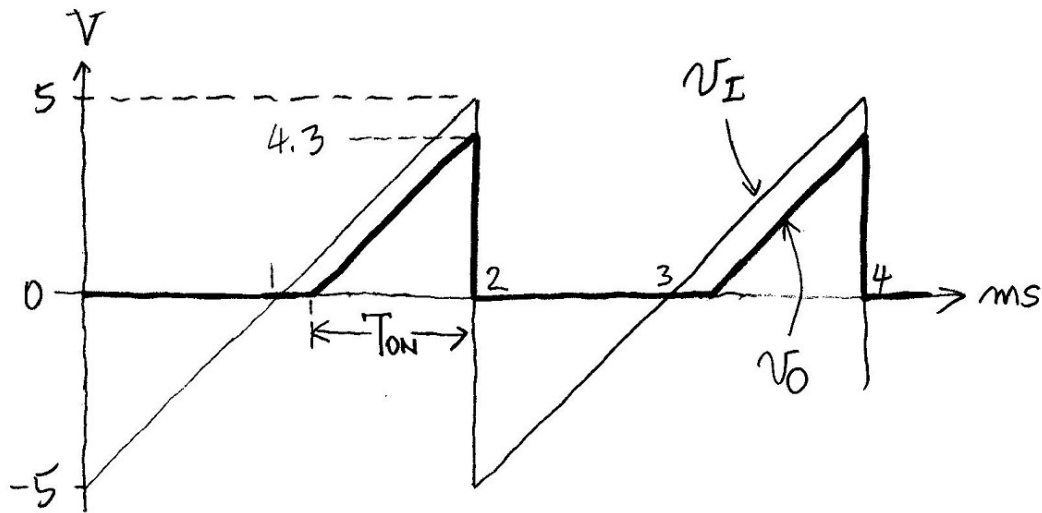


$$\frac{4.3}{T_{ON}} = \frac{5}{1 \text{ ms}} \Rightarrow T_{ON} = \frac{4.3}{5} = 0.86 \text{ ms} = 43\% \text{ of } T.$$

$$V_O(\text{avg}) = \frac{1}{T} \int_0^T V_O(t) dt = \frac{\text{Area under } V_O}{T} = \frac{(0.86 \times 4.3)/2}{2} = 0.9245 \text{ V}.$$

If the diode were ideal, we'd have $T_{ON} = T/2 = 1 \text{ ms}$ (50% of T) and $V_O(\text{avg}) = \frac{(1 \times 5)/2}{2} = 1.25 \text{ V}$. The error is therefore $100 \frac{0.9245 - 1.25}{1.25} = -26\%$.

1.56

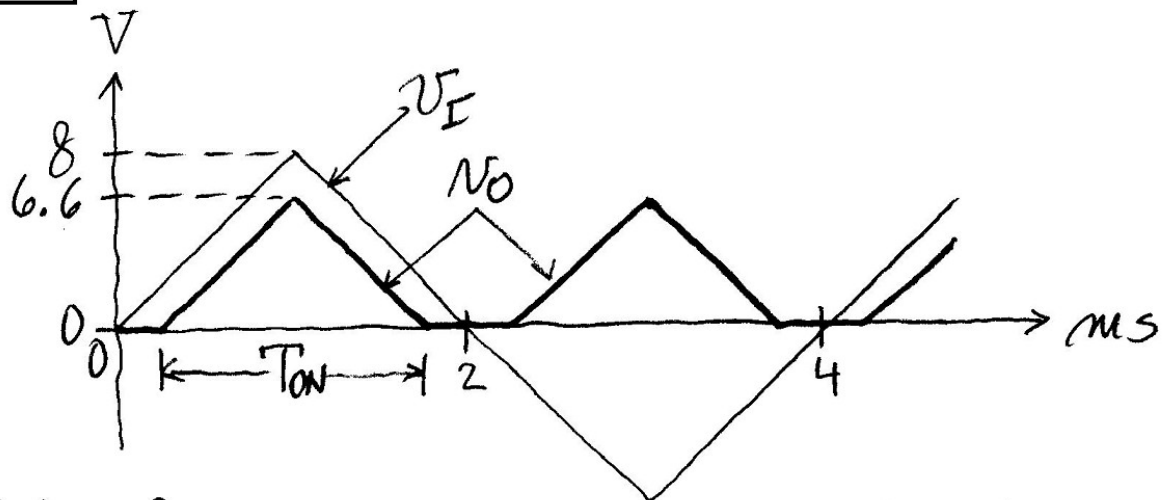

$$\frac{6.6}{T_{ON}} = \frac{8}{2} \Rightarrow T_{ON} = 1.65 \text{ ms} = 82.5\% \text{ of } T.$$

$$V_O(\text{avg}) = \frac{0.5 (1.65 \times 6.6)}{2} = 2.7225 \text{ V}.$$

Each diode conducts for $\frac{82.5}{2} = 41.75\%$.


Ideally, $V_O(\text{avg}) = 4\text{V}$, conduction = 50%.

1.57


(a)

$i_D (\mu A)$	$V_S (mV)$	$V_T (mV)$
1	520	520
4	556	558
10	580	584
20	598	606
40	616	632
100	640	680
200	658	738
400	676	836
500	682	882
800	694	1014
1000	700	1100


$$V_T = V_S + 400 i_D$$

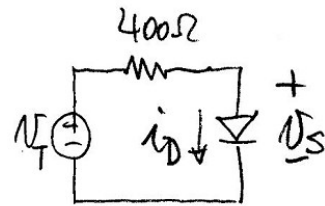

(b) $V_S (mV)$

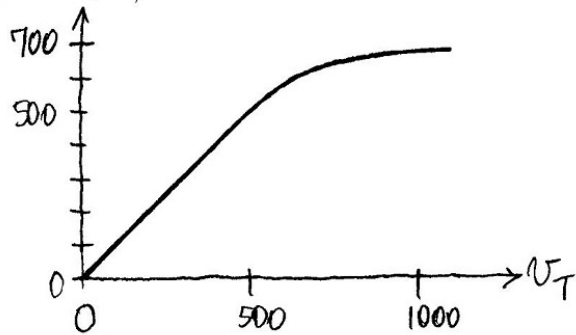

(c)


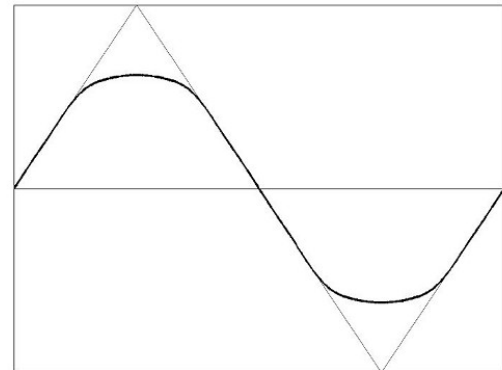


1.58 (a) Impose $I_{R_1} = I_{mA} + I_{R_2}$ at $V_T = V_{em} = 2.2\text{ V}$:

$$\frac{2.2 - 1.4}{R_1} = 1 + \frac{0.7}{R_2}. \text{ Moreover, } \frac{R_2}{R_1 + R_2} = \frac{1}{\sqrt{2}} \Rightarrow R_2 = \frac{R_1}{\sqrt{2} - 1},$$

or $R_2 = 2.41 R_1$. Substituting R_2 , we get

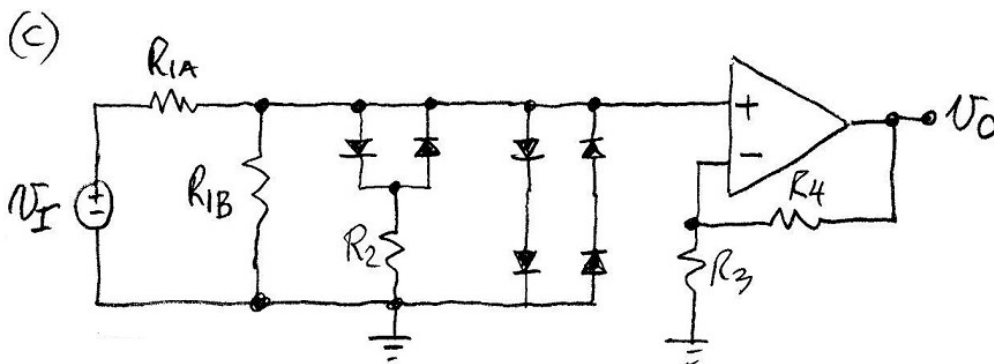
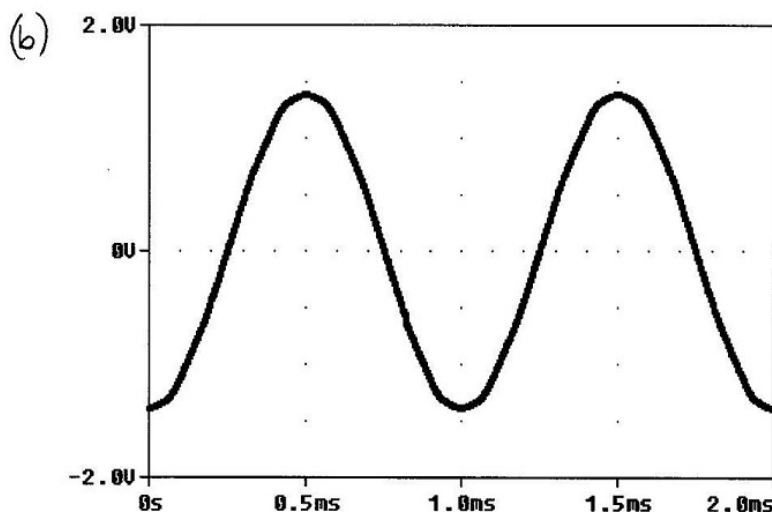
$$\frac{0.8}{R_1} = 1 + \frac{0.7}{2.41 R_1}, \text{ or } R_1 = 0.51\text{ k}\Omega, R_2 = 1.3\text{ k}\Omega.$$



Impose $R_{1A} // R_{1B} = 0.51\text{ k}\Omega$, or $\frac{1}{R_{1A}} + \frac{1}{R_{1B}} = \frac{1}{0.51}$, and $\frac{1}{1 + R_{1A}/R_{1B}} 5 = 2.2$, or $R_{1A}/R_{1B} = 1.27$. Eliminating R_{1A} , $1/(1.27 R_{1B}) + 1/R_{1B} = 1/0.51 \Rightarrow R_{1B} = 0.91\text{ k}\Omega, R_{1A} = 1.16\text{ k}\Omega$. Finally, $5 = (1 + R_4/R_3) 1.4 \Rightarrow R_4/R_3 = 2.57 \Rightarrow R_3 = 20\text{ k}\Omega, R_4 = 51\text{ k}\Omega$.

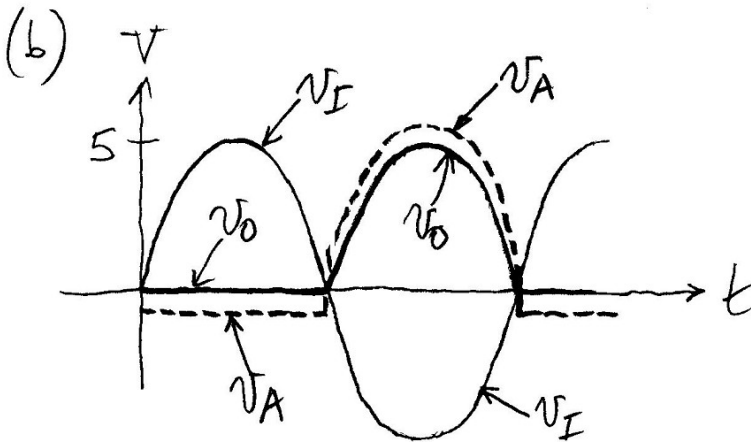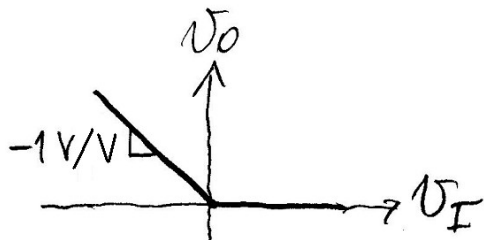1.59 (a) $v_I > 0 \Rightarrow D_1 = \text{ON}, D_2 = \text{OFF}, v_O = 0, v_A = -0.7 \text{ V}.$



$v_I < 0 \Rightarrow D_1 = \text{OFF}, D_2 = \text{ON}, v_O = (-R_2/R_1)v_I = -v_I,$
 $v_A = v_O + 0.7 \text{ V}$




1.60 (a) $V_N = V_P = 2.5V$; $V_E > 2.5V \Rightarrow D_1 = 0N, D_2 = OFF$,
 $V_O = 2.5V, V_A = 2.5 - 0.7 = 1.8V$

$V_E < 2.5V \Rightarrow D_1 = OFF, D_2 = 0N, V_O = V_N + R_2 I_{R2}$
 $= V_N + R_2 I_{R1} = V_N + R_2 (V_N - V_E)/R_1 = 5 - V_E$.

$$V_A = V_O + 0.7$$

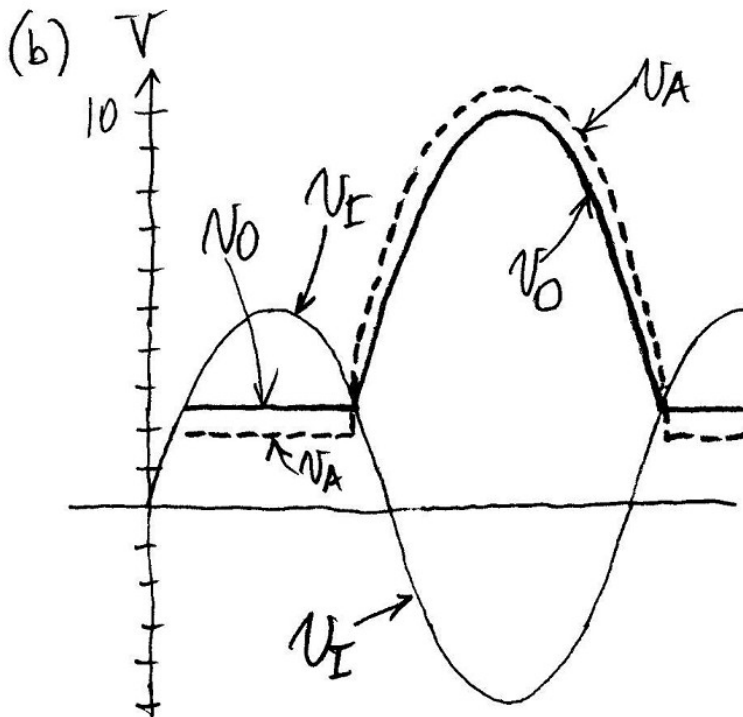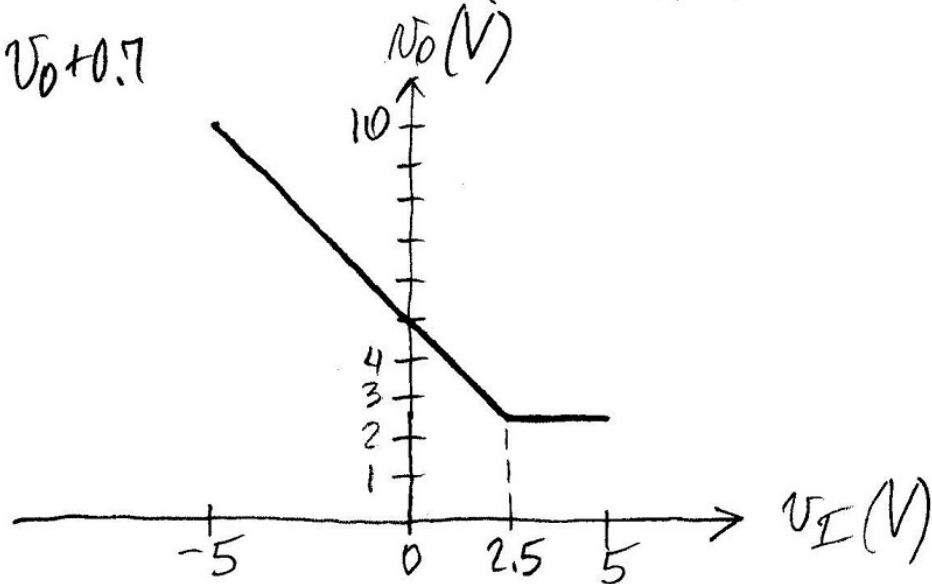

1.61

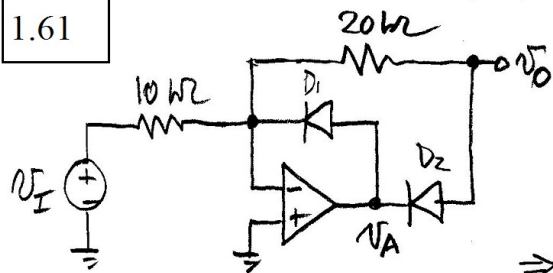

$$v_I > 0 \Rightarrow i_{10k\Omega} \rightarrow "$$



$$\Rightarrow D_1 = CO, D_2 = ON,$$

$$v_O = -(20/10)v_I = -2v_I$$

$$\Rightarrow v_{OA} = v_O - V_{D2(on)} = -2v_I - 0.7V.$$

$$v_I < 0 \Rightarrow i_{10k\Omega} \leftarrow " \Rightarrow D_1 = ON, D_2 = CO, i_{10k\Omega} = 0 \Rightarrow v_O = 0.$$
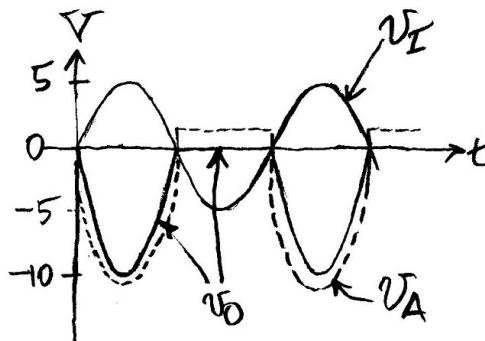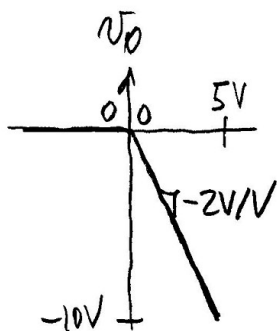
$$v_A = v_N + V_{D1(on)} = 0 + 0.7 = 0.7V.$$




1.62

[V, mA, kΩ]

1.63


$$v_I > 0 \Rightarrow D = OFF \Rightarrow i_{R_3} = 0 \Rightarrow v_{P1} = v_I;$$

$$v_I < 0 \Rightarrow D = ON \Rightarrow v_{N2} = v_{P2} = 0 \Rightarrow v_{P1} = 0 \Rightarrow v_O = (-R_2/R_1)v_I = -v_I, v_O > 0. \text{ In summary, } v_O = |v_I|.$$

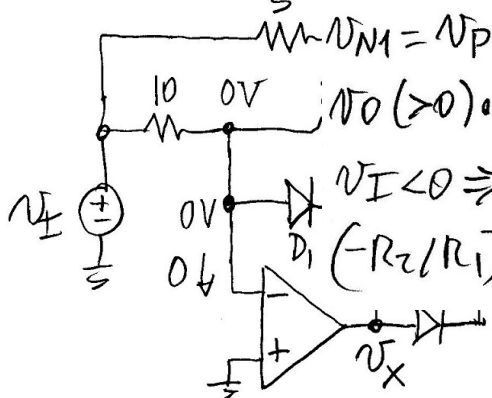


Inverting amp:

$$v_O = -\frac{20}{10}v_I = -2v_I.$$

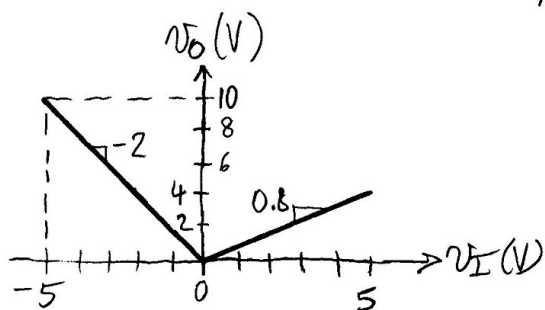

1.64

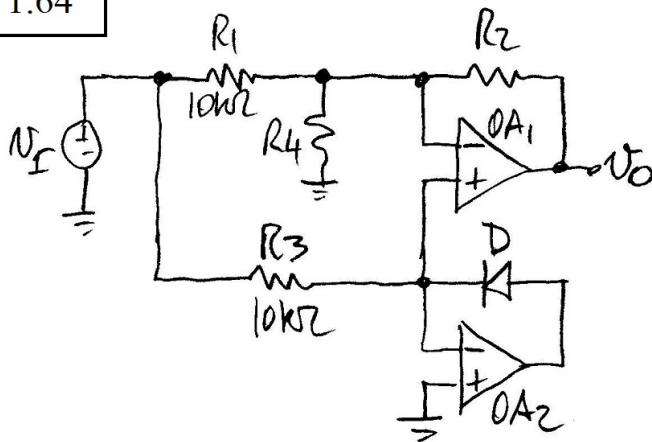

$V_I > 0 \Rightarrow D = \text{OFF} \Rightarrow i_{R3} = 0 \Rightarrow V_{P1} = V_I; V_{N1} = V_{P1} = V_I \Rightarrow i_{R1} = 0; V_0 = (1 + R_2/R_4)V_I, V_0 > 0.$


$V_I < 0 \Rightarrow D = \text{ON} \Rightarrow V_{N2} = V_{P2} = 0; V_{N1} = V_{P1} = V_{R2} = 0; i_{R4} = 0; V_0 = -(R_2/R_1)V_I, V_0 > 0.$

To achieve $V_0 = 2|V_I|$ we need $R_2/R_1 = 2 \Rightarrow R_2 = 20\text{k}\Omega$, and $(1 + R_2/R_4) = 2 \Rightarrow R_4 = R_2 = 20\text{k}\Omega$.

In summary, $R_1 = 10\text{k}\Omega, R_2 = 20\text{k}\Omega, R_3 = 10\text{k}\Omega, R_4 = 20\text{k}\Omega$.

1.65

(a)

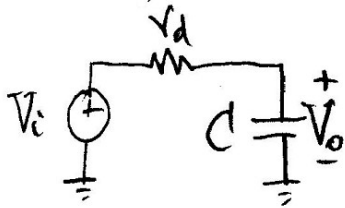

$$H = \frac{V_o}{V_i} = \frac{1/j\omega C}{r_d + 1/j\omega C} = \frac{1}{1 + j\omega/\omega_0}, \quad \omega_0 = \frac{1}{r_d C}$$

$$= \frac{1}{(V_T/I_C)C} = \frac{I_C}{V_T C}$$

$$(b) 10^5 = \frac{0.1}{26 \times C} \Rightarrow C = 38.5 \text{ nF}$$

$$(c) |H| = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}; |H|_{dB} = -6 \Rightarrow |H| = 10^{-6/20} = \frac{1}{2}$$

$$\frac{1}{2} = \frac{1}{[1 + (\frac{50 \times 10^3}{\omega_0})^2]^{1/2}} \Rightarrow \omega_0 = 28.9 \times 10^3 = \frac{I_D}{0.026 \times 38.5 \times 10^{-9}}$$


$$\Rightarrow I_D = 28.9 \mu A$$

$$(d) \angle H = -\tan^{-1} \frac{\omega}{\omega_0} \Rightarrow -30^\circ = \tan^{-1} \frac{500 \times 10^3}{\omega_0} \Rightarrow \omega_0 = 866 \text{ kr/s}$$

$$\Rightarrow I_D = 0.866 \text{ mA}$$

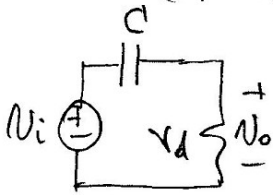1.66

$$(a) r_d = V_T / I_D, \quad H(j\omega) = \frac{r_d}{1/j\omega C + r_d} = \frac{j\omega r_d C}{1 + j\omega r_d C} = \frac{j\omega/\omega_0}{1 + j\omega/\omega_0},$$



$$\omega_0 = \frac{1}{r_d C} = \frac{I_D}{V_T C}$$

$$(b) I_D = 0.1 \text{ mA} \Rightarrow r_d = 260 \Omega \Rightarrow \omega_0 = \frac{1}{260 \times 33 \times 10^{-9}} = 116.6 \frac{\text{krad}}{\text{s}}.$$

$$(c) \omega/\omega_0 = 10^5 / (2 \times 116.6 \times 10^3) = 0.429;$$

$$\frac{j0.429}{1 + j0.429} = \frac{0.429}{\sqrt{1 + 0.429^2}} \angle 90^\circ - \tan^{-1} 0.429 = 0.394 \angle 66.8^\circ;$$

$$5 \text{ mV} \times 0.394 = 1.971 \text{ mV};$$

$$v_o(t) = (1.971 \text{ mV}) \cos(10^5 t + 66.8^\circ).$$

$$0.1 \text{ mA} = (1 \text{ mA})/10 \Rightarrow V_0 = 700 - 60 = 640 \text{ mV}.$$

$$(d) I_D = 50 \mu\text{A} = (1 \text{ mA})/(10 \times 2) \Rightarrow V_0 = 700 - 60 - 18 = 622 \text{ mV},$$


$$r_d = 520 \Omega, \quad \omega_0 = 58.275 \text{ krad/s}, \quad \omega/\omega_0 = 1.716,$$

$$H = 0.864 \angle 40.8^\circ$$

$$v_o(t) = (4.32 \text{ mV}) \cos(10^5 t + 40.8^\circ).$$

1.67

(a)

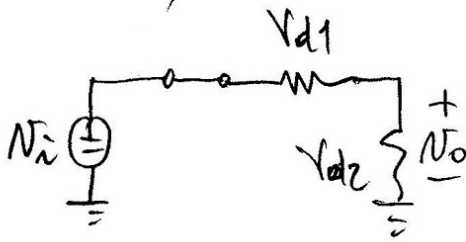

$$v_{d1} = V_T/I; \quad v_{d2} = V_T(I_{REF} - I).$$

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{v_{d2}}{v_{d1} + v_{d2}} = \frac{1}{1 + v_{d1}/v_{d2}} \\ &= \frac{1}{1 + (V_T/I) / [V_T/(I_{REF} - I)]} \end{aligned}$$

$$\frac{v_o}{v_i} = \frac{1}{1 + (I_{REF} - I)/I} = \frac{1}{1 + I_{REF}/I - 1} = \frac{I}{I_{REF}}.$$

(b) With $I_{REF} = 1 \text{ mA}$, $v_o/v_i = I/10^{-3} = 10^3 I$, I in A.

For $v_o/v_i = 1 \text{ V/V}$, use $I = 1 \text{ mA}$; $R_{eq} = v_{d1} + \infty = \infty$.

For $v_o/v_i = 0.75 \text{ V/V}$, use $I = 0.75 \text{ mA}$; $R_{eq} = v_{d1} + v_{d2} = 26/0.75 + 26/0.25 \approx 139 \Omega$.


For $v_o/v_i = 0.5 \text{ V/V}$, use $I = 0.5 \text{ mA}$; $R_{eq} = 52 + 52 = 104 \Omega$.

For $v_o/v_i = 0.25 \text{ V/V}$, use $I = 0.25 \text{ mA}$; $R_{eq} = 139 \Omega$.

For $v_o/v_i = 0$, use $I = 0$; $R_{eq} = \infty + v_{d2} = \infty$.

(c) $R_{eq} = v_{d1} + v_{d2} = V_T/I + V_T/(I_{REF} - I) = V_T / [(I_{REF} - I)I]$; this is minimized for $I = 0.5 \text{ mA}$, where $R_{eq} = 26/0.5 + 26/0.5 = 104 \Omega$. Impose $C \gg 1/(10^6 \times 104) = 9.6 \text{ nF}$. Use 100 nF .

1.68

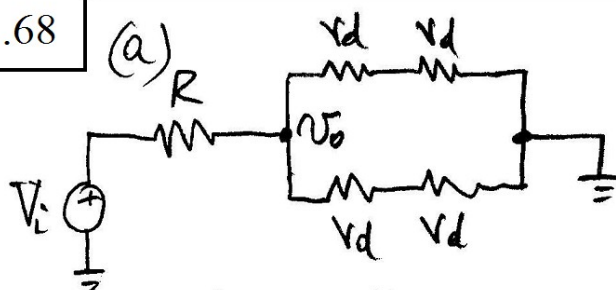

Since I splits evenly between the two halves,

$$r_d = \frac{V_T}{0.5I} = \frac{2V_T}{I}.$$


But, $r = (r_d + r_d) \parallel (r_d + r_d) = (2r_d) \parallel (2r_d) = r_d = \frac{2V_T}{I}.$

$$\frac{v_o}{v_i} = \frac{r}{R+r} = \frac{1}{1+R/r} = \frac{1}{1+R/(2V_T/I)} = \frac{1}{1+(R/2V_T)I}.$$

(b) Since $v_o = 2v_d$, $|v_d| \leq 5 \text{ mV} \Rightarrow |v_o| \leq 10 \text{ mV}.$

(c) Impose $\frac{10 \text{ mV}}{1 \text{ V}} = \frac{1}{1+(10^4/0.052)I} \Rightarrow I = 515 \mu\text{A}.$

1.69

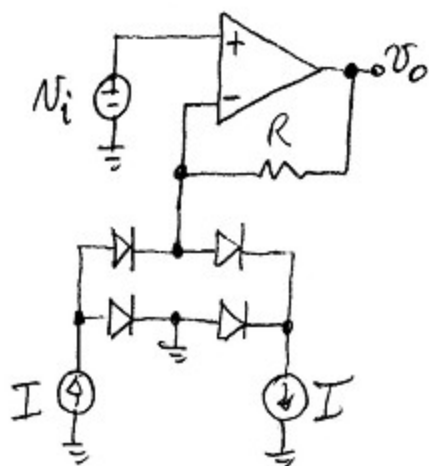

The diode bridge presents a net resistance towards ground of

$$r = (2r_d) \parallel (2r_d) = r_d, \text{ where } r_d = \frac{V_T}{I/2} = 2 \frac{V_T}{I}. \text{ Then,}$$


$$v_o = \left(1 + \frac{R}{r}\right) v_i = \left(1 + \frac{RI}{2V_T}\right) v_i$$

$$10 = 1 + \frac{R \times 0.5}{2 \times 26} \Rightarrow R = 936 \Omega.$$

(b) $v_o = (10 \text{ mV}) \left(1 + \frac{936 \times 1}{2 \times 26}\right) \cos \omega t = (190 \text{ mV}) \cos \omega t.$

$$v_o = (10 \text{ mV}) \left(1 + \frac{936 \times 0.1}{2 \times 26}\right) \cos \omega t = (28 \text{ mV}) \cos \omega t.$$

1.70

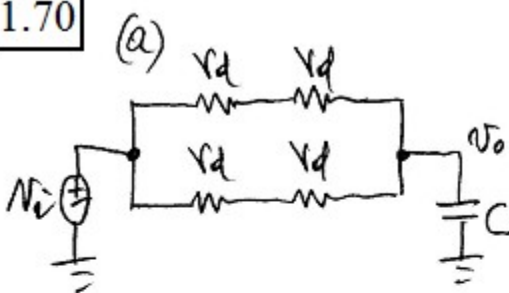

$$r = (r_d + r_d) // (r_d + r_d) = r_d$$

$$= V_T / 0.5 I_S = 2 V_T / I_S.$$

(b) $H = \frac{1}{1 + j\omega/\omega_0}$, $\omega_0 = \frac{1}{rC} =$

$$I_S / (2 V_T C). \quad (c) 10^6 = 0.1 / (2 \times 26 \times C) \Rightarrow C = 1.92 \text{ mF}.$$

(d) $I_S = 1 \text{ mA} \Rightarrow \omega_0 = 10^7 \text{ rad/s} \Rightarrow$

$$H = \frac{1}{1 + j1/10} = \frac{1}{1 + j0.1} = 0.995 \angle -5.7^\circ.$$

$$v_o = (9.95 \text{ mV}) \cos(10^6 t - 5.7^\circ).$$



$I_S = 0.01 \text{ mA} \Rightarrow \omega_0 = 0.1 \times 10^6 \text{ rad/s} \Rightarrow$

$$H = \frac{1}{1 + j10/1} = 0.0995 \angle -84.3^\circ.$$

$$v_o = (0.995 \text{ mV}) \cos(10^6 t - 84.3^\circ).$$

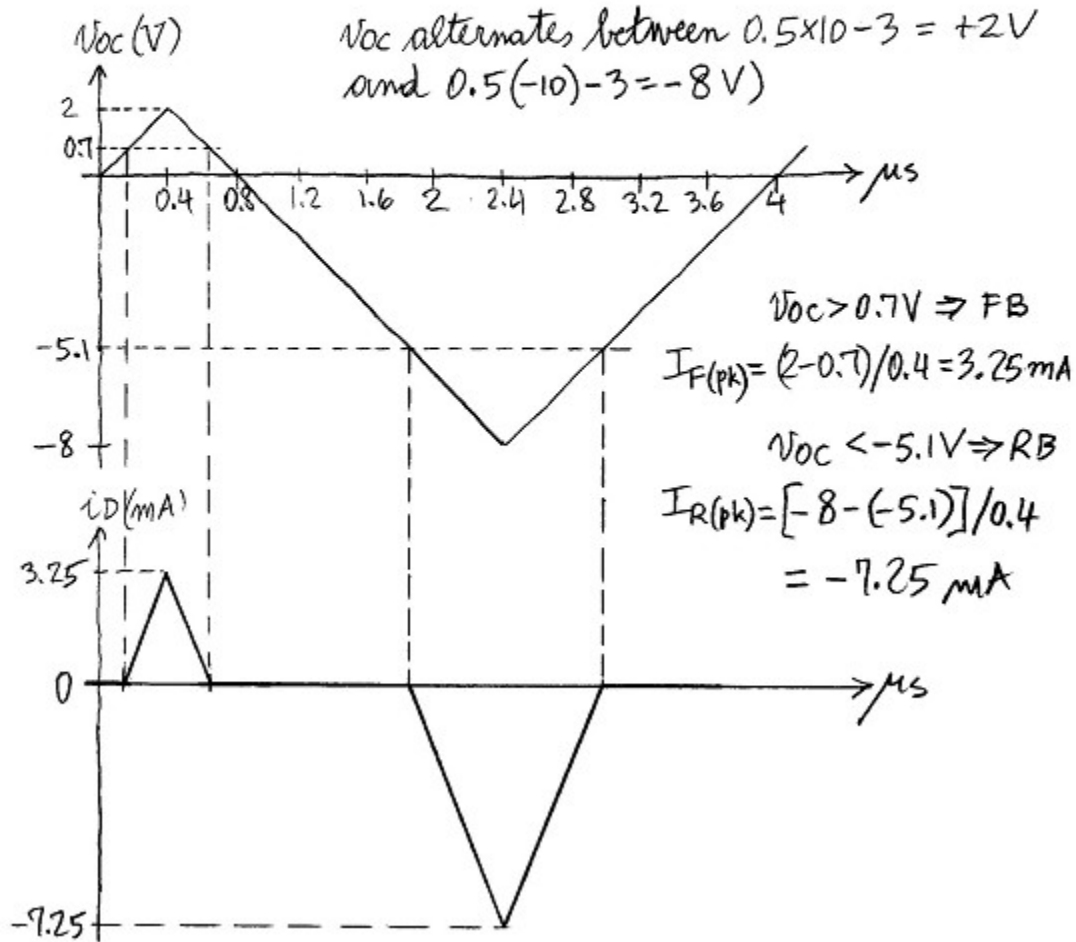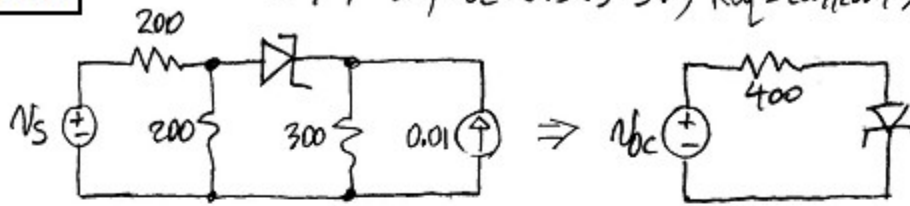1.71


$$[V, A, \Omega]; V_{oc} = 0.5V_S - 3V; R_{eq} = 200/200 + 300 = 400\Omega$$




1.72

[V, mA, μ R].


Apply Thévenin to the circuit

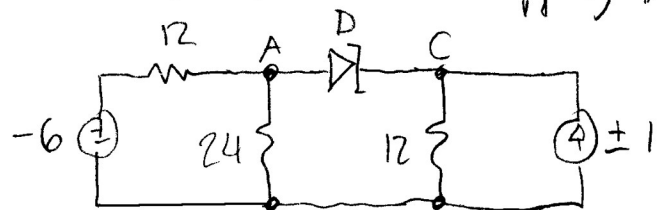

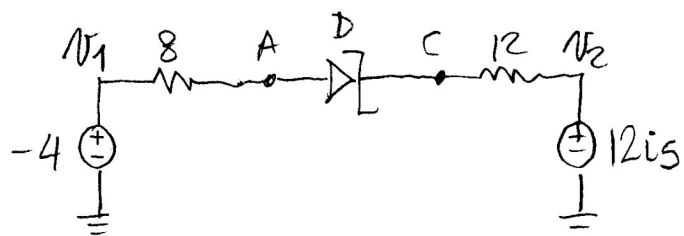left of A, a source transformation to the circuit right of C.



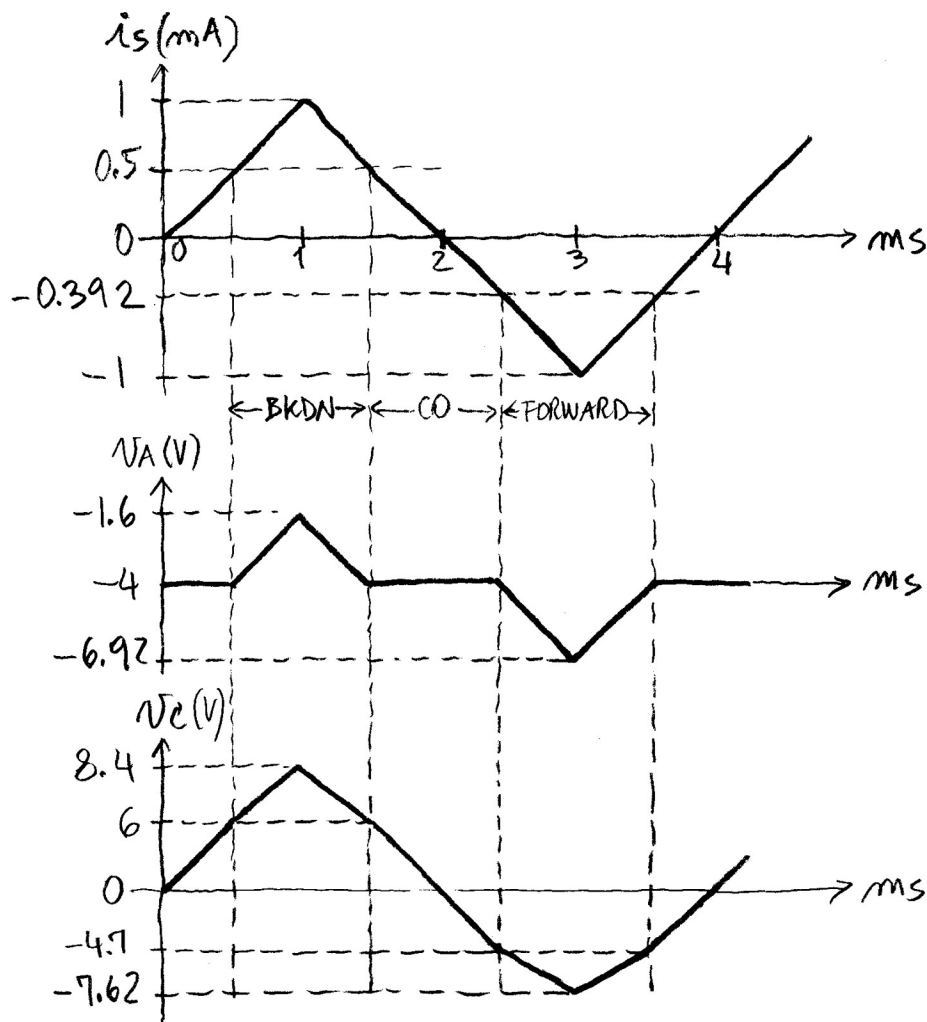$D = \text{OFF}$ for $(-4 - 0.7)V < v_2 < 6V$, or $(-4.7/12) < i_s < (6/2)$,
or $-0.392 \text{ mA} < i_s < 0.5 \text{ mA}$.



1.72 cont.d

$$D = CO \Rightarrow V_A = -4V, V_C = V_2 = 12 \text{ V}.$$

$$D = \text{Bk DN: } V_A = -4 + 8[(V_2 - 10 - (-4))/(8+12)] = -6.4 + 4.8 \text{ V},$$


$$V_C = V_A + 10 \text{ V}. V_A(1 \text{ ms}) = -1.6 \text{ V}, V_C(1 \text{ ms}) = 8.4 \text{ V}.$$

$$D = \text{FORWARD: } V_C = -4 - 8[(-4 - 0.7 - 12 \text{ V})/20] = -2.12 + 4.8 \text{ V}.$$

$$V_C = V_A - 0.7 \text{ V}. V_A(3 \text{ ms}) = -2.12 - 4.8 = -6.92 \text{ V}; V_C(3 \text{ ms}) = -6.92 - 0.7 = -7.62 \text{ V}.$$

1.73

(a) $[V, \Omega, A]$:

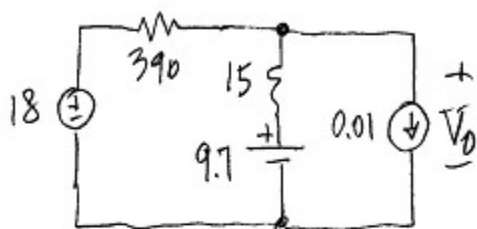

$$V_Z = \frac{10.0 - 9.85}{(20 - 10) \times 10^{-3}} = 15 \Omega$$

$$V_{Z0} = 10.0 - 15 \times 20 \times 10^{-3} = 9.7 \text{ V}.$$

$$V_0 = \frac{15}{390 + 15} 18 + \frac{390}{390 + 15} 9.7 - \frac{390 \times 15}{390 + 15} 0.01 = 9.863 \text{ V}.$$

(b) V_0 is minimized (maximized) when V_Z , V_{Z0} , and V_Z are minimized (maximized), and R and I_L are maximized (minimized).

$$V_{0(\min)} \cong \frac{(0.9 \times 15)(0.9 \times 18) + (1.1 \times 390)(0.9 \times 9.7) - (390 \times 15)(1.1 \times 0.01)}{(1.1 \times 390) + (0.9 \times 15)} \cong 8.9 \text{ V}$$

$$V_{0(\max)} \cong \frac{(1.1 \times 15)(1.1 \times 18) + (0.9 \times 390)(1.1 \times 9.7) - (390 \times 15)(0.9 \times 0.01)}{(0.9 \times 390) + (1.1 \times 15)} \cong 11.0 \text{ V}$$

1.74

$$V_{Z0} = 12 - 0.012 \times 25 = 11.7 \text{ V};$$

$$V_Z(4 \text{ mA}) = 11.7 + 0.012 \times 4 = 11.75 \text{ V}.$$

$$(a) R \leq [(24 - 6) - 11.75] / [11.75/3 + 8 + 4] = 390 \Omega.$$

$$(b) \text{line reg} = \frac{12/3000}{390 + 12/3000} \approx 31 \text{ mV/V}$$

$$\text{load reg} = -370 // 12 // 3000 \approx -11.6 \text{ mV/mA}.$$

$$(c) V_{O(\min)} = \frac{12(24 - 6) + 390 \times 11.7 - (390 \times 12)(12/3 + 8) \times 10^{-3}}{390 + 12}$$

$$= 11.75 \text{ V}$$

$$V_{O(\max)} = \frac{12(24 + 6) + 390 \times 11.7 - (390 \times 12)(12/3) \times 10^{-3}}{390 + 12}$$

$$= 12.2 \text{ V. Total variation is } < 4\%.$$

1.75

$$(a) V_{Z0} = 6.2 - 10 \times 0.020 = 6.0 \text{ V.}$$

$$R \leq \frac{(15-3)-6}{3+4+6/2} = 600 \Omega (\text{use } 580 \Omega, 5\%).$$

$$(b) \text{ Line regulation} = \frac{10//2500}{580 + (10//2500)} \approx 16.9 \text{ mV/V}$$

$$(c) \text{ Load regulation} = + (580//10//2500) \approx +9.78 \text{ mV/mA}$$

(positive because an increase in I_L increases V_O (which is negative)).

(d) V_O (which is negative) is maximized (minimized) when $V_I = -12 \text{ V} (-18 \text{ V})$, $R_L = 2 \text{ k}\Omega$ ($3 \text{ k}\Omega$), and $I_L = 4 \text{ mA}$ (0 mA). Using superposition:

$$V_{O(\max)} = (-12) \frac{10//2000}{580 + (10//2000)} + (-6) \frac{580//2000}{10 + (580//2000)} + (580//10//2000) 0.004$$

$$= -0.202 - 5.869 + 0.039 = -6.032 \text{ V}$$

$$V_{O(\min)} = (-18) \frac{10//3000}{580 + (10//3000)} + (-6) \frac{580//3000}{10 + (580//3000)} + 0$$

$$= -0.304 - 5.879 + 0 = -6.183 \text{ V.}$$

1.76


$$(a) R = \frac{12-6.9}{3+2} = 1.0 \text{ k}\Omega.$$

$$(b) r_d = 26/3 = 8.7 \Omega; r = r_d + r_z = 16.7 \Omega.$$

$$\text{Line regulation} = \frac{16.7}{16.7 + 1000} = 16.4 \text{ mV/V.}$$


$$\text{Load regulation} = - (1000//16.7) = -16.4 \text{ mV/mA.}$$

1.77

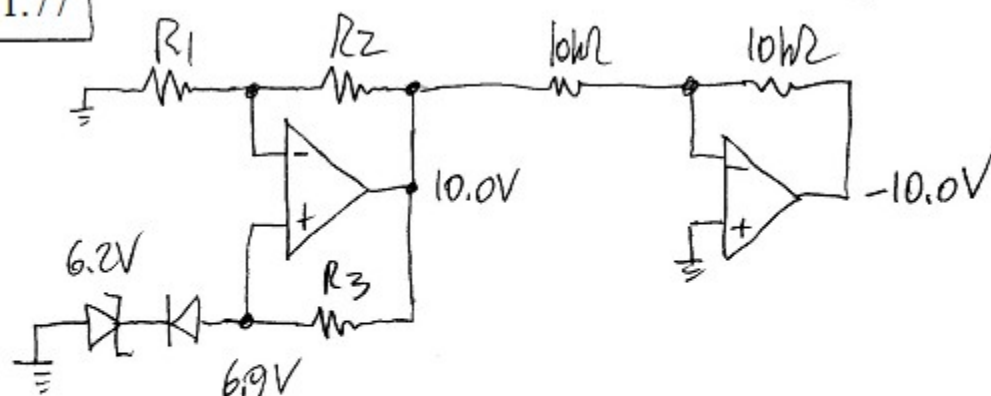

$$R_3 = (10 - 6.9)/3 = 620 \Omega; 10 = (1 + R_2/R_1)6.9 \Rightarrow R_2/R_1 = 0.45. \text{ Use } R_1 = 6.8k\Omega, R_2 = 3.0k\Omega$$


1.78

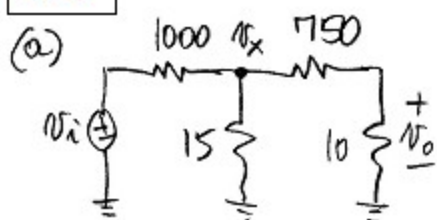

$$v_o = \frac{10}{750+10} v_x = \frac{1}{76} v_x$$

$$v_x = \frac{15 \parallel (750+10)}{1000 + (15 \parallel 760)} v_i = \frac{1}{70} v_i$$
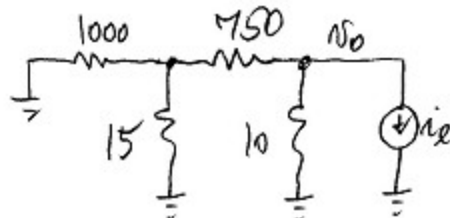
$$\text{Line reg} = \frac{1}{76 \times 70} = 0.19 \text{ mV/V!}$$



$$v_o = -i_e \left\{ 10 \parallel [750 + (1000 \parallel 15)] \right\}$$

$$\text{Load reg} = -9.87 \text{ mV/mA}$$

(b) $\frac{v_o}{v_i} = \frac{10}{1750+10} = \frac{1}{176} \Rightarrow \text{line reg} = \frac{1}{176} = 5.68 \text{ mV/V, quite an increase!}$

Load reg = $-10/1750 \approx -10 \text{ mV/mA}$ (about the same as with D_1 in place.)

1.79

$$(a) V_{Z1}(\min) = 14.7 + 15 \times 0.005 = 14.8 \text{ V}$$

$$V_{Z2}(\min) = 9.8 + 10 \times 0.005 = 9.85 \text{ V.}$$



$$R_2 \leq \frac{14.8 - 9.85}{5 + 10} = 330 \Omega; R_1 \leq \frac{(30 - 5) - 14.8}{5 + 5 + 10} = 510 \Omega.$$

$$\text{Line reg} \approx \frac{10}{340} \times \frac{15}{525} = 0.84 \text{ mV/V.}$$

$$\text{Load reg} \approx -10 // 345 = -9.7 \text{ mA/mV.}$$



1.80

(a) When $D_1 = D_2 = \text{OFF}$, $V_O = [10/(10+20)]V_I = (1/3)V_I$.
 Either diode goes on for $|V_I - V_O| = 4.3 + 0.7 = 5\text{V}$, or for
 $|V_I - V_I/3| = 5 \Rightarrow V_I = \pm 7.5\text{V}$. For $|V_I| > 7.5\text{V}$ we
 have $V_O = V_I - 5$ for $V_I > 7.5$, $V_O = V_I + 5$ for $V_I < -7.5$.

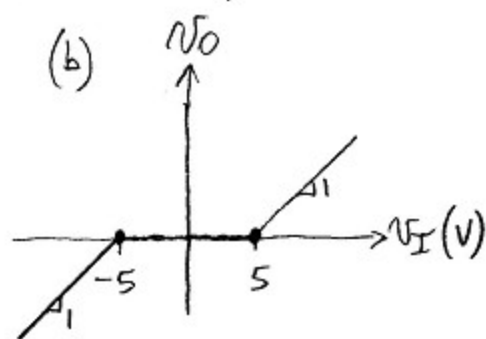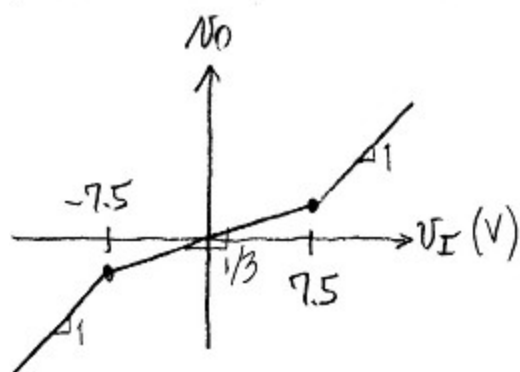



With the $20\text{-k}\Omega$ resistance removed, $V_O = 0$ for $|V_I| \leq 5\text{V}$,
 $V_O = V_I - 5$ for $V_I > 5$, and $V_O = V_I + 5$ for $V_I < -5\text{V}$.

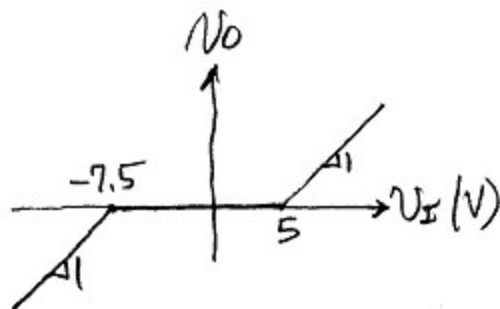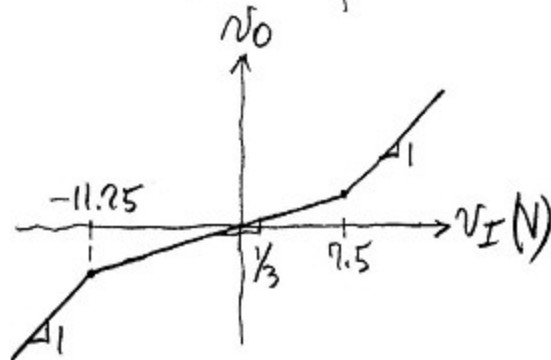(c) With $V_{Z1} = 6.8\text{V}$, the location of the breakpoint
 on the negative V_I -axis changes from -5V to -7.5V
 V in (b), and from -7.5V to $(3/2)(-7.5) = -11.25\text{V}$ in (b).





1.81

(a)

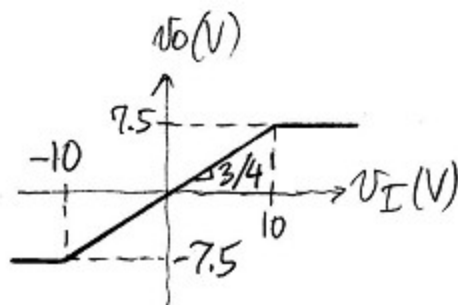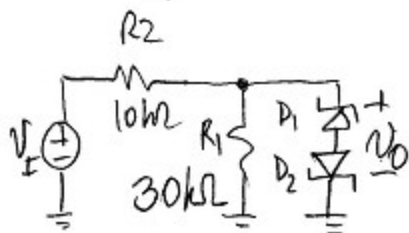



As long as both diodes are off, $v_O = (3/4)v_I$. When diodes go on, they clamp v_O at $\pm (V_Z + V_D) = \pm (6.8 + 0.7) = \pm 7.5$ V. Clamping occurs for $|v_I| \geq \frac{4}{3} \times 7.5 = 10$ V.

(b)

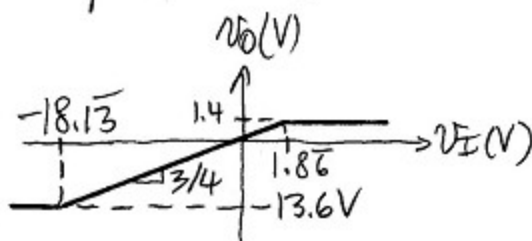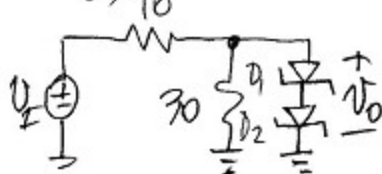


Now v_O is clamped at $+2V_D = 1.4$ V, and at $-2V_Z = -13.6$ V. Positive clamping occurs for $v_I \geq \frac{4}{3} \times 1.4 = 1.86$ V, and negative clamping for $v_I \leq -\frac{4}{3} \times 13.6 = -18.13$ V.

(c)

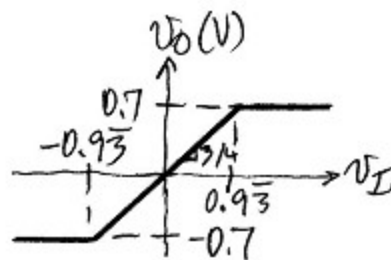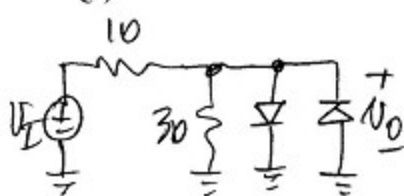

Now v_O is clamped at ± 0.7 V, and clamping occurs for $|v_I| > \frac{4}{3} \times 0.7 = 0.93$ V.


1.82

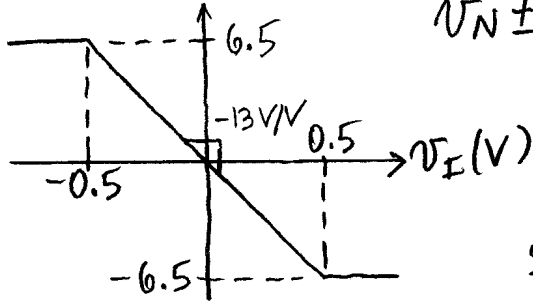(a) $v_o(V)$ 

When diodes go on, v_o is clamped at $v_N \pm (V_Z + 2V_D(on)) = 0 \pm (5.1 + 1.4) = \pm 6.5V$

When diodes are off, gain is $-13/1 = -13 V/V$. Clamping starts when $v_i = \pm \frac{6.5}{13} = \pm 0.5 V$.

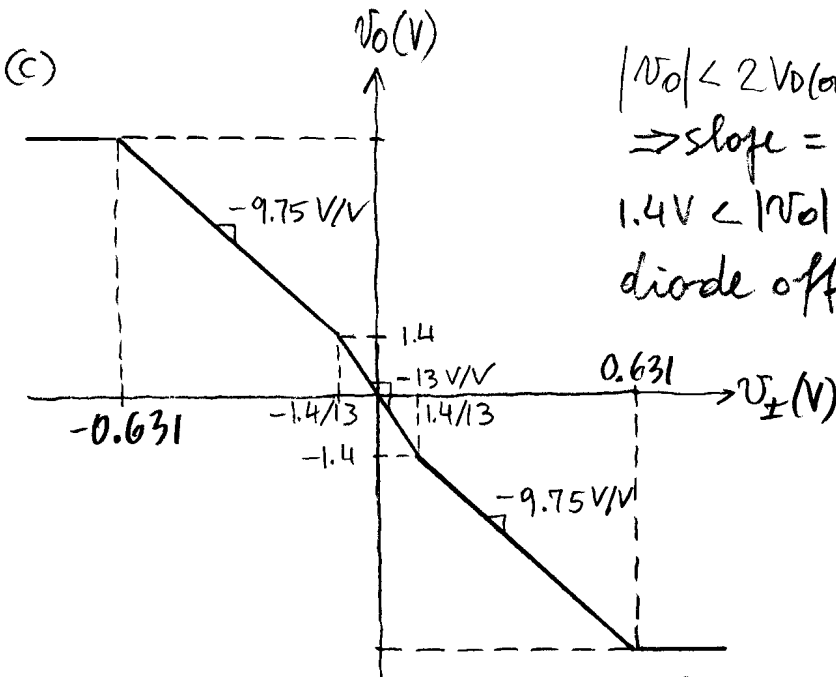(b) Slope is still $-13 V/V$, but output clamping occurs at $v_o = \pm 3V_D(on) = \pm 2.1V$ instead of $\pm 6.5V$.



$|v_o| < 2V_D(on) = 1.4V \Rightarrow$ diodes off \Rightarrow slope $= -13 V/V$


$1.4V < |v_o| < 6.5V \Rightarrow$ Zener diode off \Rightarrow slope $=$

$$-\frac{R_2 \parallel R_3}{R_1}$$

$$= -13/39$$

$$= -9.75 V/V.$$

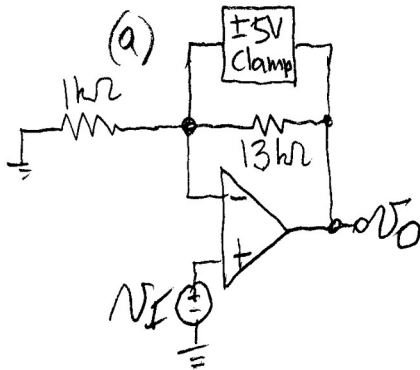v_o reaches $\pm 6.5V$ for $v_i = \pm \left(\frac{1.4}{13} + \frac{6.5 - 1.4}{9.75} \right) = \pm 0.631 V$




When diodes are off, we have

$$V_O = \left(1 + \frac{13}{1}\right) V_I = 14 V_I.$$

Clamping occurs for $|V_O - V_I| = |V_O - V_I| = V_Z + 2V_{D(on)}$

$$= 5.1 + 1.4 = 6.5 \text{ V. This occurs}$$

for $|14V_I - V_I| = 6.5$, or $V_I = \pm 0.5 \text{ V}$. For $|V_I| > 0.5 \text{ V}$, we have $V_O = V_I - 7$ for $V_I > 0.5$, $V_O = V_I + 7$ for $V_I < -0.5$.

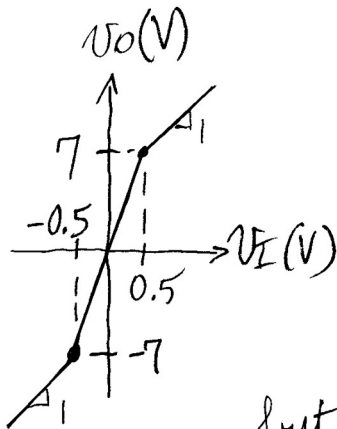

(b) We still have $V_O = 14V_I$,

but only for $|V_O - V_I| \leq 2V_{D(on)}$

$$= 1.4 \text{ V, or for } |V_I| \leq \frac{1.4}{13} \text{ V} =$$


$$0.1077 \text{ V. Once the diode}$$

bridge starts conducting,

but D_Z is still off, slope changes to

$1 + (13/39) = 10.75 \text{ V/V}$. Once D_Z goes on, slope = 1 V/V .

D_Z goes on for $|V_I| = 0.5 \text{ V}$.

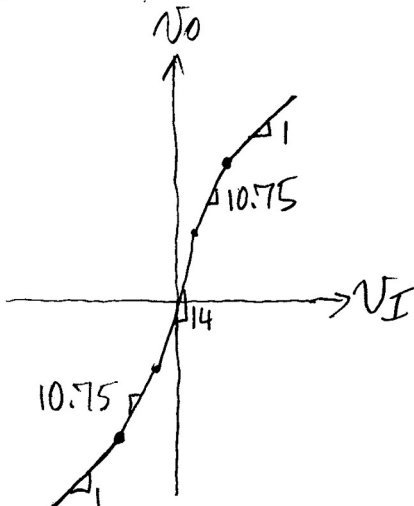

1.84

$$(a) V_p = 24\sqrt{2} \approx 34 \text{ V}; C = \frac{V_p}{2fRV_r} = \frac{34}{2 \times 60 \times 10^3 \times 2} \approx 142 \mu\text{F}.$$

$$(b) V_0 = V_p - V_{D(\text{on})} - \frac{1}{2}V_r \approx 34 - 0.8 - 2/1 = 32.2 \text{ V}.$$

$$i_{D(\text{max})} = \frac{34}{1} \left(1 + 2\pi \sqrt{34 / (2 \times 2)} \right) = 657 \text{ mA}.$$

$$i_{D(\text{avg})} \approx \frac{1}{2} 657 \approx 330 \text{ mA}. T_{\text{ON}} \approx \frac{1}{2\pi 60} \sqrt{2 \frac{2}{34}} \approx 0.91 \text{ ms}$$

$$(5.5\%). \text{ PIV} = 2V_p \approx 68 \text{ V (Use 100 V to be safe).}$$

(c) Circuit becomes a 1/2-wave rectifier.

$$V_r \approx 2 \times 2 = 4 \text{ V}; V_0 \approx 34 - 0.8 - \frac{1}{2} 4 = 31.2 \text{ V}$$

$$i_{D(\text{max})} \approx \frac{34}{1} \left(1 + 2\pi \sqrt{2 \times 34 / 4} \right) \approx 915 \text{ mA (an increase}$$

by approx $(\sqrt{2}-1)$, or 41%). $i_{D(\text{avg})}$ and T_{ON} also increase by approx 41%. PIV remains the same.

1.85 (a) $V_p = 18\sqrt{2} = 25.5V$, $I_L = 10mA$

$$C = \frac{I_L}{2fV_r} = \frac{10 \times 10^{-3}}{2 \times 60 \times 1.5} = 56\mu F.$$

(b) $V_o = 25.5 - 2 \times 0.8 - 1.5/2 = 23.2V$

$$i_D(\max) = 10 \left(1 + 2\pi \sqrt{\frac{25.5}{2 \times 1.5}} \right) = 193mA$$

$$i_D(\text{avg}) \approx 100mA$$

$$T_{ON} = \frac{1}{2\pi 60} \sqrt{\frac{2 \times 1.5}{25.5}} = 0.91ms = 5.5\% \text{ of } T.$$

$$PIV \approx V_p \approx 25V \text{ (use } 40V \text{ for safety).}$$

(c) If D_4 becomes an open, D_1 will never go on.

Only D_2 and D_3 will conduct during the negative alternations of v_s , in effect resulting in half-wave rectification, but with two diode drops. So, V_r doubles to $2 \times 1.5 = 3V$; $V_o = 25.5 - 2 \times 0.8 - 3/2 = 22.4V$.


$i_D(\max) \approx 10 \left(1 + 2\pi \sqrt{\frac{2 \times 25.5}{3}} \right) \approx 270mA$ (an increase by approximately $(\sqrt{2} - 1)$, or 41%). A similar increase affects $i_D(\text{avg})$. The conduction interval of D_2 & D_3 is

$$T_{ON} = \frac{1}{2\pi 60} \sqrt{2 \times 3 / 25.5} = 1.29ms \text{ (41\% increase).}$$

$$PIV = \frac{1}{2} V_p \approx 13V \text{ (specify } 20V \text{ for safety).}$$

1.86

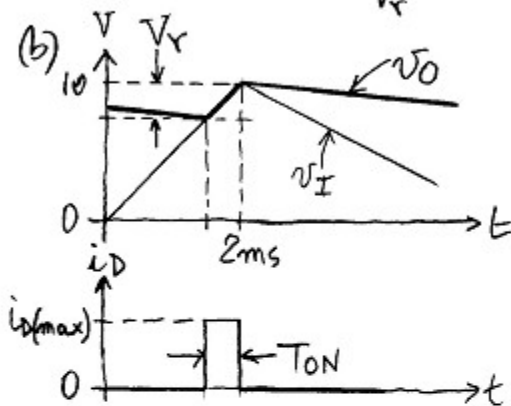(a) $V_0 = V_m - V_{D(on)} - \frac{1}{2} V_r = 10 - 0.7 - \frac{0.5}{2} \approx 9 \text{ V}$. $T_{OFF} \approx T = 6 \text{ ms}$. $C \approx \frac{I_{total} \cdot T_{OFF}}{V_r} \approx \frac{(10 + 9/1) 10^{-3} \times 6 \times 10^{-3}}{0.5} \approx 230 \text{ } \mu\text{F}$.



Proportionality:

$$\frac{V_r}{T_{ON}} = \frac{V_m}{2 \text{ ms}} \Rightarrow T_{ON} = 2 \frac{V_r}{V_m} = 2 \frac{0.5}{10} = 0.1 \text{ ms} \quad (T_{ON} \ll T_{OFF} \approx T)$$

(c) $V_0 \approx 9 \text{ V}$; $i_{D(avg)} = i_{D(max)} = C \frac{V_r}{T_{ON}} = 230 \times 10^{-6} \frac{0.5}{0.1 \times 10^{-3}} \approx 1.15 \text{ A (!)}$. $\text{PIV} = 2V_m = 20 \text{ V}$ (Use 30 V).

doubles to $2 \times 1.5 = 3 \text{ V}$; $V_0 = 25.5 - 2 \times 0.8 - 3/2 = 22.4 \text{ V}$.


$i_{D(max)} \approx 10 \left(1 + 2\pi \sqrt{\frac{2 \times 25.5}{3}} \right) \approx 270 \text{ mA}$ (an increase by approximately $(\sqrt{2} - 1)$, or 41%). A similar increase affects $i_{D(avg)}$. The conduction interval of D_2 & D_3 is

$T_{ON} = \frac{1}{2\pi 60} \sqrt{2 \times 3 / 25.5} = 1.29 \text{ ms}$ (41% increase).

$\text{PIV} = \frac{1}{2} V_p \sim 13 \text{ V}$ (specify 20 V for safety).

1.87

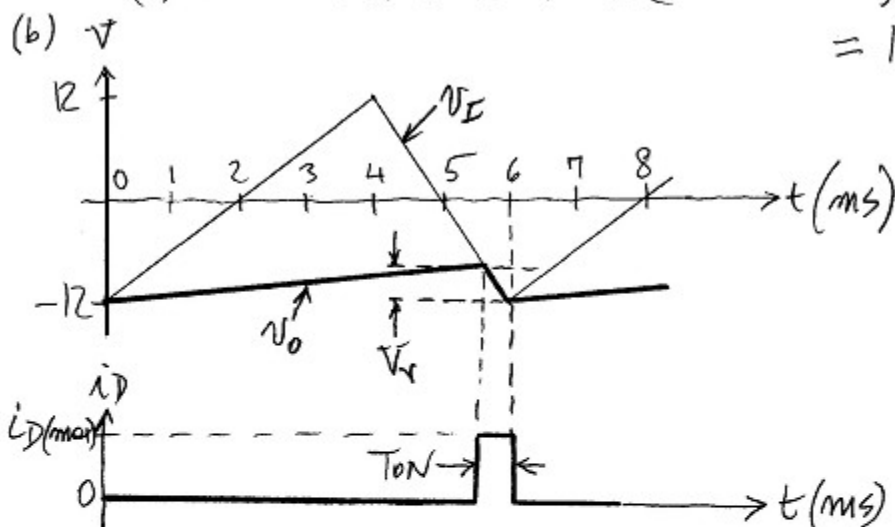(a) $CV_r \approx I_L T_{off} \approx I_L T \Rightarrow C \approx (10 \times 10^{-3} \times 6 \times 10^{-6}) / 0.5$
 $= 120 \mu\text{F}.$



(c) $V_O \approx -12 + 0.85 + 0.5/2 = -10.9 \text{ V}.$

$i_D(\text{avg}) = i_D(\text{max}) = C \frac{dv_O}{dt} = 120 \times 10^{-6} \frac{12}{1 \times 10^{-3}} = 1.44 \text{ A}$

Proportionality:


$V_r / T_{ON} = V_m / t_{ms} \Rightarrow T_{ON} = \frac{V_r}{V_m} t_{ms} = \frac{0.5}{12} 10^{-3} \approx 42 \mu\text{s} (0.7\%).$

$\text{PIV} = 2V_p = 24 \text{ V (use 40 V to be safe).}$

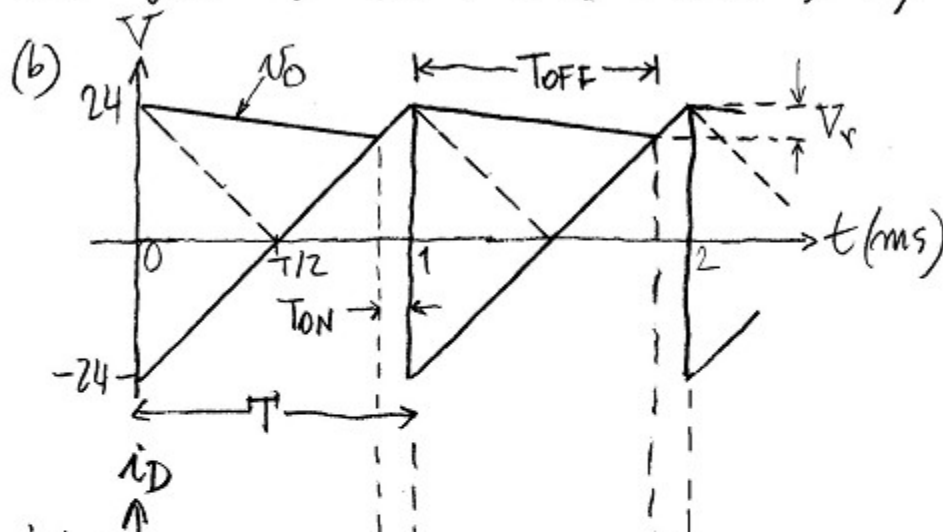
1.88

$$(a) V_0 = 24 - 2 \times 0.95 - \frac{1}{2} \times 1 = 22 \text{ V}; I = 22/2 = 11 \text{ mA}.$$

$$CV_r = I_0 T_{\text{OFF}} \cong I_0 T = I_0/4 \Rightarrow C = (11 \times 10^{-3}) / (10^3 \times 1) = 11 \text{ nF}.$$



1.89

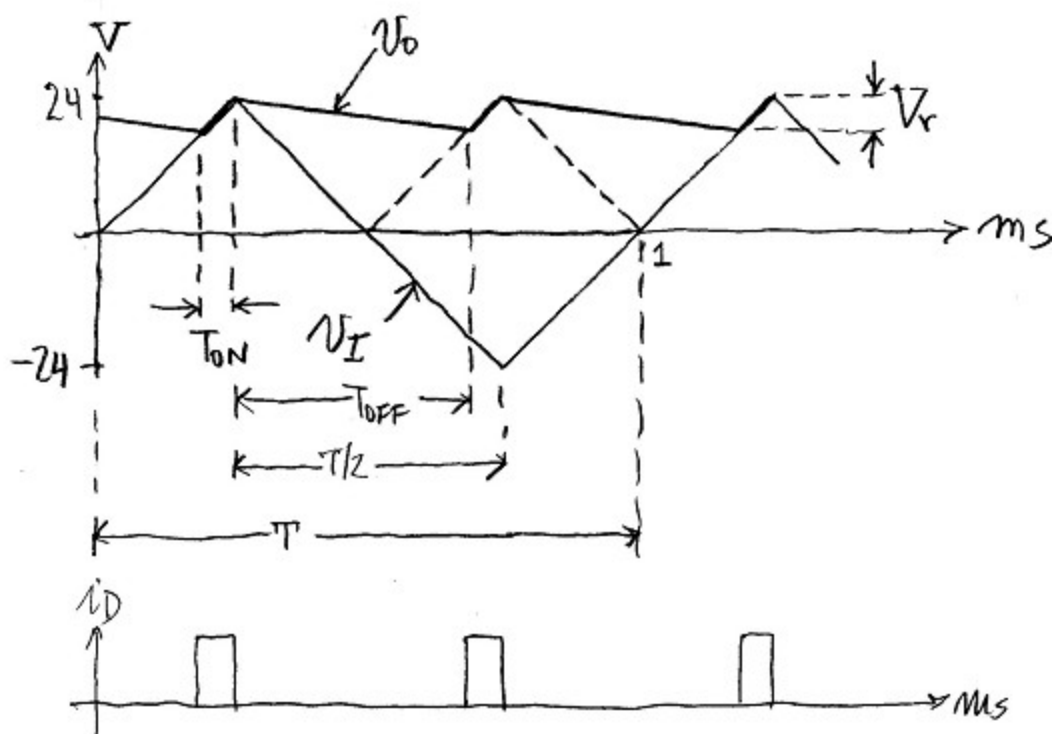

$$V_0 = 24 - 2 \times 0.75 - \frac{1}{2} \times 1 = 22 \text{ V}; I_0 = 22/2 = 11 \text{ mA}.$$

$$CV_r = I_0 T_{\text{OFF}} \cong I_0 T/2 = I_0/(2f) \Rightarrow C \cong 11 \times 10^{-3} / (2 \times 10^3 \times 1) = 5.5 \text{ nF}.$$


$$T_{\text{ON}} = (1/24)(T/4) = (1/24)(10^{-3}/4) \cong 10.4 \text{ ns}$$

$$i_D(\text{avg}) = i_D(\text{max}) = C \frac{V_r}{T_{\text{ON}}} + I_0 = (5.5 \times 10^{-6}) \frac{1}{10.4 \times 10^{-6}} + 11 \times 10^{-3}$$

$$= 540 \text{ mA}. \text{ PIV} = 24 \text{ V (make 35V to be safe).}$$

1.90

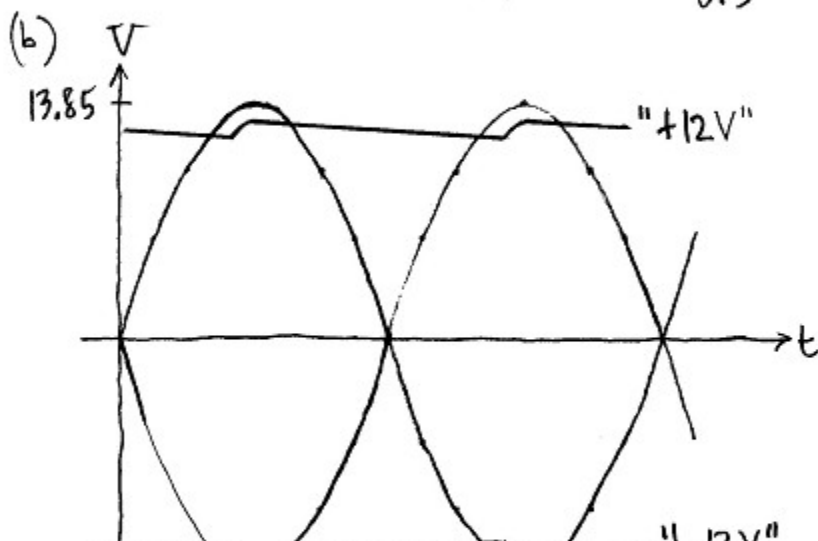(a) We want $12 = V_p - 2 \times 0.8 - 0.5/2 \Rightarrow V_p = 13.85 \text{ V}$
 $2V_p = 27.7 \text{ V}$. $C_1 = C_2 = \frac{I_L \times T_{\text{OFF}}}{V_r} = \frac{0.1 \times 1/(2 \times 60)}{0.5} = 1.67 \text{ mF}$.



1.91

(a) let $V_p \approx 25 \text{ V}$. Then, $n = 25/(120 \times \sqrt{2}) = 0.1493$.
 Pick $n = 0.15$ (easier number). Then, $V_p = 0.15 \times 120 \sqrt{2} = 25.5 \text{ V}$.
 let $V_r = 2 \text{ V}$. Then, $V_{I(\text{min})} = 25.5 - 0.8 - 2 = 22.7 \text{ V}$.
 $V_{Z0} = 15 - 0.01 \times 25 = 14.75 \text{ V}$. let $I_{Z(\text{min})} = 5 \text{ mA}$. Then,

$$R \leq \frac{22.7 - 15}{5 + 25} = 253 \Omega. \text{ Use } 240 \Omega \text{ to be safe.}$$

During capacitor discharge, $I_C \sim I_R = \frac{22.7 + 2/2 - 15}{0.240} \approx 36 \text{ mA}$.
 $C V_r \approx I_R T_{\text{OFF}} \approx I_R T \Rightarrow C \approx [36 \times 10^{-3} / 60] / 2$

$$= 300 \mu\text{F}. \text{ In summary, } n = 0.15, R = 240 \Omega, C = 300 \mu\text{F}.$$

Diode D_1 , beside $V_D(\text{m}) = 0.8 \text{ V}$, must be capable of carrying

$$i_D(\text{max}) \approx 36 \left(1 + 2\pi \sqrt{\frac{2 \times 25.5}{2}} \right) = 1.2 \text{ A}, i_D(\text{avg}) \approx 0.6 \text{ A},$$

and $\text{PIV} = 2V_p = 51 \text{ V}$ (use 80 V to be safe).

(b) $V_{r0} \approx \frac{10}{10 + 240} V_{ri} = \frac{1}{25} 2 = 80 \text{ mV}$.

