

- 1.11 The charge entering the positive terminal of an element is $q(t) = -30e^{-4t}$ mC. If the voltage across the element is $120e^{-2t}$ V, determine the energy delivered to the element in the time interval $0 < t < 50$ ms.

SOLUTION:

$$q(t) = 30e^{-4t} \text{ mC}$$

$$v(t) = 120e^{-2t} \text{ V}$$

$$W = \int_{t_1}^{t_2} P \, dt = \int_{t_1}^{t_2} v i \, dt$$

$$i(t) = \frac{dq(t)}{dt} = -4(-30)e^{-4t} \text{ mA}$$

$$i(t) = 120e^{-4t} \text{ mA}$$

$$W = \int_{t_1}^{t_2} (120e^{-2t})(120e^{-4t} \text{ m}) \, dt$$

$$W = 14.4 \int_0^{50\text{m}} e^{-6t} \, dt$$

$$W = 14.4 \left[\frac{e^{-6t}}{-6} \right]^{50\text{m}}$$

$$W = 14.4 \left[\frac{e^{-6(50\text{m})}}{-6} + \frac{e^{-6(0)}}{6} \right]$$

$$W = 622.04 \text{ mJ}$$