

1.33 Find V_x in the network in Fig. P1.33 using Tellegen's theorem.

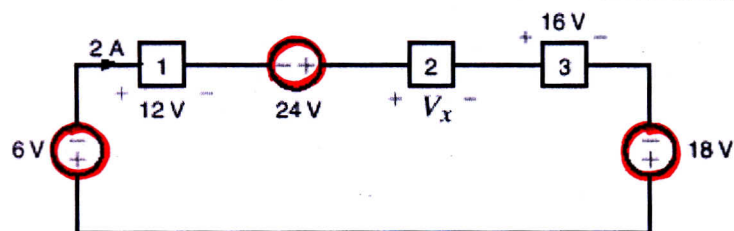


Figure P1.33

SOLUTION:

$$P_1 = 12(2) = 24\text{ W absorbed}$$

$$P_2 = V_x(2) = 2V_x \text{ absorbed}$$

$$P_3 = 16(2) = 32\text{ W absorbed}$$

$$P_{6V} = 6(2) = 12\text{ W absorbed}$$

$$P_{24V} = 24(-2) = -48\text{ W}$$

$$P_{24V} = 48\text{ W supplied}$$

Power supplied = Power absorbed

$$P_{24V} + P_{18V} = P_1 + P_2 + P_3$$

$$48 + 36 = 24 + 2V_x + 32$$

$$V_x = 8\text{ V}$$