

- 1.39 Find I_o in the network in Fig. P1.39 using Tellegen's theorem.

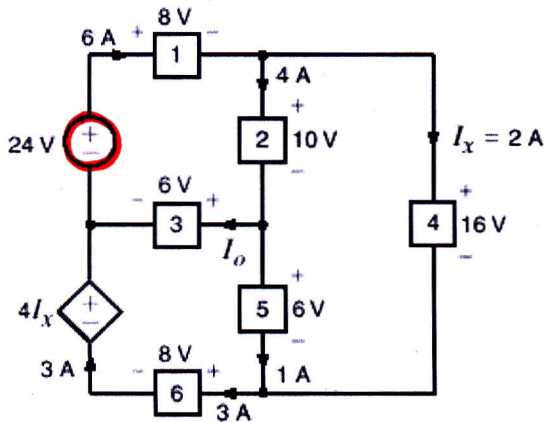


Figure P1.39

SOLUTION:

$$P_{24V} = 24(-6) = -144 \text{ W}$$

$$P_{24V} = 144 \text{ W supplied}$$

$$P_1 = 8(6) = 48 \text{ W absorbed}$$

$$P_2 = 10(4) = 40 \text{ W absorbed}$$

$$P_3 = 6I_o \text{ ABSORBED}$$

$$P_4 = 16(2) = 32 \text{ W absorbed}$$

$$P_5 = 6(1) = 6 \text{ W absorbed}$$

$$P_6 = 8(3) = 24 \text{ W absorbed}$$

$$P_{4I_x} = 4I_x(-3) = -12(2) = -24 \text{ W}$$

$$P_{4I_x} = 24 \text{ W supplied}$$

$$\text{Power supplied} = \text{Power absorbed}$$

$$P_{24V} + P_{4I_x} = P_1 + P_2 + P_3 + P_4 + P_5 + P_6$$

$$144 + 24 = 48 + 40 + 6I_o + 32 + 6 + 24$$

$$I_o = 3 \text{ A}$$