

Instructor's Solutions Manual to Accompany Circuit Analysis: Theory and Practice, 5e

Allan H. Robbins
Wilhelm C. Miller



Instructor's Solutions Manual to accompany:
Circuit Analysis: Theory and Practice, 5th edition
Allan H. Robbins and Wilhelm C. Miller

Vice President, Editorial: Dave Garza
Director of Learning Solutions: Sandy Clark
Acquisitions Editor: Stacy Masucci
Managing Editor: Larry Main
Product Manager: Mary Clyne
Editorial Assistant: Kaitlin Murphy
Vice President, Marketing: Jennifer Baker
Marketing Director: Deborah Yarnell
Associate Marketing Manager: Erica Glisson
Production Director: Wendy Troeger
Production Manager: Mark Bernard
Content Project Manager: Andy Baker
Art Director: David Arsenault

© 2013. 2007 Delmar, Cengage Learning

ALL RIGHTS RESERVED. No part of this work covered by the copyright herein may be reproduced, transmitted, stored, or used in any form or by any means graphic, electronic, or mechanical, including but not limited to photocopying, recording, scanning, digitizing, taping, Web distribution, information networks, or information storage and retrieval systems, except as permitted under Section 107 or 108 of the 1976 United States Copyright Act, or applicable copyright law of another jurisdiction, without the prior written permission of the publisher.

For product information and technology assistance, contact us at
Cengage Learning Customer & Sales Support,
1-800-354-9706

For permission to use material from this text or product,
submit all requests online at **www.cengage.com/permissions**.
Further permissions questions can be e-mailed to
permissionrequest@cengage.com

Multisim is a trademark of National Instruments. This publication is independent of National Instruments, which is not affiliated with the publisher or the author, and does not authorize, sponsor, endorse or otherwise approve this publication.

Library of Congress Control Number:

ISBN-13: 978-1-1332-8101-6

ISBN-10: 1-1332-8101-X

Delmar
5 Maxwell Drive
Clifton Park, NY 12065-2919
USA

Cengage Learning is a leading provider of customized learning solutions with office locations around the globe, including Singapore, the United Kingdom, Australia, Mexico, Brazil, and Japan. Locate your local office at: **international.cengage.com/region**

Cengage Learning products are represented in Canada by Nelson Education, Ltd.

To learn more about Delmar, visit **www.cengage.com/delmar**

Purchase any of our products at your local college store or at our preferred online store **www.cengagebrain.com**

Notice to the Reader

Publisher does not warrant or guarantee any of the products described herein or perform any independent analysis in connection with any of the product information contained herein. Publisher does not assume, and expressly disclaims, any obligation to obtain and include information other than that provided to it by the manufacturer. The reader is expressly warned to consider and adopt all safety precautions that might be indicated by the activities described herein and to avoid all potential hazards. By following the instructions contained herein, the reader willingly assumes all risks in connection with such instructions. The publisher makes no representations or warranties of any kind, including but not limited to, the warranties of fitness for particular purpose or merchantability, nor are any such representations implied with respect to the material set forth herein, and the publisher takes no responsibility with respect to such material. The publisher shall not be liable for any special, consequential, or exemplary damages resulting, in whole or part, from the readers' use of, or reliance upon, this material.

Contents

Answers to Odd-Numbered Questions

Chapter	1	Introduction	1
	2	Voltage and Current	3
	3	Resistance	5
	4	Ohm's Law, Power, and Energy	8
	5	Series Circuits	11
	6	Parallel Circuits	15
	7	Series-Parallel Circuits	19
	8	Methods of Analysis	24
	9	Network Theorems	28
	10	Capacitors and Capacitance	34
	11	Capacitor Charging, Discharging, and Simple Waveshaping Circuits	38
	12	Magnetism and Magnetic Circuits	43
	13	Inductance and Inductors	46
	14	Inductive Transients	49
	15	ac Fundamentals	54
	16	R , L , and C Elements and the Impedance Concept	59
	17	Power in ac Circuits	62
	18	AC Series-Parallel Circuits	65
	19	Methods of ac Analysis	72
	20	ac Network Theorems	78
	21	Resonance	87
	22	Filters and the Bode Plot	92
	23	Transformers and Coupled Circuits	100
	24	Three-Phase Systems	105
	25	Nonsinusoidal Waveforms	110

Answers to Even-Numbered Questions

Chapter	1	Introduction	117
	2	Voltage and Current	119
	3	Resistance	121
	4	Ohm's Law, Power, and Energy	124
	5	Series Circuits	127
	6	Parallel Circuits	131
	7	Series-Parallel Circuits	135
	8	Methods of Analysis	139
	9	Network Theorems	144
	10	Capacitors and Capacitance	150
	11	Capacitor Charging, Discharging, and Simple Waveshaping Circuits	155
	12	Magnetism and Magnetic Circuits	161
	13	Inductance and Inductors	165
	14	Inductive Transients	168
	15	ac Fundamentals	173
	16	R , L , and C Elements and the Impedance Concept	180
	17	Power in ac Circuits	183
	18	ac Series-Parallel Circuits	186
	19	Methods of ac Analysis	194
	20	ac Network Theorems	200
	21	Resonance	210
	22	Filters and the Bode Plot	216
	23	Transformers and Coupled Circuits	226
	24	Three-Phase Systems	230
	25	Nonsinusoidal Waveforms	235

Lab Manual Answers

Lab 1	Voltage and Current Measurement and Ohm's Law	243
Lab 2	Series dc Circuits	251
Lab 3	Parallel dc Circuits	263
Lab 4	Series-Parallel dc Circuits	269
Lab 5	Potentiometers and Rheostats	277
Lab 6	Superposition Theorem	283
Lab 7	Thévenin's and Norton's Theorems (dc)	293

Lab 8	Capacitors	299
Lab 9	Capacitor Charging and Discharging	367
Lab 10	Inductors in dc Circuits	319
Lab 11	The Oscilloscope (Part 1) Familiarization and Basic Measurements	333
Lab 12	Basic ac Measurements: Period, Frequency, and Voltage (The Oscilloscope Part 2)	341
Lab 13	ac Voltage and Current (The Oscilloscope Part 3, Additional Measurement Techniques)	347
Lab 14	Capacitive Reactance	357
Lab 15	Inductive Reactance	365
Lab 16	Power in ac Circuits	375
Lab 17	Series ac Circuits	383
Lab 18	Parallel ac Circuits	391
Lab 19	Series-Parallel ac Circuits	397
Lab 20	Thévenin's and Norton's Theorems (ac)	481
Lab 21	Series Resonance	415
Lab 22	Parallel Resonance	425
Lab 23	<i>RC</i> and <i>RL</i> Low-Pass Filter Circuits	433
Lab 24	<i>RC</i> and <i>RL</i> High-Pass Filter Circuits	445
Lab 25	Bandpass Filter	455
Lab 26	Voltage, Current, and Power in Balanced Three-Phase Systems	461
Lab 27	The Iron-Core Transformer	471
Lab 28	Mutual Inductance and Loosely Coupled Circuits	483

Introduction

1.3 Converting Units

1. a. $27 \text{ min} \times (60 \text{ s/min}) = 1620 \text{ s}$
 b. $0.8 \text{ h} \times (3600 \text{ s/h}) = 2880 \text{ s}$
 c. $\left(2 \text{ h} \times \frac{3600 \text{ s}}{\text{h}}\right) + \left(3 \text{ min} \times \frac{60 \text{ s}}{\text{min}}\right) + 47 \text{ s} = 7427 \text{ s}$
 d. $35 \text{ hp} \times (746 \text{ W/hp}) = 26\,110 \text{ W}$
 e. $1827 \text{ W} \times \frac{1 \text{ hp}}{746 \text{ W}} = 2.45 \text{ hp}$
 f. $23 \text{ rev.} \times 360^\circ/\text{rev} = 8280^\circ$
3. a. $1.2 \text{ m} \times 70 \text{ cm} \times \frac{1 \text{ m}}{100 \text{ cm}} = 0.84 \text{ m}^2$
 b. $\frac{1}{2} \left(25 \text{ cm} \times \frac{1 \text{ m}}{100 \text{ cm}}\right) (0.5 \text{ m}) = 0.0625 \text{ m}^2$
 c. $\left(10 \text{ cm} \times \frac{1 \text{ m}}{100 \text{ cm}}\right) \left(25 \text{ cm} \times \frac{1 \text{ m}}{100 \text{ cm}}\right) \left(80 \text{ cm} \times \frac{1 \text{ m}}{100 \text{ cm}}\right) = 0.02 \text{ m}^3$
 d. $\frac{4\pi}{3} \left(10 \text{ in} \times \frac{2.54 \text{ cm}}{\text{in}} \times \frac{1 \text{ m}}{100 \text{ cm}}\right)^3 = 0.0686 \text{ m}^3$
5. $\frac{15 \text{ parts}}{12 \text{ s}} \times \frac{3600 \text{ s}}{\text{h}} = 4500 \text{ parts/h}$
7. $\frac{27 \text{ mi}}{\text{gal}} \times \frac{1.609 \text{ km}}{\text{mi}} \times \frac{1 \text{ gal}}{3.785 \text{ liters}} = 11.5 \text{ km/liter}$
9. $\frac{18^\circ}{0.02 \text{ s}} \times \frac{1 \text{ rev}}{360^\circ} \times \frac{60 \text{ s}}{1 \text{ min}} = 150 \text{ rpm}$
11. $\frac{60 \text{ mi}}{\text{h}} \times 500 \text{ s} \times \frac{1 \text{ h}}{3600 \text{ s}} = 8.33 \text{ mi}$
13. $\frac{2000 \text{ yd}}{\text{h}} \times \frac{0.914 \text{ m}}{\text{yd}} \times \frac{1 \text{ h}}{3600 \text{ s}} = 0.508 \text{ m/s}$
15. $\frac{3 \text{ km}}{\text{h}} \times \frac{8}{60} \text{ h} + \frac{5 \text{ km}}{\text{h}} \times 1.25 \text{ h} + \frac{4 \text{ km}}{\text{h}} \times \frac{12}{60} \text{ h} = 7.45 \text{ km}$
17. $\frac{2 \text{ km}}{\text{h}} \times \frac{15}{60} \text{ h} + \frac{5 \text{ km}}{\text{h}} + \frac{18 \text{ h}}{60} \text{ h} + \frac{2.5 \text{ km}}{\text{h}} \times t_3 = 2.85 \text{ km}$
 Thus, $t_3 = 0.34 \text{ h} = 20.4 \text{ minutes}$.
19. Machine 1: $\frac{\$0.43}{\text{min}} \times \frac{60 \text{ min}}{\text{h}} = \$25.80/\text{h}$
 Machine 2: $\frac{\$200}{8 \text{ h}} = \$25.00/\text{h}$ (This one is cheaper to operate. Buy it.)

1.4 Power of Ten Notation

21. a. 8.675×10^3
 b. 8.72×10^{-3}
 c. 1.24×10^3
 d. 3.72×10^{-1}
 e. 3.48×10^2
 f. 2.15×10^{-7}
 g. 1.47×10^1
23. a. $\frac{1.25 \times 10^2}{1 \times 10^3} = 1.25 \times 10^{-1}$
 b. $\frac{8 \times 10^4}{1 \times 10^{-3}} = 8 \times 10^7$
 c. $\frac{3 \times 10^4}{1.5 \times 10^6} = 2 \times 10^4 \times 10^{-6} = 2 \times 10^{-2}$
 d. $\frac{(16)(21.8) \times 10^{-7} \times 10^6}{(14.2)(12) \times 10^{-5}} = 2.05 \times 10^4$
25. a. $(4 \times 10^3)(5 \times 10^{-2})^2 = (4 \times 10^3)(25 \times 10^{-4}) = 100 \times 10^{-1} = 10$
 b. $(4 \times 10^3)(-5 \times 10^{-2})^2 = (4 \times 10^3)(25 \times 10^{-4}) = 10$
 c. $\frac{(6 \times 10)^2}{(10 \times 10^{-1})} = \frac{36 \times 10^2}{1} = 3.6 \times 10^3$
 d. $\frac{(50)^{-2}(2.5 \times 10^6)(6 \times 10^3)}{(1 \times 10^3)(2 \times 10^{-1})^2} = \frac{(2.5)(6) \times 10^6 \times 10^3}{(5 \times 10)^2(1 \times 10^3)(4 \times 10^{-2})}$

$$= \frac{15 \times 10^9}{25 \times 10^2 \times 10^3 \times 4 \times 10^{-2}} = \frac{15 \times 10^9}{100 \times 10^3}$$

$$= 0.15 \times 10^6 = 15 \times 10^4$$

 e. $\frac{(-0.027)^{1/3}(-0.2)^2}{(24)^0 \times 10^{-3}} = \frac{(-0.3)(-2 \times 10^{-1})^2}{1 \times 10^{-3}}$

$$= \frac{(-0.3)(4 \times 10^{-2})}{1 \times 10^{-3}} = -12$$

27. i. $(8.42 \times 10^2)(1.4 \times 10^{-3}) = 11.79 \times 10^{-1} = 1.179$

ii. $\frac{3.52 \times 10^{-2}}{7.91 \times 10^{-3}} = 0.445 \times 10^1 = 4.45$

Direct computation for these examples is less work.

29. 6.24×10^{18}

31. $\frac{6.24 \times 10^{18} \text{ electrons}}{1 \text{ s}} \times 10.03 \times 10^3 \text{ s}$
 $= 62.6 \times 10^{21} \text{ electrons}$

33. $t = \frac{3.47 \times 10^5 \text{ km}}{299\,792.458 \text{ km/s}} = 1.16 \text{ s}$

35. $\frac{3.73 \times 10^4 \text{ m}^3}{1 \text{ s}} \times \frac{3600 \text{ s}}{1 \text{ h}} \times \frac{1 \text{ liter}}{1 \times 10^{-3} \text{ m}^3}$
 $= 13.4 \times 10^{10} \text{ liters/h}$

1.5 Prefixes

37. a. kilo, k
 b. mega, M
 c. giga, G
 d. micro, μ
 e. milli, m
 f. pico, p

39. a. 1.5 ms
 b. $27 \mu\text{s}$
 c. 350 ns

41. a. $150 \times 10^3 \text{ V}$; $0.15 \times 10^6 \text{ V}$
 b. $0.33 \times 10^{-3} \text{ W}$; $33 \times 10^{-5} \text{ W}$

43. a. $330 \text{ V} + 150 \text{ V} + 200 \text{ V} = 680 \text{ V}$
 b. $60 \text{ W} + 100 \text{ W} + 2.7 \text{ W} = 162.7 \text{ W}$

45. $1500 \text{ W} = 1.5 \times 10^3 \text{ W} = 1.5 \text{ kW}$

47. $I_3 = I_1 + I_2 + I_4 = 12 \text{ A} + 150 \text{ A} + 25 \text{ A} = 187 \text{ A}$

49. $39 \text{ mmfd} = 39 \mu\text{F} = 39 \times 10^{-6} \times 10^{-6} = 39 \times 10^{-12} \text{ F}$
 $= 39 \text{ pF}$

51. Radio signal: $t = \frac{5000 \text{ km}}{299\,792.458 \text{ km/s}} = 16.68 \text{ ms}$

Telephone signal: $t = \frac{5000 \times 10^3 \text{ m}}{150 \text{ m}/\mu\text{s}} = 33.33 \text{ ms}$

$\therefore$ Radio signal arrives first by 16.65 ms.

53. a. $R = \frac{V}{I} = \frac{50 \text{ V}}{24 \text{ mA}} = 2.083 \text{ k}\Omega$. (Since V and I are specified as exact, you can use as many digits as you like.)

b. $R_{\text{max}} = \frac{V_{\text{max}}}{I_{\text{min}}} = \frac{50.1 \text{ V}}{23.9 \text{ mA}} = 2.096 \text{ k}\Omega = 2.10 \text{ k}\Omega$

when rounded to 3 digits

$R_{\text{min}} = \frac{V_{\text{min}}}{I_{\text{max}}} = \frac{49.9 \text{ V}}{24.1 \text{ mA}} = 2.071 \text{ k}\Omega = 2.07 \text{ k}\Omega$

when rounded to 3 digits.

The actual value of R lies somewhere between $2.07 \text{ k}\Omega$ and $2.10 \text{ k}\Omega$.

55. See CD in the back of the book.

1.6 Circuit Diagrams

57. Same as Figure 1–7(a) of the text.

Voltage and Current

2.1 Atomic Theory

1. There are of the order of 10^{23} free electrons per cm^3 at room temperature in copper.
- a. $1 \text{ m}^3 = (100 \text{ cm})^3 = 10^6 \text{ cm}^3$. Thus, the number of electrons is

$$N = \frac{10^{23} \text{ electrons}}{\text{cm}^3} \times 10^6 \text{ cm}^3 = 10^{29} \text{ electrons}$$
- b. Volume =

$$\frac{\pi d^2}{4} \times l = \frac{\pi}{4} (0.163 \text{ cm})^2 (500 \text{ cm}) = 10.4 \text{ cm}^3$$

$$N = \frac{10^{23} \text{ electrons}}{\text{cm}^3} \times 10.4 \text{ cm}^3$$

$$= 10.4 \times 10^{23} \text{ electrons}$$
3. Original: $F_1 = k \frac{Q_1 Q_2}{r_1^2}$
 New: $F_2 = \frac{k(2Q_1)(3Q_2)}{\left(\frac{r_1}{2}\right)^2} = \frac{(2)(3)}{\left(\frac{1}{2}\right)^2} \left[k \frac{Q_1 Q_2}{r_1^2} \right] = 24 F_1$
 $\therefore$ Force increases by a factor of 24.
5. a. It has a lot of free electrons. This results from having few (e.g., 1) electrons in its valence shell
 b. Inexpensive and easily formed into wires.
 c. Has a full valence shell. Therefore, no free electrons.
 d. The electrical force is so great that electrons are torn from their parent atoms. This movement of electrons constitutes a current. We see the effect as a lightning discharge.

2.2 The Unit of Electrical Charge: The Coulomb

7. a. $F = \frac{9 \times 10^9 (1 \times 10^{-6} \text{ C})(7 \times 10^{-6} \text{ C})}{(10 \times 10^{-3})^2}$
 $= 630 \text{ N (repulsive)}$
- b. $F = \frac{9 \times 10^9 (8 \times 10^{-6})(4 \times 10^{-6})}{(0.12)^2}$
 $= 20 \text{ N (attractive)}$
- c. $F = \frac{9 \times 10^9 (1.602 \times 10^{-19})^2}{(12 \times 10^{-8})^2}$
 $= 1.60 \times 10^{-14} \text{ N (repulsive)}$
- d. $F = \frac{9 \times 10^9 (1.602 \times 10^{-19})^2}{(5.3 \times 10^{-11})^2}$
 $= 8.22 \times 10^{-8} \text{ N (attractive)}$
- e. Neutron is uncharged $\therefore F = 0$
9. $180 \text{ N} = \frac{9 \times 10^9 (4 \times 10^{-6}) Q_2}{(2 \times 10^{-2})^2} \therefore Q_2 = 2 \mu\text{C}$
 (Attractive)
11. $0.02 \text{ N} = \frac{9 \times 10^9 Q_1 (5 Q_1)}{(0.5)^2}$
 $0.02 = 180 \times 10^9 Q_1^2$
 $\therefore Q_1 = 0.333 \mu\text{C}$ and $Q_2 = 1.67 \mu\text{C}$, both (+) or both (-).
13. $19 \times 10^{13} \text{ electron} \times 1.6 \times 10^{-19} \text{ coulomb/electron}$
 $= 30.4 \mu\text{C}$
15. $Q_1 = - (14.6 \times 10^{13} \times 1.60 \times 10^{-19}) = -23.4 \mu\text{C}$
 $Q_2 = 1.3 \mu\text{C}$
 $Q_{\text{final}} = Q_{\text{initial}} + Q_1 + Q_2$
 $5.6 \mu\text{C} = Q_{\text{initial}} - 23.4 \mu\text{C} + 1.3 \mu\text{C}$
 $\therefore Q_{\text{initial}} = 27.7 \mu\text{C (positive)}$

2.3 Voltage

17. $V = \frac{W}{Q} = \frac{360 \text{ J}}{15 \text{ C}} = 24 \text{ V}$
19. $V = \frac{W}{Q} = \frac{1200 \text{ J}}{0.5 \text{ C}} = 2400 \text{ V}$
21. $W = QV = (0.5 \times 10^{-6} \text{ C})(8.5 \times 10^3 \text{ V}) = 4.25 \text{ mJ}$
23. $Q = \frac{W}{V} = \frac{57 \text{ J}}{12 \text{ V}} = 4.75 \text{ C}$

2.4 Current

$$25. \quad I = \frac{Q}{t} = \frac{250 \mu\text{C}}{5 \text{ ms}} = 50 \text{ mA}$$

$$27. \quad Q = It = (16.7 \text{ mA})(20 \text{ ms}) = 334 \mu\text{C}$$

$$29. \quad Q = (93.6 \times 10^{12})(1.6 \times 10^{-19}) = 15 \mu\text{C}$$

$$I = \frac{Q}{t} = \frac{15 \times 10^{-6} \text{ C}}{5 \times 10^{-3} \text{ s}} = 3 \text{ mA}$$

$$31. \quad \text{At } t = 0, q_0 = 20 \text{ C. At } t = 1 \text{ s, } q_1 = 100 \text{ C.}$$

$$I = \frac{\Delta q}{\Delta t} = \frac{100 \text{ C} - 20 \text{ C}}{1 \text{ s}} = \frac{80 \text{ C}}{1 \text{ s}} = 80 \text{ C/s} = 80 \text{ A}$$

$$33. \quad Q = \frac{47 \times 10^{19} \text{ electrons}}{6.24 \times 10^{18} \text{ electrons/C}} = 75.3 \text{ C}$$

$$V = \frac{W}{Q} = \frac{1353.6 \text{ J}}{75.3} = 18.0 \text{ V}$$

$$I = \frac{Q}{t} = \frac{75.3 \text{ C}}{78 \text{ s}} = 0.966 \text{ A}$$

2.5 Practical DC Sources

$$35. \text{ a. } E_T = 1.47 + 1.61 + 1.58 = 4.66 \text{ V}$$

$$\text{b. } E_T = 1.47 + 1.61 - 1.58 = 1.50 \text{ V}$$

$$37. \quad \text{Life} = \frac{\text{capacity}}{\text{drain}} = \frac{1400 \text{ mAh}}{28 \text{ mA}} = 50 \text{ h}$$

$$39. \quad \text{From Figure 2-15, capacity at } 5^\circ\text{C is 90\% of its value MAX at } 25^\circ\text{C. Therefore, capacity} = 0.9 \text{ Max} = 81 \text{ Ah. Thus, Max} = 81/0.9 = 90 \text{ Ah. At } -15^\circ\text{C, capacity} = 0.65 \text{ Max} = 0.65 (90) = 58.5 \text{ Ah. Thus, life} \approx 58.5 \text{ Ah}/5 \text{ A} = 11.7 \text{ h.}$$

2.6 Measuring Voltage and Current

$$41. \quad \text{Both}$$

$$43. \quad \text{The voltmeter and ammeter are interchanged.}$$

$$45. \quad \text{Meter 1: Reading is 7 A, Meter 2: Reading is } -7 \text{ A}$$

2.7 Switches, Fuses, and Circuit Breakers

$$47. \quad \text{When a fuse "blows," it becomes an open circuit with source voltage across it. The voltage rating tells you how much voltage you can use the fuse with so that it does not arc over when it blows.}$$

Resistance

3.1 Resistance of Conductors

$$1. \quad a. \quad R = \frac{(2.825 \times 10^{-18} \Omega \cdot \text{m})(100 \text{ m})}{\pi(0.5 \times 10^{-3} \text{ m})^2} = 3.60 \Omega$$

$$b. \quad R = \frac{2.825 \times 10^{-8} \Omega \cdot \text{m}(100 \text{ m})}{\pi(1.0 \times 10^{-3} \text{ m})^2} = 0.900 \Omega$$

$$c. \quad R = \frac{(2.825 \times 10^{-8} \Omega \cdot \text{m})(100 \text{ m})}{\pi(0.005 \times 10^{-3} \text{ m})^2} = 36.0 \text{ k}\Omega$$

$$d. \quad R = \frac{(2.825 \times 10^{-8} \Omega \cdot \text{m})(100 \text{ m})}{\pi(0.05 \times 10^{-2} \text{ m})^2} = 36.0 \text{ m}\Omega$$

$$3. \quad L = 250 \text{ ft} = 250 \text{ ft} \left(\frac{0.3048 \text{ m}}{1 \text{ ft}} \right) = 76.2 \text{ m}$$

$$A = \frac{\rho L}{R} = \frac{(1.723 \times 10^{-8} \Omega \cdot \text{m})(76.2 \text{ m})}{0.02 \Omega}$$

$$= 6.56 \times 10^{-5} \text{ m}^2$$

$$w = 0.25 \text{ inch} = 0.25 \text{ inch} \left(\frac{2.54 \times 10^{-2} \text{ m}}{1 \text{ inch}} \right)$$

$$= 0.00635 \text{ m}$$

$$h = \frac{A}{w} = \frac{6.56 \times 10^{-5} \text{ m}^2}{0.00635 \text{ m}} = 0.0103 \text{ m} = 0.407 \text{ inch}$$

$$5. \quad R = \frac{\rho L}{A} \quad L = \frac{RA}{\rho} \\ = \frac{(10.3 \Omega)(\pi)(0.40 \times 10^{-3} \text{ m})^2}{1.723 \times 10^{-8} \Omega \cdot \text{m}}$$

$$L = 300 \text{ m}$$

$$L = 986 \text{ ft}$$

$$7. \quad R = \frac{\rho L}{A} \quad \rho = \frac{RA}{L} \\ = \frac{(3.0 \Omega)(\pi)(0.25 \times 10^{-3} \text{ m})^2}{6.00 \times 10^{-2} \text{ m}} \\ = 982 \times 10^{-8} \Omega \cdot \text{m}$$

Resistivity is less than ρ for carbon.

$$9. \quad R = \frac{\rho L}{A} \quad \rho = \frac{R \cdot A}{L} \\ = \frac{(32 \Omega)(\pi)(0.75 \times 10^{-3} \text{ m})^2}{2500 \text{ m}} \\ = 2.26 \times 10^{-8} \Omega \cdot \text{m}$$

This alloy is not as good a conductor as copper.

3.2 Electrical Wire Tables

$$11. \quad \text{AWG 22 : } R = (300 \text{ ft}) \left(\frac{16.2 \Omega}{1000 \text{ ft}} \right) = 4.86 \Omega$$

$$\text{AWG 19: } R = (300 \text{ ft}) \left(\frac{8.05 \Omega}{1000 \text{ ft}} \right) = 2.42 \Omega$$

Diameter of AWG 19 is 1.42 times the diameter of AWG 22.

The resistance of AWG 19 is $\frac{1}{2}$ the resistance of AWG 22.

13. From Table 3-2, AWG 22 can handle about 2 A of current. Since AWG 19 is 3 sizes larger, it should handle about 4 A of current.

Since AWG 30 is ten sizes smaller than AWG 20 (which can handle 3 A), AWG 30 can handle about 0.30 A.

$$15. \quad R = \left(\frac{415 \Omega}{1000 \text{ ft}} \right) L = 550 \Omega \\ L = (550 \Omega) \left(\frac{1000 \text{ ft}}{415 \Omega} \right) \approx 1330 \text{ ft} \approx 405 \text{ m}$$

3.3 Resistance of Wires—Circular Mills

$$17. \quad a. \quad D = 0.016 \text{ in} = 16 \text{ mil}$$

$$A = 16^2 = 256 \text{ CM}$$

$$b. \quad D = 2.0 \text{ mm} = 2.0 \text{ mm} \left(\frac{1 \text{ in}}{25.4 \text{ mm}} \right) = 0.0787 \text{ in} \\ = 78.4 \text{ mil}$$

$$A = 78.4^2 = 6200 \text{ CM}$$

$$c. \quad A = (0.25 \text{ in})(6.0 \text{ in}) \\ = (250 \text{ mil})(6000 \text{ mil})A \\ = 1.50 \times 10^6 \text{ sq mil} \\ A = 1.91 \times 10^6 \text{ CM} \\ = 1910 \text{ MCM}$$

19. a. $R = \frac{\rho M}{A} = \frac{\left(1036 \frac{\text{CM} \cdot \Omega}{\text{ft}}\right)(400 \text{ ft})}{256 \text{ CM}} = 16.2 \Omega$

b. $R = \frac{\left(1036 \frac{\text{CM} \cdot \Omega}{\text{ft}}\right)(400 \text{ ft})}{6200 \text{ CM}} = 0.668 \Omega$

c. $R = \frac{\left(1036 \frac{\text{CM} \cdot \Omega}{\text{ft}}\right)(400 \text{ ft})}{1.91 \times 10^6 \text{ CM}} = 2.17 \times 10^{-3} \Omega$

21. a. $R = \frac{\rho L}{A}$
 $A = \frac{\left(10.36 \frac{\text{CM} \cdot \Omega}{\text{ft}}\right)(200 \text{ ft})}{0.5 \Omega} = 4144 \text{ CM}$

$A = 4144 \text{ CM} \left(\frac{\pi \text{ sq mil}}{4 \text{ CM}}\right) = 3255 \text{ sq mil}$

b. $D = \sqrt{A} = 64.4 \text{ mil} = 0.0644 \text{ in}$

23. $D = 0.040 \text{ in} = 40 \text{ mil}$

a. $A = D^2 = 1600 \text{ CM}$

$A = 1600 \text{ CM} \left(\frac{\pi \text{ sq mil}}{4 \text{ CM}}\right) = 1260 \text{ sq mil}$

b. $R = \frac{\rho L}{A} L = \frac{R \cdot A}{\rho} = \frac{(12.5 \Omega)(1600 \text{ CM})}{\left(10.37 \frac{\text{CM} \cdot \pi}{\text{ft}}\right)} = 1930 \text{ ft}$

25. At $T = -30^\circ\text{C}$:

$R = \frac{-30^\circ - (-236^\circ)}{20^\circ - (-236^\circ)} (50 \Omega) = 40.2 \Omega$

At $T = 0^\circ\text{C}$:

$R = \frac{0^\circ - (-236^\circ)}{20^\circ - (-236^\circ)} (50 \Omega) = 46.1 \Omega$

At $T = 200^\circ\text{C}$:

$R = \frac{200^\circ - (-236^\circ)}{20^\circ - (-236^\circ)} (50 \Omega) = 85.2 \Omega$

27. a. Positive temperature coefficient since as temperature increases, resistance also increases.

b. $R_2 = R_1[1 + \alpha_1(T_2 - T_1)]$

$\alpha_1 = \frac{\left(\frac{R_2}{R_1} - 1\right)}{T_2 - T_1} = \frac{\left(\frac{25 \Omega}{20 \Omega} - 1\right)}{85^\circ\text{C} - 20^\circ\text{C}} = 0.00385(^\circ\text{C})^{-1}$

c. Temperature intercept:

$\frac{20^\circ - T}{20 \Omega} = \frac{85^\circ - 20^\circ}{25 \Omega - 20 \Omega}$

$T = -\frac{20 \Omega(85^\circ - 20^\circ)}{25 \Omega - 20 \Omega} + 20^\circ = -240^\circ\text{C}$

At $T = 0^\circ\text{C}$:

$R = \frac{100^\circ - (-240^\circ)}{20^\circ - (-240^\circ)} (20 \Omega) = 18.5 \Omega$

At $T = 100^\circ\text{C}$:

$R = \frac{100^\circ - (-240^\circ)}{20^\circ - (-240^\circ)} (20 \Omega) = 26.2 \Omega$


29. $R = \frac{260^\circ - (-2270^\circ)}{20^\circ - (-2270^\circ)} (15.2 \Omega) = 16.8 \Omega$

31. $m = \frac{70 \Omega}{140^\circ\text{C}} = 0.5 \Omega/^\circ\text{C}$

$R = (0.5 \Omega/^\circ\text{C})T + 130 \Omega$

$T = \frac{-130 \Omega}{0.5 \Omega/^\circ\text{C}} = -260^\circ\text{C}$

3.5 Types of Resistors

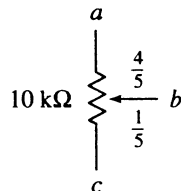33. 

a. $R_{ab} = 10 \text{ k}\Omega$ $R_{bc} = 0$
 b. $R_{ab} = 8 \text{ k}\Omega$ $R_{bc} = 2 \text{ k}\Omega$
 c. $R_{ab} = 2 \text{ k}\Omega$ $R_{bc} = 8 \text{ k}\Omega$
 d. $R_{ab} = 0$ $R_{bc} = 10 \text{ k}\Omega$

3.6 Color Coding of Resistors

35. a. $15 \times 10^4 \pm 10\% = 150 \text{ k}\Omega \pm 10\% = 150 \text{ k}\Omega \pm 15 \text{ k}\Omega$

b. $28 \times 0.1 \pm 5\% = 2.8 \Omega \pm 5\%$
 $= 2.8 \Omega \pm 0.14 \Omega$
 (with a reliability of 0.001%)

c. $47 \times 10^6 \pm 5\% = 47 \text{ M}\Omega \pm 5\% = 47 \text{ M}\Omega \pm 2.4 \text{ M}\Omega$

d. $39 \times 10^0 \pm 5\% = 39 \Omega \pm 5\%$
 $= 39 \Omega \pm 2 \Omega$
 (with a reliability of 0.1%)

3.7 Measuring Resistance—The Ohmmeter

37. Connect the ohmmeter between the two terminals of the light bulb. If the resistance is measured to be low (about 0Ω), the bulb is functional. If the

ohmmeter indicates an open circuit, the light bulb is burned out.

39. AWG 24 has a resistance of $25.7 \Omega/1000 \text{ ft}$
(Table 3-2)

Measure the resistance between the two ends of the wire. Calculate the approximate length (in feet) from:

$$L = \frac{R}{0.0257} \quad (L\text{--in feet})$$

3.8 Thermistors

41. a. At $T = 20^\circ\text{C}$, $R \cong 380 \Omega$
 b. At $T = 40^\circ\text{C}$, $R \cong 150 \Omega$
 c. The thermistor has a negative temperature coefficient since resistance decreases as temperature is increased.

3.11 Conductance



43. a. $G = \frac{1}{R} = \frac{1}{0.25 \Omega} = 4.0 \text{ S}$
 b. $G = \frac{1}{500 \Omega} = 2.0 \text{ mS}$
 c. $G = \frac{1}{250 \text{ k}\Omega} = 4.0 \mu\text{S}$
 d. $G = \frac{1}{12.5 \text{ M}\Omega} = 0.08 \mu\text{S}$
45. $R = (1000 \text{ m}) \left(\frac{1 \text{ ft}}{0.3048 \text{ m}} \right) \left(\frac{104 \Omega}{1000 \text{ ft}} \right) = 341 \Omega$
 $G = \frac{1}{341 \Omega} = 2.93 \text{ mS}$

Ohm's Law, Power, and Energy

4.1 Ohm's Law

1. a. $I = \frac{E}{R} = \frac{40 \text{ V}}{20 \Omega} = 2 \text{ A}$
 b. $\frac{35 \text{ mV}}{5 \text{ m}\Omega} = 7.0 \text{ A}$
 c. $\frac{200 \text{ V}}{40 \text{ k}\Omega} = 5 \text{ mA}$
 d. $\frac{10 \text{ V}}{2.5 \text{ M}\Omega} = 4 \mu\text{A}$
 e. $\frac{7.5 \text{ V}}{2.5 \times 10^3 \Omega} = 3 \text{ mA}$
 f. $\frac{12 \times 10^3 \text{ V}}{2 \times 10^6 \Omega} = 6 \text{ mA}$
3. a. $V = IR = (1 \times 10^{-3} \text{ A})(40 \times 10^3 \Omega) = 40 \text{ V}$
 b. $(10 \times 10^{-6} \text{ A})(30 \times 10^3 \Omega) = 0.3 \text{ V}$
 c. $(10 \times 10^{-3} \text{ A})(4 \times 10^4 \Omega) = 400 \text{ V}$
 d. $(12 \text{ A})(3 \times 10^{-2} \Omega) = 0.36 \text{ V}$
5. $R = \frac{E}{I} = \frac{120 \text{ V}}{1.25 \text{ A}} = 96 \Omega$
7. $V = IR = (50 \times 10^{-3} \text{ A})(560 \Omega) = 28 \text{ V}$
9. $I = GE = (0.2 \text{ S})(30 \text{ V}) = 6 \text{ A}$
11. $R = \frac{V}{I} = \frac{33 \text{ V}}{15 \text{ mA}} = 2.2 \text{ k}\Omega$
 $\therefore$ Color code is Red, Red, Red
13. From its color code, $R = 22 \Omega$. Fuse blows at 1 A. This corresponds to $V = IR = (1 \text{ A})(22 \Omega) = 22 \text{ V}$.
15. $\ell = (800 \text{ t})(3 \text{ inches/t}) = 2400 \text{ in} = 200 \text{ ft}$.
 From the wire table (Chapter 3), resistance is $104 \Omega/1000 \text{ ft}$. Thus, $R = (0.2)(104 \Omega) = 20.8 \Omega$ at 20°C .
- a. At 20°C , $I = \frac{48 \text{ V}}{20.8 \Omega} = 2.31 \text{ A}$
- b. At 40°C , (using the method of Chapter 3),
 $R = \left(\frac{274.5}{254.5} \right) (20.8 \Omega) = 22.43 \Omega$
 Thus, $I = \frac{48 \text{ V}}{22.43 \Omega} = 2.14 \text{ A}$
17. $R = \rho \frac{\ell}{A} = \frac{(2.825 \times 10^{-8})(100 \text{ m})}{\frac{\pi}{4}(0.5 \times 10^{-3} \text{ m})^2} = 14.39 \Omega$
 $E = IR = (200 \times 10^{-3} \text{ A})(14.39 \Omega) = 2.88 \text{ V}$
19. This is a linear graph. Therefore, choose any V - I point, for example, 80 V and 20 A . Thus,
 $R = \frac{V}{I} = \frac{80 \text{ V}}{20 \text{ A}} = 4 \Omega$
21. $I_{\text{old}} = \frac{100 \text{ V}}{R}$ $I_{\text{new}} = 2 I_{\text{old}} = 2 \left(\frac{100 \text{ V}}{R} \right)$
 Also: $I_{\text{new}} = \frac{E_{\text{new}}}{2R}$
 $\therefore \frac{2(100 \text{ V})}{R} = \frac{E_{\text{new}}}{2R}$
 Cancel R . $\therefore E_{\text{new}} = 400 \text{ V}$
23. $A = \frac{\pi d^2}{4} = \frac{\pi}{4} (0.1 \times 10^{-3})^2 = 0.7854 \times 10^{-8} \text{ m}^2$
 $\rho = 99.72 \times 10^{-8} \Omega \cdot \text{m}$
 $R = \frac{\rho \ell}{A} = \frac{(99.72 \times 10^{-8})(25)}{0.7854 \times 10^{-8}} = 3174 \Omega$
 $I = \frac{12 \text{ V}}{3174 \Omega} = 3.78 \text{ mA}$

4.2 Voltage Polarity and Current Direction

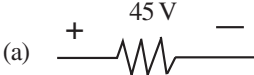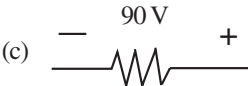25. (a)  (c) 
- (b)  (d) 

4.3 Power

$$27. \quad P = \frac{W}{t} = \frac{723 \text{ J}}{227 \text{ s}} = 3.19 \text{ J/s} = 3.19 \text{ W}$$

$$29. \quad P = EI = (12 \text{ V})(3 \text{ A}) = 36 \text{ W}$$

$$31. \quad P = I^2 R$$

$$I^2 = \frac{P}{R} = \frac{1200 \text{ W}}{6 \Omega} = 200$$

$$\therefore I = \sqrt{200} = 14.1 \text{ A}$$

$$33. \quad P = \frac{V^2}{R} \therefore V^2 = PR$$

$$V^2 = (752 \text{ W})(3 \Omega) = 2256$$

$$V = 47.5 \text{ V}$$

$$35. \quad R = 10\,000 \Omega$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{0.25 \text{ W}}{10\,000 \Omega}} = 5 \text{ mA}$$

$$V = \frac{P}{I} = \frac{0.25 \text{ W}}{0.005 \text{ A}} = 50 \text{ V}$$

$$37. \quad I = \frac{P}{V} = \frac{445 \text{ W}}{12 \text{ V}} = 37.9 \text{ A}$$

$$39. \quad P = (3.56 \text{ hp})(746 \text{ W/hp}) = 2656 \text{ W}$$

$$41. \quad V = \sqrt{PR} = \sqrt{(2 \text{ W})(270 \Omega)} = 23.2 \text{ V}$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{2 \text{ W}}{270 \Omega}} = 86.1 \text{ mA}$$

$$43. \quad V_{\min} = 95 \text{ V}; V_{\max} = 105 \text{ V}$$

$$\therefore P_{\min} = \frac{(95 \text{ V})^2}{25 \Omega} = 361 \text{ W}$$

$$P_{\max} = \frac{(105 \text{ V})^2}{25 \Omega} = 441 \text{ W}$$

4.4 Power Direction Convention

$$45. \text{ a. } P = (12 \text{ V})(4 \text{ A}) = 48 \text{ W} \rightarrow$$

$$\text{b. } P = (15 \text{ V})(2 \text{ A}) = 30 \text{ W} \leftarrow$$

$$\text{c. } P = (8 \text{ V})(16 \text{ A}) = 128 \text{ W} \leftarrow$$

$$\text{d. } P = (30 \text{ V})(8 \text{ A}) = 240 \text{ W} \rightarrow$$

4.5 Energy

$$47. \text{ a. } W = Pt = (40 \text{ W})(9 \text{ h} \times 3600 \text{ s/h}) \\ = 1.296 \times 10^6 \text{ W} \cdot \text{s} = 1.296 \times 10^6 \text{ J}$$

$$\text{b. } W = (40 \text{ W})(9 \text{ h}) = 360 \text{ Wh}$$

$$\text{c. } \text{Cost} = (0.360 \text{ kWh})(\$0.08/\text{kWh}) = 2.88 \text{ cents}$$

$$49. \quad W = (900) \left(\frac{5}{60} \right) + (120)(8)(1.7) + \\ (1100) \left(\frac{36}{60} \right) + \frac{(120)^2}{288} \left(\frac{24}{60} \right) = 2.387 \text{ kWh}$$

$$\text{Cost} = (2.387)(\$0.11) = \$0.26$$

$$51. \quad \text{Per day: } W = (200 \text{ W} \times 24 \text{ h}) + (4000 \text{ W})(24 \text{ h}) + \\ (3600 \text{ W})(12 \text{ h}) = 144 \text{ kWh}$$

$$\text{Per year: } W_T = 365 \times 144 \text{ kWh} = 52\,560 \text{ kWh}$$

$$\text{Cost at } \$0.10/\text{kWh} = \$5256$$

$$53. \quad \text{It takes } 12 (1.75 \text{ min}) = 21 \text{ minutes to toast the loaf.}$$

$$W = (1100 \text{ W}) \left(\frac{21}{60} \right) = 385 \text{ Wh} = 0.385 \text{ kWh}$$

$$\text{Cost} = (0.385)(\$0.13) = \$0.05 = 5 \text{ cents}$$

4.6 Efficiency

$$55. \quad P_{\text{in}} = \frac{P_{\text{out}}}{\eta} = \frac{50 \text{ kW}}{0.97} = 51.5 \text{ kW}$$

$$57. \quad P_{\text{out}} = P_{\text{in}} - P_{\text{loss}} = 1100 \text{ W} - 190 \text{ W} = 910 \text{ W}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\% = \frac{910 \text{ W}}{1100 \text{ W}} \times 100\% = 82.7\%$$

$$59. \quad P_{\text{in}} = (120 \text{ V})(15 \text{ A}) = 1800 \text{ W}$$

$$P_{\text{out}} = (0.89)(1800 \text{ W}) = 1602 \text{ W}$$

$$P_{\text{out}} = 1602 \text{ W}/(746 \text{ W/hp}) = 2.15 \text{ hp}$$

$$61. \quad \eta_T = \eta_1 \times \eta_2 = (0.95)(0.80) = 0.76$$

$$P_{\text{in}} = (48 \text{ V})(180 \text{ A}) = 8640 \text{ W}$$

$$P_{\text{out}} = \eta_T P_{\text{in}} = (0.76)(8640 \text{ W}) = 6566 \text{ W}$$

$$\therefore P_{\text{out}} = \frac{6566 \text{ W}}{746 \text{ W/hp}} = 8.8 \text{ hp}$$

$$63. \quad 1600 \text{ W} \rightarrow \boxed{\eta_1} \xrightarrow{P_m} \boxed{0.75} \rightarrow 1100 \text{ W}$$

$$P_m = \frac{1100 \text{ W}}{0.75} = 1467 \text{ W} = \frac{1467}{746} = 1.97 \text{ hp}$$

$$65. \quad W_{\text{out}} = Pt = (35 \text{ kW})(24 \text{ h}) = 840 \text{ kWh}$$

$$W_{\text{in}} = \frac{W_{\text{out}}}{\eta} = \frac{840 \text{ kWh}}{0.55} = 1527 \text{ kWh}$$

$$\text{Cost} = (1527 \text{ kWh})(\$0.09/\text{kWh}) = \$137.45$$


4.7 Nonlinear and Dynamic Resistances

67. a. From the graph, $I = 2.5 \text{ A} \therefore R_{dc} = \frac{25 \text{ V}}{2.5 \text{ A}} = 10 \Omega$
 b. From the graph, $I = 4.5 \text{ A} \therefore R_{dc} = \frac{60 \text{ V}}{4.5 \text{ A}} = 13.3 \Omega$


c. Because, for this resistor, R varies with current.

4.8 Computer-Aided Circuit Analysis

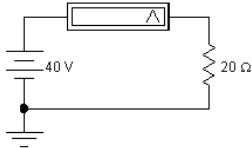
69. Use the following circuit. Set the source voltage and resistance as shown. Click the power ON/OFF switch and read the ammeter.




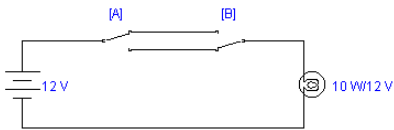
71. Click the power ON/OFF switch to the ON position, then operate switches A and B.



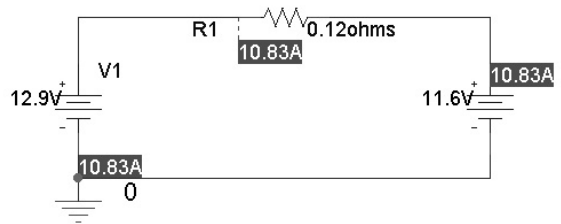73. Following the procedure outlined in the text, build the circuit on the screen. Double-click the default voltage value beside the V1 source symbol and change it to 12.9 V, then click OK. Similarly, set V2 to 11.6 V. Double-click the 1k default resistance value and set it to 0.12 ohm. Click the New Simulation Profile icon, enter a name, click Create, select Bias Point Analysis and click OK. Click the Run icon and when simulation is complete, close the inactive window that appears. Click the Bias Point Current Display icon to read the current—see below.



75. See below.

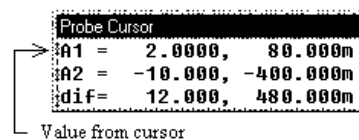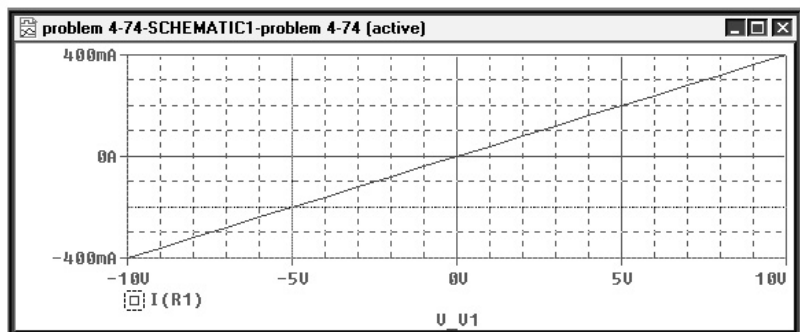

Series Circuits

5.2 Kirchhoff's Voltage Law

1. a. $V = +(3 \text{ A})(10 \Omega) = +30 \text{ V}$
b. $V = -(6 \text{ A})(15 \Omega) = -90 \text{ V}$
3. a. $V = +(3 \text{ A})(15 \Omega) = +45 \text{ V}$
b. $V = +(-4 \text{ A})(15 \Omega) = -60 \text{ V}$
c. $V = +(6 \text{ A})(15 \Omega) = +90 \text{ V}$
d. $V = +(-7 \text{ A})(15 \Omega) = -105 \text{ V}$
5. a. $V_1 = 33 \text{ V} - 16 \text{ V} - 10 \text{ V} = 7 \text{ V}$
b. $V_2 = \frac{12 \text{ W}}{3 \text{ A}} = 4 \text{ V}$
 $V_1 = 6 \text{ V} - 9 \text{ V} + 3 \text{ V} + 4 \text{ V} = 4 \text{ V}$
7. $V_3 = \frac{36 \text{ W}}{3 \text{ A}} = 12 \text{ V}$
 $V_4 = 24 \text{ V} - 10 \text{ V} - 12 \text{ V} = 2 \text{ V}$

5.3 Resistors in Series


9. a. $R_T = 3 \text{ k}\Omega + 2 \text{ k}\Omega + 5 \text{ k}\Omega = 10 \text{ k}\Omega$
b. $R_T = 360 \text{ k}\Omega + 580 \text{ k}\Omega + 2000 \text{ k}\Omega$
 $= 2940 \text{ k}\Omega$
 $= 2.94 \text{ M}\Omega$
c. $R = 3900 \Omega$
 $R_T = 6(3900 \Omega) = 23\,400 \Omega = 23.4 \text{ k}\Omega$
11. a. $R_T = 200 \Omega + 400 \Omega + 1000 \Omega + 50 \Omega = 1650 \Omega$
 $I = \frac{10 \text{ V}}{1.65 \text{ k}\Omega} = 6.06 \text{ mA}$
b. $R_T = 1.2 \text{ k}\Omega + 3.3 \text{ k}\Omega + 5.6 \text{ k}\Omega + 0.82 \text{ k}\Omega + 2.2 \text{ k}\Omega + 0.33 \text{ k}\Omega + 4.7 \text{ k}\Omega = 18.15 \text{ k}\Omega$
 $I = \frac{300 \text{ V}}{18.15 \text{ k}\Omega} = 16.5 \text{ mA}$
13. a. $I = \sqrt{\frac{P}{R}} = \sqrt{\frac{100 \text{ mW}}{1 \text{ k}\Omega}} = 10 \text{ mA}$
b. $R_T = \frac{130 \text{ V}}{10 \text{ mA}} = 13 \text{ k}\Omega$
c. $R = 13 \text{ k}\Omega - (3 \text{ k}\Omega + 4 \text{ k}\Omega + 1 \text{ k}\Omega) = 5 \text{ k}\Omega$
d. $V_{3 \text{ k}\Omega} = (3 \text{ k}\Omega)(10 \text{ mA}) = 30 \text{ V}$
 $V_{4 \text{ k}\Omega} = 40 \text{ V}$
 $V_{1 \text{ k}\Omega} = 10 \text{ V}$
 $V_R = 50 \text{ V}$
e. $P_T = (130 \text{ V})(10 \text{ mA}) = 1300 \text{ mW}$
 $P_{3 \text{ k}\Omega} = (10 \text{ mA})^2(3 \text{ k}\Omega) = 300 \text{ mW}$
 $P_{4 \text{ k}\Omega} = 400 \text{ mW}$
 $P_R = 500 \text{ mW}$
 $P_T = 300 \text{ mW} + 400 \text{ mW} + 100 \text{ mW} + 500 \text{ mW}$
 $= 1300 \text{ mW (as required.)}$
15. a. $I = \frac{4 \text{ V}}{100 \Omega} = 0.04 \text{ A} = 40 \text{ mA}$
- b. $V_{R_1} = (300 \text{ W})(0.04 \text{ A}) = 12 \text{ V}$
 $V_{R_3} = (250 \text{ W})(0.04 \text{ A}) = 10 \text{ V}$
- c. $V = 12 \text{ V} + 4 \text{ V} + 10 \text{ V} = 26 \text{ V}$
17. a. $V_{R_2} + V_{R_3} = 16 \text{ V} - 7.5 \text{ V} = 8.5 \text{ V}$
 $V_{R_2} = \frac{4.7 \text{ k}\Omega}{4.7 \text{ k}\Omega + 3.6 \text{ k}\Omega}(8.5 \text{ V}) = 4.81 \text{ V}$
 $V_{R_3} = \frac{3.6 \text{ k}\Omega}{4.7 \text{ k}\Omega + 3.6 \text{ k}\Omega}(8.5 \text{ V}) = 3.69 \text{ V}$
b. $I = \frac{8.5 \text{ V}}{(4.7 \text{ k}\Omega + 3.6 \text{ k}\Omega)} = 1.02 \text{ mA}$
c. $R_1 + \frac{7.5 \text{ V}}{1.02 \text{ mA}} + 7.32 \text{ k}\Omega$
19. a. $R_T = 120 \Omega + 39 \Omega + 78 \Omega + 220 \Omega = 457 \Omega$
b. $I = \frac{36 \text{ V}}{457 \Omega} = 0.0788 \text{ A} = 78.8 \text{ mA}$
c. $V_1 = (120 \Omega)(0.0788 \text{ A}) = 9.45 \text{ V}$
 $V_2 = 3.07 \text{ V}$
 $V_3 = 6.14 \text{ V}$
 $V_4 = 17.33 \text{ V}$
d. $V_T = 9.45 \text{ V} + 3.07 \text{ V} + 6.14 \text{ V} + 17.33 \text{ V}$
 $= 35.99 \text{ V} \cong E$
e. $P_1 = (0.0788 \text{ A})^2(120 \Omega) = 0.745 \text{ W}$
 $P_2 = 0.242 \text{ W}$
 $P_3 = 0.484 \text{ W}$
 $P_4 = 1.365 \text{ W}$
f. $R_1 : 1 \text{ W}$
 $R_2 : \frac{1}{4} \text{ W}$
 $R_3 : \frac{1}{2} \text{ W}$
 $R_4 : 2 \text{ W}$

$$\begin{aligned}
 \text{g. } P_T &= (36 \text{ V})(0.0788 \text{ A}) \\
 &= 2.836 \text{ W} \\
 &= 0.745 \text{ W} + 0.242 \text{ W} + 0.484 \text{ W} + 1.365 \text{ W}
 \end{aligned}$$

5.5 Interchanging Series Components

$$\begin{aligned}
 21. \quad R &= \frac{E - V_F}{I_F} \\
 &= \frac{24 \text{ V} - 3.8 \text{ V}}{10 \text{ mA}} \\
 &= 2.02 \text{ k}\Omega
 \end{aligned}$$

23.

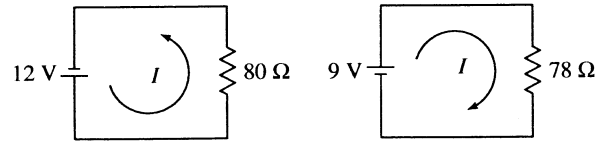

$$\text{Circuit 1: } I = \frac{12 \text{ V}}{80 \Omega} = 0.15 \text{ A}$$

$$\text{Circuit 2: } I = \frac{9 \text{ V}}{78 \text{ k}\Omega} = 0.115 \text{ mA}$$

5.6 Voltage Divider Rule

$$\begin{aligned}
 25. \quad &\text{Circuit 1:} \\
 &R_T = 24 \Omega \\
 &V_{6\Omega} = \left(\frac{6 \Omega}{24 \Omega} \right) 24 \text{ V} = 6 \text{ V} \\
 &V_{3\Omega} = 3 \text{ V} \\
 &V_{5\Omega} = 5 \text{ V} \\
 &V_{8\Omega} = 8 \text{ V} \\
 &V_{2\Omega} = 2 \text{ V} \\
 &V_T = 6 \text{ V} + 3 \text{ V} + 5 \text{ V} + 8 \text{ V} + 2 \text{ V} = 24 \text{ V} = E \\
 &\text{Circuit 2:} \\
 &R_T = 4.3 \text{ k}\Omega + 2.7 \text{ k}\Omega + 7.8 \text{ k}\Omega + 9.1 \text{ k}\Omega = 23.9 \text{ k}\Omega \\
 &V_{4.3 \text{ k}\Omega} = \left(\frac{4.3 \Omega}{23.9 \text{ k}\Omega} \right) (120 \text{ V}) = 21.6 \text{ V} \\
 &V_{2.7 \text{ k}\Omega} = 13.6 \text{ V} \\
 &V_{7.8 \text{ k}\Omega} = 39.2 \text{ V} \\
 &V_{9.1 \text{ k}\Omega} = 45.7 \text{ V} \\
 &V_T = 21.6 \text{ V} + 13.6 \text{ V} + 39.2 \text{ V} + 45.7 \text{ V} = 120.1 \text{ V} \\
 &\quad \cong (170 \text{ V} - 50 \text{ V}) \\
 &\quad = E_T
 \end{aligned}$$

$$\begin{aligned}
 27. \text{ a. } &\text{circuit (a)} \\
 &R_T = \frac{24 \text{ V}}{20 \text{ mA}} = 1.2 \text{ k}\Omega = R_1 + R_2 + R_3 \\
 &R_1 + 3.5 R_1 + 2(3.5 R_1) = 1.2 \text{ k}\Omega \\
 &R_1 + 0.104 \text{ k}\Omega \\
 &R_2 = 0.365 \text{ k}\Omega \\
 &R_3 = 0.730 \text{ k}\Omega \\
 \text{b. } &V_1 = \left(\frac{0.104 \text{ k}\Omega}{1.2 \text{ k}\Omega} \right) 24 \text{ V} = 2.09 \text{ V} \\
 &V_2 = 7.30 \text{ V} \\
 &V_3 = 14.61 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{c. } P_1 &= (20 \text{ mA})^2 (0.104 \text{ k}\Omega) = 41.7 \text{ mW} \\
 P_2 &= 146.1 \text{ mW} \\
 P_3 &= 292.2 \text{ mW}
 \end{aligned}$$

$$\begin{aligned}
 \text{a. } &\text{circuit (b)} \\
 &V_2 = \frac{R_2}{R_1 + R_2 + R_3} (50 \text{ V}) = \frac{R_2}{8 R_2} (50 \text{ V}) = 6.25 \text{ V} \\
 &R_2 = \frac{V_2^2}{P_2} = \frac{(6.25 \text{ V})^2}{0.160 \text{ W}} = 244 \Omega
 \end{aligned}$$

$$\begin{aligned}
 R_1 &= 4(244 \Omega) = 977 \Omega \\
 R_3 &= 3(244 \Omega) = 732 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \text{b. } V_2 &= 6.25 \text{ V} \\
 V_1 &= 25.0 \text{ V} \\
 V_3 &= 8.75 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{c. } P_1 &= \frac{(25.0 \text{ V})^2}{977 \Omega} = 640 \text{ mW} \\
 P_3 &= 480 \text{ mW} \\
 P_2 &= 160 \text{ mW (given)}
 \end{aligned}$$

$$\begin{aligned}
 29. \text{ a. } R_T &= 24(25 \Omega) = 600 \Omega \\
 I &= \frac{120 \text{ V}}{600 \Omega} = 0.2 \text{ A} \\
 \text{b. } V &= \left(\frac{25 \Omega}{600 \Omega} \right) 120 \text{ V} = 5.0 \text{ V} \\
 \text{c. } P &= \frac{(5 \text{ V})^2}{25 \Omega} = 1 \text{ W} \\
 \text{d. } R_T &= 22(25 \Omega) = 550 \Omega \\
 I &= \frac{120 \text{ V}}{550 \Omega} = 0.218 \text{ A} \\
 V &= \left(\frac{25 \Omega}{550 \Omega} \right) 120 \text{ V} = 5.45 \text{ V} \\
 P &= \frac{(5.45 \text{ V})^2}{25 \Omega} = 1.19 \text{ W}
 \end{aligned}$$

e. Since each of the remaining bulbs now dissipates 20% more power, the life expectancy will decrease.

5.8 Voltage Subscripts


31. circuit (a)
 $V_{ab} = V_1 + V_2 = 2.09 \text{ V} + 7.30 \text{ V} = 9.39 \text{ V}$
 $V_{bc} = V_3 = 14.61 \text{ V}$

circuit (b)
 $V_{ab} = 25.0 \text{ V}$
 $V_{bc} = 6.25 \text{ V}$

33. circuit (a)
 $I = \frac{54 \text{ V}}{3 \text{ k}\Omega + 9 \text{ k}\Omega + 6 \text{ k}\Omega} = 3 \text{ mA}$
 $V_{3 \text{ k}\Omega} = (3 \text{ mA})(3 \text{ k}\Omega) = 9 \text{ V}$
 $V_{9 \text{ k}\Omega} = 27 \text{ V}$
 $V_{6 \text{ k}\Omega} = 18 \text{ V}$
 $V_a = +(3 \text{ mA})(9 \text{ k}\Omega + 6 \text{ k}\Omega) = 45 \text{ V}$

circuit (b)
 $E_T = 6 \text{ V} + 3 \text{ V} = 9 \text{ V}$
 $V_{330 \Omega} = \left(\frac{330 \Omega}{330 \Omega + 670 \Omega} \right) 9 \text{ V} = 2.97 \text{ V}$
 $V_{670 \Omega} = 6.03 \text{ V}$
 $V_a = 6.03 - 3 \text{ V} = 3.03 \text{ V}$

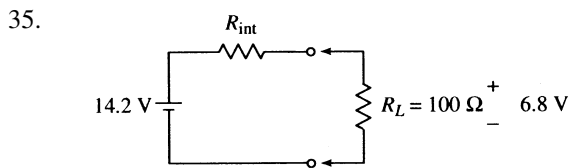5.9 Internal Resistance of Voltage Sources



a. $V_R = 14.2 \text{ V} - 6.8 \text{ V} = 7.4 \text{ V}$

$$I = \frac{6.8 \text{ V}}{100 \Omega} = 0.068 \text{ A}$$

$$R_{\text{int}} = \frac{7.4 \text{ V}}{0.068 \text{ A}} = 109 \Omega$$



b. $V_L = \left(\frac{200 \Omega}{(109 \Omega + 200 \Omega)} \right) 14.2 \text{ V} = 9.20 \text{ V}$

5.10 Ammeter Loading Effects


37. circuit (a)
 $I_{\text{actual}} = \frac{15 \text{ V}}{(10 \text{ k}\Omega + 12 \text{ k}\Omega + 18 \text{ k}\Omega)} = 0.375 \text{ mA}$
 $I_{\text{measured}} = \frac{15 \text{ V}}{(10 \text{ k}\Omega + 12 \text{ k}\Omega + 18 \text{ k}\Omega + 0.050 \text{ k}\Omega)} = 0.374532 \text{ mA}$
 loading error = $\left(\frac{0.375 \text{ mA} - 0.374532 \text{ mA}}{0.375 \text{ mA}} \right) \times 100\% = 0.125\%$

circuit (b)
 $I_{\text{actual}} = \frac{0.15 \text{ V}}{(100 \Omega + 120 \Omega + 180 \Omega)} = 0.375 \text{ mA}$
 $I_{\text{measured}} = \frac{0.15 \text{ V}}{(100 \Omega + 120 \Omega + 180 \Omega + 50 \Omega)} = 0.333 \text{ mA}$
 loading error = $\frac{(0.375 \text{ mA} - 0.333 \text{ mA})}{0.375 \text{ mA}} \times 100\% = 11.1\%$

5.11 Circuit Analysis Using Computers

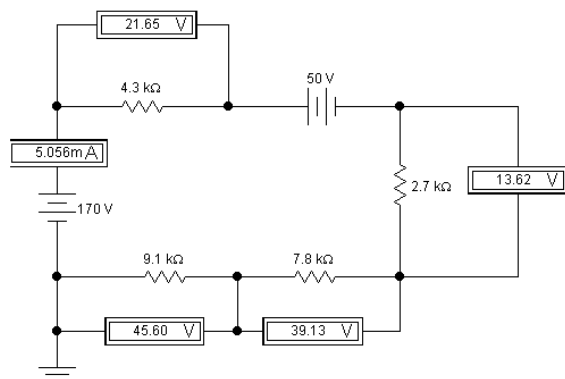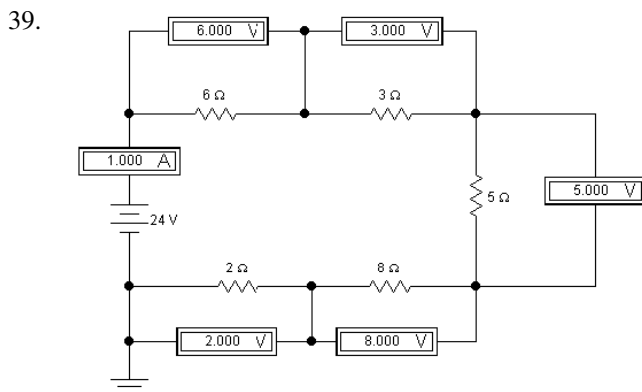

41.

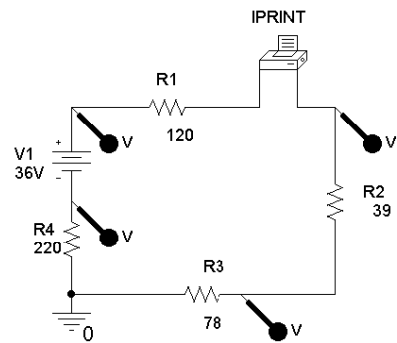


Parallel Circuits

6.1 Parallel Circuits

1. a. A and B are in series
D and E are in series
C and F are in parallel
- b. B, C, and D are in parallel
- c. A and B are in parallel
D and F are in parallel
C and E are in series
- d. A, B, C, and D are in parallel

3.

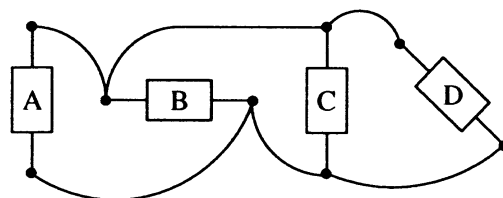

6.2 Kirchhoff's Current Law

5. a. $I_1 = 5\text{ A} - 2\text{ A} = 3\text{ A}$ (downward)
 $I_2 = 4\text{ A} - 3\text{ A} = 1\text{ A}$ (left)
- b. $I_1 = 6\text{ A} + 1\text{ A} = 7\text{ A}$ (right)
 $I_2 = 7\text{ A} - 2\text{ A} - 3\text{ A} = 2\text{ A}$ (upward)
 $I_3 = 4\text{ A} + 3\text{ A} = 7\text{ A}$ (downward)
- c. $I_1 = 15\text{ mA} - 5\text{ mA} - 6\text{ mA} = 4\text{ mA}$ (right)
 $I_2 = 5\text{ mA} + 4\text{ mA} + 6\text{ mA} + 7\text{ mA} - 2\text{ mA} = 20\text{ mA}$ (right)
7. a. $I_1 = \frac{50\text{ V}}{40\ \Omega} = 1.25\text{ A}$
 $I_2 = \frac{5\text{ V}}{60\ \Omega} = 0.0833\text{ A}$
 $I_3 = 1.25\text{ A} - 0.0833\text{ A} = 1.167\text{ A}$
 $I_4 = 0.0833 + 1.167\text{ A} = 1.25\text{ A}$
- b. $R_3 = \frac{5\text{ V}}{1.167\text{ A}} = 4.29\ \Omega$
9. a. $I_1 = 500\text{ mA} - 200\text{ mA} - 100\text{ mA} = 200\text{ mA}$
 $I_2 = 500\text{ mA}$
 $I_3 = 200\text{ mA} - 50\text{ mA} = 150\text{ mA}$
 $I_4 = 200\text{ mA}$
- b. $V = (25\ \Omega)(100\text{ mA}) = 2500\text{ mV}$
 $= 2.5\text{ V}$
- c. $R_1 = \frac{2.5\text{ V}}{200\text{ mA}} = 12.5\ \Omega$
 $R_3 = \frac{2.5\text{ V}}{150\text{ mA}} = 15.7\ \Omega$
 $R_4 = \frac{2.5\text{ V}}{50\text{ mA}} = 50\ \Omega$

6.3 Resistors in Parallel

11. a. $R_T = \frac{(4\ \Omega)(6\ \Omega)}{4\ \Omega + 6\ \Omega} = 2.4\ \Omega$
- b. $R_T = \frac{1}{\frac{1}{480\ \Omega} + \frac{1}{240\ \text{k}\Omega} + \frac{1}{40\ \text{k}\Omega}} = 32\ \text{k}\Omega$
- c. $R_T = \frac{1}{\frac{1}{8.2\ \text{k}\Omega} + \frac{1}{10\ \text{k}\Omega} + \frac{1}{39\ \text{k}\Omega}} = 4.04\ \text{k}\Omega$
13. a. $\frac{1}{R} = \frac{1}{400\ \text{k}\Omega} - \frac{1}{500\ \text{k}\Omega} = 0.5\ \mu\text{S}$
 $R = 2.0\ \text{M}\Omega$
- b. $\frac{1}{R} = \frac{1}{30\ \Omega} - \left(\frac{1}{50\ \Omega} + \frac{1}{90\ \Omega} \right) = 2.22\ \text{mS}$
 $R = 450\ \Omega$
15. a. $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{4R_1} + \frac{1}{\frac{R_1}{5}} = \frac{6.25}{R_1} = \frac{1}{200}\ \Omega$
 $R_1 = 1250\ \Omega$
 $R_2 = 5000\ \Omega$
 $R_3 = 250\ \Omega$

- b. $I_{R_1} = \frac{2 \text{ A}}{5} = 0.40 \text{ A}$
 $I_{R_2} = \frac{2 \text{ A}}{(5)(4)} = 0.10 \text{ A}$
- c. $I = 0.40 \text{ A} + 0.10 \text{ A} + 2.0 \text{ A} = 2.5 \text{ A}$
17. a. $V_{R_1} = V_{R_2} = (2 \text{ mA})(450 \Omega) = 900 \text{ mV}$
- b. $I_2 = \frac{900 \text{ mV}}{200 \Omega} = 4.5 \text{ mA}$
19. a. $R_T = \frac{1}{\frac{1}{600 \Omega} + \frac{1}{800 \Omega} + \frac{1}{800 \Omega}} = 240 \Omega$
- b. $R_T = \frac{1}{\frac{1}{27 \text{ k}\Omega} + \frac{1}{33 \text{ k}\Omega} + \frac{1}{56 \text{ k}\Omega} + \frac{1}{47 \text{ k}\Omega}} = 9.392 \text{ k}\Omega$
- c. $R_{T_1} = 6 \text{ k}\Omega \parallel 3 \text{ k}\Omega = 2 \text{ k}\Omega$
 $R_{T_2} = 9 \text{ k}\Omega \parallel 9 \text{ k}\Omega \parallel 9 \text{ k}\Omega = 3 \text{ k}\Omega$
 $R_T = \frac{(2 \text{ k}\Omega)(3 \text{ k}\Omega)}{2 \text{ k}\Omega + 3 \text{ k}\Omega} = 1.2 \text{ k}\Omega$
21. $I_T = \frac{32 \text{ V}}{16 \text{ k}\Omega} = 2.0 \text{ mA}$
 $I_1 + 3I_1 + 1.5(3I_1) = 2.0 \text{ mA}$
 $I_1 = 0.2353 \text{ mA}$
 $I_2 = 0.7059 \text{ mA}$
 $I_3 = 1.0589 \text{ mA}$
 $R_1 = \frac{32 \text{ V}}{0.2353 \text{ mA}} = 136 \text{ k}\Omega$
 $R_2 = \frac{32 \text{ V}}{0.7059 \text{ mA}} = 45.3 \text{ k}\Omega$
 $R_3 = \frac{32 \text{ V}}{1.0589 \text{ mA}} = 30.2 \text{ k}\Omega$
23. a. $R_T = 12.5 \text{ k}\Omega$
- b. $R_T = 0 \Omega$ (short circuit)
- c. $R_T = 75 \Omega$
25. $R_T \equiv 30 \Omega \parallel 30 \Omega = 15 \Omega$

6.4 Voltage Sources in Parallel

27. $I = \frac{20 \text{ V}}{100 \Omega} = 0.2 \text{ A}$
 $I_1 = \frac{0.2 \text{ A}}{2} = 0.1 \text{ A} = I_2$

6.5 Current Divider Rule

29. a. $I_1 = \left(\frac{2 \Omega}{2 \Omega + 8 \Omega} \right) (10 \text{ A}) = 2 \text{ A}$
 $I_2 = \left(\frac{8 \Omega}{2 \Omega + 8 \Omega} \right) (10 \text{ A}) = 8 \text{ A}$
- b. $I_1 = \left(\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 3 \text{ k}\Omega} \right) (16 \text{ mA}) = 4 \text{ mA}$
 $I_2 = \left(\frac{3 \text{ k}\Omega}{1 \text{ k}\Omega + 3 \text{ k}\Omega} \right) (16 \text{ mA}) = 12 \text{ mA}$
31. a. $R_T = \frac{1}{\frac{1}{4.7 \text{ k}\Omega} + \frac{1}{3.3 \text{ k}\Omega} + \frac{1}{1.0 \text{ k}\Omega} + \frac{1}{2.2 \text{ k}\Omega}} = 0.508 \text{ k}\Omega$
 $I_1 = \left(\frac{0.508 \text{ k}\Omega}{4.7 \text{ k}\Omega} \right) 60 \text{ mA} = 6.48 \text{ mA}$
 $I_2 = \left(\frac{0.508 \text{ k}\Omega}{3.3 \text{ k}\Omega} \right) 60 \text{ mA} = 9.23 \text{ mA}$
 $I_3 = 30.45 \text{ mA}$
 $I_4 = 13.84 \text{ mA}$
- b. $R'_T = \frac{1}{\frac{1}{200 \Omega} + \frac{1}{400 \Omega} + \frac{1}{600 \Omega}} = 109.1 \Omega$
 $I_4 = \left(\frac{109.1 \Omega}{109.1 \Omega + 300 \Omega} \right) 150 \text{ mA} = 40 \text{ mA}$
33. $I_5 = \left(\frac{300 \Omega}{109.1 \Omega + 300 \Omega} \right) 150 \text{ mA} = 110 \text{ mA}$
 $I_1 = \left(\frac{109.1 \Omega}{200 \Omega} \right) 110 \text{ mA} = 60 \text{ mA}$
 $I_2 = \left(\frac{109.1 \Omega}{400 \Omega} \right) 110 \text{ mA} = 30 \text{ mA}$
 $I_3 = \left(\frac{109.1 \Omega}{600 \Omega} \right) 110 \text{ mA} = 20 \text{ mA}$
35. a. $R_T = 24 \Omega \parallel 48 \Omega \parallel 16 \Omega = 8 \Omega$
- b. $I = \frac{12 \text{ V}}{8 \Omega} = 1.50 \text{ A}$
- c. $I_1 = \left(\frac{8 \Omega}{24 \Omega} \right) 1.50 \text{ A} = 0.50 \text{ A}$
 $I_2 = \frac{I_1}{2} = 0.25 \text{ A}$
 $I_3 = \left(\frac{8 \Omega}{16 \Omega} \right) 1.50 \text{ A} = 0.75 \text{ A}$

$$\begin{aligned} \text{d. } \sum I_{\text{in}} &= 1.50 \text{ A} \\ \sum I_{\text{out}} &= 0.50 \text{ A} + 0.25 \text{ A} + 0.75 \text{ A} = 1.50 \text{ A} \\ \sum I_{\text{in}} &= \sum I_{\text{out}} \end{aligned}$$

6.6 Analysis of Parallel Circuits

$$37. \text{ a. } R_T = 60\Omega \parallel 100\Omega \parallel 75\Omega = 25\Omega$$

$$\text{b. } I = \frac{240 \text{ V}}{25\Omega} = 9.60 \text{ A}$$

$$I_1 = \frac{240 \text{ V}}{60\Omega} = 4.0 \text{ A}$$

$$I_2 = \frac{240 \text{ V}}{100\Omega} = 2.40 \text{ A}$$

$$I_3 = \frac{240 \text{ V}}{75\Omega} = 3.20 \text{ A}$$

$$I_4 = 2.40 \text{ A} + 3.20 \text{ A} = 5.60 \text{ A}$$

$$\text{c. } \sum I_{\text{in}} = 9.60 \text{ A}$$

$$\sum I_{\text{out}} = 4.0 \text{ A} + 2.40 \text{ A} + 3.20 \text{ A} + 5.60 \text{ A} = 9.60 \text{ A}$$

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

$$\text{d. } P_1 = (4.0 \text{ A})^2(60\Omega) = 960 \text{ W}$$

$$P_2 = (2.40 \text{ A})^2(100\Omega) = 576 \text{ W}$$

$$P_3 = (3.20 \text{ A})^2(75\Omega) = 768 \text{ W}$$

$$P_T = (240 \text{ V})(9.60 \text{ A}) = 2304 \text{ W}$$

$$P_T = P_1 + P_2 + P_3$$

$$39. \text{ a. } I_1 = \frac{20 \text{ V}}{20\Omega} = 1.00 \text{ A}$$

$$I_2 = 2.0 \text{ A}$$

$$I_3 = 5.0 \text{ A}$$

$$I_4 = 4.0 \text{ A}$$

$$\text{b. } I = 1.0 \text{ A} + 2.0 \text{ A} + 5.0 \text{ A} + 4.0 \text{ A} = 12.0 \text{ A}$$

$$\text{c. } P_1 = 20 \text{ W}$$

$$P_2 = 40 \text{ W}$$

$$P_3 = 100 \text{ W}$$

$$P_4 = 80 \text{ W}$$

$$41. \text{ a. } R_3 = \frac{48 \text{ V}}{12 \text{ mA}} = 4 \text{ k}\Omega$$

$$R_4 = \frac{48 \text{ V}}{(50 \text{ mA} - 30 \text{ mA} - 12 \text{ mA})} = 6 \text{ k}\Omega$$

$$R_1 = \frac{V^2}{P} = \frac{(48 \text{ V})^2}{1.152 \text{ W}} = 2 \text{ k}\Omega$$

$$R_T = \frac{48 \text{ V}}{50 \text{ mA}} = 0.96 \text{ k}\Omega$$

$$R_2 = \frac{1}{\frac{1}{0.96 \text{ k}\Omega} - \frac{1}{4 \text{ k}\Omega} - \frac{1}{6 \text{ k}\Omega} - \frac{1}{2 \text{ k}\Omega}} = 8 \text{ k}\Omega$$

$$\text{b. } I_{R1} = \frac{1.152 \text{ W}}{48 \text{ V}} = 24 \text{ mA}$$

$$I_{R2} = 30 \text{ mA} - 24 \text{ mA} = 6 \text{ mA}$$

$$I_{R4} = 50 \text{ mA} - 30 \text{ mA} - 12 \text{ mA} = 8 \text{ mA}$$

$$\text{c. } I_1 = 12 \text{ mA} + 8 \text{ mA} = 20 \text{ mA}$$

$$I_2 = 20 \text{ mA} + 24 \text{ mA} + 6 \text{ mA} = 50 \text{ mA}$$

$$\text{d. } P_2 = (6 \text{ mA})(48 \text{ V}) = 288 \text{ mW}$$

$$P_3 = (12 \text{ mA})(48 \text{ V}) = 576 \text{ mW}$$

$$P_4 = (8 \text{ mA})(48 \text{ V}) = 384 \text{ mW}$$

$$43. \quad I_1 = \frac{1000 \text{ W}}{120 \text{ V}} = 8.33 \text{ A}$$

$$I_2 = \frac{120 \text{ V}}{24\Omega} = 5.00 \text{ A}$$

$$I_3 = \frac{120 \text{ V}}{48\Omega} = 2.50 \text{ A}$$

$$I_4 = 7.50 \text{ A}$$

$$I_T = 15.83 \text{ A}$$

The rated current of the fuse will be exceeded; the fuse will “blow” open.

6.7 Voltmeter Loading Effects

$$45. \text{ a. } V_{\text{meas}} = \left(\frac{M\Omega}{1 \text{ M}\Omega + 0.5 \text{ M}\Omega} \right) 30 \text{ V} = 20 \text{ V}$$

$$\text{b. } V_{ab} = 30 \text{ V}$$


$$\text{loading effect} = \frac{30 \text{ V} - 20 \text{ V}}{30 \text{ V}} \times 100\% = 33.3\%$$

$$47. \quad 1.2 \text{ V} = \left(\frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 1000 \text{ k}\Omega} \right) E$$


$$E = 25.2 \text{ V}$$

6.8 Computer Analysis


49.

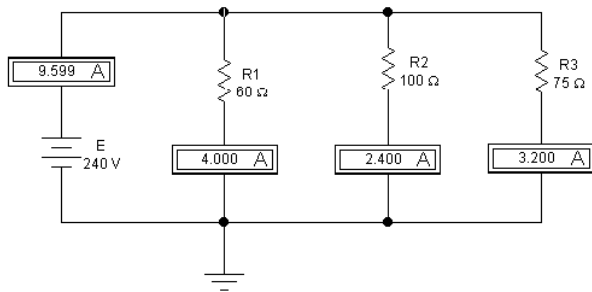

53.

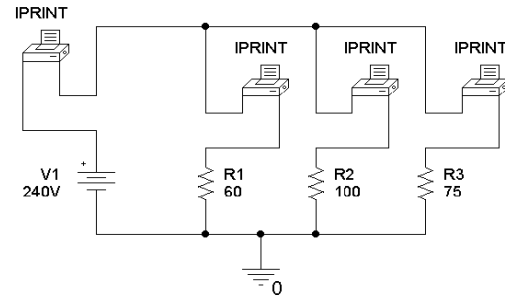

51.

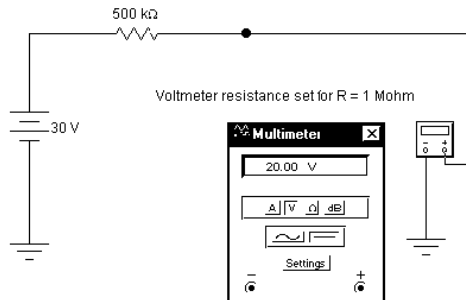


Series-Parallel Circuits

7.1 The Series-Parallel Network


1. a. $R_T = R_1 + R_5 + [(R_2 + R_3) \parallel R_4]$
 b. $R_T = (R_1 \parallel R_2) + (R_3 \parallel R_4)$
3. a. $R_{T1} = R_1 + [(R_3 + R_4) \parallel R_2] + R_5$
 $R_{T2} = R_5$
 b. $R_{T1} = R_1 + (R_2 \parallel R_3 \parallel R_5)$
 $R_{T1} = R_5 \parallel R_3 \parallel R_2$
 (R_4 is shorted)

5. a.

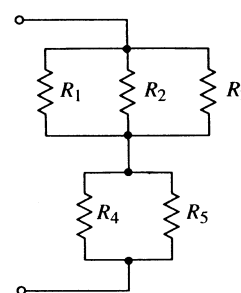

(one possible solution)


b.

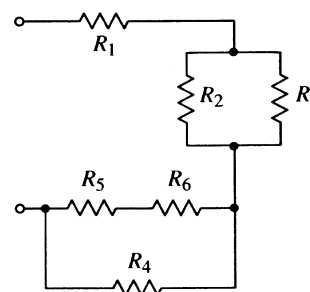

(one possible solution)

7.2 Analysis of Series-Parallel Circuits

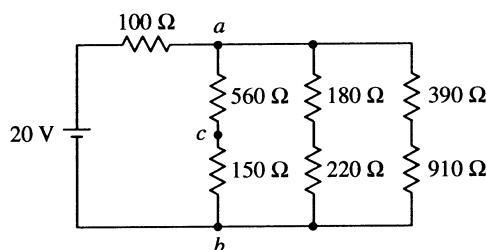7. a. $R_T = 300 \Omega + [4 \text{ k}\Omega \parallel (200 \Omega + 300 \Omega + 500 \Omega)] + 400 \Omega = 1500 \Omega$
 b. $R_T = 5.1 \text{ k}\Omega \parallel [1.2 \text{ k}\Omega + \{4.7 \text{ k}\Omega \parallel (3.3 \text{ k}\Omega + 5.6 \Omega)\}] = 2.33 \text{ k}\Omega$
9. $R_{ab} = 80 \Omega + 40 \Omega + [60 \Omega \parallel 60 \Omega \parallel (10 \Omega + 20 \Omega + 30 \Omega)] = 140 \Omega$
 $R_{cd} = 10 \Omega \parallel [20 \Omega + 30 \Omega + (60 \Omega \parallel 60 \Omega)] = 8.89 \Omega$
11. a. $R_T = 100 \Omega + [(560 \Omega + 150 \Omega) \parallel (180 \Omega + 220 \Omega \parallel (390 \Omega + 910 \Omega))]$
 $= 100 \Omega + 710 \Omega \parallel 400 \Omega \parallel 1300 \Omega$
 $= 313.78 \Omega \cong 314 \Omega$



- b. $I_T = \frac{20 \text{ V}}{314 \Omega} = 63.7 \text{ mA}$

$$I_1 = \left(\frac{213.78 \Omega}{560 \Omega + 150 \Omega} \right) 63.7 \text{ mA} = 19.2 \text{ mA}$$

$$I_2 = 63.7 \text{ mA} - 19.2 \text{ mA} = 44.5 \text{ mA}$$

$$I_3 = \left(\frac{213.78 \Omega}{180 \Omega + 220 \Omega} \right) 63.7 \text{ mA} = 34.1 \text{ mA}$$

$$I_4 = \left(\frac{213.78 \Omega}{390 \Omega + 910 \Omega} \right) 63.7 \text{ mA} = 10.4 \text{ mA}$$

- c. $V_{ab} = +(34.1 \text{ mA})(180 \Omega + 220 \Omega) = 13.6 \text{ V}$
 $V_{bc} = -(19.2 \text{ mA})(150 \Omega) = -2.88 \text{ V}$

13. a. $R_T = 1 \text{ k}\Omega + 2 \text{ k}\Omega + 5 \text{ k}\Omega \parallel [1 \text{ k}\Omega + \{6 \text{ k}\Omega \parallel (3 \text{ k}\Omega + 6 \text{ k}\Omega)\}] = 5.396 \text{ k}\Omega$

$$I_1 = \frac{28 \text{ V}}{5.396 \text{ k}\Omega} = 5.189 \text{ mA}$$

$$I_2 = \left(\frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + 4.6 \text{ k}\Omega} \right) 5.189 \text{ mA} = 2.702 \text{ mA}$$

$$I_3 = \left(\frac{6 \text{ k}\Omega}{6 \text{ k}\Omega + 3 \text{ k}\Omega + 6 \text{ k}\Omega} \right) 2.702 \text{ mA} = 1.081 \text{ mA}$$

$$I_4 = 5.189 \text{ mA} - 2.702 \text{ mA} = 2.486 \text{ mA}$$

$$I_5 = 2.702 \text{ mA} - 1.081 \text{ mA} = 1.621 \text{ mA}$$

$$I_6 = 2.702 \text{ mA}$$

b. $V_{ab} = +(5 \text{ k}\Omega)(2.486 \text{ mA}) = 12.432 \text{ V}$

$$V_{cd} = +(6 \text{ k}\Omega)(1.621 \text{ mA}) = 9.729 \text{ V}$$

c. $P_T = (28 \text{ V})(5.189 \text{ mA}) = 145.3 \text{ mW}$

$$P_1 = 26.9 \text{ mW} \quad P_5 = 15.8 \text{ mW}$$

$$P_2 = 7.3 \text{ mW} \quad P_6 = 7.0 \text{ mW}$$


$$P_3 = 3.5 \text{ mW} \quad P_7 = 53.9 \text{ mW}$$

$$P_4 = 30.9 \text{ mW}$$

$$P_T = \sum_{n=1}^7 P_n = 145.3 \text{ mW}$$

15. circuit (a)

a.

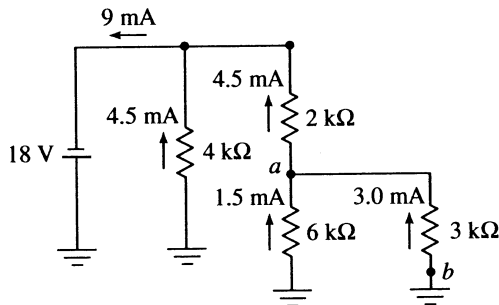

$$R_T = 4 \text{ k}\Omega \parallel (2 \text{ k}\Omega + 6 \text{ k}\Omega \parallel 3 \text{ k}\Omega) = 2 \text{ k}\Omega$$

$$I_T = \frac{18 \text{ V}}{2 \text{ k}\Omega} = 9.0 \text{ mA}$$

$$I_2 = \frac{18 \text{ V}}{4 \text{ k}\Omega} = 4.5 \text{ mA}$$

$$I_1 = \frac{18 \text{ V}}{2 \text{ k}\Omega + (6 \text{ k}\Omega \parallel 3 \text{ k}\Omega)} = 4.5 \text{ mA}$$

$$I_3 = \left(\frac{3 \text{ k}\Omega}{6 \text{ k}\Omega + 3 \text{ k}\Omega} \right) 4.5 \text{ mA} = 1.5 \text{ mA}$$

b. $V_{ab} = -(1.5 \text{ mA})(6 \text{ k}\Omega) = -9.0 \text{ V}$

c. $P_T = \frac{(18 \text{ V})^2}{2 \text{ k}\Omega} = 162 \text{ mW}$

$$P_{6\text{k}\Omega} = (1.5 \text{ mA})^2(6 \text{ k}\Omega) = 13.5 \text{ mW}$$

$$P_{3\text{k}\Omega} = (3.0 \text{ mA})^2(3 \text{ k}\Omega) = 27.0 \text{ mW}$$

$$P_{2\text{k}\Omega} = (4.5 \text{ mA})^2(2 \text{ k}\Omega) = 40.5 \text{ mW}$$

$$P_{4\text{k}\Omega} = (4.5 \text{ mA})^2(4 \text{ k}\Omega) = 81.0 \text{ mW}$$

$$P_T = \sum_{n=1}^4 P_n = 162 \text{ mW}$$

15. circuit (b)

a. $R_T = 10 \Omega + 16 \Omega \parallel [5 \Omega \parallel (8 \Omega + 4 \Omega)] = 15.76 \Omega$

$$I_T = I_1 = \frac{12 \text{ V} - 3 \text{ V}}{15.76 \Omega} = 0.571 \text{ A}$$

$$I_2 = \left(\frac{16 \Omega}{16 \Omega + 9 \Omega} \right) 0.571 \text{ A} = 0.365 \text{ A}$$

$$I_3 = \left(\frac{6 \Omega}{6 \Omega + 12 \Omega} \right) 0.365 \text{ A} = 0.122 \text{ A}$$

$$I_4 = 0.471 \text{ A} - 0.122 \text{ A} = 0.449 \text{ A}$$

b. $V_{ab} = -(0.365 \text{ A})(5 \Omega) = -1.827 \text{ V}$

c. $P_T = (9 \text{ V})(0.571 \text{ A}) = 5.14 \text{ W}$

$$P_{10\Omega} = (0.571 \text{ A})^2(10 \Omega) = 3.26 \text{ W}$$

$$P_{16\Omega} = (0.206 \text{ A})^2(16 \Omega) = 0.68 \text{ W}$$

$$P_{5\Omega} = (0.365 \text{ A})^2(5 \Omega) = 0.67 \text{ W}$$

$$P_{6\Omega} = (0.244 \text{ A})^2(6 \Omega) = 0.36 \text{ W}$$

$$P_{8\Omega} = (0.122 \text{ A})^2(8 \Omega) = 0.12 \text{ W}$$

$$P_{4\Omega} = (0.122 \text{ A})^2(4 \Omega) = 0.06 \text{ W}$$

$$P_T = \sum_{n=1}^6 P_n = 5.15 \text{ W}$$

7.3 Applications of Series—Parallel Circuits

17. Zener is on:

$$V_1 = 14.0 \text{ V}$$

$$I_1 = \frac{24 \text{ V} - 10 \text{ V}}{150 \Omega} = 93.3 \text{ mA}$$

$$V_2 = 2.06 \text{ V}$$

$$V_3 = 7.94 \text{ V}$$

$$I_2 = I_3 = \frac{10 \text{ V}}{39 \Omega + 150 \Omega} = 52.9 \text{ mA}$$

$$I_Z = 93.3 \text{ mA} - 52.9 \text{ mA} = 40.4 \text{ mA}$$

$$P_T = (24 \text{ V})(93.3 \text{ mA}) = 2240 \text{ mW}$$

$$P_Z = 404.2 \text{ mW}$$

$$P_1 = 1306.7 \text{ mW}$$

$$P_2 = 109.2 \text{ mW}$$

$$P_3 = 419.9 \text{ mW}$$

19. $R_{\min}$:

$$V_L = \left(\frac{R}{R + 80 \, \Omega} \right) 20 \, \text{V} = 5.6 \, \text{V}$$

$$(20 \, \text{V})R = (5.6 \, \text{V})R + 448 \, \text{V} \cdot \Omega$$

$$R_{\min} \frac{448 \, \text{V} \cdot \Omega}{14.4 \, \text{V}} = 31.1 \, \Omega$$
 $R_{\max}$:

$$I_1 = \frac{20 \, \text{V} - 5.6 \, \text{V}}{80 \, \Omega} = 180 \, \text{mA}$$

$$I_{Z(\max)} = \frac{1 \, \text{W}}{5.6 \, \text{V}} = 178.57 \, \text{mA}$$

$$I_{L(\min)} = 1.43 \, \text{mA}$$

$$R_{\max} = \frac{5.6 \, \text{V}}{1.43 \, \text{mA}} = 3.92 \, \text{k}\Omega$$

$$R = 31.1 \, \Omega \rightarrow 3900 \, \Omega$$
21. Using KVL: $(750 \, \Omega)I_E + 0.6 \, \text{V} + (7.5 \, \text{k}\Omega)I_B - 2 \, \text{V} = 0$
 But $I_E \cong 100 I_B$

$$(750 \, \Omega)(100I_B) + (7.5 \, \text{k}\Omega)I_B = 1.4 \, \text{V}$$

$$I_B = \frac{1.4 \, \text{V}}{82.5 \, \text{k}\Omega} = 17.0 \, \mu\text{A}$$

$$I_E \cong 1.70 \, \text{mA} \cong I_C$$

$$V_B = (7.5 \, \text{k}\Omega)(17.0 \, \mu\text{A}) - 2.0 \, \text{V} = -1.87 \, \text{V}$$

$$V_{CE} = -16 \, \text{V} + (3.9 \, \text{k}\Omega)(1.7 \, \text{mA}) + (0.75 \, \text{k}\Omega)(1.7 \, \text{mA}) = -8.10 \, \text{V}$$
23. a. $I_D = 3.6 \, \text{mA}$

$$V_S = -(-2.0 \, \text{V}) = 2.0 \, \text{V}$$
- b.
$$R_S = \frac{2.0 \, \text{V}}{3.6 \, \text{mA}} = 0.556 \, \text{k}\Omega = 556 \, \Omega$$
- c.
$$V_{DS} = 15 \, \text{V} - (3.6 \, \text{mA})(1.5 \, \text{k}\Omega + 0.556 \, \text{k}\Omega) = +7.6 \, \text{V}$$
25.
$$V_B = \left(\frac{4 \, \text{k}\Omega}{4 \, \Omega + 32 \, \text{k}\Omega} \right) (18 \, \text{V}) = 2.00 \, \text{V}$$

$$V_E = 2.00 - 0.7 \, \text{V} = 1.30 \, \text{V}$$

$$I_E = \frac{1.30 \, \text{V}}{0.4 \, \text{k}\Omega} = 3.25 \, \text{mA} \cong I_C$$

$$V_{CE} = 18 \, \text{V} - 3.25 \, \text{mA} (2.40 \, \text{k}\Omega + 0.40 \, \text{k}\Omega) = 8.90 \, \text{V}$$

7.4 Potentiometers

27. a. For $R_2 = 0 \, \Omega$: $V_{bc} = V_L = 0 \, \text{V}$
 For $R_2 = 10 \, \text{k}\Omega$:

$$V_{bc} = V_L = \left(\frac{10 \, \text{k}\Omega \parallel 10 \, \text{k}\Omega}{20 \, \text{k}\Omega + 10 \, \text{k}\Omega \parallel 10 \, \text{k}\Omega} \right) 36 \, \text{V} = 7.2 \, \text{V}$$

$$V_L = 0 \rightarrow 7.2 \, \text{V}$$
- b.
$$V_L = \frac{(2.5 \, \text{k}\Omega \parallel 10 \, \text{k}\Omega)}{(2.5 \, \text{k}\Omega \parallel 10 \, \text{k}\Omega) + 20 \, \text{k}\Omega + (10 \, \text{k}\Omega - 2.5 \, \text{k}\Omega)} \times 36 \, \text{V} = 2.44 \, \text{V}$$
 If R_L is removed:

$$V_{ab} = \frac{7.5 \, \text{k}\Omega}{20 \, \text{k}\Omega + 10 \, \text{k}\Omega} = 9.0 \, \text{V}$$
29.
$$R_T = (200 \, \Omega \parallel 50 \, \Omega) + (800 \, \Omega \parallel 100 \, \Omega) = 40 \, \Omega + 88.8 \, \Omega = 128.8 \, \Omega$$

$$V_{bc} = \frac{50 \, \Omega \parallel 200 \, \Omega}{128.8 \, \Omega} \times 24 \, \text{V} = 7.45 \, \text{V}$$

$$V_{ab} = 24 \, \text{V} - 7.448 \, \text{V} = 16.6 \, \text{V}$$

31. a. $V_{\text{out(min)}} = 0 \text{ V}$

$$V_{\text{out(max)}} = \left(\frac{(10 \text{ k}\Omega \parallel 10 \text{ k}\Omega)}{(10 \text{ k}\Omega \parallel 10 \text{ k}\Omega) + (R_1 \parallel 10 \text{ k}\Omega) + 10 \text{ k}\Omega} \right) 120 \text{ V} = 40 \text{ V}$$

b. $V_{\text{out}} = \frac{R_2 \parallel 10 \text{ k}\Omega}{(R_2 \parallel 10 \text{ k}\Omega) + (R_1 \parallel 10 \text{ k}\Omega) + 10 \text{ k}\Omega} \times 120 \text{ V}$

But $R_1 = 10 \text{ k}\Omega - R_2$

$$20 \text{ V} = \frac{\frac{(R_2)(10 \text{ k}\Omega)}{R_2 + 10 \text{ k}\Omega} \times 120 \text{ V}}{\frac{(R_2)(10 \text{ k}\Omega)}{R_2 + 10 \text{ k}\Omega} + \frac{10 \text{ k}\Omega - R_2}{10 \text{ k}\Omega} + 10 \text{ k}\Omega}$$

$R_2 = 3.82 \text{ k}\Omega$

33. $R_L = 0 \text{ }\Omega$: $V_{\text{out}} = 0 \text{ V}$

$R_L = 250 \text{ }\Omega$:

$$V_{\text{out}} = \frac{(250 \text{ }\Omega \parallel 100 \text{ }\Omega)(20 \text{ V})}{(250 \text{ }\Omega \parallel 100 \text{ }\Omega) + 100 \text{ }\Omega} = 8.33 \text{ V}$$

$R_L = 500 \text{ }\Omega$:

$$V_{\text{out}} = \frac{(500 \text{ }\Omega \parallel 100 \text{ }\Omega)(20 \text{ V})}{(500 \text{ }\Omega \parallel 100 \text{ }\Omega) + 100 \text{ }\Omega} = 9.09 \text{ V}$$

7.5 Loading Effects of Instruments

35. a. $5.0 \text{ V} = \frac{750 \text{ k}\Omega \parallel 200 \text{ k}\Omega}{750 \text{ k}\Omega \parallel 200 \text{ k}\Omega + 200 \text{ k}\Omega} \times E = 0.4412E$

$E = 11.3 \text{ V}$

b. Unloaded voltage:

$$V_{NL} = \frac{750 \text{ k}\Omega}{750 \text{ k}\Omega + 200 \text{ k}\Omega} \times 11.3 \text{ V} = 8.95 \text{ V}$$

c. Loading effect = $\frac{8.95 \text{ V} - 5.00 \text{ V}}{8.95 \text{ V}} \times 100\% = 44.1\%$

d. $V = \left(\frac{200 \text{ k}\Omega \parallel 200 \text{ k}\Omega}{(200 \text{ k}\Omega \parallel 200 \text{ k}\Omega) + 750 \text{ k}\Omega} \right) 11.3 \text{ V} = 1.33 \text{ V}$

37. a. Break the circuit between the $5.6 \text{ }\Omega$ resistor and the voltage source. Insert the ammeter at the break, connecting the red (+) lead of the ammeter to the positive terminal of the voltage source and the black (–) lead to the $5.6 \text{ }\Omega$ resistor.

b. Measuring I_1

$$I_1(\text{loaded}) = \frac{0.2 \text{ V}}{2 \text{ }\Omega + 5.6 \text{ }\Omega + 6.8 \text{ }\Omega \parallel 3.9 \text{ }\Omega} = 19.84 \text{ mA}$$

Measuring I_2

$$I_1(\text{loaded}) = \frac{0.2 \text{ V}}{5.6 \text{ }\Omega + (6.8 \text{ }\Omega + 2 \text{ }\Omega) \parallel 3.9 \text{ }\Omega} = 24.09 \text{ mA}$$

$$I_2(\text{loaded}) = \left(\frac{3.9 \text{ }\Omega}{3.9 \text{ }\Omega + 6.8 \text{ }\Omega + 2 \text{ }\Omega} \right) (24.1 \text{ mA}) = 7.40 \text{ mA}$$

Measuring I_3

$$I_1 = \frac{0.2 \text{ V}}{5.6 \text{ }\Omega + 6.8 \text{ }\Omega \parallel (3.9 \text{ }\Omega + 2 \text{ }\Omega)} = 22.83 \text{ mA}$$

$$I_3(\text{loaded}) = \left(\frac{6.8 \text{ }\Omega}{3.9 \text{ }\Omega + 6.8 \text{ }\Omega + 2 \text{ }\Omega} \right) 22.83 \text{ mA} = 12.22 \text{ mA}$$

c. $I_1(\text{NL}) + \frac{0.2 \text{ V}}{5.6 \text{ }\Omega + 6.8 \text{ }\Omega + 3.9 \text{ }\Omega} = \frac{0.2 \text{ V}}{8.0785 \text{ }\Omega} = 24.76 \text{ mA}$

$$I_2(\text{NL}) = \left(\frac{3.9 \text{ }\Omega}{2.9 \text{ }\Omega + 6.8 \text{ }\Omega} \right) 24.76 \text{ mA} = 9.02 \text{ mA}$$



$$I_3(\text{NL}) + \left(\frac{6.8 \text{ }\Omega}{3.9 \text{ }\Omega + 6.8 \text{ }\Omega} \right) 24.76 \text{ mA} = 15.73 \text{ mA}$$

Loading(I_1) = 19.9%


Loading(I_2) = 18.0%

Loading(I_3) = 22.3%



7.6 Circuit Analysis Using Computers

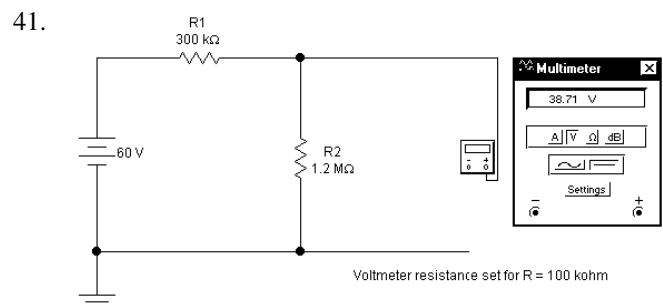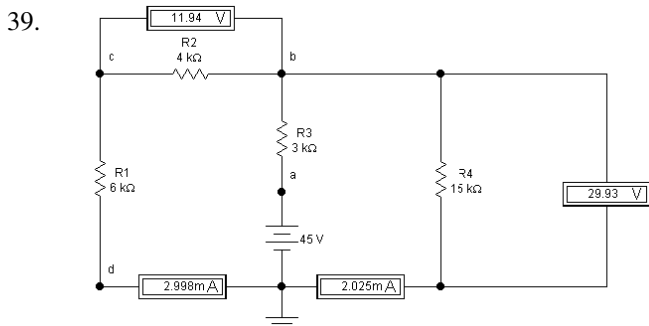

43.

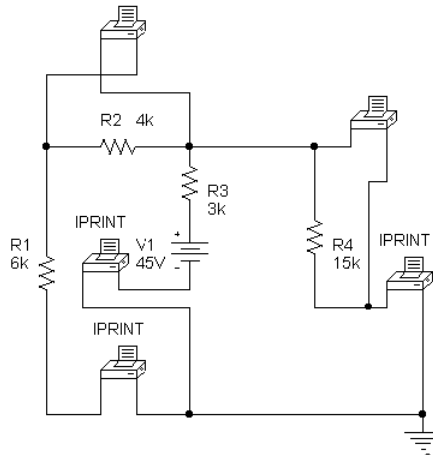

45.

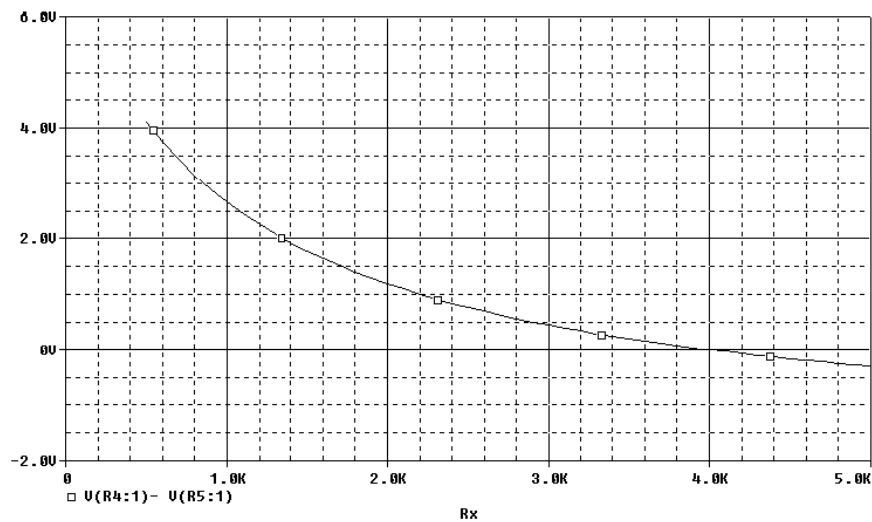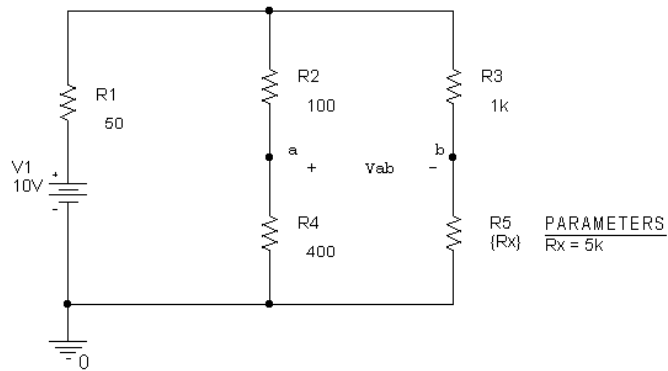

Methods of Analysis

8.1 Current Sources

1. $V_S = 18 \text{ V} + 20 \text{ V} = 38 \text{ V}$

3. a. $I_3 = \left(\frac{300 \Omega}{200 \Omega + 300 \Omega} \right) 20 \text{ mA} = 12 \text{ mA}$

b. $V_S = (20 \text{ mA})(0.1 \text{ k}\Omega) + (12 \text{ mA})(0.2 \text{ k}\Omega) = 4.4 \text{ V}$
 $V_1 = (20 \text{ mA})(0.1 \text{ k}\Omega) = 2.0 \text{ V}$

5. $I_{50\text{k}\Omega} = \frac{15 \text{ V}}{50 \text{ k}\Omega} = 300 \mu\text{A}$

$$I_{150\text{k}\Omega} = \frac{15 \text{ V}}{150 \text{ k}\Omega} = 100 \mu\text{A}$$

$$I_1 = 300 \mu\text{A} + 100 \mu\text{A} = 400 \mu\text{A}$$

$$I_2 = 400 \mu\text{A} + 100 \mu\text{A} = 500 \mu\text{A}$$

7. Power provided by voltage source:

$$P = (15 \text{ V})(500 \mu\text{A}) = 7.5 \text{ mW}$$

Power dissipated by resistors:

$$P_{150\text{k}\Omega} = (300 \mu\text{A})^2 50 \text{ k}\Omega = 4.5 \text{ mW}$$

$$P_{150\text{k}\Omega} = (100 \mu\text{A})^2 150 \text{ k}\Omega = 1.5 \text{ mW}$$

Power absorbed by current source:

$$P = (0.1 \mu\text{A})(15 \text{ V}) = 1.5 \text{ mW}$$


$$P_{\text{in}} = 7.5 \text{ mW} = \sum P_{\text{out}}$$

Note:


The current source is taking energy from the circuit rather than providing energy.

8.2 Source Conversions

9. a.

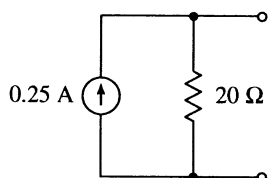

b.

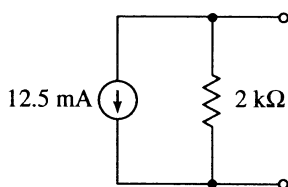


11. a. $I_L = \left(\frac{450 \Omega}{450 \Omega + 50 \Omega} \right) 8 \text{ A} = 7.2 \text{ A}$

b. $E = (8 \text{ A})(450 \Omega) = 3600 \text{ V}$

$$I_L = \frac{3600 \text{ V}}{450 \Omega + 50 \Omega} = 7.2 \text{ A}$$

13. a.

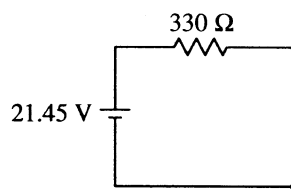

b. $I = \frac{21.45 \text{ V} - 16 \text{ V}}{330 \Omega + 470 \Omega + 100 \Omega} = 6.05 \text{ mA}$

c. $V_{ab} = (6.05 \text{ mA})(0.1 \text{ k}\Omega) = 0.605 \text{ V}$

8.3 Current Sources in Parallel and Series


15. $I_T = 100 \text{ mA} - 50 \text{ mA} = 50 \text{ mA}$ (down)

$$R_T = 3 \text{ k}\Omega \parallel 6 \text{ k}\Omega \parallel 8 \text{ k}\Omega = 1.6 \text{ k}\Omega$$

$$V_2 = -(50 \text{ mA})(1.6 \text{ k}\Omega) = -80 \text{ V}$$

$$I_1 = -\left(\frac{1.6 \text{ k}\Omega}{3 \text{ k}\Omega} \right) 50 \text{ mA} = -26.7 \text{ mA}$$

17.

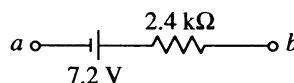

$$E = (3 \text{ mA})(2.4 \text{ k}\Omega) = 7.2 \text{ V}$$

$$I_3 = \frac{8 \text{ V} - 7.2 \text{ V}}{2.4 \text{ k}\Omega + 1.6 \text{ k}\Omega + 2.0 \text{ k}\Omega} = 0.133 \text{ mA}$$

$$V_{ab} = -7.2 \text{ V} - (0.133 \text{ mA})(2.4 \text{ k}\Omega) = -7.52 \text{ V}$$