

Project 1 for chapters 1 and 2
Design of Smart Power Grid Renewable Energy Systems
Wiley 2011

Simulation Problem 1. Write a report and a general Matlab M-code to solve the problem below. Your report should have the following sections.

1. Problem statement.
2. Mathematical formulation
3. Solution in a tabular form.
4. Appendix for your Matlab M-Code

Problem: The operation of AC machines (in particular, transformers and induction machines) can be studied with the aid of the T-circuit shown in Fig. 1 below.

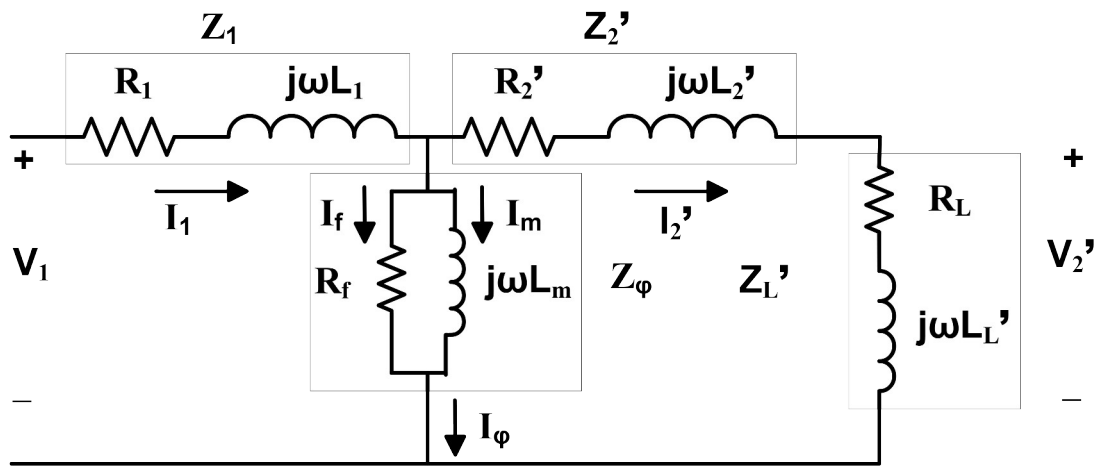


Figure 1 Equivalent Circuit for Problem 1.

Assume the frequency is 60 Hz. The circuit elements are given in table 1 below.

Table 1: Data for problem 1

C a s e	R_1	L_1	R_f	L_m	R_2'	L_2'	R_L	L_L	V_1	V_2	I_1	I_2'	I_f
1	1	0.01	1000	8	1	0.01	Open		480	?	?	?	?
2	1	0.01	1000	8	1	0.01	200	0	480	?	?	?	?
3	0.0	0.0026	Open		0	0	Open		1	?	?	?	?

	2	5											
4	0.0 2	0.0026 5	Open		0	0	1	0	1	?	?	?	?
5	0.0 2	0.0026 5	Open		0	0	0.707	1.87 5 $j10^{-3}$	?	1	?	?	?
6	0	0	100	0.1	0.01	106 $j10^{-6}$	1	0	1	?	?	?	?
7	0	0	100	0.01	0.01	106 $j10^{-6}$	1.414	3.75 $j10^{-3}$	1	?	?	?	?
8	0.3	1.33 $j10^{-3}$	Ope n	3.45 $j10^{-2}$	0.15	0.56 $j10^{-3}$	7.35	0	127	?	?	?	?
9	10	5.2 $j10^{-2}$	Ope n	0	0	200	0.4	0	500	?	?	?	?
10	0.1 5	2.54 $j10^{-3}$	Ope n	1.57	6.24 $j10^{-3}$	98.5	0.178	0	240	?	?	?	?
11	0.3	0.003	1	4.25 $j10^{-2}$	0.2	0.003	10	0	440	?	?	?	?
12	0.3	0.003	0	4.25 $j10^{-2}$	0.2	0.003	1	0	380	?	?	?	?

Use the polar form for all complex numbers and solve set 1 through set 12.

Hint: Use $Z = R + jX$. When an element is shorted, set that element to zero. When an element is open, set the value to a high value

Solutions

Case 1:

$$Z_L = R_L + j X_L = \text{open}$$

$$Z_1 = R_1 + j X_1 = 1 + j 0.01 \times 2\pi \times 60 = 1 + j 3.77 \Omega$$

$$Z_{\phi} = R_f || j X_m = \frac{R_f \times j X_m}{R_f + j X_m} = 900.95 + j 298.73 \Omega$$

$$I_1 = I_{\phi} = \frac{V_1}{Z_1 + Z_{\phi}} = 0.504 \angle -18.5407^{\circ} A$$

$$V_2 = Z_{\phi} I_{\phi} = (900.95 + j 298.73) 0.504 \angle -18.5407^{\circ} = 478.91 \angle -0.19^{\circ} V$$

$$I_2 = 0$$

Case 2:

$$\frac{V_{\phi} - V_1}{Z_1} + \frac{V_{\phi} - V_2}{Z_2'} + \frac{V_{\phi}}{Z_{\phi}} = 0$$

$$\frac{V_2 - V_{\phi}}{Z_2'} + \frac{V_2}{Z_L'} = 0$$

$$(V_{\phi} - V_1) Y_1 + (V_{\phi} - V_2) Y_2' + V_{\phi} Y_{\phi} = 0$$

$$(V_2 - V_{\phi}) Y_2' + V_2 Y_L' = 0$$

$$Y_1 = \frac{1}{Z_1}, Y_2' = \frac{1}{Z_2'}, Y_{\phi} = \frac{1}{Z_{\phi}}$$

Where

Rearranging,

$$\begin{bmatrix} Y_1 + Y_2' + Y_{\phi} & -Y_2' \\ -Y_2' & Y_2' + Y_L' \end{bmatrix} \begin{bmatrix} V_{\phi} \\ V_2 \end{bmatrix} = \begin{bmatrix} V_1 Y_1 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V_{\phi} \\ V_2 \end{bmatrix} = \begin{bmatrix} Y_1 + Y_2' + Y_{\phi} & -Y_2' \\ -Y_2' & Y_2' + Y_L' \end{bmatrix}^{-1} \begin{bmatrix} V_1 Y_1 \\ 0 \end{bmatrix}$$

The MATLAB program for solving the above (Case 2) is given below.

```
clc;
V1 = 480;
f = 60;
w = 2*pi*f;
R1 = 1;
L1 = 0.01;
X1 = L1*w;
Z1 = R1 + X1*1j;
```

```

Y1 = 1/Z1;
Rf = 1000;
Lm = 8;
Xm = Lm*w;
Zf = Rf*Xm*1j/(Rf+Xm*1j);
Yf = 1/Zf;
R2 = 1;
L2 = 0.01;
X2 = L2*w;
Z2 = R2+X2*1j;
Y2 = 1/Z2;
Rload = 200;
Lload = 0;
Xload = Lload*w;
Zload = Rload + Xload*1j;
Yload = 1/Zload;
Ybus = [Y1+Y2+Yf    -Y2; -Y2    Y2+Yload];
VfV2 = inv(Ybus)*[V1*Y1; 0];
Vf = VfV2(1);
V2 = VfV2(2);
abs_V2 = abs(V2)
angle_V2 = angle(V2)*180/pi
Iphi = Vf*Yf;
abs_Iphi = abs(Iphi)
angle_Iphi = angle(Iphi)*180/pi
Irf = Iphi*Xm*1j/(Rf+Xm*1j);
abs_Irf = abs(Irf)
angle_Irf = angle(Irf)*180/pi
I2 = V2*Yload;
abs_I2 = abs(I2)
angle_I2 = angle(I2)*180/pi
I1 = (V1-Vf)*Y1;
abs_I1 = abs(I1)
angle_I1 = angle(I1)*180/pi

```

The above program can be used to solve other cases by using the data from the problem by substituting the values of impedances and voltages. When a part of circuit is specified as open, its value can be substituted with a large number so that branch acts as open and when as a short with zero impedance. The results are tabulated in table below:

The results for all cases.

Case	V_1	V_2	I_1	I_2'	I_f
1	480	478.91 $\angle -0.19^\circ$	0.505 $\angle -18.5^\circ$	0	0.48 $\angle -0.2^\circ$
2	480	473.82 $\angle -2.33^\circ$	2.85 $\angle -5.32^\circ$	2.37 $\angle -2.33^\circ$	0.48 $\angle -1.26^\circ$
3	1	1	0	0	0

		$\angle 0^\circ$			
4	1	0.7 $\angle -44.4^\circ$	0.7 $\angle -44.4^\circ$	0.7 $\angle -44.4^\circ$	0
5	1.85 $\angle 21.9^\circ$	1	1 $\angle -45^\circ$	1 $\angle -45^\circ$	0
6	1	0.989 $\angle -2.27^\circ$	1 $\angle -3.76^\circ$	0.989 $\angle -2.27^\circ$	0.01 $\angle 0^\circ$
7	1	0.983 $\angle -0.6^\circ$	0.71 $\angle -60^\circ$	0.491 $\angle -45.6^\circ$	0.01 $\angle 0^\circ$
8	127	115.1 $\angle -3.87^\circ$	18.29 $\angle -33.4^\circ$	15.65 $\angle -3.87^\circ$	0
9	500	0	22.71 $\angle -62.97$	0	0
10	240	0.0011 $\angle -89.86$	0.411 $\angle -89.98$	0.0065 $\angle -89.86$	0
11	440	229.90 $\angle -47.12$	259 $\angle -44.61$	22.99 $\angle -47.13$	235.93 $\angle -40.80$
12	380	0	324.76 $\angle -75.14$	0	324.76 $\angle -75.14$