

 This work is protected by
US copyright laws and is for
instructors' use only.

Instructor's Resource Manual
to accompany


Electronics Fundamentals and Electric Circuits Fundamentals

Seventh Edition

Thomas L. Floyd



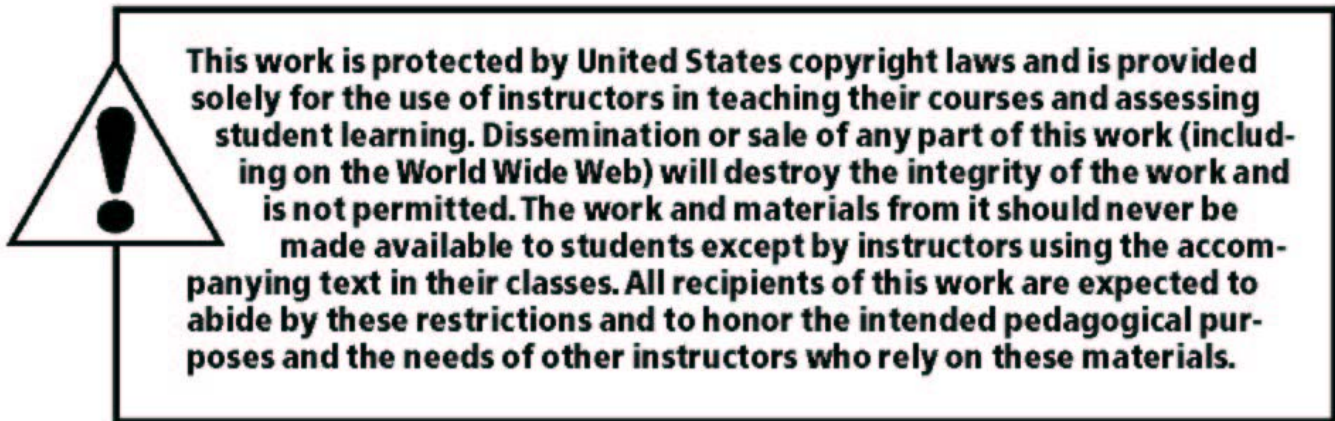Upper Saddle River, New Jersey
Columbus, Ohio



Copyright © 2007 by Pearson Education, Inc., Upper Saddle River, New Jersey 07458.

Pearson Prentice Hall. All rights reserved. Printed in the United States of America. This publication is protected by Copyright and permission should be obtained from the publisher prior to any prohibited reproduction, storage in a retrieval system, or transmission in any form or by any means, electronic, mechanical, photocopying, recording, or likewise. For information regarding permission(s), write to: Rights and Permissions Department.

Pearson Prentice Hall™ is a trademark of Pearson Education, Inc.

Pearson® is a registered trademark of Pearson plc

Prentice Hall® is a registered trademark of Pearson Education, Inc.

Instructors of classes using Floyd, *Electronics Fundamentals*, Seventh Edition, and *Electric Circuits Fundamentals*, Seventh Edition, may reproduce material from the Instructor's Resource Manual for classroom use.

10 9 8 7 6 5 4 3 2 1



ISBN 0-13-188972-9

CONTENTS

PART 1	Solutions to End-of-Chapter Problems	1
PART 2	Solutions to Application Assignments	193
PART 3	Summary of Multisim Circuit Results	237
PART 4	Special Topics	247
PART 5	Test Item File	263
PART 6	Laboratory Solutions for <i>Experiments in Electronics Fundamentals</i> and <i>Electric Circuits Fundamentals</i> by David Buchla	453
PART 7	Partial List of CEMA Skills	545

PART ONE

Solutions to End-of-Chapter Problems

CHAPTER 1

QUANTITIES AND UNITS

SECTION 1-1 Scientific and Engineering Notation

1. (a) $3000 = 3 \times 10^3$ (b) $75,000 = 7.5 \times 10^4$ (c) $2,000,000 = 2 \times 10^6$
2. (a) $\frac{1}{500} = 0.002 = 2 \times 10^{-3}$
(b) $\frac{1}{2000} = 0.0005 = 5 \times 10^{-4}$
(c) $\frac{1}{5,000,000} = 0.0000002 = 2 \times 10^{-7}$
3. (a) $8400 = 8.4 \times 10^3$ (b) $99,000 = 9.9 \times 10^4$ (c) $0.2 \times 10^6 = 2 \times 10^5$
4. (a) $0.0002 = 2 \times 10^{-4}$ (b) $0.6 = 6 \times 10^{-1}$
(c) 7.8×10^{-2} (already in scientific notation)
5. (a) $2.5 \times 10^{-6} = 0.0000025$ (b) $5.0 \times 10^2 = 500$ (c) $3.9 \times 10^{-1} = 0.39$
6. (a) $4.5 \times 10^{-6} = 0.0000045$
(b) $8 \times 10^{-9} = 0.000000008$
(c) $4.0 \times 10^{-12} = 0.0000000000040$
7. (a) $9.2 \times 10^6 + 3.4 \times 10^7 = 9.2 \times 10^6 + 34 \times 10^6 = 4.32 \times 10^7$
(b) $5 \times 10^3 + 8.5 \times 10^{-1} = 5 \times 10^3 + 0.00085 \times 10^3 = 5.00085 \times 10^3$
(c) $5.6 \times 10^{-8} + 4.6 \times 10^{-9} = 56 \times 10^{-9} + 4.6 \times 10^{-9} = 6.06 \times 10^{-8}$
8. (a) $3.2 \times 10^{12} - 1.1 \times 10^{12} = 2.1 \times 10^{12}$
(b) $2.6 \times 10^8 - 1.3 \times 10^7 = 26 \times 10^7 - 1.3 \times 10^7 = 24.7 \times 10^7$
(c) $1.5 \times 10^{-12} - 8 \times 10^{-13} = 15 \times 10^{-13} - 8 \times 10^{-13} = 7 \times 10^{-13}$

9. (a) $(5 \times 10^3)(4 \times 10^5) = 5 \times 4 \times 10^{3+5} = 20 \times 10^8 = \mathbf{2 \times 10^9}$
 (b) $(1.2 \times 10^{12})(3 \times 10^2) = 1.2 \times 3 \times 10^{12+2} = \mathbf{3.6 \times 10^{14}}$
 (c) $(2.2 \times 10^{-9})(7 \times 10^{-6}) = 2.2 \times 7 \times 10^{-9-6} = 15.4 \times 10^{-15} = \mathbf{1.54 \times 10^{-14}}$
10. (a) $\frac{1.0 \times 10^3}{2.5 \times 10^2} = 0.4 \times 10^{3-2} = 0.4 \times 10^1 = \mathbf{4}$
 (b) $\frac{2.5 \times 10^{-6}}{5.0 \times 10^{-8}} = 0.5 \times 10^{-6-(-8)} = 0.5 \times 10^2 = \mathbf{50}$
 (c) $\frac{4.2 \times 10^8}{2 \times 10^{-5}} = 2.1 \times 10^{8-(-5)} = \mathbf{2.1 \times 10^{13}}$
11. (a) $89,000 = \mathbf{89 \times 10^3}$
 (b) $450,000 = \mathbf{450 \times 10^3}$
 (c) $12,040,000,000,000 = \mathbf{12.04 \times 10^{12}}$
12. (a) $2.35 \times 10^5 = \mathbf{235 \times 10^3}$
 (b) $7.32 \times 10^7 = \mathbf{73.2 \times 10^6}$
 (c) $\mathbf{1.333 \times 10^9}$ (already in engineering notation)
13. (a) $0.000345 = \mathbf{345 \times 10^{-6}}$
 (b) $0.025 = \mathbf{25 \times 10^{-3}}$
 (c) $0.00000000129 = \mathbf{1.29 \times 10^{-9}}$
14. (a) $9.81 \times 10^{-3} = \mathbf{9.81 \times 10^{-3}}$
 (b) $4.82 \times 10^{-4} = \mathbf{482 \times 10^{-6}}$
 (c) $4.38 \times 10^{-7} = \mathbf{438 \times 10^{-9}}$
15. (a) $2.5 \times 10^{-3} + 4.6 \times 10^{-3} = (2.5 + 4.6) \times 10^{-3} = \mathbf{7.1 \times 10^{-3}}$
 (b) $68 \times 10^6 + 33 \times 10^6 = (68 + 33) \times 10^6 = \mathbf{101 \times 10^6}$
 (c) $1.25 \times 10^6 + 250 \times 10^3 = 1.25 \times 10^6 + 0.25 \times 10^6 = (1.25 + 0.25) \times 10^6 = \mathbf{1.50 \times 10^6}$
16. (a) $(32 \times 10^{-3})(56 \times 10^3) = 1792 \times 10^{(-3+3)} = 1792 \times 10^0 = \mathbf{1.792 \times 10^3}$
 (b) $(1.2 \times 10^{-6})(1.2 \times 10^{-6}) = 1.44 \times 10^{(-6-6)} = \mathbf{1.44 \times 10^{-12}}$

$$(c) \quad (100)(55 \times 10^{-3}) = 5500 \times 10^{-3} = \mathbf{5.5}$$

$$17. \quad (a) \quad \frac{50}{2.2 \times 10^3} = \mathbf{22.7 \times 10^{-3}}$$

$$(b) \quad \frac{5 \times 10^3}{25 \times 10^{-6}} = 0.2 \times 10^{(3 - (-6))} = 0.2 \times 10^9 = \mathbf{200 \times 10^6}$$

$$(c) \quad \frac{560 \times 10^3}{660 \times 10^3} = 0.848 \times 10^{(3 - 3)} = 0.848 \times 10^0 = \mathbf{848 \times 10^{-3}}$$

SECTION 1-2 Units and Metric Prefixes

$$18. \quad (a) \quad 89,000 \, \Omega = 89 \times 10^3 = \mathbf{89 \, k\Omega}$$

$$(b) \quad 450,000 \, \Omega = 450 \times 10^3 = \mathbf{450 \, k\Omega}$$

$$(c) \quad 12,040,000,000,000 \, \Omega = 12.04 \times 10^{12} = \mathbf{12.04 \, T\Omega}$$

$$19. \quad (a) \quad 0.000345 \, \text{A} = 345 \times 10^{-6} \, \text{A} = \mathbf{345 \, \mu\text{A}}$$

$$(b) \quad 0.025 \, \text{A} = 25 \times 10^{-3} \, \text{A} = \mathbf{25 \, \text{mA}}$$

$$(c) \quad 0.00000000129 \, \text{A} = 1.29 \times 10^{-9} \, \text{A} = \mathbf{1.29 \, \text{nA}}$$

$$20. \quad (a) \quad 31 \times 10^{-3} \, \text{A} = \mathbf{31 \, \text{mA}} \quad (b) \quad 5.5 \times 10^3 \, \text{V} = \mathbf{5.5 \, \text{kV}} \quad (c) \quad 20 \times 10^{-12} \, \text{F} = \mathbf{20 \, \text{pF}}$$

$$21. \quad (a) \quad 3 \times 10^{-6} \, \text{F} = \mathbf{3 \, \mu\text{F}} \quad (b) \quad 3.3 \times 10^6 \, \Omega = \mathbf{3.3 \, \text{M}\Omega} \quad (c) \quad 350 \times 10^{-9} \, \text{A} = \mathbf{350 \, \text{nA}}$$

$$22. \quad (a) \quad 5 \, \mu\text{A} = \mathbf{5 \times 10^{-6} \, \text{A}} \quad (b) \quad 43 \, \text{mV} = \mathbf{43 \times 10^{-3} \, \text{V}}$$

$$(c) \quad 275 \, \text{k}\Omega = \mathbf{275 \times 10^3 \, \Omega} \quad (d) \quad 10 \, \text{MW} = \mathbf{10 \times 10^6 \, \text{W}}$$

SECTION 1-3 Metric Unit Conversions

$$23. \quad (a) \quad (5 \, \text{mA})(1 \times 10^3 \, \mu\text{A}/\text{mA}) = 5 \times 10^3 \, \mu\text{A} = \mathbf{5000 \, \mu\text{A}}$$

$$(b) \quad (3200 \, \mu\text{W})(1 \times 10^{-3} \, \text{W}/\mu\text{W}) = \mathbf{3.2 \, \text{mW}}$$

$$(c) \quad (5000 \, \text{kV})(1 \times 10^{-3}) \, \text{MV}/\text{kV} = \mathbf{5 \, \text{MV}}$$

$$(d) \quad (10 \, \text{MW})(1 \times 10^3 \, \text{kW}/\text{MW}) = 10 \times 10^3 \, \text{kW} = \mathbf{10,000 \, \text{kW}}$$

24. (a) $\frac{1 \text{ mA}}{1 \mu\text{A}} = \frac{1 \times 10^{-3} \text{ A}}{1 \times 10^{-6} \text{ A}} = 1 \times 10^3 = \mathbf{1000}$
- (b) $\frac{0.05 \text{ kV}}{1 \text{ mV}} = \frac{0.05 \times 10^3 \text{ V}}{1 \times 10^{-3} \text{ V}} = 0.05 \times 10^6 = \mathbf{50,000}$
- (c) $\frac{0.02 \text{ k}\Omega}{1 \text{ M}\Omega} = \frac{0.02 \times 10^3 \Omega}{1 \times 10^6 \Omega} = 0.02 \times 10^{-3} = \mathbf{2 \times 10^{-5}}$
- (d) $\frac{155 \text{ mW}}{1 \text{ kW}} = \frac{155 \times 10^{-3} \text{ W}}{1 \times 10^3 \text{ W}} = 155 \times 10^{-6} = \mathbf{1.55 \times 10^{-4}}$
25. (a) $50 \text{ mA} + 680 \mu\text{A} = 50 \text{ mA} + 0.68 \text{ mA} = \mathbf{50.68 \text{ mA}}$
- (b) $120 \text{ k}\Omega + 2.2 \text{ M}\Omega = 0.12 \text{ M}\Omega + 2.2 \text{ M}\Omega = \mathbf{2.32 \text{ M}\Omega}$
- (c) $0.02 \mu\text{F} + 3300 \text{ pF} = 0.02 \mu\text{F} + 0.0033 \mu\text{F} = \mathbf{0.0233 \mu\text{F}}$
26. (a) $\frac{10 \text{ k}\Omega}{2.2 \text{ k}\Omega + 10 \text{ k}\Omega} = \frac{10 \text{ k}\Omega}{12.2 \text{ k}\Omega} = \mathbf{0.8197}$
- (b) $\frac{250 \text{ mV}}{50 \mu\text{V}} = \frac{250 \times 10^{-3}}{50 \times 10^{-6}} = \mathbf{5000}$
- (c) $\frac{1 \text{ MW}}{2 \text{ kW}} = \frac{1 \times 10^6}{2 \times 10^3} = \mathbf{500}$

SECTION 1-4 Measured Numbers

27. (a) 1.00×10^3 has 3 significant digits. (b) 0.0057 has 4 significant digits.
- (c) 1502.0 has 5 significant digits. (d) 0.000036 has 6 significant digits.
- (e) 0.105 has 3 significant digits. (f) 2.6×10^2 has 2 significant digits.
28. (a) $50,505 \cong \mathbf{50.5 \times 10^3}$ (b) $220.45 \cong \mathbf{220}$
- (c) $4646 \cong \mathbf{4.65 \times 10^3}$ (d) $10.99 \cong \mathbf{11.0}$
- (e) $1.005 \cong \mathbf{1.00}$

CHAPTER 2

VOLTAGE, CURRENT, AND RESISTANCE

BASIC PROBLEMS

SECTION 2-2 Electrical Charge

1. $Q = (\text{charge per electron})(\text{number of electrons}) = (1.6 \times 10^{-19} \text{ C/e})(50 \times 10^{31} \text{ e}) = \mathbf{80 \times 10^{12} \text{ C}}$
2. $(6.25 \times 10^{18} \text{ e/C})(80 \times 10^{-6} \text{ C}) = \mathbf{5 \times 10^{14} \text{ e}}$
3. $(1.6 \times 10^{-19} \text{ C/e})(29 \text{ e}) = \mathbf{4.64 \times 10^{-18} \text{ C}}$
4. $(1.6 \times 10^{-19} \text{ C/e})(17 \text{ e}) = \mathbf{2.72 \times 10^{-18} \text{ C}}$

SECTION 2-3 Voltage

5. (a) $V = \frac{W}{Q} = \frac{10 \text{ J}}{1 \text{ C}} = \mathbf{10 \text{ V}}$ (b) $V = \frac{W}{Q} = \frac{5 \text{ J}}{2 \text{ C}} = \mathbf{2.5 \text{ V}}$
(c) $V = \frac{W}{Q} = \frac{100 \text{ J}}{25 \text{ C}} = \mathbf{4 \text{ V}}$
6. $V = \frac{W}{Q} = \frac{500 \text{ J}}{100 \text{ C}} = \mathbf{5 \text{ V}}$
7. $V = \frac{W}{Q} = \frac{800 \text{ J}}{40 \text{ C}} = \mathbf{20 \text{ V}}$
8. $W = VQ = (12 \text{ V})(2.5 \text{ C}) = \mathbf{30 \text{ J}}$

SECTION 2-4 Current

9. (a) $I = \frac{Q}{t} = \frac{75 \text{ C}}{1 \text{ s}} = \mathbf{75 \text{ A}}$ (b) $I = \frac{Q}{t} = \frac{10 \text{ C}}{0.5 \text{ s}} = \mathbf{20 \text{ A}}$

$$(c) \quad I = \frac{Q}{t} = \frac{5 \text{ C}}{2 \text{ s}} = \mathbf{2.5 \text{ A}}$$

$$10. \quad I = \frac{Q}{t} = \frac{0.6 \text{ C}}{3 \text{ s}} = \mathbf{0.2 \text{ A}}$$

$$11. \quad I = \frac{Q}{t}; \quad t = \frac{Q}{I} = \frac{10 \text{ C}}{5 \text{ A}} = \mathbf{2 \text{ s}}$$

$$12. \quad Q = I \times t = (1.5 \text{ A})(0.1 \text{ s}) = \mathbf{0.15 \text{ C}}$$


SECTION 2-5 Resistance

13. A: Blue, gray, red, silver: **6800 $\Omega \pm 10\%$**
 B: Orange, orange, black, silver: **33 $\Omega \pm 10\%$**
 C: Yellow, violet, orange, gold: **47,000 $\Omega \pm 5\%$**
14. A: $R_{\min} = 6800 \Omega - 0.1(6800 \Omega) = 6800 \Omega - 680 \Omega = \mathbf{6120 \Omega}$
 $R_{\max} = 6800 \Omega + 680 \Omega = \mathbf{7480 \Omega}$
 B: $R_{\min} = 33 \Omega - 0.1(33 \Omega) = 33 \Omega - 3.3 \Omega = \mathbf{29.7 \Omega}$
 $R_{\max} = 33 \Omega + 3.3 \Omega = \mathbf{36.3 \Omega}$
 C: $R_{\min} = 47,000 \Omega - (0.05)(47,000 \Omega) = 47,000 \Omega - 2350 \Omega = \mathbf{44,650 \Omega}$
 $R_{\max} = 47,000 \Omega + 2350 \Omega = \mathbf{49,350 \Omega}$
15. (a) 1st band = **red**, 2nd band = **violet**, 3rd band = **brown**, 4th band = **gold**
 (b) 330 Ω : **orange, orange, brown, (B)**
 2.2 k Ω : **red, red, red (D)**
 39 k Ω : **orange, white, orange (A)**
 56 k Ω : **green, blue, orange (L)**
 100 k Ω : **brown, black, yellow (F)**
16. (a) **36.5 $\Omega \pm 2\%$**
 (b) **2.74 k $\Omega \pm 0.25\%$**
 (c) **82.5 k $\Omega \pm 1\%$**
17. (a) Brown, black, black, gold: **10 $\Omega \pm 5\%$**
 (b) Green, brown, green, silver: 5,100,000 $\Omega \pm 10\% = \mathbf{5.1 \text{ M}\Omega \pm 10\%}$
 (c) Blue, gray, black, gold: **68 $\Omega \pm 5\%$**
18. (a) 0.47 $\Omega \pm 5\%$: **yellow, violet, silver, gold**

- (b) $270\text{ k}\Omega \pm 5\%$: **red, violet, yellow, gold**
- (c) $5.1\text{ M}\Omega \pm 5\%$: **green, brown, green, gold**
- 19. (a) Red, gray, violet, red, brown: $28,700\text{ }\Omega \pm 1\% = \mathbf{28.7\text{ k}\Omega \pm 1\%}$
- (b) Blue, black, yellow, gold, brown: $\mathbf{60.4\text{ }\Omega \pm 1\%}$
- (c) White, orange, brown, brown, brown: $9310 \pm 1\% = \mathbf{9.31\text{ k}\Omega \pm 1\%}$
- 20. (a) $14.7\text{ k}\Omega \pm 1\%$: **brown, yellow, violet, red, brown**
- (b) $39.2\text{ }\Omega \pm 1\%$: **orange, white, red, gold, brown**
- (c) $9.76\text{ k}\Omega \pm 1\%$: **white, violet, blue, brown, brown**
- 21. (a) $220 = \mathbf{22\text{ }\Omega}$ (b) $472 = \mathbf{4.7\text{ k}\Omega}$
- (c) $823 = \mathbf{82\text{ k}\Omega}$ (d) $3\text{K}3 = \mathbf{3.3\text{ k}\Omega}$
- (e) $560 = \mathbf{56\text{ }\Omega}$ (f) $10\text{M} = \mathbf{10\text{ M}\Omega}$
- 22. $\mathbf{500\text{ }\Omega}$, equal resistance on each side of the contact.



SECTION 2-6 The Electric Circuit

- 23. There is current through **Lamp 2**.
- 24. See Figure 2-1.

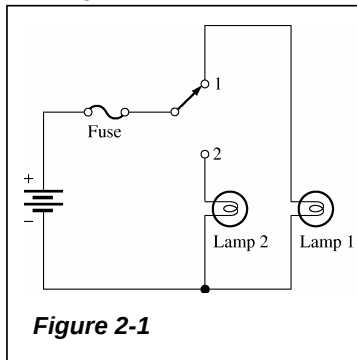


SECTION 2-7 Basic Circuit Measurements

- 25. See Figure 2-2(a).

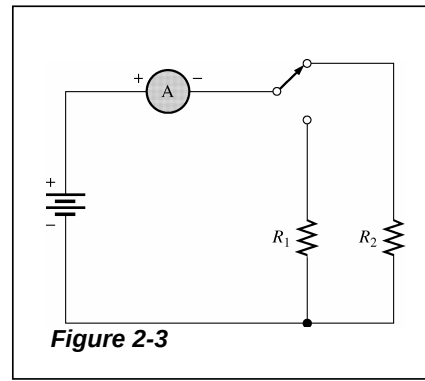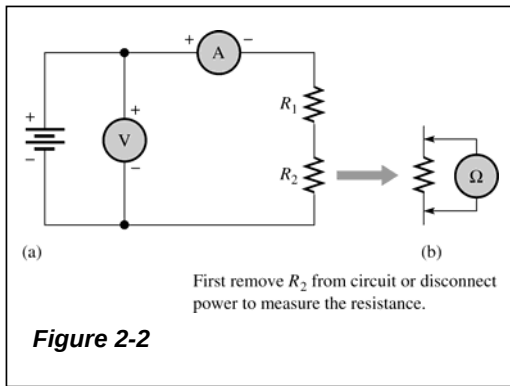


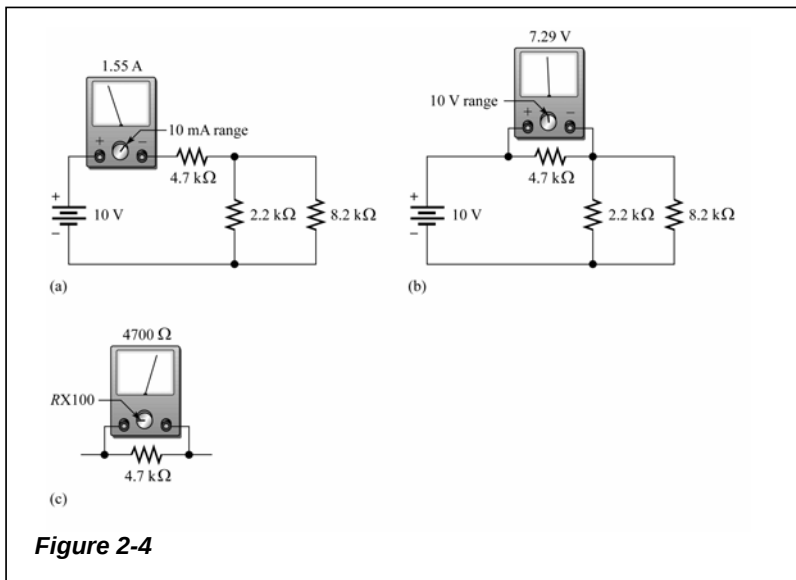26. See Figure 2-2(b).
27. Position 1: $V_1 = 0 \text{ V}$, $V_2 = V_s$
Position 2: $V_1 = V_s$, $V_2 = 0 \text{ V}$
28. See Figure 2-3.
29. On the 600 V DC scale: **250 V**
30. $R = (10)(10 \Omega) = \mathbf{100 \Omega}$
31. (a) $2(100 \Omega) = \mathbf{200 \Omega}$ (b) $15(10 \text{ M}\Omega) = \mathbf{150 \text{ M}\Omega}$
(c) $45(100 \Omega) = \mathbf{4500 \Omega}$
32. See Figure 2-4.




ADVANCED PROBLEMS

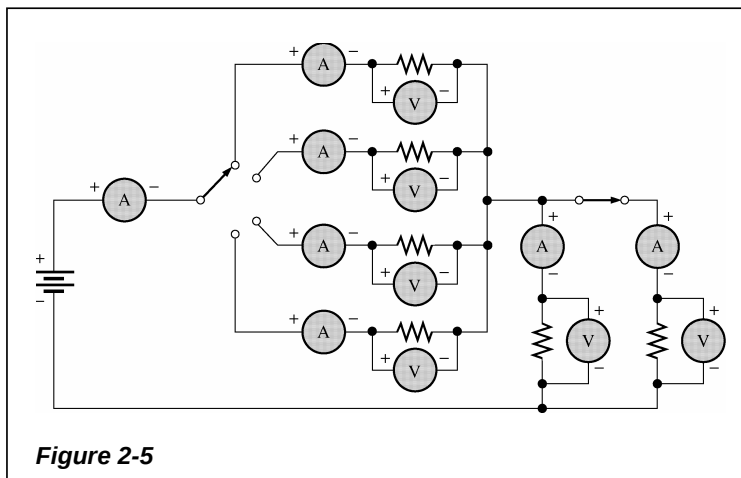33. $I = \frac{Q}{t}$
 $Q = I \times t = (2 \text{ A})(15 \text{ s}) = 30 \text{ C}$
 $V = \frac{W}{Q} = \frac{1000 \text{ J}}{30 \text{ C}} = \mathbf{33.3 \text{ V}}$
34. $I = \frac{Q}{t}$
 $Q = (\text{number of electrons}) / (\text{number of electrons/coulomb})$
 $Q = \frac{574 \times 10^{15} \text{ e}}{6.25 \times 10^{18} \text{ e/C}} = 9.184 \times 10^{-2} \text{ C}$
 $I = \frac{Q}{t} = \frac{9.184 \times 10^{-2} \text{ C}}{250 \times 10^{-3} \text{ s}} = \mathbf{0.367 \text{ A}}$
35. Total wire length = 100 ft
 Resistance per 1000 ft = (1000 ft)(6 Ω /100 ft) = 60 Ω
 Smallest wire size is **AWG 27** which has 51.47 Ω /1000 ft
36. (a) 4R7J = **4.7 $\Omega \pm 5\%$**
 (b) 560KF = **560 k $\Omega \pm 1\%$**
 (c) 1M5G = **1.5 M $\Omega \pm 2\%$**
37. The circuit in (b) can have both lamps on at the same time.
38. There is always current through R_5 .
39. See Figure 2-5.




40. See Figure 2-5.

41. See Figure 2-6.

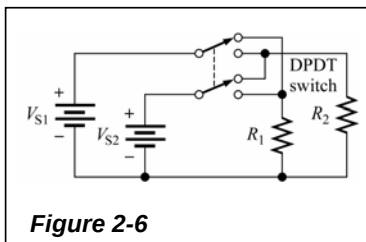

42. See Figure 2-7.

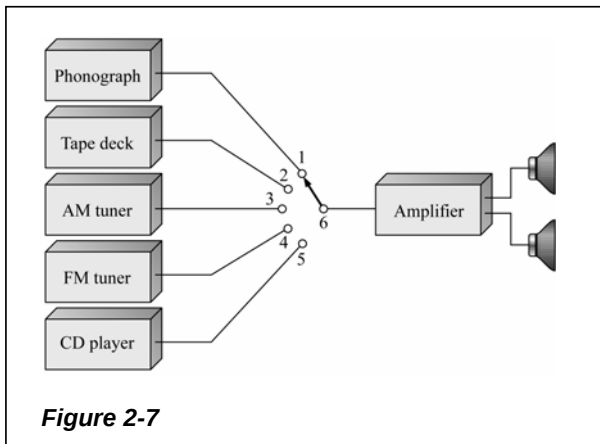

CHAPTER 3

OHM'S LAW, ENERGY, AND POWER

BASIC PROBLEMS

SECTION 3-1 Ohm's Law

1. I is directly proportional to V and will change the same percentage as V .
 - (a) $I = 3(1\text{ A}) = \mathbf{3\text{ A}}$
 - (b) $I = 1\text{ A} - (0.8)(1\text{ A}) = 1\text{ A} - 0.8\text{ A} = \mathbf{0.2\text{ A}}$
 - (c) $I = 1\text{ A} + (0.5)(1\text{ A}) = 1\text{ A} + 0.5\text{ A} = \mathbf{1.5\text{ A}}$
2.
 - (a) When the resistance doubles, the current is halved from 100 mA to **50 mA**.
 - (b) When the resistance is reduced by 30%, the current increases from 100 mA to $I = V/0.7R = 1.429(V/R) = (1.429)(100\text{ mA}) \cong \mathbf{143\text{ mA}}$
 - (c) When the resistance is quadrupled, the current decreases from 100 mA to **25 mA**.
3. Tripling the voltage triples the current from 10 mA to 30 mA, but doubling the resistance halves the current to **15 mA**.

SECTION 3-2 Application of Ohm's Law

4.
 - (a) $I = \frac{V}{R} = \frac{5\text{ V}}{1\ \Omega} = \mathbf{5\text{ A}}$
 - (b) $I = \frac{V}{R} = \frac{15\text{ V}}{10\ \Omega} = \mathbf{1.5\text{ A}}$
 - (c) $I = \frac{V}{R} = \frac{50\text{ V}}{100\ \Omega} = \mathbf{0.5\text{ A}}$
 - (d) $I = \frac{V}{R} = \frac{30\text{ V}}{15\text{ k}\Omega} = \mathbf{2\text{ mA}}$
 - (e) $I = \frac{V}{R} = \frac{250\text{ V}}{4.7\text{ M}\Omega} = \mathbf{53.2\ \mu\text{A}}$
5.
 - (a) $I = \frac{V}{R} = \frac{9\text{ V}}{2.7\text{ k}\Omega} = \mathbf{3.33\text{ mA}}$
 - (b) $I = \frac{V}{R} = \frac{5.5\text{ V}}{10\text{ k}\Omega} = \mathbf{550\ \mu\text{A}}$
 - (c) $I = \frac{V}{R} = \frac{40\text{ V}}{68\text{ k}\Omega} = \mathbf{588\ \mu\text{A}}$
 - (d) $I = \frac{V}{R} = \frac{1\text{ kV}}{2\text{ k}\Omega} = \mathbf{500\text{ mA}}$
 - (e) $I = \frac{V}{R} = \frac{66\text{ kV}}{10\text{ M}\Omega} = \mathbf{6.60\text{ mA}}$

6. $I = \frac{V}{R} = \frac{12 \text{ V}}{10 \Omega} = \mathbf{1.2 \text{ A}}$

7. (a) $I = \frac{V}{R} = \frac{25 \text{ V}}{10 \text{ k}\Omega} = \mathbf{2.50 \text{ mA}}$

(b) $I = \frac{V}{R} = \frac{5 \text{ V}}{2.2 \text{ M}\Omega} = \mathbf{2.27 \mu\text{A}}$

(c) $I = \frac{V}{R} = \frac{15 \text{ V}}{1.8 \text{ k}\Omega} = \mathbf{8.33 \text{ mA}}$

8. Orange, violet, yellow, gold, brown $\equiv 37.4 \Omega \pm 1\%$

$$I = \frac{V_s}{R} = \frac{12 \text{ V}}{37.4 \Omega} = \mathbf{0.321 \text{ A}}$$

9. $I = \frac{24 \text{ V}}{37.4 \Omega} = 0.642 \text{ A}$

0.642 A is greater than 0.5 A, so **the fuse will blow.**

10. (a) $V = IR = (2 \text{ A})(18 \Omega) = \mathbf{36 \text{ V}}$

(b) $V = IR = (5 \text{ A})(47 \Omega) = \mathbf{235 \text{ V}}$

(c) $V = IR = (2.5 \text{ A})(620 \Omega) = \mathbf{1550 \text{ V}}$

(d) $V = IR = (0.6 \text{ A})(47 \Omega) = \mathbf{28.2 \text{ V}}$

(e) $V = IR = (0.1 \text{ A})(470 \Omega) = \mathbf{47 \text{ V}}$

11. (a) $V = IR = (1 \text{ mA})(10 \Omega) = \mathbf{10 \text{ mV}}$

(b) $V = IR = (50 \text{ mA})(33 \Omega) = \mathbf{1.65 \text{ V}}$

(c) $V = IR = (3 \text{ A})(4.7 \text{ k}\Omega) = \mathbf{14.1 \text{ kV}}$

(d) $V = IR = (1.6 \text{ mA})(2.2 \text{ k}\Omega) = \mathbf{3.52 \text{ V}}$

(e) $V = IR = (250 \mu\text{A})(1 \text{ k}\Omega) = \mathbf{250 \text{ mV}}$

(f) $V = IR = (500 \text{ mA})(1.5 \text{ M}\Omega) = \mathbf{750 \text{ kV}}$

(g) $V = IR = (850 \mu\text{A})(10 \text{ M}\Omega) = \mathbf{8.5 \text{ kV}}$

(h) $V = IR = (75 \mu\text{A})(47 \Omega) = \mathbf{3.53 \text{ mV}}$

12. $V_s = IR = (3 \text{ A})(27 \Omega) = \mathbf{81 \text{ V}}$

13. (a) $V = IR = (3 \text{ mA})(27 \text{ k}\Omega) = \mathbf{81 \text{ V}}$

(b) $V = IR = (5 \mu\text{A})(100 \text{ M}\Omega) = \mathbf{500 \text{ V}}$

(c) $V = IR = (2.5 \text{ A})(47 \Omega) = \mathbf{117.5 \text{ V}}$

14. (a) $R = \frac{V}{I} = \frac{10 \text{ V}}{2 \text{ A}} = \mathbf{5 \Omega}$

(b) $R = \frac{V}{I} = \frac{90 \text{ V}}{45 \text{ A}} = \mathbf{2 \Omega}$

(c) $R = \frac{V}{I} = \frac{50 \text{ V}}{5 \text{ A}} = \mathbf{10 \Omega}$

(d) $R = \frac{V}{I} = \frac{5.5 \text{ V}}{10 \text{ A}} = \mathbf{0.55 \Omega}$

(e) $R = \frac{V}{I} = \frac{150 \text{ V}}{0.5 \text{ A}} = \mathbf{300 \Omega}$

15. (a) $R = \frac{V}{I} = \frac{10 \text{ kV}}{5 \text{ A}} = \mathbf{2 \text{ k}\Omega}$

(b) $R = \frac{V}{I} = \frac{7 \text{ V}}{2 \text{ mA}} = \mathbf{3.5 \text{ k}\Omega}$

(c) $R = \frac{V}{I} = \frac{500 \text{ V}}{250 \text{ mA}} = \mathbf{2 \text{ k}\Omega}$

(d) $R = \frac{V}{I} = \frac{50 \text{ V}}{500 \mu\text{A}} = \mathbf{100 \text{ k}\Omega}$

$$(e) \quad R = \frac{V}{I} = \frac{1 \text{ kV}}{1 \text{ mA}} = 1 \text{ M}\Omega$$

$$16. \quad R = \frac{V}{I} = \frac{6 \text{ V}}{2 \text{ mA}} = 3 \text{ k}\Omega$$

$$17. \quad (a) \quad R = \frac{V}{I} = \frac{8 \text{ V}}{2 \text{ A}} = 4 \Omega$$

$$(b) \quad R = \frac{V}{I} = \frac{12 \text{ V}}{4 \text{ mA}} = 3 \text{ k}\Omega$$

$$(c) \quad R = \frac{V}{I} = \frac{30 \text{ V}}{150 \mu\text{A}} = 0.2 \text{ M}\Omega = 200 \text{ k}\Omega$$

SECTION 3-3 Energy and Power

$$18. \quad \text{Since } 1 \text{ watt} = 1 \text{ joule}, P = 350 \text{ J/s} = \mathbf{350 \text{ W}}$$

$$19. \quad P = \frac{W}{t} = \frac{7500 \text{ J}}{5 \text{ h}}$$

$$\left(\frac{7500 \text{ J}}{5 \text{ h}} \right) \left(\frac{1 \text{ h}}{3600 \text{ s}} \right) = \frac{7500 \text{ J}}{18,000 \text{ s}} = 0.417 \text{ J/s} = \mathbf{417 \text{ mW}}$$

$$20. \quad (a) \quad 1000 \text{ W} = 1 \times 10^3 \text{ W} = \mathbf{1 \text{ kW}} \quad (b) \quad 3750 \text{ W} = 3.750 \times 10^3 \text{ W} = \mathbf{3.75 \text{ kW}}$$

$$(c) \quad 160 \text{ W} = 0.160 \times 10^3 \text{ W} = \mathbf{0.160 \text{ kW}} \quad (d) \quad 50,000 \text{ W} = 50 \times 10^3 \text{ W} = \mathbf{50 \text{ kW}}$$

$$21. \quad (a) \quad 1,000,000 \text{ W} = 1 \times 10^6 \text{ W} = \mathbf{1 \text{ MW}} \quad (b) \quad 3 \times 10^6 \text{ W} = \mathbf{3 \text{ MW}}$$

$$(c) \quad 15 \times 10^7 \text{ W} = 150 \times 10^6 \text{ W} = \mathbf{150 \text{ MW}} \quad (d) \quad 8700 \text{ kW} = 8.7 \times 10^6 \text{ W} = \mathbf{8.7 \text{ MW}}$$

$$22. \quad (a) \quad 1 \text{ W} = 1000 \times 10^{-3} \text{ W} = \mathbf{1000 \text{ mW}} \quad (b) \quad 0.4 \text{ W} = 400 \times 10^{-3} \text{ W} = \mathbf{400 \text{ mW}}$$

$$(c) \quad 0.002 \text{ W} = 2 \times 10^{-3} \text{ W} = \mathbf{2 \text{ mW}} \quad (d) \quad 0.0125 \text{ W} = 12.5 \times 10^{-3} \text{ W} = \mathbf{12.5 \text{ mW}}$$

$$23. \quad (a) \quad 2 \text{ W} = \mathbf{2,000,000 \mu\text{W}} \quad (b) \quad 0.0005 \text{ W} = \mathbf{500 \mu\text{W}}$$

$$(c) \quad 0.25 \text{ mW} = \mathbf{250 \mu\text{W}} \quad (d) \quad 0.00667 \text{ mW} = \mathbf{6.67 \mu\text{W}}$$

$$24. \quad (a) \quad 1.5 \text{ kW} = 1.5 \times 10^3 \text{ W} = \mathbf{1500 \text{ W}} \quad (b) \quad 0.5 \text{ MW} = 0.5 \times 10^6 \text{ W} = \mathbf{500,000 \text{ W}}$$

$$(c) \quad 350 \text{ mW} = 350 \times 10^{-3} \text{ W} = \mathbf{0.350 \text{ W}} \quad (d) \quad 9000 \mu\text{W} = 9000 \times 10^{-6} \text{ W} = \mathbf{0.009 \text{ W}}$$

$$25. \quad P = \frac{W}{t} \text{ in watts}$$

$$V = \frac{W}{Q}$$

$$I = \frac{Q}{t}$$

$$P = VI = \frac{W}{t}$$

$$\text{So, } (1 \text{ V})(1 \text{ A}) = 1 \text{ W}$$

$$26. \quad P = \frac{W}{t} = \frac{1 \text{ J}}{1 \text{ s}} = 1 \text{ W}$$

$$1 \text{ kW} = 1000 \text{ W} = \frac{1000 \text{ J}}{1 \text{ s}}$$

$$1 \text{ kW-second} = 1000 \text{ J}$$

$$1 \text{ kWh} = 3600 \times 1000 \text{ J}$$

$$\mathbf{1 \text{ kWh} = 3.6 \times 10^6 \text{ J}}$$

SECTION 3-4 Power in an Electric Circuit

$$27. \quad P = VI = (5.5 \text{ V})(3 \text{ mA}) = \mathbf{16.5 \text{ mW}}$$

$$28. \quad P = VI = (115 \text{ V})(3 \text{ A}) = \mathbf{345 \text{ W}}$$

$$29. \quad P = I^2 R = (500 \text{ mA})^2 (4.7 \text{ k}\Omega) = \mathbf{1.18 \text{ kW}}$$

$$30. \quad P = I^2 R = (100 \times 10^{-6} \text{ A})^2 (10 \times 10^3 \Omega) = 1 \times 10^{-4} \text{ W} = \mathbf{100 \mu\text{W}}$$

$$31. \quad P = \frac{V^2}{R} = \frac{(60 \text{ V})^2}{620 \Omega} = \mathbf{5.81 \text{ W}}$$

$$32. \quad P = \frac{V^2}{R} = \frac{(1.5 \text{ V})^2}{56 \Omega} = 0.0402 \text{ W} = \mathbf{40.2 \text{ mW}}$$

$$33. \quad P = I^2 R$$

$$R = \frac{P}{I^2} = \frac{100 \text{ W}}{(2 \text{ A})^2} = \mathbf{25 \Omega}$$

34. $5 \times 10^6 \text{ watts for 1 minute} = 5 \times 10^3 \text{ kWmin}$

$$\frac{5 \times 10^3 \text{ kWmin}}{60 \text{ min/1 hr}} = \mathbf{83.3 \text{ kWh}}$$

35. $\frac{6700 \text{ W/s}}{(1000 \text{ W/kW})(3600 \text{ s/h})} = \mathbf{0.00186 \text{ kWh}}$

36. $(50 \text{ W})(12 \text{ h}) = \mathbf{600 \text{ Wh}}$
 $50 \text{ W} = 0.05 \text{ kW}$
 $(0.05 \text{ kW})(12 \text{ h}) = \mathbf{0.6 \text{ kWh}}$

37. $I = \frac{V}{R_L} = \frac{1.25 \text{ V}}{10 \Omega} = 0.125 \text{ A}$

$$P = VI = (1.25 \text{ V})(0.125 \text{ A}) = 0.156 \text{ W} = \mathbf{156 \text{ mW}}$$

38. $P = \frac{W}{t}$

$$156 \text{ mW} = \frac{156 \text{ mJ}}{1 \text{ s}}$$

$$W_{\text{tot}} = (156 \text{ mJ/s})(90 \text{ h})(3600 \text{ s/h}) = \mathbf{50,544 \text{ J}}$$

SECTION 3-5 The Power Rating of Resistors

39. $P = I^2 R = (10 \text{ mA})^2 (6.8 \text{ k}\Omega) = 0.68 \text{ W}$
 Use the next highest standard power rating of **1 W**.

40. If the 8 W resistor is used, it will be operating in a marginal condition.
 To allow for a **safety margin of 20%**, use a **12 W** resistor.

SECTION 3-6 Energy Conversion and Voltage Drop in a Resistance

41. (a) + at top, – at bottom of resistor (b) + at bottom, – at top of resistor
 (c) + on right, – on left of resistor

SECTION 3-7 Power Supplies

42. $V_{\text{OUT}} = \sqrt{P_L R_L} = \sqrt{(1 \text{ W})(50 \Omega)} = \mathbf{7.07 \text{ V}}$

43. Ampere-hour rating = $(1.5 \text{ A})(24 \text{ h}) = \mathbf{36 \text{ Ah}}$

$$44. \quad I = \frac{80 \text{ Ah}}{10 \text{ h}} = \mathbf{8 \text{ A}}$$

$$45. \quad I = \frac{650 \text{ mAh}}{48 \text{ h}} = \mathbf{13.5 \text{ mA}}$$

$$46. \quad P_{\text{LOST}} = P_{\text{IN}} - P_{\text{OUT}} = 500 \text{ mW} - 400 \text{ mW} = \mathbf{100 \text{ mW}}$$

$$\% \text{ efficiency} = \left(\frac{P_{\text{OUT}}}{P_{\text{IN}}} \right) 100\% = \left(\frac{400 \text{ mW}}{500 \text{ mW}} \right) 100\% = \mathbf{80\%}$$

$$47. \quad P_{\text{OUT}} = (\text{efficiency})P_{\text{IN}} = (0.85)(5 \text{ W}) = \mathbf{4.25 \text{ W}}$$

SECTION 3-8 Introduction to Troubleshooting

48. The 4th bulb from the left is open.

49. If should take **five** (maximum) resistance measurements.

ADVANCED PROBLEMS

50. Assume that the total consumption of the power supply is the input power plus the power lost.

$$P_{\text{OUT}} = 2 \text{ W}$$

$$\% \text{ efficiency} = \left(\frac{P_{\text{OUT}}}{P_{\text{IN}}} \right) 100\%$$

$$P_{\text{IN}} = \left(\frac{P_{\text{OUT}}}{\% \text{ efficiency}} \right) 100\% = \left(\frac{2 \text{ W}}{60\%} \right) 100\% = 3.33 \text{ W}$$


The power supply itself uses

$$P_{\text{IN}} - P_{\text{OUT}} = 3.33 \text{ W} - 2 \text{ W} = 1.33 \text{ W}$$

$$\text{Energy} = W = Pt = (1.33 \text{ W})(24 \text{ h}) = 31.9 \text{ Wh} \cong \mathbf{0.032 \text{ kWh}}$$


$$51. \quad R_f = \frac{V}{I} = \frac{120 \text{ V}}{0.8 \text{ A}} = \mathbf{150 \Omega}$$

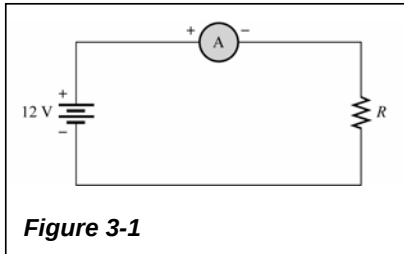52. Measure the current with an ammeter connected as shown in Figure 3-1. Then calculate the unknown resistance with the formula, $R = 12 \text{ V}/I$.



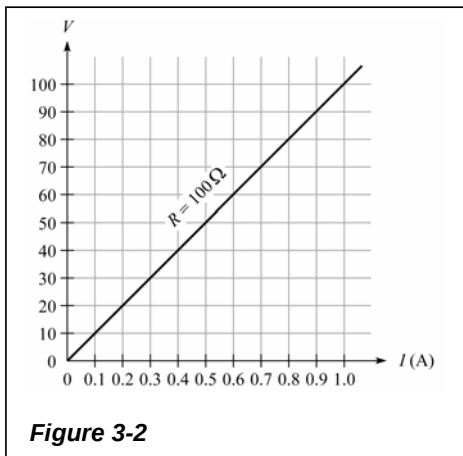53. Calculate I for each value of V :

$$\begin{aligned}
 I_1 &= \frac{0 \text{ V}}{100 \Omega} = \mathbf{0 \text{ A}} & I_2 &= \frac{10 \text{ V}}{100 \Omega} = \mathbf{100 \text{ mA}} \\
 I_3 &= \frac{20 \text{ V}}{100 \Omega} = \mathbf{200 \text{ mA}} & I_4 &= \frac{30 \text{ V}}{100 \Omega} = \mathbf{300 \text{ mA}} \\
 I_5 &= \frac{40 \text{ V}}{100 \Omega} = \mathbf{400 \text{ mA}} & I_6 &= \frac{50 \text{ V}}{100 \Omega} = \mathbf{500 \text{ mA}} \\
 I_7 &= \frac{60 \text{ V}}{100 \Omega} = \mathbf{600 \text{ mA}} & I_8 &= \frac{70 \text{ V}}{100 \Omega} = \mathbf{700 \text{ mA}} \\
 I_9 &= \frac{80 \text{ V}}{100 \Omega} = \mathbf{800 \text{ mA}} & I_{10} &= \frac{90 \text{ V}}{100 \Omega} = \mathbf{900 \text{ mA}} \\
 I_{11} &= \frac{100 \text{ V}}{100 \Omega} = \mathbf{1 \text{ A}}
 \end{aligned}$$



The graph is a straight line as shown in Figure 3-2. This indicates a *linear* relationship between I and V .

$$54. \quad R = \frac{V_s}{I} = \frac{1 \text{ V}}{5 \text{ mA}} = \mathbf{200 \, \Omega}$$

$$(a) \quad I = \frac{V_s}{R} = \frac{1.5 \text{ V}}{200 \, \Omega} = \mathbf{7.5 \text{ mA}}$$

$$(b) \quad I = \frac{V_s}{R} = \frac{2 \text{ V}}{200 \, \Omega} = \mathbf{10 \text{ mA}}$$

$$(c) \quad I = \frac{V_s}{R} = \frac{3 \text{ V}}{200 \, \Omega} = \mathbf{15 \text{ mA}}$$

$$(d) \quad I = \frac{V_s}{R} = \frac{4 \text{ V}}{200 \, \Omega} = \mathbf{20 \text{ mA}}$$

$$(e) \quad I = \frac{V_s}{R} = \frac{10 \text{ V}}{200 \, \Omega} = \mathbf{50 \text{ mA}}$$

$$55. \quad R_1 = \frac{V}{I} = \frac{1 \text{ V}}{2 \text{ A}} = \mathbf{0.5 \, \Omega} \quad R_2 = \frac{V}{I} = \frac{1 \text{ V}}{1 \text{ A}} = \mathbf{1 \, \Omega} \quad R_3 = \frac{V}{I} = \frac{1 \text{ V}}{0.5 \text{ A}} = \mathbf{2 \, \Omega}$$

$$56. \quad \frac{V_2}{30 \text{ mA}} = \frac{10 \text{ V}}{50 \text{ mA}}$$

$$V_2 = \frac{(10 \text{ V})(30 \text{ mA})}{50 \text{ mA}} = 6 \text{ V} \quad \mathbf{\text{new value}}$$

The voltage decreased by 4 V, from 10 V to 6 V.

57. The current increase is 50%, so the voltage increase must be the same; that is, the voltage must be increased by $(0.5)(20 \text{ V}) = \mathbf{10 \text{ V}}$.

The new value of voltage is $V_2 = 20 \text{ V} + (0.5)(20 \text{ V}) = 20 \text{ V} + 10 \text{ V} = \mathbf{30 \text{ V}}$

$$58. \quad R = \frac{100 \text{ V}}{750 \text{ mA}} \quad 0.133 \text{ k}\Omega = \mathbf{133 \, \Omega}; \quad R = \frac{100 \text{ V}}{1 \text{ A}} = \mathbf{100 \, \Omega}$$

If $R = 0 \, \Omega$, the voltage source will be shorted causing possible damage.

59. Resistance value = $3300 \, \Omega \pm 5\%$

$$R_{\max} = 3300 \, \Omega + (0.05)(3300 \, \Omega) = 3465 \, \Omega$$

$$R_{\min} = 3300 \, \Omega - (0.05)(3300 \, \Omega) = 3135 \, \Omega$$

$$I_{\max} = \frac{V_s}{R_{\min}} = \frac{12 \text{ V}}{3135 \, \Omega} = \mathbf{3.83 \text{ mA}}$$

$$I_{\min} = \frac{V_s}{R_{\max}} = \frac{12 \text{ V}}{3465 \, \Omega} = \mathbf{3.46 \text{ mA}}$$

60. Wire resistance: $R_W = \frac{(10.4 \text{ CM} \cdot \Omega/\text{ft})(24 \text{ ft})}{1624.3 \text{ CM}} = 0.154 \Omega$
- (a) $I = \frac{V}{R + R_W} = \frac{6 \text{ V}}{100.154 \Omega} = \mathbf{59.9 \text{ mA}}$
- (b) $V_R = (59.9 \text{ mA})(100 \Omega) = \mathbf{5.99 \text{ V}}$
- (c) $V_{R_W} = 6 \text{ V} - 5.99 \text{ V} = 0.01 \text{ V}$
- For one length of wire, $V = \frac{0.01 \text{ V}}{2} = \mathbf{0.005 \text{ V}}$
61. $300 \text{ W} = 0.3 \text{ kW}$
 $30 \text{ days} = (30 \text{ days})(24 \text{ h/day}) = 720 \text{ h}$
 $\text{Energy} = (0.3 \text{ kW})(720 \text{ h}) = \mathbf{216 \text{ kWh}}$
62. $\frac{1500 \text{ kWh}}{31 \text{ days}} = 48.39 \text{ kWh/day}$
 $P = \frac{48.39 \text{ kWh/day}}{24 \text{ h/day}} = \mathbf{2.02 \text{ kW}}$
63. The minimum power rating you should use is **12 W** so that the power dissipation does not exceed the rating.
64. (a) $P = \frac{V^2}{R} = \frac{(12 \text{ V})^2}{10 \Omega} = \mathbf{14.4 \text{ W}}$
- (b) $W = Pt = (14.4 \text{ W})(2 \text{ min})(1/60 \text{ h/min}) = \mathbf{0.48 \text{ Wh}}$
- (c) Neither, the power is the same because it is not time dependent.
65. $V_{R(\text{max})} = 120 \text{ V} - 100 \text{ V} = 20 \text{ V}$
 $I_{\text{max}} = \frac{V_{R(\text{max})}}{R_{\text{min}}} = \frac{20 \text{ V}}{8 \Omega} = 2.5 \text{ A}$
 A fuse with a rating of less than 2.5 A must be used. **A 2 A fuse is recommended.**

Multisim Troubleshooting Problems


66. R is open.
67. No fault
68. R_1 is shorted.
69. Lamp 4 is shorted.
70. Lamp 6 is open.

CHAPTER 4 SERIES CIRCUITS

BASIC PROBLEMS


SECTION 4-1 Resistors in Series

1. See Figure 4-1.

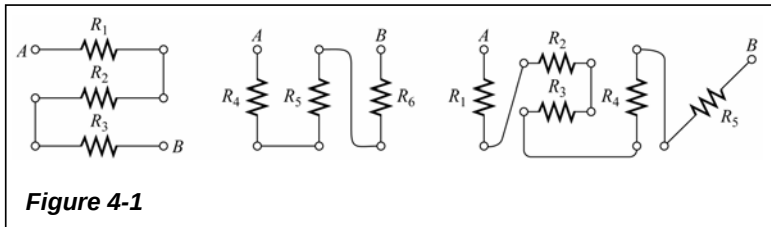

2. The groups of series resistors are
 $R_1, R_2, R_3, R_9, R_4;$ $R_{13}, R_7, R_{14}, R_{16};$ $R_6, R_8, R_{12};$ $R_{10}, R_{11}, R_{15}, R_5$

See Figure 4-2.

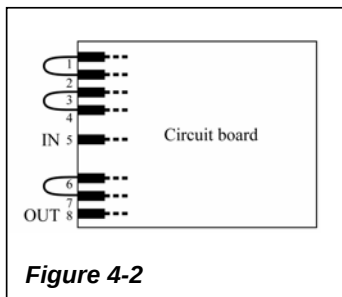


3. $R_{1-8} = R_{13} + R_7 + R_{14} + R_{16}$
 $= 68 \text{ k}\Omega + 33 \text{ k}\Omega + 47 \text{ k}\Omega + 22 \text{ k}\Omega$
 $= \mathbf{170 \text{ k}\Omega}$
4. $R_{2-3} = R_{12} + R_8 + R_6 = 10 \text{ }\Omega + 18 \text{ }\Omega + 22 \text{ }\Omega = \mathbf{50 \text{ }\Omega}$

SECTION 4-2 Total Series Resistance

5. $R_T = 82\ \Omega + 56\ \Omega = \mathbf{138\ \Omega}$
6.
 - (a) $R_T = 560\ \Omega + 1.0\ \text{k}\Omega = \mathbf{1560\ \Omega}$
 - (b) $R_T = 47\ \Omega + 33\ \Omega = \mathbf{80\ \Omega}$
 - (c) $R_T = 1.5\ \text{k}\Omega + 2.2\ \text{k}\Omega + 10\ \text{k}\Omega = \mathbf{13.7\ \text{k}\Omega}$
 - (d) $R_T = 1.0\ \text{k}\Omega + 1.8\ \text{k}\Omega + 100\ \text{k}\Omega + 1.0\ \text{M}\Omega = \mathbf{1,102,800\ \Omega}$
7.
 - (a) $R_T = 1.0\ \text{k}\Omega + 4.7\ \text{k}\Omega + 2.2\ \text{k}\Omega = \mathbf{7.9\ \text{k}\Omega}$
 - (b) $R_T = 10\ \Omega + 10\ \Omega + 12\ \Omega + 1.0\ \Omega = \mathbf{33\ \Omega}$
 - (c) $R_T = 1.0\ \text{M}\Omega + 560\ \text{k}\Omega + 1.0\ \text{M}\Omega + 680\ \text{k}\Omega + 10\ \text{M}\Omega = \mathbf{13.24\ \text{M}\Omega}$

See Figure 4-3.

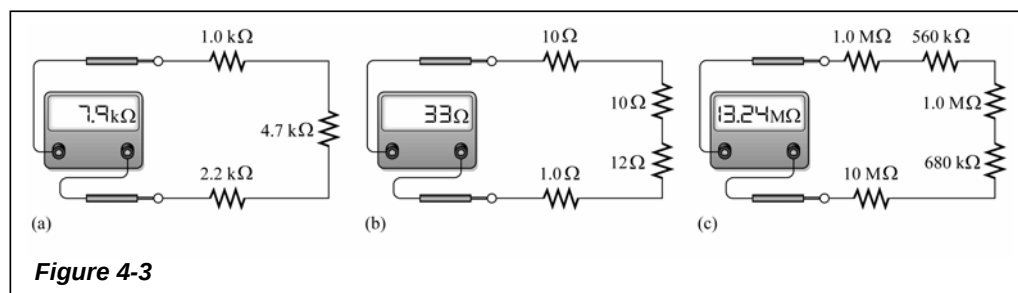

8. $R_T = 12(5.6\ \text{k}\Omega) = \mathbf{67.2\ \text{k}\Omega}$
9. $R_T = 6(47\ \Omega) + 8(100\ \Omega) + 2(22\ \Omega) = 282\ \Omega + 800\ \Omega + 44\ \Omega = \mathbf{1126\ \Omega}$
10.

$$R_T = R_1 + R_2 + R_3 + R_4 + R_5$$

$$R_5 = R_T - (R_1 + R_2 + R_3 + R_4)$$

$$= 20\ \text{k}\Omega - (4.7\ \text{k}\Omega + 1.0\ \text{k}\Omega + 2.2\ \text{k}\Omega + 3.9\ \text{k}\Omega)$$

$$= 20\ \text{k}\Omega - 11.8\ \text{k}\Omega$$

$$= \mathbf{8.2\ \text{k}\Omega}$$
11.
 - (a) $R_{1-8} = R_{13} + R_7 + R_{14} + R_{16}$
 $= 68\ \text{k}\Omega + 33\ \text{k}\Omega + 47\ \text{k}\Omega + 22\ \text{k}\Omega = \mathbf{170\ \text{k}\Omega}$
 - (b) $R_{2-3} = R_{12} + R_8 + R_6$
 $= 10\ \Omega + 18\ \Omega + 22\ \Omega = \mathbf{50\ \Omega}$
 - (c) $R_{4-7} = R_{10} + R_{11} + R_{15} + R_5$
 $= 2.2\ \text{k}\Omega + 8.2\ \text{k}\Omega + 1.0\ \text{k}\Omega + 1.0\ \text{k}\Omega = \mathbf{12.4\ \text{k}\Omega}$
 - (d) $R_{5-6} = R_1 + R_2 + R_3 + R_9 + R_4$
 $= 220\ \Omega + 330\ \Omega + 390\ \Omega + 470\ \Omega + 560\ \Omega = \mathbf{1.97\ \text{k}\Omega}$

$$\begin{aligned}
 12. \quad R_T &= R_{1-8} + R_{2-3} + R_{4-7} + R_{5-6} \\
 &= 170 \text{ k}\Omega + 50 \text{ }\Omega + 12.4 \text{ k}\Omega + 1.97 \text{ k}\Omega = \mathbf{184.42 \text{ k}\Omega}
 \end{aligned}$$

SECTION 4-3 Current in a Series Circuit

$$13. \quad I = \frac{V_S}{R_T} = \frac{12 \text{ V}}{120 \text{ }\Omega} = \mathbf{0.1 \text{ A}}$$

$$14. \quad I = \mathbf{5 \text{ mA}} \text{ at all points in the circuit.}$$

SECTION 4-4 Application of Ohm's Law


$$15. \quad (a) \quad R_T = 2.2 \text{ k}\Omega + 5.6 \text{ k}\Omega + 1.0 \text{ k}\Omega = 8.8 \text{ k}\Omega$$

$$I = \frac{V}{R_T} = \frac{5.5 \text{ V}}{8.8 \text{ k}\Omega} = \mathbf{625 \text{ }\mu\text{A}}$$

$$(b) \quad R_T = 1.0 \text{ M}\Omega + 2.2 \text{ M}\Omega + 560 \text{ k}\Omega = 3.76 \text{ M}\Omega$$

$$I = \frac{16 \text{ V}}{3.76 \text{ M}\Omega} = \mathbf{4.26 \text{ }\mu\text{A}}$$

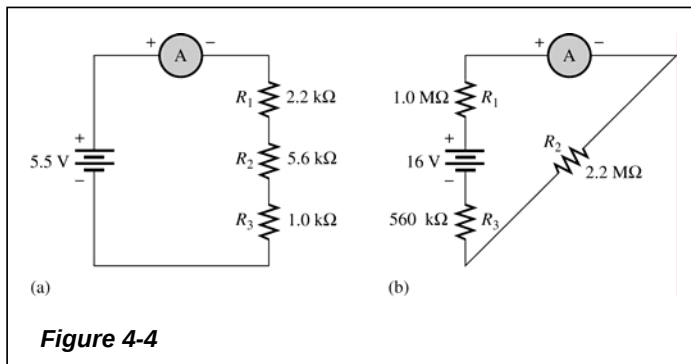The ammeters are connected in series. See Figure 4-4.



$$16. \quad (a) \quad V_1 = \left(\frac{R_1}{R_T} \right) V_S = \left(\frac{2.2 \text{ k}\Omega}{8.8 \text{ k}\Omega} \right) 5.5 \text{ V} = \mathbf{1.375 \text{ V}}$$

$$V_2 = \left(\frac{R_2}{R_T} \right) V_S = \left(\frac{5.6 \text{ k}\Omega}{8.8 \text{ k}\Omega} \right) 5.5 \text{ V} = \mathbf{3.5 \text{ V}}$$

$$V_3 = \left(\frac{R_3}{R_T} \right) V_S = \left(\frac{1.0 \text{ k}\Omega}{8.8 \text{ k}\Omega} \right) 5.5 \text{ V} = \mathbf{625 \text{ mV}}$$

$$\begin{aligned} \text{(b)} \quad V_1 &= \left(\frac{R_1}{R_T} \right) V_S = \left(\frac{1.0 \text{ M}\Omega}{3.76 \text{ M}\Omega} \right) 16 \text{ V} = \mathbf{4.26 \text{ V}} \\ V_2 &= \left(\frac{R_2}{R_T} \right) V_S = \left(\frac{2.2 \text{ M}\Omega}{3.76 \text{ M}\Omega} \right) 16 \text{ V} = \mathbf{9.36 \text{ V}} \\ V_3 &= \left(\frac{R_3}{R_T} \right) V_S = \left(\frac{560 \text{ k}\Omega}{3.76 \text{ M}\Omega} \right) 16 \text{ V} = \mathbf{2.38 \text{ V}} \end{aligned}$$

$$\begin{aligned} 17. \quad \text{(a)} \quad R_T &= 3(470 \text{ }\Omega) = 1410 \text{ }\Omega \\ I &= \frac{48 \text{ V}}{1410 \text{ }\Omega} = \mathbf{34.0 \text{ mA}} \end{aligned}$$

$$\text{(b)} \quad V_R = IR = (34.0 \text{ mA})(470 \text{ }\Omega) = \mathbf{16 \text{ V}}$$

$$\text{(c)} \quad P_{\min} = I^2 R = (34.0 \text{ mA})^2 470 \text{ }\Omega = \mathbf{0.543 \text{ W}}$$

$$\begin{aligned} 18. \quad R_T &= \frac{V_S}{I_T} = \frac{5 \text{ V}}{1 \text{ mA}} = 5 \text{ k}\Omega \\ R_{\text{each}} &= \frac{5 \text{ k}\Omega}{4} = \mathbf{1.25 \text{ k}\Omega} \end{aligned}$$

SECTION 4-5 Voltage Sources in Series

$$19. \quad V_T = 5 \text{ V} + 9 \text{ V} = \mathbf{14 \text{ V}}$$

$$20. \quad \text{(a)} \quad V_{S(\text{tot})} = 10 \text{ V} + 5 \text{ V} + 8 \text{ V} = \mathbf{23 \text{ V}}$$

$$\text{(b)} \quad V_{S(\text{tot})} = 10 \text{ V} + 50 \text{ V} - 25 \text{ V} = \mathbf{35 \text{ V}}$$

$$\text{(c)} \quad V_{S(\text{tot})} = 8 \text{ V} - 8 \text{ V} = \mathbf{0 \text{ V}}$$

SECTION 4-6 Kirchhoff's Voltage Law

$$21. \quad V_S = 5.5 \text{ V} + 8.2 \text{ V} + 12.3 \text{ V} = \mathbf{26 \text{ V}}$$


$$\begin{aligned} 22. \quad V_S &= V_1 + V_2 + V_3 + V_4 + V_5 \\ V_5 &= V_S - (V_1 + V_2 + V_3 + V_4) = 20 \text{ V} - (1.5 \text{ V} + 5.5 \text{ V} + 3 \text{ V} + 6 \text{ V}) = 20 \text{ V} - 16 \text{ V} = \mathbf{4 \text{ V}} \end{aligned}$$

$$\begin{aligned} 23. \quad \text{(a)} \quad &\text{By Kirchhoff's voltage law:} \\ &15 \text{ V} = 2 \text{ V} + V_2 + 3.2 \text{ V} + 1 \text{ V} + 1.5 \text{ V} + 0.5 \text{ V} \\ &V_2 = 15 \text{ V} - (2 \text{ V} + 3.2 \text{ V} + 1 \text{ V} + 1.5 \text{ V} + 0.5 \text{ V}) = 15 \text{ V} - 8.2 \text{ V} = \mathbf{6.8 \text{ V}} \end{aligned}$$

See Figure 4-5(a).

(b) $V_R = 8 \text{ V}$; $V_{2R} = 16 \text{ V}$; $V_{3R} = 24 \text{ V}$; $V_{4R} = 32 \text{ V}$

See Figure 4-5(b).

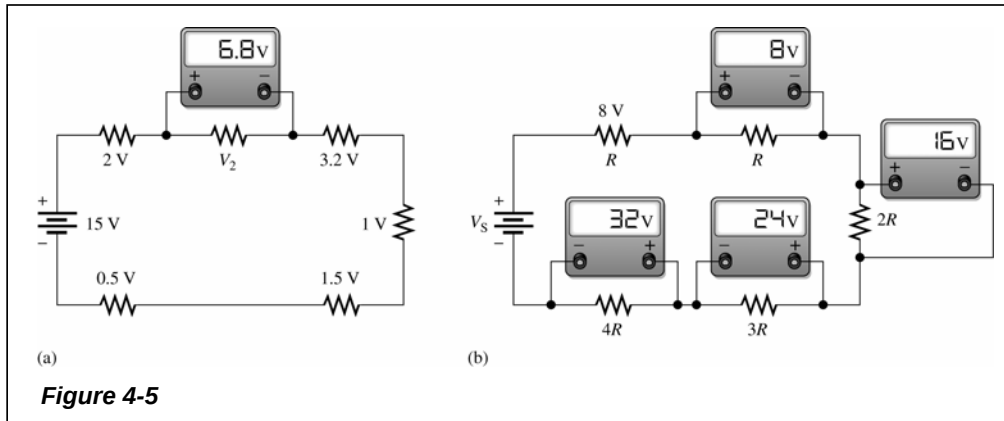

SECTION 4-7 Voltage Dividers

24. $\left(\frac{22 \Omega}{500 \Omega}\right)100 = 4.4\%$

25. (a) $V_{AB} = \left(\frac{47 \Omega}{147 \Omega}\right)12 \text{ V} = 3.84 \text{ V}$

(b) $V_{AB} = \left(\frac{2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega}{1.0 \text{ k}\Omega + 2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega}\right)8 \text{ V} = \left(\frac{5.5 \text{ k}\Omega}{6.5 \text{ k}\Omega}\right)8 \text{ V} = 6.77 \text{ V}$

26. $V_A = V_S = 15 \text{ V}$

$$V_B = \left(\frac{R_2 + R_3}{R_1 + R_2 + R_3}\right)V_S = \left(\frac{13.3 \text{ k}\Omega}{18.9 \text{ k}\Omega}\right)15 \text{ V} = 10.6 \text{ V}$$

$$V_C = \left(\frac{R_3}{R_1 + R_2 + R_3}\right)V_S = \left(\frac{3.3 \text{ k}\Omega}{18.9 \text{ k}\Omega}\right)15 \text{ V} = 2.62 \text{ V}$$

27. $V_{\min} = \left(\frac{R_3}{R_1 + R_2 + R_3}\right)V_S = \left(\frac{680 \Omega}{2150 \Omega}\right)12 \text{ V} = 3.80 \text{ V}$

$$V_{\max} = \left(\frac{R_2 + R_3}{R_1 + R_2 + R_3}\right)V_S = \left(\frac{1680 \Omega}{2150 \Omega}\right)12 \text{ V} = 9.38 \text{ V}$$

28. $R_T = R + 2R + 3R + 4R + 5R = 15R$

$$V_R = \left(\frac{R}{15R} \right) 9 \text{ V} = \mathbf{0.6 \text{ V}} \quad V_R = \left(\frac{2R}{15R} \right) 9 \text{ V} = \mathbf{1.2 \text{ V}} \quad V_R = \left(\frac{3R}{15R} \right) 9 \text{ V} = \mathbf{1.8 \text{ V}}$$

$$V_R = \left(\frac{4R}{15R} \right) 9 \text{ V} = \mathbf{2.4 \text{ V}} \quad V_R = \left(\frac{5R}{15R} \right) 9 \text{ V} = \mathbf{3.0 \text{ V}}$$

29. $V_{5.6k} = \mathbf{10 \text{ V}}$ (by measurement); $I = \frac{10 \text{ V}}{5.6 \text{ k}\Omega} = 1.79 \text{ mA}$;
 $V_{1k} = (1.79 \text{ mA})(1 \text{ k}\Omega) = \mathbf{1.79 \text{ V}}$; $V_{560} = (1.79 \text{ mA})(560 \Omega) = \mathbf{1 \text{ V}}$;
 $V_{10k} = (1.79 \text{ mA})(10 \text{ k}\Omega) = \mathbf{17.9 \text{ V}}$

SECTION 4-8 Power in a Series Circuit

30. $P_T = 5(50 \text{ mW}) = \mathbf{250 \text{ mW}}$

31. $R_T = 5.6 \text{ k}\Omega + 1 \text{ k}\Omega + 560 \Omega + 10 \text{ k}\Omega = 17.16 \text{ k}\Omega$
 $P = I^2 R_T = (1.79 \text{ mA})^2 (17.16 \text{ k}\Omega) = 0.055 \text{ W} = \mathbf{55 \text{ mW}}$

SECTION 4-9 Voltage Measurement

32. Voltage from point A to ground (G): $V_{AG} = \mathbf{10 \text{ V}}$

Resistance between A and G: $R_{AG} = 5.6 \text{ k}\Omega + 5.6 \text{ k}\Omega + 1.0 \text{ k}\Omega + 1.0 \text{ k}\Omega = 13.2 \text{ k}\Omega$

Resistance between B and G: $R_{BG} = 5.6 \text{ k}\Omega + 1.0 \text{ k}\Omega + 1.0 \text{ k}\Omega = 7.6 \text{ k}\Omega$

Resistance between C and G: $R_{CG} = 1.0 \text{ k}\Omega + 1.0 \text{ k}\Omega = 2 \text{ k}\Omega$

$$V_{BG} = \left(\frac{R_{BG}}{R_{AG}} \right) 10 \text{ V} = \left(\frac{7.6 \text{ k}\Omega}{13.2 \text{ k}\Omega} \right) 10 \text{ V} = \mathbf{5.76 \text{ V}}$$

$$V_{CG} = \left(\frac{R_{CG}}{R_{AG}} \right) 10 \text{ V} = \left(\frac{2 \text{ k}\Omega}{13.2 \text{ k}\Omega} \right) 10 \text{ V} = \mathbf{1.52 \text{ V}}$$

$$V_{DG} = \left(\frac{R_{DG}}{R_{AG}} \right) 10 \text{ V} = \left(\frac{1.0 \text{ k}\Omega}{13.2 \text{ k}\Omega} \right) 10 \text{ V} = \mathbf{0.758 \text{ V}}$$

33. Measure the voltage at point A with respect to ground and the voltage at point B with respect to ground. The difference of these two voltages is V_{R2} .

$$V_{R2} = V_A - V_B$$

$$34. \quad R_T = R_1 + R_2 + R_3 + R_4 + R_5 \\ = 560 \text{ k}\Omega + 560 \text{ k}\Omega + 100 \text{ k}\Omega + 1.0 \text{ M}\Omega + 100 \text{ k}\Omega = 2.32 \text{ M}\Omega$$

$$V_T = 15 \text{ V}$$

$$V_A = \left(\frac{R_{AG}}{R_T} \right) V_T = \left(\frac{1.76 \text{ M}\Omega}{2.32 \text{ M}\Omega} \right) 15 \text{ V} = \mathbf{11.4 \text{ V}}$$

$$V_B = \left(\frac{R_{BG}}{R_T} \right) V_T = \left(\frac{1.2 \text{ M}\Omega}{2.32 \text{ M}\Omega} \right) 15 \text{ V} = \mathbf{7.76 \text{ V}}$$

$$V_C = \left(\frac{R_{CG}}{R_T} \right) V_T = \left(\frac{1.1 \text{ M}\Omega}{2.32 \text{ M}\Omega} \right) 15 \text{ V} = \mathbf{7.11 \text{ V}}$$

$$V_D = \left(\frac{R_{DG}}{R_T} \right) V_T = \left(\frac{100 \text{ k}\Omega}{2.32 \text{ M}\Omega} \right) 15 \text{ V} = \mathbf{647 \text{ mV}}$$

SECTION 4-10 Troubleshooting

35. (a) Zero current indicates an open. **R_4 is open** since all the voltage is dropped across it.

$$(b) \quad \frac{V_s}{R_1 + R_2 + R_3} = \frac{10 \text{ V}}{300 \Omega} = 33.3 \text{ mA}$$

R_4 and R_5 have no effect on the current. There is a **short from A to B**.

36. $R_T = 10 \text{ k}\Omega + 8.2 \text{ k}\Omega + 12 \text{ k}\Omega + 2.2 \text{ k}\Omega + 5.6 \text{ k}\Omega = 38 \text{ k}\Omega$
The meter reads about 28 k Ω . It should read 38 k Ω . **The 10 k Ω resistor is shorted.**

ADVANCED PROBLEMS

$$37. \quad V_1 = IR_1 = (10 \text{ mA})(680 \Omega) = 6.8 \text{ V} \\ V_2 = IR_2 = (10 \text{ mA})(1.0 \text{ k}\Omega) = 10 \text{ V} \\ V_4 = IR_4 = (10 \text{ mA})(270 \Omega) = 2.7 \text{ V} \\ V_5 = IR_5 = (10 \text{ mA})(270 \Omega) = 2.7 \text{ V} \\ V_3 = V_s - (V_1 + V_2 + V_4 + V_5) \\ V_3 = 30 \text{ V} - (6.8 \text{ V} + 10 \text{ V} + 2.7 \text{ V} + 2.7 \text{ V}) = 30 \text{ V} - 22.2 \text{ V} = 7.8 \text{ V} \\ R_3 = \frac{V_3}{I} = \frac{7.8 \text{ V}}{10 \text{ mA}} = 0.78 \text{ k}\Omega = \mathbf{780 \Omega}$$

38. $R_T = 3(5.6 \text{ k}\Omega) + 1.0 \text{ k}\Omega + 2(100 \Omega) = 18 \text{ k}\Omega$
Three 5.6 k Ω resistors, one 1 k Ω resistor, and two 100 Ω resistors

$$39. \quad V_A = \mathbf{10 \text{ V}}, \quad R_T = 22 \text{ k}\Omega + 10 \text{ k}\Omega + 47 \text{ k}\Omega + 12 \text{ k}\Omega + 5.6 \text{ k}\Omega = 96.6 \text{ k}\Omega \\ V_B = V_A - V_{22k} = 10 \text{ V} - \left(\frac{22 \text{ k}\Omega}{96.6 \text{ k}\Omega} \right) 10 \text{ V} = 10 \text{ V} - 2.28 \text{ V} = \mathbf{7.72 \text{ V}}$$

$$V_C = V_B - V_{10k} = 7.72 \text{ V} - \left(\frac{10 \text{ k}\Omega}{96.6 \text{ k}\Omega} \right) 10 \text{ V} = 7.72 \text{ V} - 1.04 \text{ V} = \mathbf{6.68 \text{ V}}$$

$$V_D = V_C - V_{47k} = 6.68 \text{ V} - \left(\frac{47 \text{ k}\Omega}{96.6 \text{ k}\Omega} \right) 10 \text{ V} = 6.68 \text{ V} - 4.87 \text{ V} = \mathbf{1.81 \text{ V}}$$

$$V_E = V_D - V_{12k} = 1.81 \text{ V} - \left(\frac{12 \text{ k}\Omega}{96.6 \text{ k}\Omega} \right) 10 \text{ V} = 1.81 \text{ V} - 1.24 \text{ V} = \mathbf{0.57 \text{ V}}$$

$$V_F = \mathbf{0 \text{ V}}$$

40. $V_2 = IR_2 = (20 \text{ mA})(100 \Omega) = \mathbf{2 \text{ V}}$

$$R_5 = \frac{V_S}{I} = \frac{6.6 \text{ V}}{20 \text{ mA}} = \mathbf{330 \Omega}$$

$$R_6 = \frac{P_6}{I^2} = \frac{112 \text{ mW}}{(20 \text{ mA})^2} = \mathbf{280 \Omega}$$

$$V_6 = IR_6 = (20 \text{ mA})(280 \Omega) = \mathbf{5.6 \text{ V}}$$

$$V_1 = V_S - (20 \text{ V} + V_6) = 30 \text{ V} - (20 \text{ V} + 5.6 \text{ V}) = \mathbf{4.4 \text{ V}}$$

$$R_1 = \frac{V_1}{I} = \frac{4.4 \text{ V}}{20 \text{ mA}} = \mathbf{220 \Omega}$$

$$V_3 + V_4 = 20 \text{ V} - V_2 - V_5 = 20 \text{ V} - 2 \text{ V} - 6.6 \text{ V} = 11.4 \text{ V}$$

$$V_3 = V_4 = \frac{11.4 \text{ V}}{2} = \mathbf{5.7 \text{ V}} \quad R_3 = R_4 = \frac{V_3}{I} = \frac{5.7 \text{ V}}{20 \text{ mA}} = \mathbf{285 \Omega}$$

41. $V_S = IR_T = (250 \text{ mA})(1.5 \text{ k}\Omega) = 375 \text{ V}$

$$I_{\text{new}} = 250 \text{ mA} - 0.25(250 \text{ mA}) = 250 \text{ mA} - 62.5 \text{ mA} = 188 \text{ mA}$$

$$R_{\text{new}} = \frac{V_S}{I_{\text{new}}} = \frac{375 \text{ V}}{188 \text{ mA}} \cong 2000 \Omega$$

500 Ω must be added to the existing 1500 Ω to reduce I by 25%.

42. $P = I^2 R$

$$I_{\text{max}} = \sqrt{\frac{P}{R}} = \sqrt{\frac{0.5 \text{ W}}{120 \Omega}} = 0.0645 \text{ A} = 64.5 \text{ mA}$$

Since all resistors in series have the same current, use the largest R to determine the maximum current allowable because the largest R has the greatest power.

Thus, the **120 Ω resistor burns out first.**

43. (a) $P_T = \frac{1}{8} \text{ W} + \frac{1}{4} \text{ W} + \frac{1}{2} \text{ W} = 0.125 \text{ W} + 0.25 \text{ W} + 0.5 \text{ W} = 0.875 \text{ W}$

$$I = \sqrt{\frac{P_T}{R_T}} = \sqrt{\frac{0.875 \text{ W}}{2400 \Omega}} = \mathbf{19.1 \text{ mA}}$$

(b) $V_S = I_T R_T = (19.1 \text{ mA})(2400 \Omega) = \mathbf{45.8 \text{ V}}$



(c) $R = \frac{P}{I^2}$

$$R_{1/8} = \frac{P}{I^2} = \frac{0.125 \text{ W}}{(19.1 \text{ mA})^2} = \mathbf{343 \Omega}$$

$$R_{1/4} = \frac{0.25 \text{ W}}{(19.1 \text{ mA})^2} = \mathbf{686 \Omega}$$

$$R_{1/2} = \frac{0.5 \text{ W}}{(19.1 \text{ mA})^2} = \mathbf{1371 \Omega}$$

44. See Figure 4-6.

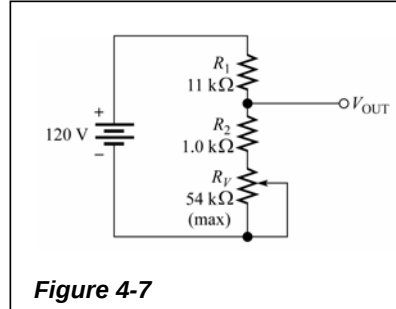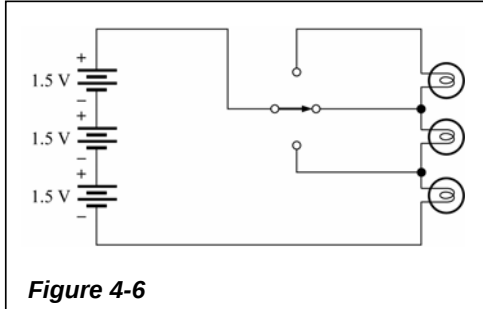

45. See Figure 4-7.

When the potentiometer is at minimum setting (0Ω), $V_{\text{OUT}} = 10 \text{ V}$:

$$R_1 + R_2 = \frac{120 \text{ V}}{10 \text{ mA}} = 12 \text{ k}\Omega$$

$$\left(\frac{R_2}{R_1 + R_2} \right) 120 \text{ V} = 10 \text{ V}$$

$$R_2 = \frac{10 \text{ V}(12 \text{ k}\Omega)}{120 \text{ V}} = \mathbf{1.0 \text{ k}\Omega}$$

$$R_1 = 12 \text{ k}\Omega - 1.0 \text{ k}\Omega = \mathbf{11 \text{ k}\Omega}$$

When the potentiometer is at maximum setting, $V_{\text{OUT}} = 100 \text{ V}$:

$$\left(\frac{R_2 + R_V}{R_1 + R_2 + R_V} \right) 120 \text{ V} = 100 \text{ V}$$

$$\left(\frac{1.0 \text{ k}\Omega + R_V}{12 \text{ k}\Omega + R_V} \right) 120 \text{ V} = 100 \text{ V}$$

$$(1.0 \text{ k}\Omega + R_V)120 \text{ V} = (12 \text{ k}\Omega + R_V)100 \text{ V}$$

$$120 \text{ k}\Omega + 120R_V = 1200 \text{ k}\Omega + 100R_V$$

$$20R_V = 1080 \text{ k}\Omega$$

$$R_V = \mathbf{54 \text{ k}\Omega}$$

46. See Figure 4-8.

$$R_1 = \frac{(30 \text{ V} - 24.6 \text{ V})}{1 \text{ mA}} = 5.4 \text{ k}\Omega$$

$$R_2 = \frac{(24.6 \text{ V} - 14.7 \text{ V})}{1 \text{ mA}} = 9.9 \text{ k}\Omega$$

$$R_3 = \frac{(14.7 \text{ V} - 8.18 \text{ V})}{1 \text{ mA}} = 6.52 \text{ k}\Omega$$

$$R_4 = \frac{8.18 \text{ V}}{1 \text{ mA}} = 8.18 \text{ k}\Omega$$

A series of standard value resistors must be used to approximately achieve each resistance as follows:

$$R_1 = 4700 \Omega + 680 \Omega + 22 \Omega = 5.4 \text{ k}\Omega$$

$$R_2 = 8200 \Omega + 1500 \Omega + 220 \Omega = 9.92 \text{ k}\Omega$$


$$R_3 = 5600 \Omega + 820 \Omega + 100 \Omega = 6.52 \text{ k}\Omega$$

$$R_4 = 6800 \Omega + 1000 \Omega + 180 \Omega + 100 \Omega + 100 \Omega = 8.18 \text{ k}\Omega$$

The highest power dissipation is in the 8200 Ω resistor.

$$P = (1 \text{ mA})^2 8200 \Omega = 8.2 \text{ mW}$$

All resistors must be at least 1/8 W.

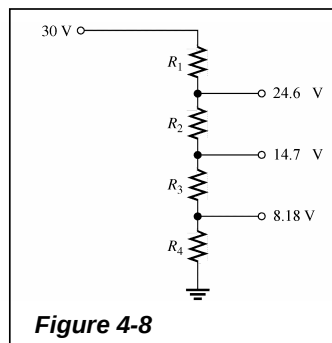

47. The groups are:


$R_1, R_7, R_8, \text{ and } R_{10}; \quad R_2, R_4, R_6, \text{ and } R_{11}; \quad R_3, R_5, R_9, \text{ and } R_{12}$

See Figure 4-9.

$$R_1 + R_7 + R_8 + R_{10} = 2.2 \text{ k}\Omega + 560 \Omega + 470 \Omega + 1.0 \text{ k}\Omega = 4.23 \text{ k}\Omega$$

$$R_2 + R_4 + R_6 + R_{11} = 4.7 \text{ k}\Omega + 5.6 \text{ k}\Omega + 3.3 \text{ k}\Omega + 10 \text{ k}\Omega = 23.6 \text{ k}\Omega$$
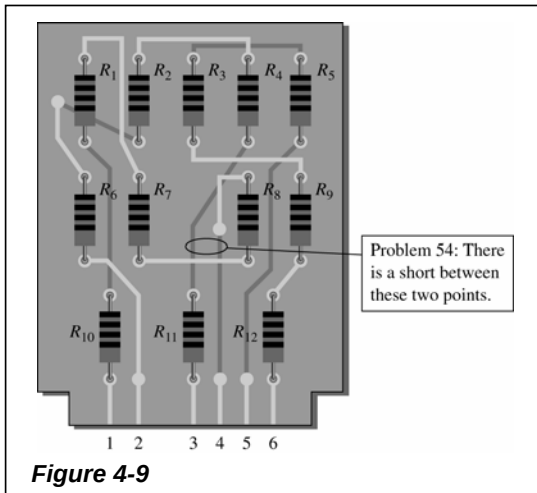
$$R_3 + R_5 + R_9 + R_{12} = 1.0 \text{ k}\Omega + 3.9 \text{ k}\Omega + 8.2 \text{ k}\Omega + 6.8 \text{ k}\Omega = 19.9 \text{ k}\Omega$$



48. *Position 1:*
 $R_T = R_1 + R_3 + R_5 = 510\ \Omega + 820\ \Omega + 680\ \Omega = \mathbf{2.01\ k\Omega}$
- Position 2:*
 $R_T = R_1 + R_2 + R_3 + R_4 + R_5$
 $= 510\ \Omega + 910\ \Omega + 820\ \Omega + 750\ \Omega + 680\ \Omega = \mathbf{3.67\ k\Omega}$
49. *Position A:*
 $R_T = R_1 + R_2 + R_3 + R_4 = 220\ \Omega + 470\ \Omega + 510\ \Omega + 1.0\ k\Omega = 2.2\ k\Omega$
 $I = \frac{V}{R_T} = \frac{12\ V}{2.2\ k\Omega} = \mathbf{5.45\ mA}$
- Position B:*
 $R_T = R_2 + R_3 + R_4 = 470\ \Omega + 510\ \Omega + 1.0\ k\Omega = 1.98\ k\Omega$
 $I = \frac{V}{R_T} = \frac{12\ V}{1.98\ k\Omega} = \mathbf{6.06\ mA}$
- Position C:*
 $R_T = R_3 + R_4 = 510\ \Omega + 1.0\ k\Omega = 1.51\ k\Omega$
 $I = \frac{V}{R_T} = \frac{12\ V}{1.51\ k\Omega} = \mathbf{7.95\ mA}$
- Position D:*
 $R_T = R_4 = 1.0\ k\Omega$
 $I = \frac{V}{R_T} = \frac{12\ V}{1.0\ k\Omega} = \mathbf{12\ mA}$
50. *Position A:*
 $R_T = R_1 = 1.0\ k\Omega$
 $I = \frac{V}{R_T} = \frac{9\ V}{1.0\ k\Omega} = \mathbf{9\ mA}$

Position B:

$$R_T = R_1 + R_2 + R_5 = 1.0 \text{ k}\Omega + 33 \text{ k}\Omega + 22 \text{ k}\Omega = 56 \text{ k}\Omega$$

$$I = \frac{V}{R_T} = \frac{9 \text{ V}}{56 \text{ k}\Omega} = \mathbf{161 \text{ }\mu\text{A}}$$

Position C:

$$R_T = R_1 + R_2 + R_3 + R_4 + R_5 = 1.0 \text{ k}\Omega + 33 \text{ k}\Omega + 68 \text{ k}\Omega + 27 \text{ k}\Omega + 22 \text{ k}\Omega = 151 \text{ k}\Omega$$

$$I = \frac{V}{R_T} = \frac{9 \text{ V}}{151 \text{ k}\Omega} = \mathbf{59.6 \text{ }\mu\text{A}}$$

51. First, find the value of R_5 with the switch in Position *D*.

$$6 \text{ mA} = \frac{18 \text{ V}}{R_5 + 1.8 \text{ k}\Omega}$$

$$R_5 = \frac{18 \text{ V}}{6 \text{ mA}} - 1.8 \text{ k}\Omega = 1.2 \text{ k}\Omega$$

Position A:

$$R_T = 5.38 \text{ k}\Omega \quad I = 18 \text{ V} / 5.38 \text{ k}\Omega = 3.35 \text{ mA}$$

$$V_1 = (3.35 \text{ mA})(1.8 \text{ k}\Omega) = \mathbf{6.03 \text{ V}}$$

$$V_2 = (3.35 \text{ mA})(1.0 \text{ k}\Omega) = \mathbf{3.35 \text{ V}}$$

$$V_3 = (3.35 \text{ mA})(820 \text{ }\Omega) = \mathbf{2.75 \text{ V}}$$

$$V_4 = (3.35 \text{ mA})(560 \text{ }\Omega) = \mathbf{1.88 \text{ V}}$$

$$V_5 = \mathbf{4 \text{ V}}$$

Position B:

$$R_T = 4.82 \text{ k}\Omega \quad I = 18 \text{ V} / 4.82 \text{ k}\Omega = 3.73 \text{ mA}$$

$$V_1 = (3.73 \text{ mA})(1.8 \text{ k}\Omega) = \mathbf{6.71 \text{ V}}$$

$$V_2 = (3.73 \text{ mA})(1.0 \text{ k}\Omega) = \mathbf{3.73 \text{ V}}$$

$$V_3 = (3.73 \text{ mA})(820 \text{ }\Omega) = \mathbf{3.06 \text{ V}}$$

$$V_5 = \mathbf{4.5 \text{ V}}$$

Position C:

$$R_T = 4 \text{ k}\Omega \quad I = 18 \text{ V} / 4 \text{ k}\Omega = 4.5 \text{ mA}$$

$$V_1 = (4.5 \text{ mA})(1.8 \text{ k}\Omega) = \mathbf{8.1 \text{ V}}$$

$$V_2 = (4.5 \text{ mA})(1.0 \text{ k}\Omega) = \mathbf{4.5 \text{ V}}$$

$$V_5 = \mathbf{5.4 \text{ V}}$$

Position D:

$$R_T = 3 \text{ k}\Omega \quad I = 18 \text{ V} / 3 \text{ k}\Omega = 6 \text{ mA}$$

$$V_1 = (6 \text{ mA})(1.8 \text{ k}\Omega) = \mathbf{10.8 \text{ V}}$$

$$V_5 = \mathbf{7.2 \text{ V}}$$

Note: The voltage approach can also be used.

52. See Figure 4-9. The results in the table are correct.
53. Yes, R_3 and R_5 are each shorted. Refer to Figure 4-9.
54. Yes, there is a short between the points indicated in Figure 4-9.

55. (a) R_{11} burned open due to excessive power because it had the largest value in ohms.
(b) Replace R_{11} (10 k Ω).
(c) $R_T = 47.7 \text{ k}\Omega$

$$I_{\max} = \sqrt{\frac{P_{11}}{R_{11}}} = \sqrt{\frac{0.5 \text{ W}}{10 \text{ k}\Omega}} = 7.07 \text{ mA}$$

$$V_{\text{TOTAL}} = I_{\max} R_T = (7.07 \text{ mA})(47.7 \text{ k}\Omega) = 338 \text{ V}$$

Multisim Troubleshooting Problems



56. R_1 is open.
57. R_6 is shorted.
58. R_2 is open.
59. Lamp 4 is open.
60. No fault
61. The 82 Ω resistor is shorted.

CHAPTER 5 PARALLEL CIRCUITS

BASIC PROBLEMS

SECTION 5-1 Resistors in Parallel

- See Figure 5-1.
- See Figure 5-2.

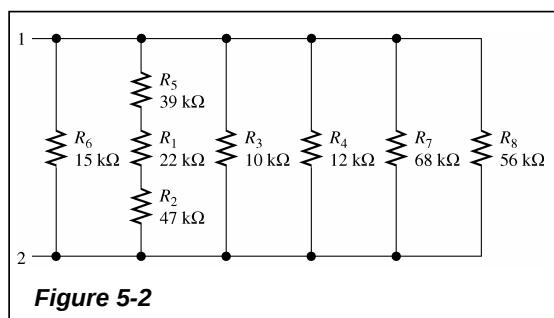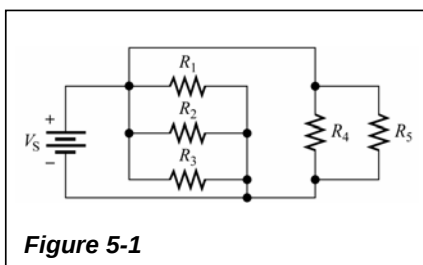

SECTION 5-2 Total Parallel Resistance

- From Problem 2: $R_T = R_6 \parallel R_3 \parallel R_4 \parallel R_7 \parallel R_8 \parallel (R_1 + R_2 + R_5)$
 $= 15 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 12 \text{ k}\Omega \parallel 68 \text{ k}\Omega \parallel 56 \text{ k}\Omega \parallel 108 \text{ k}\Omega = 3.43 \text{ k}\Omega$
- $R_T = \frac{1}{\frac{1}{1.0 \text{ M}\Omega} + \frac{1}{2.2 \text{ M}\Omega} + \frac{1}{4.7 \text{ M}\Omega} + \frac{1}{12 \text{ M}\Omega} + \frac{1}{22 \text{ M}\Omega}} = 557 \text{ k}\Omega$
- $R = 47 \text{ }\Omega \parallel 6 \text{ k}\Omega = 25.6 \text{ }\Omega$
 - $R = 560 \text{ }\Omega \parallel 1.0 \text{ k}\Omega = 359 \text{ }\Omega$
 - $R = 1.5 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 819 \text{ }\Omega$
 - $R = 1.0 \text{ k}\Omega \parallel 2.2 \text{ M}\Omega \parallel 1.0 \text{ M}\Omega \parallel 470 \text{ k}\Omega = 996 \text{ }\Omega$

$$6. \quad (a) \quad R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(4.7 \text{ k}\Omega)(2.2 \text{ k}\Omega)}{4.7 \text{ k}\Omega + 2.2 \text{ k}\Omega} = \mathbf{1.5 \text{ k}\Omega}$$

$$(b) \quad R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(27 \text{ }\Omega)(56 \text{ }\Omega)}{27 \text{ }\Omega + 56 \text{ }\Omega} = \mathbf{18.2 \text{ }\Omega}$$

$$(c) \quad R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(1.5 \text{ k}\Omega)(2.2 \text{ k}\Omega)}{1.5 \text{ k}\Omega + 2.2 \text{ k}\Omega} = \mathbf{892 \text{ }\Omega}$$

$$7. \quad R_T = \frac{22 \text{ k}\Omega}{11} = \mathbf{2 \text{ k}\Omega}$$

$$8. \quad R_{T1} = \frac{15 \text{ }\Omega}{5} = 3 \text{ }\Omega$$

$$R_{T2} = \frac{100 \text{ }\Omega}{10} = 10 \text{ }\Omega$$

$$R_{T3} = \frac{10 \text{ }\Omega}{2} = 5 \text{ }\Omega$$

$$R_T = \frac{1}{\frac{1}{3 \text{ }\Omega} + \frac{1}{10 \text{ }\Omega} + \frac{1}{5 \text{ }\Omega}} = \mathbf{1.58 \text{ }\Omega}$$

SECTION 5-3 Voltage in a Parallel Circuit

$$9. \quad V_1 = V_2 = V_3 = V_4 = \mathbf{12 \text{ V}}$$

$$I_T = \frac{V_T}{R_T} = \frac{12 \text{ V}}{600 \text{ }\Omega} = 20 \text{ mA}$$

The total current divides equally among the four equal resistors.

$$I_1 = I_2 = I_3 = I_4 = \frac{20 \text{ mA}}{4} = \mathbf{5 \text{ mA}}$$

10. The resistors are all in parallel across the source. The voltmeters are each measuring the voltage across a resistor, so each meter indicates **100 V**.

SECTION 5-4 Application of Ohm's Law

$$11. \quad (a) \quad R_T = 33 \text{ k}\Omega \parallel 33 \text{ k}\Omega \parallel 33 \text{ k}\Omega = 11 \text{ k}\Omega$$

$$I_T = \frac{10 \text{ V}}{11 \text{ k}\Omega} = \mathbf{909 \text{ }\mu\text{A}}$$

$$(b) \quad R_T = 1.0 \text{ k}\Omega \parallel 3.9 \text{ k}\Omega \parallel 560 \text{ }\Omega = 329 \text{ }\Omega$$

$$I_T = \frac{25 \text{ V}}{329 \text{ }\Omega} = \mathbf{76 \text{ mA}}$$

$$12. \quad R_T = \frac{33 \text{ }\Omega}{3} = 11 \text{ }\Omega$$

$$I_T = \frac{110 \text{ V}}{11 \text{ }\Omega} = \mathbf{10 \text{ A}}$$

$$13. \quad (a) \quad R_T = 56 \text{ k}\Omega \parallel 22 \text{ k}\Omega = 15.8 \text{ k}\Omega$$

$$I_T = \frac{10 \text{ V}}{15.8 \text{ k}\Omega} = 633 \text{ }\mu\text{A}$$

$$(b) \quad R_T = 18 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 15.3 \text{ k}\Omega$$

$$I_T = \frac{8 \text{ V}}{15.3 \text{ k}\Omega} = 523 \text{ }\mu\text{A}$$

Circuit (a) has more current than circuit (b).

$$14. \quad R_T = \frac{V_S}{I_T} = \frac{5 \text{ V}}{2.5 \text{ mA}} = 2 \text{ k}\Omega$$

$$R_{\text{each}} = 4(2 \text{ k}\Omega) = \mathbf{8 \text{ k}\Omega}$$

SECTION 5-5 Kirchhoff's Current Law

$$15. \quad I_T = 250 \text{ mA} + 300 \text{ mA} + 800 \text{ mA} = \mathbf{1350 \text{ mA}}$$

$$16. \quad I_T = I_1 + I_2 + I_3 + I_4 + I_5$$

$$I_5 = I_T - (I_1 + I_2 + I_3 + I_4)$$

$$I_5 = 500 \text{ mA} - (50 \text{ mA} + 150 \text{ mA} + 25 \text{ mA} + 100 \text{ mA}) = 500 \text{ mA} - 325 \text{ mA} = \mathbf{175 \text{ mA}}$$

$$17. \quad I_{2-3} = I_T - (I_1 + I_4) = 50 \text{ mA} - 35 \text{ mA} = 15 \text{ mA}$$

$$I_2 = I_3 = \mathbf{7.5 \text{ mA}}$$

See Figure 5-3.

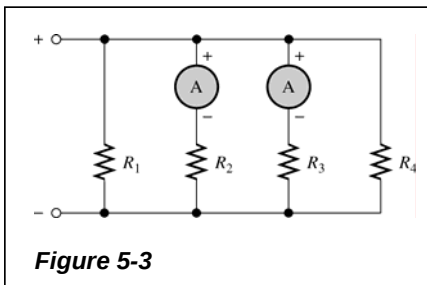


Figure 5-3