

- 1.1 If the current in an electric conductor is 2.4 A, how many coulombs of charge pass any point in a 30-second interval?
-

SOLUTION:

$$I = 2.4 \text{ A}, \Delta t = 30 \text{ s}$$

$$Q = I \Delta t$$

$$Q = 2.4 (30)$$

$$Q = 72 \text{ C}$$

- 1.2 In charging a storage battery it is found that energy of 1 watt-hr is expended in 15 minutes in sending 150 coulombs through the battery. What is the voltage between the battery terminals? What is the magnitude of the average charging current?
-

SOLUTION:

$$\begin{aligned} I &= \frac{Q}{t} \\ &= 150\text{C}/15 \times 60\text{s} \\ &= 1/6\text{A} \\ P &= VI \\ 1\text{Whr}/15\text{min} &= V \times 1/6 \\ V &= 24\text{V} \end{aligned}$$

- 1.3 A lightning bolt carrying 30,000 A lasts for 50 micro-seconds.
If the lightning strikes an airplane flying at 20,000 feet, what is the charge deposited on the plane?
-

SOLUTION:

$$I = 30,000 \text{ A}, \Delta t = 50 \mu\text{s}$$

$$Q = I \Delta t$$

$$Q = 30,000 (50 \mu)$$

$$Q = 1.5 \text{ C}$$

- 1.4 If a 12-V battery delivers 100 J in 5 s, find (a) the amount of charge delivered and (b) the current produced.
-

SOLUTION:

$$V = 12\text{ V}, \Delta W = 100\text{ J in } 5\text{ s}$$

$$\text{a) } \Delta Q = \frac{\Delta W}{V} = \frac{100}{12}$$

$$\Delta Q = 8.33\text{ C}$$

$$\text{b) } I = \frac{\Delta Q}{\Delta t} = \frac{8.33}{5}$$

$$I = 1.67\text{ A}$$

- 1.5 The charge entering the positive terminal is given by $q(t) = -10e^{-t}$ mC. The power delivered to the element is $p(t) = 2e^{-2t}$ mW. Calculate the current in the element, voltage across the element and the energy delivered to the element in the interval $0 < t < 100$ ms.

SOLUTION:

$$I = \frac{dq}{dt}$$
$$= 10e^{-t} \text{ mA}$$

Now, $P = VI$

Thus $V = 0.2e^{-t}$ V is the voltage across the element.

$$E = \int p(t) dt$$
$$= \int_0^{0.2} 2e^{-t} dt$$
$$= 0.362 \text{ mJ}$$

1.6 The current at a given point in a certain circuit may be written as $i(t) = -3 + t$ A. Find the total charge passing the point between $t = 99$ and $t = 102$ s.

SOLUTION:

$$\begin{aligned}\text{The charge passing through the circuit is } q &= \int_{99}^{102} i(t) dt \\ &= \int_{99}^{102} (-3 + t) dt \\ &= \left(-3 \times 102 + \frac{102^2}{2} \right) - \left(-3 \times 99 + \frac{99^2}{2} \right) \\ &= 292.5 \text{ C}\end{aligned}$$

- 1.7 Five coulombs of charge pass through the element in Fig. P1.7 from point A to point B . If the energy absorbed by the element is 150 J, determine the voltage across the element.


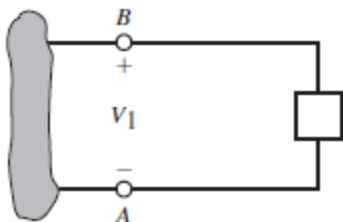


Figure P1.7

SOLUTION:

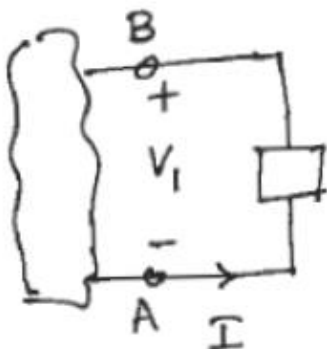

$$Q = 5 \text{ C}$$
$$W = 150 \text{ J}$$

For passive sign convention: $W = -V_1 Q$

$$V_1 = -\frac{W}{Q}$$

$$\boxed{V_1 = -30 \text{ V}}$$

- 1.8 The current that enters an element is shown in Fig. P1.8.
Find the charge that enters the element in the time interval
 $0 < t < 20$ s.

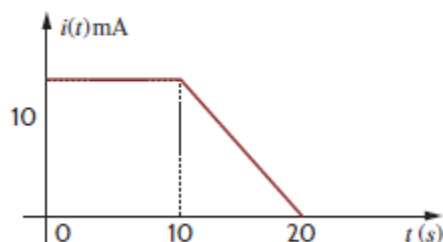


Figure P1.8

SOLUTION:

$$i(t) = m_1 t + b$$

$$m_1 = \frac{10 - 10}{10 - 20} = -1$$

$$i(t) = -t + b$$

$$10 = -10 + b$$

$$b = 20$$

$$i(t) = -t + 20 \text{ mA}$$

$$q(t) = \int_0^{20} i(t) dt$$

$$q(t) = \int_0^{10} 10 \times 10^{-3} dt + \int_{10}^{20} \frac{20-t}{1000} dt$$

$$q(t) = 10 \times 10^{-3} t \Big|_0^{10} + \frac{1}{1000} \left[20t - \frac{t^2}{2} \right]_{10}^{20}$$

$$q(t) = 0.1 + \frac{1}{1000} \left[20(20) - \frac{(20)^2}{2} - 20(10) + \frac{(10)^2}{2} \right]$$

$$q(t) = 0.1 + \frac{1}{1000} [200 - 200 + 50]$$

$$q(t) = 0.15 \text{ C}$$

- 1.9 The charge entering the positive terminal of an element is $q(t) = -30e^{-4t}$ mC. If the voltage across the element is $120e^{-2t}$ V, determine the energy delivered to the element in the time interval $0 < t < 50$ ms.

SOLUTION:

$$q(t) = 30e^{-4t} \text{ mC}$$

$$v(t) = 120e^{-2t} \text{ V}$$

$$W = \int_{t_1}^{t_2} P \, dt = \int_{t_1}^{t_2} v i \, dt$$

$$i(t) = \frac{dq(t)}{dt} = -4(-30)e^{-4t} \text{ mA}$$

$$i(t) = 120e^{-4t} \text{ mA}$$

$$W = \int_{t_1}^{t_2} (120e^{-2t})(120e^{-4t} \text{ m}) \, dt$$

$$W = 14.4 \int_0^{50 \text{ m}} e^{-6t} \, dt$$

$$W = 14.4 \left[\frac{e^{-6t}}{-6} \right]_0^{50 \text{ m}}$$

$$W = 14.4 \left[\frac{e^{-6(50 \text{ m})}}{-6} + \frac{e^{-6(0)}}{6} \right]$$

$$W = 622.04 \text{ mJ}$$

1.10 The charge entering the positive terminal of an element is given by the expression $q(t) = -12e^{-2t}$ mC. The power delivered to the element is $p(t) = 2.4e^{-3t}$ W. Compute the current in the element, the voltage across the element, and the energy delivered to the element in the time interval $0 < t < 100$ ms.

SOLUTION:

$$q(t) = -12 e^{-2t} \text{ mC}$$

$$p(t) = 2.4 e^{-3t} \text{ W}$$

$$i(t) = \frac{dq(t)}{dt}$$

$$i(t) = 2(-12)e^{-2t} \text{ m}$$

$$i(t) = 24 e^{-2t} \text{ mA}$$

$$W = \int_{t_1}^{t_2} p(t) dt = \int_0^{100\text{m}} 2.4 e^{-3t} dt$$

$$W = \left[\frac{2.4}{-3} e^{-3t} \right]_0^{100\text{m}}$$

$$W = \frac{2.4}{-3} \left[e^{-3(100\text{m})} - e^{-3(0)} \right]$$

$$W = 207.35 \text{ mJ}$$

$$v(t) = \frac{p(t)}{i(t)}$$

$$v(t) = \frac{2.4 e^{-3t}}{24 e^{-2t} \text{ m}}$$

$$v(t) = 100 e^{-t} \text{ V}$$

1.11 The charge entering the positive terminal of an element is $q(t) = -10e^{-2t}$ mC. If the voltage across the element is

$120e^{-2t}$ V. Determine the energy delivered to the element in the time interval $0 < t < 20$ ms.

SOLUTION:

$$I = \frac{dq}{dt}$$

$$I = 20e^{-2t} \text{ mA}$$

$$\text{Now } E = \int V I dt$$

$$= \int_0^{20} 2.4e^{-4t} dt$$

$$= 0.011 \text{ J}$$

- 1.12 The power absorbed by the BOX in Fig. P1.12 is $2e^{-2t}$ W.
Calculate the amount of charge that enters the BOX between 0.1 and 0.4 seconds.


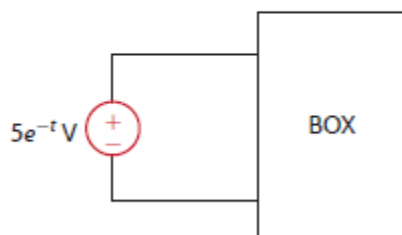


Figure P1.12

SOLUTION:

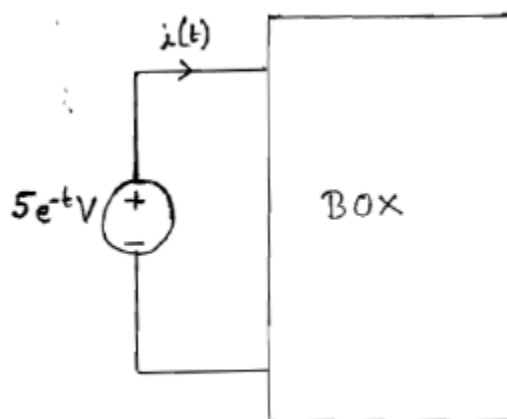

$$p = vi$$

$$2e^{-2t} = 5e^{-t}i$$

$$i = \frac{2e^{-2t}}{5e^{-t}} = 0.4e^{-t} \text{ A}$$

$$\begin{aligned}\Delta q(t) &= \int_{0.1}^{0.4} i(t) dt \\&= \int_{0.1}^{0.4} 0.4 e^{-t} dt \\&= -0.4 e^{-t} \Big|_{0.1}^{0.4} = -0.4 [e^{-0.4} - e^{-0.1}] \\&= 0.0938 \text{ C}\end{aligned}$$

1.13 The charge flowing through a point in a circuit is given as a function of time as $q(t) = -t^3 + 6t^2 - 10t$, find $i(t)$ at $t = 5s$.

SOLUTION:

$$\begin{aligned} i(t) &= \frac{dq}{dt} \\ &= -3t^2 + 12t - 10 \\ &= -3 \times 5^2 + 12 \times 5 - 10 \\ &= -25A \end{aligned}$$

1.14 The current in a circuit $i(t)$ is given as e^{4t} A for $t < 0$ and e^{-4t} A for $t > 0$. Find:

- (a) $i(0.25)$
 - (b) Average value of current over the interval $-0.25 < t < 0.25$
 - (c) The total charge that has passed during this interval
-

SOLUTION:

a. $i(0.25) = e^{-4 \times 0.25} = 0.368$ A

b. Average value of current $= \int_{-0.25}^{0.25} i(t) dt$
 $= 0.632$ A

c. Charge passed $= \text{Average current} \times \text{Time}$
 $= 0.318$ A

- 1.15 The charge that enters the BOX is shown in Fig. P1.15. Calculate and sketch the current flowing into and the power absorbed by the BOX between 0 and 9 milliseconds. Also calculate the energy absorbed by the BOX between 0 and 9 milliseconds.

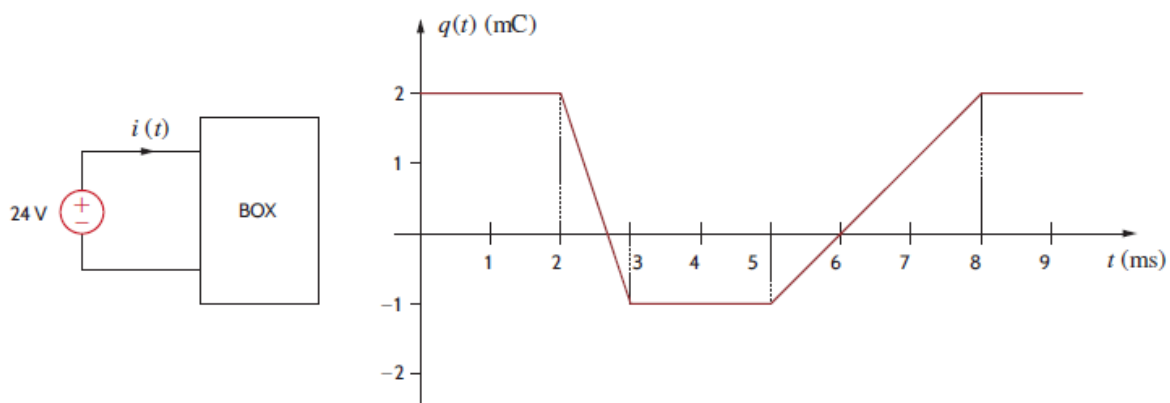


Figure P1.15

SOLUTION:

$$i(t) = \frac{dq(t)}{dt}$$

$$q(t) = 2, \quad 0 \leq t \leq 2 \text{ ms}$$

$$m = \frac{-1 - 2}{3 - 2} = \frac{-3}{1} = -3$$

$$q(t) = m(t) + b$$

$$q(t) = -3t + b$$

$$2 = -3(2) + b$$

$$b = 8$$

$$q(t) = -3t + 8, \quad 2 \text{ ms} \leq t \leq 3 \text{ ms}$$

$$q(t) = -1, \quad 3 \text{ ms} \leq t \leq 5 \text{ ms}$$

$$q(t) = mt + b$$

$$m = \frac{2 - (-1)}{8 - 5} = 1$$


$$q(t) = t + b$$

$$2 = 8 + b$$

$$b = -6$$

$$q(t) = t - 6, \quad 5\text{ms} \leq t \leq 8\text{ms}$$
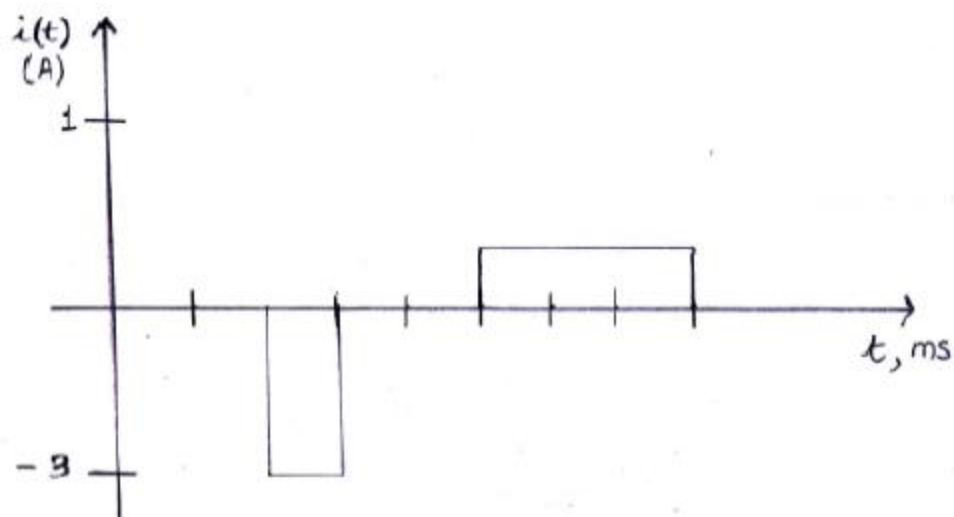
$$q(t) = 2, \quad 8\text{ms} \leq t \leq 9\text{ms}$$



$$i(t) = \begin{cases} 0, & 0 \leq t \leq 2\text{ms} \\ -3, & 2\text{ms} \leq t \leq 3\text{ms} \\ 0, & 3\text{ms} \leq t \leq 5\text{ms} \\ 1, & 5\text{ms} \leq t \leq 8\text{ms} \end{cases}$$

$$p(t) = v(t) i(t)$$

$$p(t) = \begin{cases} 0\text{ W}, & 0 \leq t \leq 2\text{ms} \\ -72\text{ W}, & 2\text{ms} \leq t \leq 3\text{ms} \\ 0\text{ W}, & 3\text{ms} \leq t \leq 5\text{ms} \\ 24\text{ W}, & 5\text{ms} \leq t \leq 8\text{ms} \end{cases}$$

$$W(t) = \int_0^t p(t) dt$$

$$= 0 + (-72) \times 1 + 0 + 24 \times 3 = 0\text{ J}$$

- 1.16 The energy absorbed by the BOX in Fig. P1.16 is given below. Calculate and sketch the current flowing into the BOX. Also calculate the charge which enters the BOX between 0 and 12 seconds.

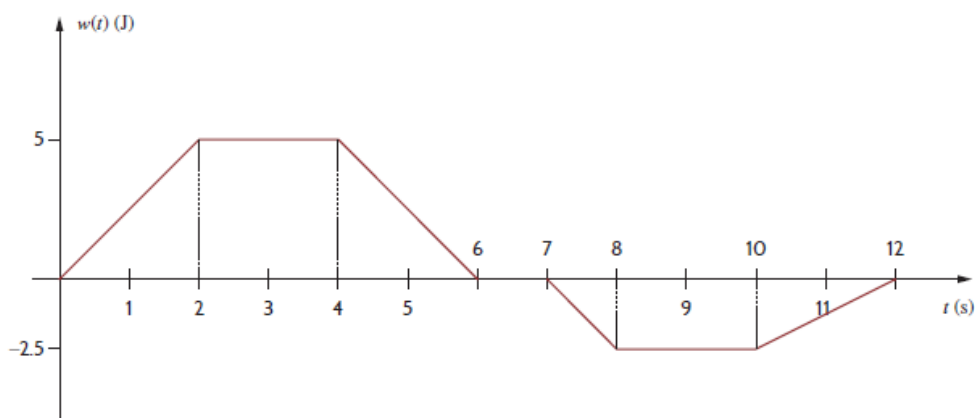
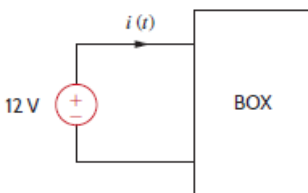


Figure P1.16

SOLUTION:

$$P = \frac{dW}{dt} \text{ (slope of the curve)}$$

$$P = Vi \Rightarrow i = \frac{P}{V} = \frac{P}{12}$$

$$\underline{0 \leq t \leq 2 \text{ s} :}$$

$$P = \frac{5 - 0}{2 - 0} = 2.5 \text{ W}, \quad i = \frac{2.5}{12} = 0.21 \text{ A}$$

$$\underline{2 \leq t \leq 4 \text{ s} :}$$

$$P = \frac{5-5}{4-2} = 0, \quad i = 0$$

$$\underline{4 \leq t \leq 6 \text{ s} :}$$

$$P = \frac{0-5}{6-4} = -2.5 \text{ W}, \quad i = \frac{-2.5}{12} = -0.21 \text{ A}$$

$$\underline{6 \leq t \leq 7 \text{ s} :}$$

$$P = \frac{0-0}{7-6} = 0, \quad i = 0$$

$$\underline{7 \leq t \leq 8 \text{ s} :}$$

$$P = \frac{-2.5-0}{8-7} = -2.5 \text{ W}, \quad i = \frac{-2.5}{12} = -0.21 \text{ A}$$

$$\underline{8 \leq t \leq 10 \text{ s} :}$$


$$P = \frac{-2.5 - (-2.5)}{10-8} = 0, \quad i = 0$$

$$10 \leq t \leq 12 \text{ s} :$$

$$P = \frac{0 - (-2.5)}{12 - 10} = 1.25 \text{ W}, \quad i = \frac{1.25}{12} = 0.104 \text{ A}$$

$$t > 12 \text{ s} :$$

$$P = 0, \quad i = 0$$

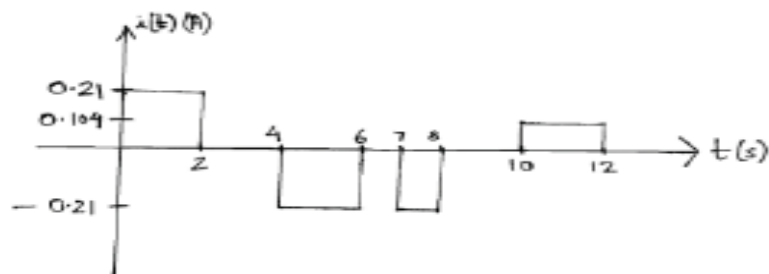


$$q = \int i \, dt$$

$$= (0.21)(2) + (-0.21)(2) + (-0.21)(1) + (0.104)(2)$$

$$= -0.002 \text{ C}$$

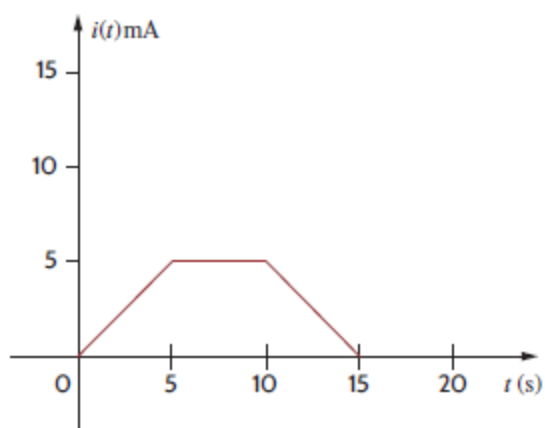- 1.17 The plot of current entering an element is shown in the figure.
Find the charge that enters the element from 5 to 15 seconds.



SOLUTION:

The charge through the element can be found by finding the area under the curve from 5 to 15 seconds.

$$\begin{aligned}\text{Thus charge flown} &= 5 \times (10-5) + \frac{1}{2} \times 5 \times (15-10) \\ &= 37.5 \text{ mC}\end{aligned}$$

1.18 Determine the amount of power absorbed or supplied by the element in Fig. P1.18 if

- (a) $V_1 = 5 \text{ V}$ and $I = 6 \text{ A}$
- (b) $V_1 = 5 \text{ V}$ and $I = -7 \text{ A}$
- (c) $V_1 = -14 \text{ V}$ and $I = 6 \text{ A}$
- (d) $V_1 = -14 \text{ V}$ and $I = -7 \text{ A}$

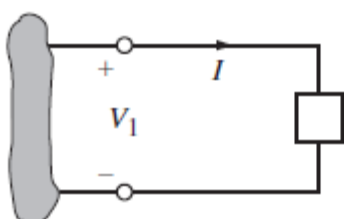


Figure P1.18

SOLUTION:


$$V_1 = 5 \text{ V}, I = 6 \text{ A}$$

For passive sign convention,

$P = V_1 I$ is power absorbed.

$$P = V_1 I = 5(6) = 30 \text{ W absorbed}$$

$$P = 30 \text{ W absorbed}$$

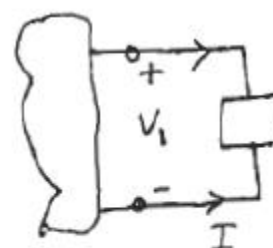

$$\text{b) } V_1 = 5 \text{ V}, I = -7 \text{ A}$$

$$P = 5(-7) = -35 \text{ W}$$

$$P = 35 \text{ W supplied}$$

$$\text{c) } V_1 = -14 \text{ V}, I = 6 \text{ A}$$

$$P = -84 \text{ W}$$

$$P = 84 \text{ W supplied}$$

$$d) \quad V_1 = -14V, \quad I = -7A$$

$$P = 98W$$

$$P = 98W \text{ absorbed}$$

1.19 Find the power absorbed by the circuit element at $t = 0$ if voltage across it is given by $v(t) = 23\cos 120\pi t$ V and current through it is $i(t) = 2.5\cos(120\pi t - 2\pi/3)$ A.

SOLUTION:

$$\begin{aligned} P &= VI \\ &= 57.5\cos(-2\pi/3) \\ &= -28.75\text{W} \end{aligned}$$

1.20 Determine the power supplied by the ideal sources shown in figures given.



SOLUTION:

Power supplied by 10V battery = $10\text{V} \times -8\text{A} = -80\text{W}$

Power supplied by 6A current source = $6\text{A} \times 5\text{V} = 30\text{W}$

1.21 Element A in the diagram in Fig. P1.21 absorbs 30 W of power. Calculate V_x .


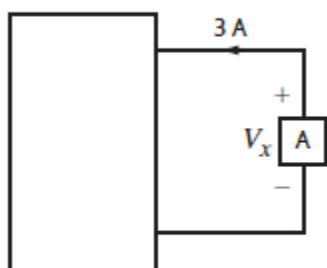
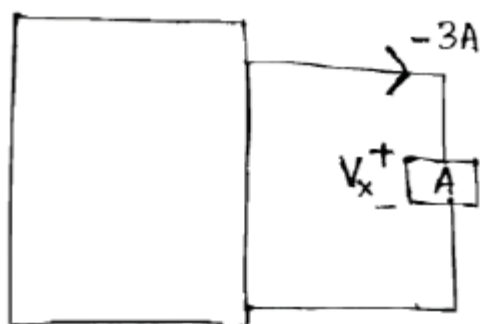


Figure P1.21

SOLUTION:

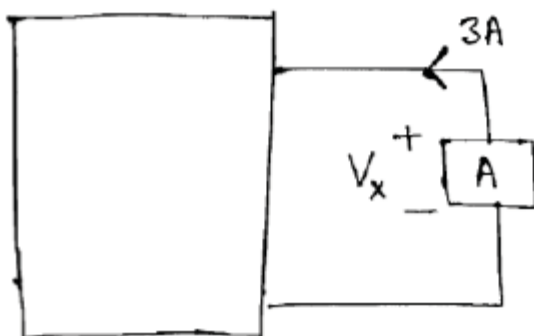

$$30 = V_x (-3)$$
$$\Rightarrow V_x = -10 \text{ V}$$

1.22 Element B in the diagram in Fig. P1.22 supplies 60 W of power. Calculate I_x .

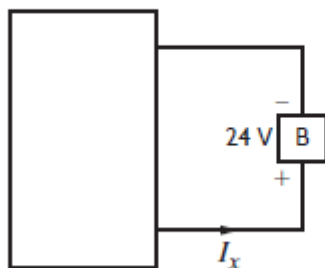


Figure P1.22

SOLUTION:

$$\begin{aligned} -60 &= 24 I_x \\ I_x &= -2.5 \text{ A} \end{aligned}$$

1.23 Let $V(t) = 10\cos 250t$ be variable voltage across a circuit.

Find.

(a) $V(1 \text{ ms})$

(b) $V(8 \text{ ms})$

(c) The energy required to move 4C charge across the circuit at 4 ms

SOLUTION:

a. $V(1\text{ms}) = 9.69\text{V}$

b. $V(8\text{ms}) = -4.16\text{V}$

c. Work done $= q \times V = 4\text{C} \times V(4\text{ms})$
 $= -21.6\text{J}$

- 1.24 The voltage across a element varies with time as $5(t-2)^2$ V. A current of 2 A enters the +ve terminal and leaves the -ve terminal of the element. Find the power delivered to the element at 0.8 s.
-

SOLUTION:

$$\begin{aligned}\text{Power delivered} &= V \times I \\ &= 5 \times (0.8-2)^2 \text{V} \times -5\text{A} \\ &= -34.68\text{W}\end{aligned}$$

- 1.25 (a) In Fig. P1.25 (a), $P_1 = 42$ W. How much power is element 2 absorbing?
- (b) In Fig. P1.25 (b), $P_2 = -72$ W. How much power is element 1 absorbing?

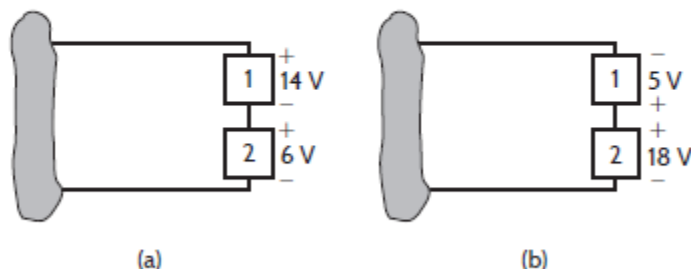


Figure P1.25

SOLUTION:

a) $P_1 = 42$ W. By default, using passive sign convention, since P_1 is positive, I flows as shown in the circuit diagram.


$P_1 = V_1 I$ $I = P_1 / V_1 = 42 / 14 = 3$ A

$I = 3$ A

For element 2, V_2 and I are defined in passive sign convention: $P_2 = V_2 I = 6(3) = 18$ W

$P_2 = 18$ W absorbed

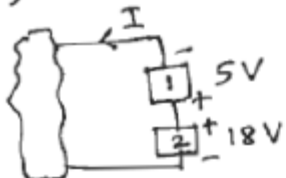b) $P_2 = -72 \text{ W}$. Again passive sign convention is the default. Since $P_2 < 0$, element 2 supplies power and I flows as shown.



$$P_2 = -V_2 I = -18 I \quad I = \frac{-72}{-18} = 4 \text{ A}$$

For element 1, V_1 and I are defined in passive sign convention. Power absorbed is $P_1 = V_1 I = 5(4) = 20 \text{ W}$

$$P_1 = 20 \text{ W absorbed}$$

- 1.26 Two elements are connected in series, as shown in Fig. P1.26. Element 1 supplies 24 W of power. Is element 2 absorbing or supplying power, and how much?

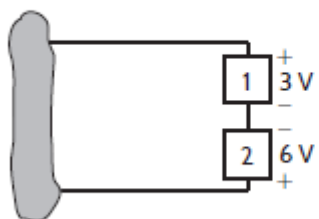


Figure P1.26

SOLUTION:

$$P_1 = 24 \text{ W}$$

$$I = \frac{P_1}{V_1} = \frac{24}{3}$$

$$I = 8 \text{ A}$$

$$P_2 = V_2 I = 6(8)$$

$$P_2 = 48 \text{ absorbed}$$

- 1.27 Element 2 in Fig. P1.27 absorbed 32 W. Find the power absorbed or supplied by elements 1 and 3.

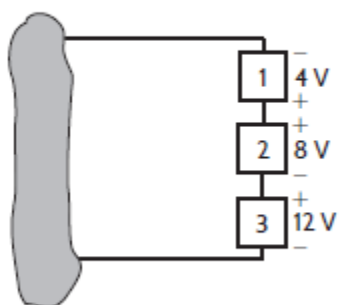


Figure P1.27

SOLUTION:

$$P_2 = 32 \text{ W} \quad \therefore I_{\downarrow} = 4 \text{ A}$$

$$P_1 = (-4)(4) = 16 \text{ W Supplied}$$

$$P_3 = (4)(12) = 48 \text{ W ABSORBED}$$

- 1.28 Choose I_s such that the power absorbed by element 2 in Fig. P1.28 is 7 W.

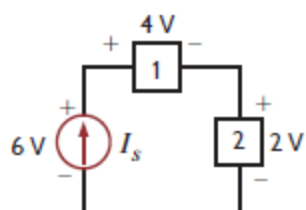


Figure P1.28

SOLUTION:


$$P_2 = 7\text{ W absorbed}$$

$$P_2 = V_2 I_s$$


$$I_s = \frac{P_2}{V_2} = \frac{7}{2}$$

$$I_s = 3.5\text{ A}$$

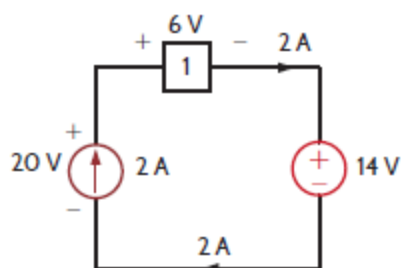1.29 Find the power that is absorbed or supplied by the circuit elements in Fig. P1.29.



(a)

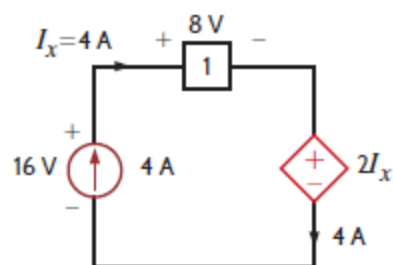

(b)

Figure P1.29

SOLUTION:


$$\begin{aligned}
 a) \quad P_{2A} &= -20(2) \\
 P_{2A} &= -40W \\
 P_{2A} &= 40W \text{ supplied}
 \end{aligned}$$

$$\begin{aligned}
 P_1 &= 6(2) = 12W \text{ absorbed} \\
 P_{14V} &= 14(2) = 28W \text{ absorbed}
 \end{aligned}$$


$$\begin{aligned} b) \quad P_{4A} &= 16(-4) = -64 \text{ W} \\ P_{4A} &= 64 \text{ W supplied} \\ P_1 &= 8(4) = 32 \text{ W absorbed} \\ P_{2I_x} &= (2I_x)(4) = 2(4)(4) \\ P_{2I_x} &= 32 \text{ W absorbed} \end{aligned}$$

1.30 Find the power that is absorbed or supplied by the network elements in Fig. P1.30.

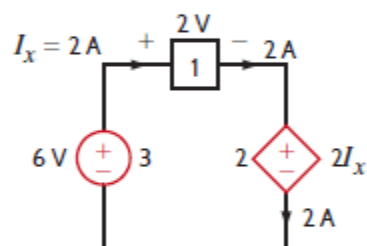- (a) Power of element 1 at figure (a).
- (b) Power of element 2 at figure (a).
- (c) Power of element 3 at figure (a).
- (d) Power of element 1 at figure (b).
- (e) Power of element 2 at figure (b).
- (f) Power of element 3 at figure (b).
- (g) Power of element 4 at figure (b).



(a)

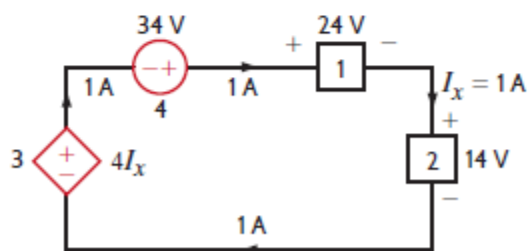

(b)

Figure P1.30

SOLUTION:

(See Next page)

a) Voltage and current for element 1 in Fig. (a) are defined in the passive sign convention.

Power supplied by element 1 in Fig. (a) is

$$P_1 = -V_1 I_x = -2(2) = -4 \text{ W}$$

$$P_1 = -4 \text{ W supplied}$$

b) Voltage and current for element 2 in Fig. (a) are defined in the passive sign convention.

Power supplied by element 2 in Fig. (a) is

$$P_2 = -(2I_x) = -4(2) = -8 \text{ W}$$

$$P_2 = -8 \text{ W supplied}$$

c) For element 3 in Fig. (a) V and I are defined in active sign convention.

Power supplied by element 3 in Fig. (a) is

$$P_3 = 6 I_x = 6(2) = 12 \text{ W}$$

$$P_3 = 12 \text{ W supplied}$$

d) V and I are defined in the passive sign convention for element 1 in Fig. (b).

Power supplied by element 1 in Fig. (b) is

$$P_1 = -V_1 I_x = -24(1) = -24 \text{ W}$$

$$P_1 = -24 \text{ W supplied}$$

- e) V and I are defined in the passive sign convention for element 2 in Fig. (b).
Power supplied by element 2 in Fig. (b) is

$$P_2 = -V_2 I_x = -14(1) = -14\text{W}$$

$$P_2 = -14\text{W supplied}$$

- f) V and I are defined in the active sign convention for element 3 in Fig. (b).
Power supplied by element 3 in Fig. (b) is

$$P_3 = (4 I_x) I_x = 4\text{W}$$

$$P_3 = 4\text{W supplied}$$

- g) V and I are defined in the active sign convention for element 4 in Fig. (b).
Power supplied by element 4 in Fig. (b) is

$$P_4 = 34(I_x) = 34\text{W supplied}$$

$$P_4 = 34\text{W supplied}$$

1.31 Compute the power that is absorbed or supplied by the elements in the network in Fig. P1.31.

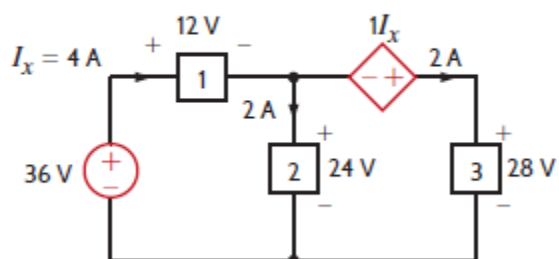


Figure P1.31

SOLUTION:

$$\begin{aligned}
 P_{36V} &= -36(4) = -144 \text{ W} \\
 P_{36V} &= 144 \text{ W supplied} \\
 P_1 &= 12(4) = 48 \text{ W absorbed} \\
 P_2 &= 24(2) = 48 \text{ W absorbed} \\
 P_{1I_x} &= (-I_x)(2) = -4(2) = -8 \text{ W} \\
 P_{1I_x} &= 8 \text{ W supplied} \\
 P_3 &= 28(2) = 56 \text{ W absorbed}
 \end{aligned}$$

1.32 Find the power that is absorbed or supplied by element 2 in Fig. P1.32.

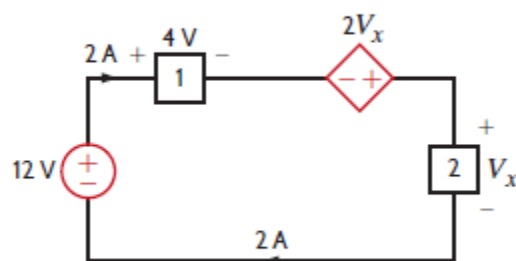


Figure P1.32

SOLUTION:

$$P_{12V} = -24W$$

$$P_1 = 8W$$

$$P_{2V_x} = -4V_xW$$

$$P_2 = 2V_xW$$

$$24 + 4V_x = 8 + 2V_x$$

$$2V_x = -16$$

$$V_x = -8V$$

$$P_2 = -16W \text{ Supplied}$$

1.33 Find I_x in the network in Fig. P1.33.

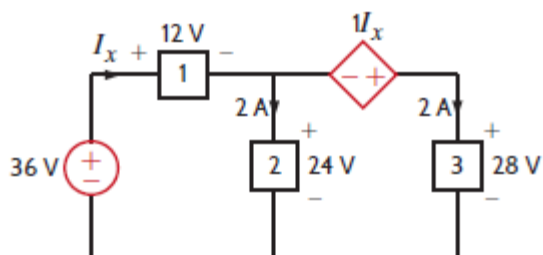


Figure P1.33

SOLUTION:

$$P_{36V} = -36I_x \text{ W}$$

$$P_1 = 12I_x \text{ W}$$

$$P_2 = 48 \text{ W}$$

$$P_{I_x} = -2I_x \text{ W}$$

$$P_3 = 56 \text{ W}$$

$$P_{36V} + P_{I_x} = P_1 + P_2 + P_3$$

$$I_x = 4 \text{ A}$$

1.34 Determine the power absorbed by element 1 in Fig. P1.34.

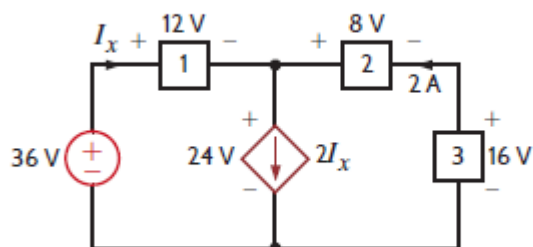


Figure P1.34

SOLUTION:

$$P_{36V} = -36I_x \text{ W}$$

$$P_1 = 12I_x \text{ W}$$

$$P_{2I_x} = 48I_x \text{ W}$$

$$P_2 = -16 \text{ W}$$

$$P_3 = -32 \text{ W}$$

$$36I_x + 16 + 32 = 12I_x + 48I_x$$

$$48 = 24I_x$$

$$I_x = 2 \text{ A}$$

$$P_1 = 24 \text{ W}$$

1.35 Find the power absorbed or supplied by element 3 in Fig. P1.35.

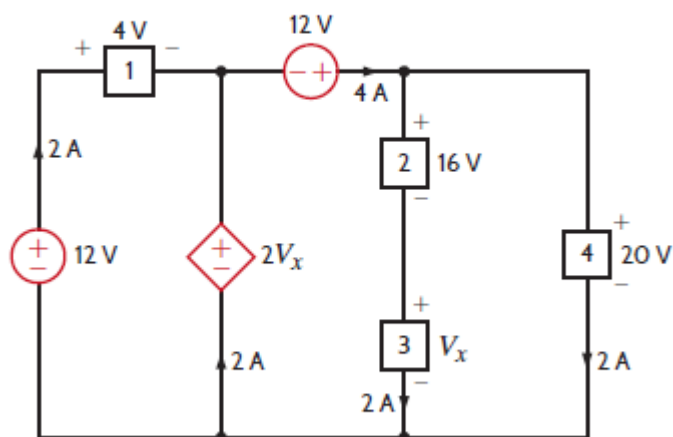


Figure P1.35

SOLUTION:

$$\begin{aligned}
 P_{12V} &= -24 & P_{12V} &= -48 & P_4 &= 40 \\
 P_1 &= 8 & P_2 &= 32 \\
 P_{2V_x} &= -4V_x & P_3 &= 2V_x
 \end{aligned}$$

$$24 + 4V_x + 48 = 8 + 32 + 2V_x + 40$$

$$2V_x = 8$$

$$V_x = 4V$$

$$P_3 = 8W \text{ ABSORBED}$$

1.36 Find V_x in the network in Fig. P1.36 using Tellegen's theorem.

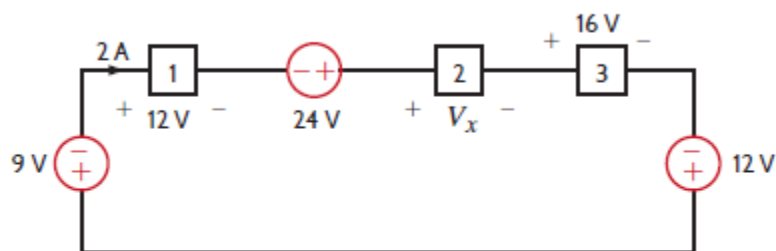


Figure P1.36

SOLUTION:

Power supplied = Power absorbed

$$P_{24} + P_{12} = P_{9V} + P_1 + P_2 + P_3$$

$$24I + 12I = 9I + 12I + P_2 + 16I$$

$$36I = 37I + P_2$$

$$P_2 = (-1)(I)$$

$$V_x(I) = -1(I)$$

$$V_x = -1V$$

1.37 Find I_x in the circuit in Fig. P1.37 using Tellegen's theorem.

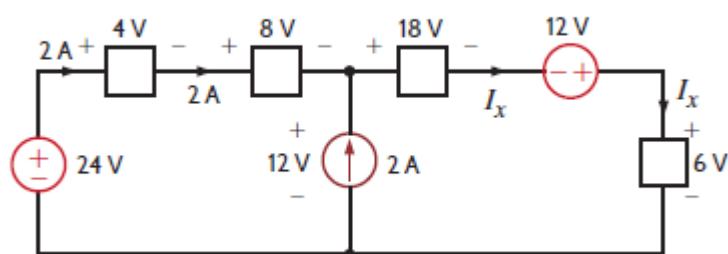


Figure P1.37

SOLUTION:

$$P_{24V} = (24)(-2) = -48W$$

$$P_{24V} = 48W \text{ supplied}$$

$$P_{4V} = (4)(2) = 8W \text{ absorbed}$$

$$P_{8V} = (8)(2) = 16W \text{ absorbed}$$

$$P_{2A} = 12(-2) = -24W$$

$$P_{2A} = 24W \text{ supplied}$$

$$P_{18V} = 18I_x \text{ absorbed}$$

$$P_{12V} = 12(-I_x) = -12I_x$$

$$P_{12V} = 12I_x \text{ supplied}$$

$$P_{6V} = 6I_x \text{ absorbed}$$

Power supplied = Power absorbed

$$P_{24V} + P_{2A} + P_{12V} = P_{4V} + P_{8V} + P_{18V} + P_{6V}$$

$$48 + 24 + 12I_x = 8 + 16 + 18I_x + 6I_x$$

$$12I_x = 48$$

$$I_x = 4A$$

1.38 Is the source V_s in the network in Fig. P1.38 absorbing or supplying power, and how much?

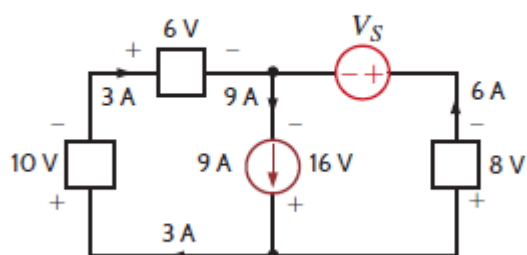


Figure P1.38

SOLUTION:

$$P_{10V} = 10(3) = 30W \text{ absorbed}$$

$$P_{6V} = 6(3) = 18W \text{ absorbed}$$

$$P_{9A} = 16(-9) = -144W$$

$$P_{9A} = 144W \text{ supplied}$$

$$P_{V_s} = V_s(6) = 6V_s \text{ absorbed}$$

$$P_{8V} = 8(6) = 48W \text{ absorbed}$$

Power supplied = Power absorbed

$$P_{9A} = P_{10V} + P_{6V} + P_{V_s} + P_{8V}$$

$$144 = 30 + 18 + 6V_s + 48$$

$$144 = 96 + 6V_s$$

$$24 = 16 + V_s$$

$$V_s = 8V$$

$$P_{V_s} = 8(6) = 48W \text{ absorbed}$$

1.39 Find I_o in the network in Fig. P1.39 using Tellegen's theorem.

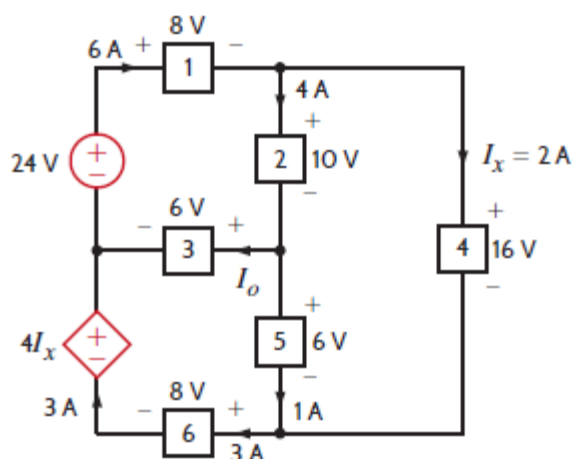


Figure P1.39

SOLUTION:

$$P_{24V} = 24(-6) = -144 \text{ W}$$

$$P_{24V} = 144 \text{ W supplied}$$

$$P_1 = 8(6) = 48 \text{ W absorbed}$$

$$P_2 = 10(4) = 40 \text{ W absorbed}$$

$$P_3 = 6I_o \text{ ABSORBED}$$

$$P_4 = 16(2) = 32 \text{ W absorbed}$$

$$P_5 = 6(1) = 6 \text{ W absorbed}$$

$$P_6 = 8(3) = 24 \text{ W absorbed}$$

$$P_{4I_x} = 4I_x(-3) = -12(2) = -24 \text{ W}$$

$$P_{4I_x} = 24 \text{ W supplied}$$

$$\text{Power supplied} = \text{Power absorbed}$$

$$P_{24V} + P_{4I_x} = P_1 + P_2 + P_3 + P_4 + P_5 + P_6$$

$$144 + 24 = 48 + 40 + 6I_o + 32 + 6 + 24$$

$$I_o = 3 \text{ A}$$

- 1.40 Calculate the power absorbed by each element in the circuit in Fig. P1.40. Also, verify that Tellegen's theorem is satisfied by this circuit.

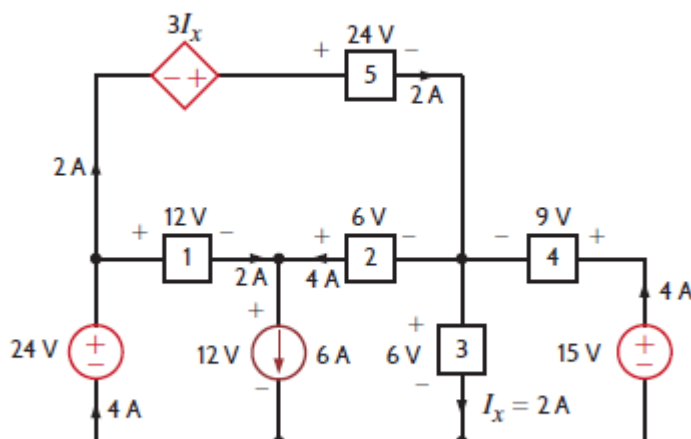


Figure P1.40

SOLUTION:

$$\begin{aligned}
 \#1: P &= (12)(2) = 24\text{ W} \\
 \#2: P &= (6)(-4) = -24\text{ W} \\
 \#3: P &= (6)(2) = 12\text{ W} \\
 \#4: P &= (9)(4) = 36\text{ W} \\
 \#5: P &= (24)(2) = 48\text{ W} \\
 24\text{V}: P &= (24)(-4) = -96\text{ W} \\
 15\text{V}: P &= (15)(-4) = -60\text{ W} \\
 6\text{A}: P &= (12)(6) = 72\text{ W} \\
 3I_x: P &= [(3)(2)](-2) = -12\text{ W} \\
 &\quad \underline{\underline{0}}
 \end{aligned}$$

1.41 Calculate the power absorbed by each element in the circuit in Fig. P1.41. Also, verify that Tellegen's theorem is satisfied by this circuit.

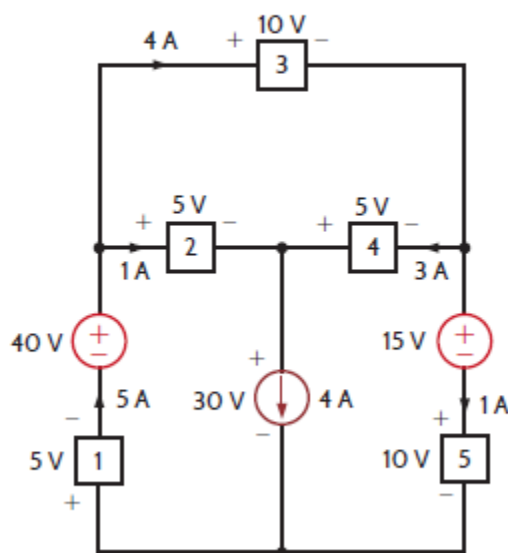


Figure P1.41

SOLUTION:

$$\begin{aligned}
 \#1: P &= (5)(5) = 25\text{W} \\
 \#2: P &= (5)(1) = 5\text{W} \\
 \#3: P &= (10)(4) = 40\text{W} \\
 \#4: P &= (5)(3) = -15\text{W} \\
 \#5: P &= (10)(1) = 10\text{W} \\
 4A: P &= (30)(4) = 120\text{W} \\
 40V: P &= (40)(-5) = -200\text{W} \\
 15V: P &= (15)(1) = 15\text{W} \\
 &\quad \underline{0}
 \end{aligned}$$

- 1.42 In the circuit in Fig. P1.42, element 1 absorbs 40 W, element 2 supplies 50 W, element 3 supplies 25 W, and element 4 absorbs 15 W. How much power is supplied by element 5?

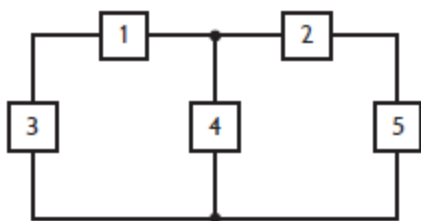


Figure P1.42

SOLUTION:

$$\sum P_{\text{absorbed}} = 0$$

$$40 - 50 - 25 + 15 + P_5 = 0$$

$$-20 + P_5 = 0$$

$$P_5 = 20 \text{ W}$$

Power absorbed by element 5
is 20 W.

Power supplied by element 5
is -20 W.