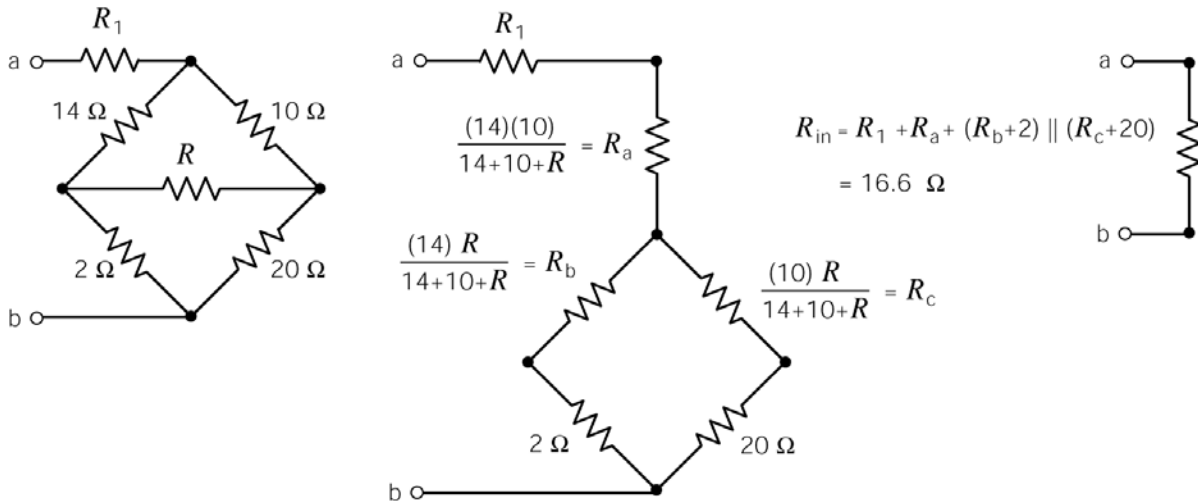


Design Problems

DP 17-1



We will need to find R and R_1 by trial and error. A Mathcad spreadsheet will help with the calculations. Given the restrictions $R \leq 10\ \Omega$ and $R_1 \leq 10\ \Omega$ we will start with $R = 10\ \Omega$ and $R_1 = 10\ \Omega$:


$$\begin{aligned} R_1 &:= 10 & R &:= 10 \\ R_a &:= \frac{14 \cdot 10}{14 + 10 + R} & R_b &:= \frac{14 R}{14 + 10 + R} & R_c &:= \frac{R \cdot 10}{14 + 10 + R} \\ R_{in} &:= R_1 + R_a + \frac{(R_b + 2) \cdot (R_c + 20)}{R_b + 2 + R_c + 20} & R_{in} &= 18.947 \end{aligned}$$

The specifications can be satisfied by reducing R_1 :

$$\begin{aligned} R_1 &:= 7.653 & R &:= 10 \\ R_a &:= \frac{14 \cdot 10}{14 + 10 + R} & R_b &:= \frac{14 R}{14 + 10 + R} & R_c &:= \frac{R \cdot 10}{14 + 10 + R} \\ R_{in} &:= R_1 + R_a + \frac{(R_b + 2) \cdot (R_c + 20)}{R_b + 2 + R_c + 20} & R_{in} &= 16.6 \end{aligned}$$

One solution is $R = 7.653\ \Omega$ and $R_1 = 10\ \Omega$.

DP 17-2

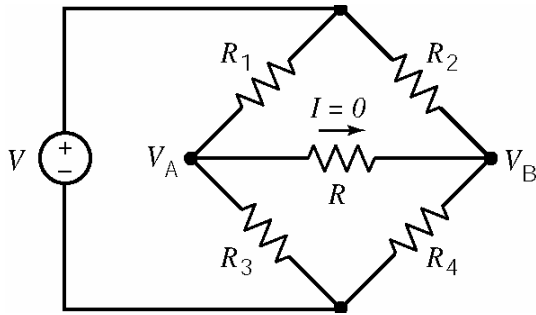

Need $V_A + V_B$ for balance

$$\frac{R_1 V}{R_1 + R_3} = \frac{R_2 V}{R_2 + R_4} \quad (1)$$

$$\frac{R_3 V}{R_1 + R_3} = \frac{R_4 V}{R_2 + R_4} \quad (2)$$

Dividing (1) by (2) yields: $\frac{R_1}{R_3} = \frac{R_2}{R_4}$.

DP 17-3

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \quad \text{and} \quad V_2 = -I_2 R_L \Rightarrow I_2 = h_{21} I_1 - h_{22} R_L I_2$$

Next

$$\frac{I_2}{I_1} = h_{21} \left(\frac{1}{1 + h_{22} R_L} \right) \Rightarrow A_i = \frac{I_L}{I_1} = -\frac{I_2}{I_1} = -h_{21} \left(\frac{1}{1 + h_{22} R_L} \right)$$

We require

$$79 = 80 \left(\frac{1}{1 + h_{22} R_L} \right) \Rightarrow \frac{79}{80} \left(1 + \frac{R_L}{80 \times 10^3} \right) = 1 \Rightarrow R_L = 1.013 \text{ k}\Omega \cong 1 \text{ k}\Omega$$

Next

$$I_2 = -\frac{V_2}{R_L} = h_{21} I_1 + h_{22} V_2 \Rightarrow V_2 (h_{22} + 1/R_L) = -h_{21} I_1$$

Substituting this expression into the second hybrid equation gives:

$$V_1 = h_{11} I_1 + \frac{h_{12} (-h_{21})}{(h_{22} + 1/R_L)} I_1$$

The input resistance can be approximated as


$$R_{in} \approx h_{11} - h_{12} R_L h_{21} \quad (\text{since } h_{22} \ll 1/R_L)$$

Finally

$$R_{in} = 45 - (5 \times 10^{-4})(10^3)(80) = 5 \Omega < 10 \Omega$$

DP 17-4
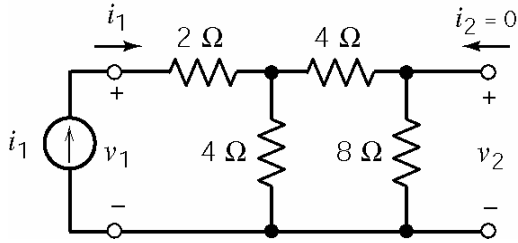
$$Z_{11} = 2 + \frac{4(12)}{4+12} = 5 \Omega \quad \text{and} \quad Z_{22} = \frac{8(8)}{8+8} = 4 \Omega$$




$$V_2 = 8 \left[\frac{4}{4+12} I_1 \right] = 2 I_1 \Rightarrow Z_{21} = \frac{V_2}{I_1} \bigg|_{I_2=0} = 2 \Omega$$

$$\text{Similarly } Z_{12} = 2 \Omega$$





Thèvenin: $Z_T = Z_{22} = 4 \Omega$ so for maximum power transfer, use $R_L = 4 \Omega$


$$P_{RL} = \frac{\left(\frac{V_s}{2} \right)^2}{4} = 89.3 \text{ W} \Rightarrow V_s = 37.8 \text{ V}$$

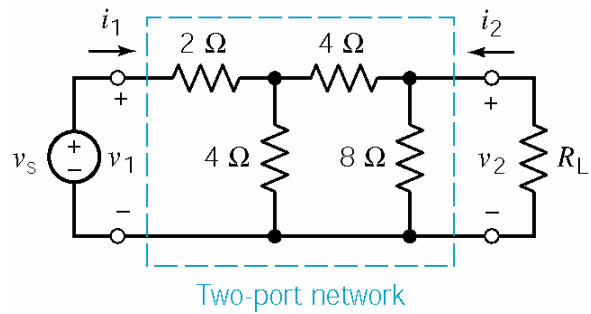

DP 17-5

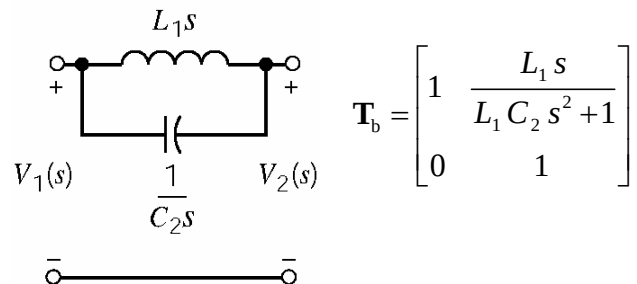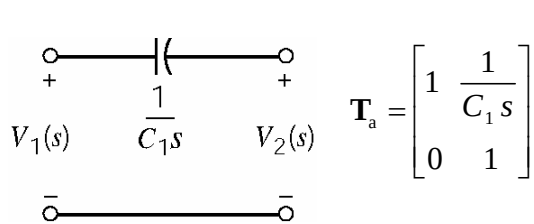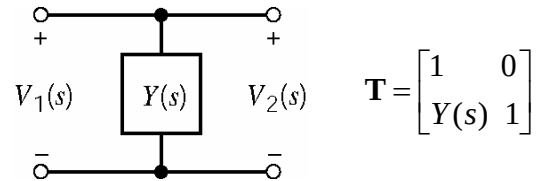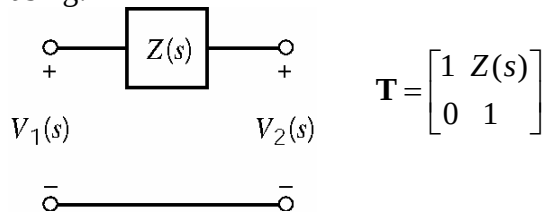The circuit consists of 4 cascaded stages. Represent each stage by a transmission matrix using:



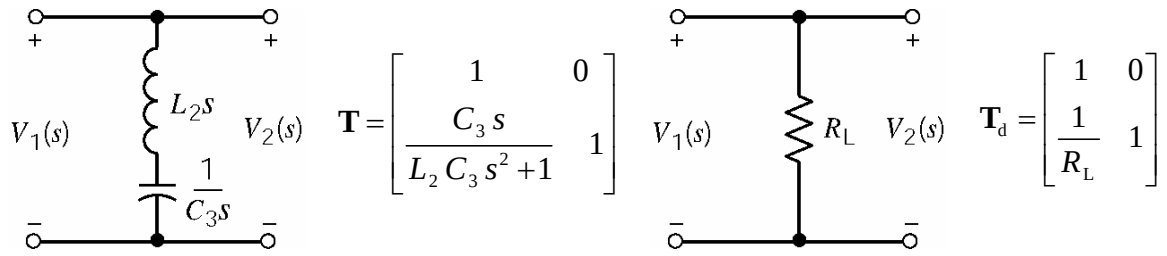

$$\mathbf{T} = \mathbf{T}_a \mathbf{T}_b \mathbf{T}_c \mathbf{T}_d = \begin{bmatrix} 1 + \frac{L_1 (C_1 + C_2) s^2 + 1}{(L_1 C_2 s^2 + 1) C_1 s} \times \frac{L_2 C_3 s^2 + R_L C_3 s + 1}{R_L (L_2 C_3 s^2 + 1)} & \frac{L_1 (C_1 + C_2) s^2 + 1}{(L_1 C_2 s^2 + 1) C_1 s} \\ \frac{L_2 C_3 s^2 + R_L C_3 s + 1}{R_L (L_2 C_3 s^2 + 1)} & 1 \end{bmatrix}$$