



c49945

Instructor's Solutions Manual Solutions to All Exercises to Accompany Electronics and Communications for Scientists and Engineers Second Edition

p5005

p5010

by Martin Plonus


2 Instructor's solutions manual: Solutions to all exercises to accompany

s0010 Chapter 1: Solutions to problems


- o0010 **1.1** $W : \frac{m\ell^2}{t^2}, F : \frac{m\ell}{t^2}, \int F \cdot d\ell = \frac{m\ell}{t^2} \cdot \ell = \frac{m\ell^2}{t^2} = W$
- p0020 $V : \frac{W}{Q}, E : \frac{F}{Q}, V = -\int E \cdot d\ell = \frac{F}{Q} \cdot \ell = \frac{m\ell}{Qt^2} \cdot \ell = \frac{m\ell^2}{Qt^2} = V$; can replace Q by It
- o0015 **1.2** $E = 5V/0.001 \text{ m} = 5000 \text{ V/m}, F = QE = -1.6 \cdot 10^{-19} \cdot 5000 \text{ V/m} = 8 \cdot 10^{-16} \text{ Newtons}$
- o0020 **1.3** Integrating $F = ma$ twice, we obtain $t = \sqrt{\frac{2ms}{F}} = \sqrt{\frac{2 \cdot 9.11 \cdot 10^{-31} \cdot 0.05}{1.9 \cdot 10^{-17}}} = 6.9 \cdot 10^{-8} \text{ s}$, where
 $F = EQ = VQ/\ell = 12 \text{ V} \cdot 1.6 \cdot 10^{-19}/10 \text{ cm} = 1.9 \cdot 10^{-17} \text{ N}$.
- o0025 **1.4** $V = RI, I = V/R, R = V/I$
- o0030 **1.5** $P = VI, P = I^2R, P = V^2/R$
- o0035 **1.6** $V = RI = 4\Omega \cdot 1.5A = 6 \text{ volts}$
- o0040 **1.7** Cross-sectional area of wire is $A = \pi r^2 = 3.14 \cdot (6.5 \cdot 10^{-4} \text{ m})^2 = 1.33 \cdot 10^{-6} \text{ m}^2$.
 Using (1.6) $\ell = \frac{RA}{\rho} = \frac{4\Omega \cdot 1.33 \cdot 10^{-6} \text{ m}^2}{10^{-8} \Omega \cdot \text{m}} = 5.32 \text{ m}$.
- o0045 **1.8** From (1.6) $R/\ell = \rho/A = 1.7 \cdot 10^{-8} \Omega \cdot \text{m}/2.081 \cdot 10^{-6} \text{ m}^2 = 8.17 \cdot 10^{-3} \Omega/\text{m}$
- o0050 **1.9** $P = VI = 300 \cdot 220 = 66,000 \text{ watts (W)}$.
- o0055 **1.10** $P = I^2R = (5)^2 \cdot 10 = 250 \text{ W}$
- o0060 **1.11** $V = IR = 5 \cdot 10 = 50 \text{ V}, P = V^2/R = (50)^2/10 = 250 \text{ W}$.
- o0065 **1.12** $W' = I^2RT = (4)^2 \cdot 5 \cdot 10 = 800 \text{ joules (J)}$.
- o0070 **1.13** $1 \text{ hp} = 1000/1.341 = 746 \text{ watts}; 1 \text{ BTU/s} = 1000/0.984 = 1055 \text{ W}; 1 \text{ cal/s} = 1000/239 = 4.18 \text{ W}$.
- o0075 **1.14** $1 \text{ kWh} = 3,600,000 \text{ W} \cdot \text{s}$. Since $1 \text{ W} \cdot \text{s} = 0.738 \text{ ft} \cdot \text{lb}$, then
 $1 \text{ kWh} = 3.6 \cdot 10^6 \cdot 0.738 = 2.66 \cdot 10^6 \text{ ft} \cdot \text{lbs}$.
- o0080 **1.15** Heat required to raise 250 g of water 90° C is $H = 90 \cdot 250 = 22,500 \text{ calories}$. Also from (1.9) $H = V^2T/R \text{ W} \cdot \text{s} = 0.239V^2T/R \text{ calories}$. Therefore, $22,500 = 0.239(110)^2T/15$.
 Solving $T = 22,500 \cdot 15/0.239 \cdot (110)^2 = 116.7 \text{ s} = 1.945 \text{ minutes}$.
- o0085 **1.16** Rating of heater is $P = IV = (120/10)120 = 1.44 \text{ kW} \cdot 8 \cdot 24 \cdot 30 = 8294 \text{ cents/month}$.
- o0090 **1.17** $12 \text{ V} - 9 \text{ V} = 3 \text{ V} = V_{R1}$.
- o0095 **1.18** $1 \text{ A} - 0.5 \text{ A} = 0.5 \text{ A} = I_{R1}$.
- o0105o0100 **1.19 (a)** $W = Pt = VIt = 120 \cdot 120/10 \cdot 5 = 7200 \text{ J}$
- o0110 **(b)** $(169.7)^2 \cdot 5/2 \cdot 10 = 7199 \text{ J}$.
- o0115 **1.20** A DC voltage of 120 V is equivalent in delivering power to a resistor as an AC voltage with peak value of $V_P = 169.7 \text{ V}$.
- o0125o0120 **1.21 (a)** $p(t) = v^2/R = V_P^2 \cos^2 10t/R$;
- p0140 $P_{\text{ave}} = \frac{1}{T} \int_0^T (V_P^2/R) \cos^2 10t dt = \frac{1}{T} \frac{V_P^2}{R} \frac{1}{10} [\frac{1}{2} 10T + \frac{1}{4} \sin 20T] = V_P^2/2R$.
- o0130 **(b)** Power flow is always from source to resistor.
- o0140o0135 **1.22 (a)** Using formula in text following (1.15), spacing between plates is
 $\ell = \epsilon A/C = 6 \cdot 8.85 \cdot 10^{-12} \cdot 10^{-2} \text{ m}^2/0.05 \cdot 10^{-6} = 1.06 \cdot 10^{-5} \text{ m}$.
- o0145 **(b)** Electric field strength between plates. $V/\ell = 100 \text{ V}/1.06 \cdot 10^{-5} \text{ m} = 9.43 \cdot 10^6 \text{ V/m}$
 which exceeds the breakdown strength of mica, which is $6 \cdot 10^6 \text{ V/m}$.
- o0150 **(c)** $6 \cdot 10^6 \text{ V/m} \cdot 1.06 \cdot 10^{-5} \text{ m} = 63.6 \text{ V}$.

Instructor's solutions manual: Solutions to all exercises to accompany 3

- o0155 **1.23** $v = 0, t < 0; v = \frac{1}{c} \int idt = \frac{1}{5\mu F} \int_0^t 20mAdt = \frac{1}{5 \cdot 10^{-6}} 20 \cdot 10^{-3} t = 4 \cdot 10^3 t, 0 \leq t \leq 3 \text{ ms};$
 $v = v(t = 3 \text{ ms}) = 4 \cdot 10^3 t = 4 \cdot 10^3 \cdot 3 \cdot 10^{-3} = 12V, t > 3 \text{ ms}.$
- o0160 **1.24** $W_c = CV_p^2 \sin^2 2\pi t / 2.$ Max when $\sin 2\pi t = 1, 5 \cdot 10^{-6} \cdot (200)^2 / 2 = 0.1 \text{ J} = W_{c, \max}.$
- o0165 **1.25** $i = \frac{1}{L} \int_{-\infty}^t 2dt = \frac{2V}{2 \cdot 10^{-3} H} t = 10^3 t \text{ A for } 0 \leq t \leq 3 \text{ ms};$
 $i|_{t > 3 \text{ ms}} = i(t = 3 \text{ ms}) + \frac{1}{L} \int_3^\infty 0dt = 10^3 t|_{t=3 \text{ ms}} + 0 = 3 \text{ A for } t > 3 \text{ ms}.$
- o0175 o0170 **1.26 (a)** $I_L = .9V / 3\Omega = .3A, R_i = (V_B - V_L) / I_L = (1.5 - .9) / .3 = .6 / .3 = 2\Omega.$
- o0180 **(b)** $(1.5 + 0.9) / 2 = 1.2 \text{ V}.$
- o0185 **(c)** $I_{\text{ave}} = V_{\text{ave}} / 3\Omega = 0.4A.$
- o0195 o0190 **1.27 (a)** $P_{\text{ave}} = I_{\text{ave}} \cdot V_{\text{ave}} = 0.4 \cdot 1.2 = 0.48 \text{ W}.$
- o0200 **(b)** $W\text{-h} = 0.48 \cdot 6 = 2.88 \text{ W-h}.$
- o0205 **(c)** Battery cost in cents/kW-h = $120 / 2.88 \cdot 10^{-3} = 41,667 \text{ cents/kW-h}.$ This is 41,667/8 = 5208 as expense as energy supplied by electric utilities.
- o0210 **1.28** $v_s = 6V, R_i = v_{oc} / i_{sc} = 6 / 2 = 3\Omega$
- o0215 **1.29** $i_s = i_{sc} = 2A, R_i = v_{oc} / i_{sc} = 3\Omega$
- o0220 **1.30** Current flowing in the series circuit is $12 / (1 + 2 + 3) = 2A; V_{R_1} = 2V, V_{R_2} = 4V, V_{R_3} = 6V.$
- o0225 **1.31** $\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3}, R_{eq} = 6 / 11\Omega; V = IR_{eq} = 11 \cdot 6 / 11 = 6V; I_{R_1} = 6A, I_{R_2} = 3A, I_{R_3} = 2A.$
- o0235 o0230 **1.32 (a)** $I_{\text{battery}} = 12 / (10 + \frac{100 \cdot 1000}{100 + 1000}) = 0.12 \text{ A},$
- o0240 **(b)** $I_{10\Omega} = 0.12A, I_{100\Omega} = 0.12 \cdot \frac{1000}{100 + 1000} = 0.11A, I_{1000\Omega} = 0.12 \cdot \frac{100}{100 + 1000} = 0.011 \text{ A}$
- o0245 **(c)** $V_{10\Omega} = (0.12 \text{ A})(10\Omega) = 1.2V, V_{100\Omega} = V_{1000\Omega} = 12V - 1.2V = 10.8 \text{ V}$

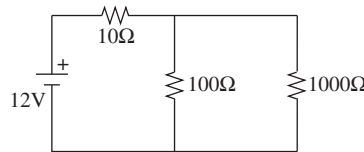


- o0255 o0250 **1.33 (a)** $I_{3\Omega} = 6 / (3 + \frac{1 \cdot 4}{1+4}) = 1.58A, I_{2\Omega} = 1.58(\frac{2 \cdot 4}{2+4}) / (2 + (\frac{2 \cdot 4}{2+4})) = 0.63 \text{ A},$
 $I_{4\Omega} = 1.58 \frac{1}{1+4} = 0.32A$
- o0260 **(b)** $V_{3\Omega} = 1.58 \cdot 3 = 4.7 \text{ V}, V_{2\Omega} = V_{4\Omega} = 6 - 4.7 = 1.3$
- o0265 **(c)** $P = V_{\text{bat.}} \cdot I_{\text{bat.}} = 6 \text{ V} \cdot 1.58 \text{ A} = 9.47 \text{ W}$

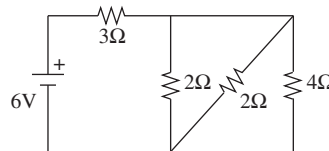

- o0270 **1.34** $6 = 2i_1 + 10i_1 - 10i_2$ but $i_2 = -3A, i_1 = -24/12 = -2A$
- o0275 **(a)** $i_{10\Omega} = i_1 - i_2 = -2 - (-3) = 1 \text{ A}, V_{10\Omega} = i_{10} \cdot 10 = 1 \cdot 10 = 10 \text{ V}$
- o0280 **(b)** $i_{2\Omega} = i_1 = -2 \text{ A}, V_{2\Omega} = -2 \cdot 2 = -4 \text{ V}$

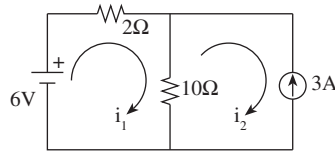4 Instructor's solutions manual: Solutions to all exercises to accompany



o0285 **1.35** Switching off the current source, we obtain $i'_{10\Omega} = (6/2 + 10) = \frac{1}{2}$ A and

$$V'_{10\Omega} = 6 \cdot \frac{10}{2+10} = 5 \text{ V}$$

p0305 Switching off the voltage source, we obtain $i''_{10\Omega} = 3 \cdot \frac{2}{2+10} = \frac{1}{2}$ A and



$$V''_{10\Omega} = 3 \cdot \frac{2 \cdot 10}{2+10} = 5 \text{ V}$$

o0290 **(a)** $i_{10\Omega} = i' + i'' = \frac{1}{2} + \frac{1}{2} = 1$ A, $V_{10\Omega} = V' + V'' = 5 + 5 = 10$ V





o0295 **(b)** Similarly $i'_{2\Omega} = 6/(2+10) = \frac{1}{2}$ A, $V'_{2\Omega} = 6 \cdot 2/(2+10) = 1$ V, $i''_{2\Omega} = 3 \cdot 10/(2+10) = 2.5$ A, $V''_{2\Omega} = 3 \cdot \frac{2 \cdot 10}{2+10} = 5$ V, $i_{2\Omega} = i' + i'' = \frac{1}{2} - 2.5 = -2$ A, $V_{2\Omega} = V' + V'' = 1 - 5 = -4$ V

o0300 **1.36** $i_{2\Omega} = (6 - 30)/2(2 + 10) = -24/12 = -2$ A $i_{10\Omega} = (3 + 3) \frac{2}{2+10} = 1$ A

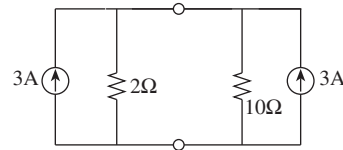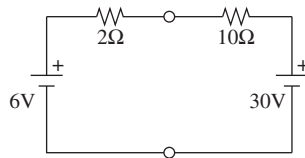p0325 $V_{2\Omega} = (-2)(2) = -4$ V $V_{10\Omega} = (1) \cdot 10 = 10$ V



o0305 **1.37**

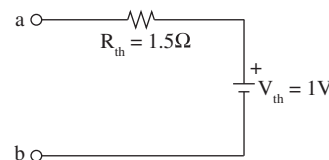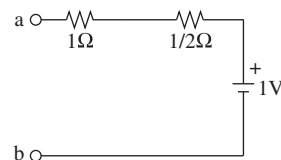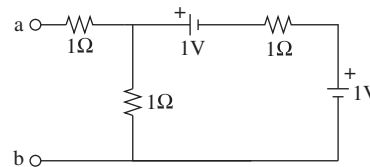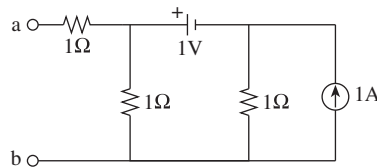


o0310 **1.38** It should have the value of $R_{th} = 1.5\Omega$. $P_{\max} = IV = \left(\frac{1}{1.5+1.5}\right) \left(1 \frac{1.5}{1.5+1.5}\right) = 1/6$ W.


o0315 **1.39** Using superposition, the open-circuit voltage at x-y is $V_{oc} = V_{th} = 12 \cdot \frac{40 \parallel 50}{10 + (40 \parallel 50)} + 1 \cdot 30 \parallel (20 + 10 \parallel 40) \cdot \frac{40 \parallel 10}{20 + 40 \parallel 10} = 8.276 + 4.138 = 12.414$ V, where $40 \parallel 50 = 40 \cdot 50 / (40 + 50) = 22.22\Omega$, $10 \parallel 40 = 8\Omega$

p0345 $R_{th} = 10 \parallel 40 \parallel 50 = 8 \parallel 50 = 8 \cdot 50 / (8 + 50) = 6.896\Omega$

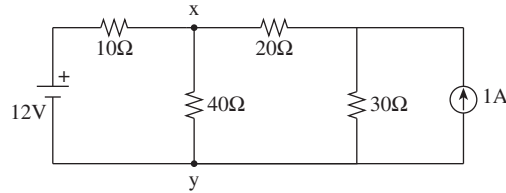
Instructor's solutions manual: Solutions to all exercises to accompany 5



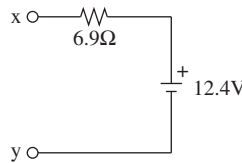p0350 R_{th} obtained by short-circuiting the 12 V source and open-circuiting the 1 A source.



- o0325 o0320 **1.40 (a)** $R_{th} = 25 \parallel (10 + 25) = 12.5\Omega$, therefore $R_L = 12.5\Omega$
o0330 **(b)** $V_{th} = \frac{6}{15+10} \cdot 25 + 12 - \frac{12}{10+15+25} \cdot 25 = 3 + 12 - 6 = 9V$, therefore
 $P_{max} = I \cdot V = \frac{9}{12.5+12.5} \cdot 9 \cdot \frac{12.5}{12.5+12.5} = 1.62 \text{ W}$
o0335 **(c)** $P_{R_L=10\Omega} = I \cdot V = \frac{9}{10+12.5} \cdot 9 \cdot \frac{10}{10+12.5} = 1.60 \text{ W}$

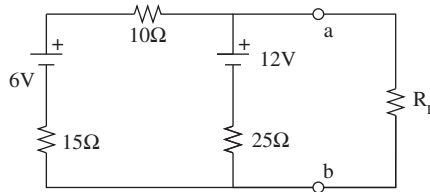

- o0340 **1.41** For maximum power transfer to a load, the equivalent source and load resistances must be matched, that is, equal to each other.
o0345 **1.42** $i_{R_1} = V/R_1$
o0350 **1.43** $i_2 = (R_2 i_1 - V_2)/(R_2 + R_3) = [2 \cdot (-0.33) - 2]/(2 + 3) = -2.66/5 = -0.532 \text{ A}$
o0355 **1.44** $i_3 = \begin{vmatrix} 8 & -2 & 1 \\ -2 & 5 & -2 \\ -5 & 0 & -3 \end{vmatrix} \div 199 = \frac{-5(4-5)-3(40-4)}{199} = -\frac{103}{199} = -0.517 \text{ A}$
o0360 **1.45** $i_1 = -0.33 \text{ A}$
o0365 **1.46** $i_{R5} = i_1 - i_3 = -0.33 - (-0.52) = 0.19 \text{ A}$
o0370 **1.47** Yes, it results in a matrix with positive diagonal terms and negative off-diagonal terms. This helps when checking the equations for errors.
o0380 o0375 **1.48 (a)** $q_0 = CV = 2\mu F \cdot 12V = 24 \cdot 10^{-6} \text{ coulombs (c)}$.
o0385 **(b)** $i_o = v_o/R = 12V/100\Omega = 0.12 \text{ A}$.
o0390 **(c)** $\tau = RC = 100\Omega \cdot 2\mu F = 200\mu s$.