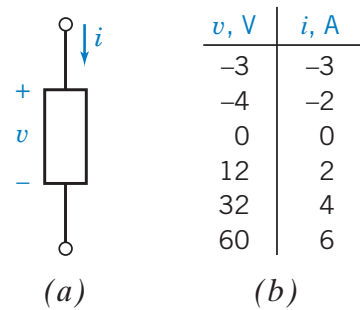


## Section 2-2 Engineering and Linear Models

**P 2.2-1** An element has voltage  $v$  and current  $i$  as shown in Figure P 2.2-1a. Values of the current  $i$  and corresponding voltage  $v$  have been tabulated as shown in Figure P 2.2-1b. Determine if the element is linear.

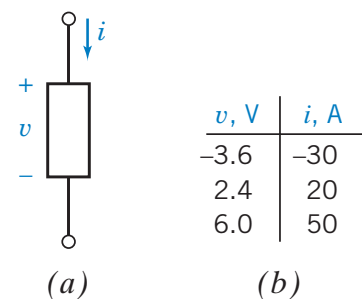


**Figure P 2.2-1**

**Solution:**

The element is not linear. For example, doubling the current from 2 A to 4 A does not double the voltage. Hence, the property of homogeneity is not satisfied.

**P 2.2-2** A linear element has voltage  $v$  and current  $i$  as shown in Figure P 2.2-2a. Values of the current  $i$  and corresponding voltage  $v$  have been tabulated as shown in Figure P 2.2-2b. Represent the element by an equation that expresses  $v$  as a function of  $i$ . This equation is a model of the element. (a) Verify that the model is linear. (b) Use the model to predict the value of  $v$  corresponding to a current of  $i = 40$  mA. (c) Use the model to predict the value of  $i$  corresponding to a voltage of  $v = 4$  V.



**Figure P 2.2-2a**

**Hint:** Plot the data. We expect the data points to lie on a straight line. Obtain a linear model of the element by representing that straight line by an equation.


**Solution:**

(a) The data points do indeed lie on a straight line. The slope of the line is 0.12 V/A and the line passes through the origin so the equation of the line is  $v = 0.12i$ . The element is indeed linear.

(b) When  $i = 40$  mA,  $v = (0.12 \text{ V/A}) \times (40 \text{ mA}) = (0.12 \text{ V/A}) \times (0.04 \text{ A}) = 4.8 \text{ mV}$

(c) When  $v = 3$  V,  $i = \frac{3}{0.12} = 25 \text{ A}$

**P 2.2-3** A linear element has voltage  $v$  and current  $i$  as shown in Figure P 2.2-3a. Values of the current  $i$  and corresponding voltage  $v$  have been tabulated as shown in Figure P 2.2-3b. Represent the element by an equation that expresses  $v$  as a function of  $i$ . This equation is a model of the element. (a) Verify that the model is linear. (b) Use the model to predict the value of  $v$  corresponding to a current of  $i = 4$  mA. (c) Use the model to predict the value of  $i$  corresponding to a voltage of  $v = 12$  V.

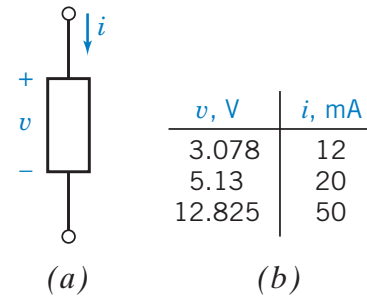

**Figure P 2.2-3**

**Hint:** Plot the data. We expect the data points to lie on a straight line. Obtain a linear model of the element by representing that straight line by an equation.

**Solution:**

(a) The data points do indeed lie on a straight line. The slope of the line is 256.5 V/A and the line passes through the origin so the equation of the line is  $v = 256.5i$ . The element is indeed linear.

(b) When  $i = 6$  mA,  $v = (256.5 \text{ V/A}) \times (6 \text{ mA}) = (256.5 \text{ V/A}) \times (0.006 \text{ A}) = 1.054 \text{ V}$

(c) When  $v = 12$  V,  $i = \frac{12}{256.5} = 0.04678 \text{ A} = 46.78 \text{ mA}$ .

**P 2.2-4** An element is represented by the relation between current and voltage as

$$v = 3i + 5$$

Determine whether the element is linear.

**Solution:**

Let  $i = 1$  A, then  $v = 3i + 5 = 8$  V. Next  $2i = 2$  A but  $16 = 2v \neq 3(2i) + 5 = 11$ . Hence, the property of homogeneity is not satisfied. The element is not linear.

**P 2.2-5** The circuit shown in Figure P 2.3-5 consists of a current source, a resistor, and element A.

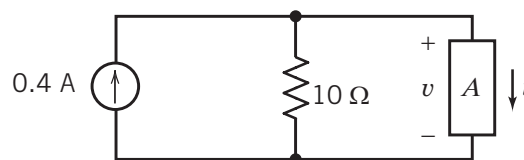


Figure P 2.3-5

Consider three cases.

- (a) When element A is a 40- $\Omega$  resistor, described by  $i = v / 40$ , then the circuit is represented by

$$0.4 = \frac{v}{10} + \frac{v}{40}$$

Determine the values of  $v$  and  $i$ . Notice that the above equation has a unique solution.

- (b) When element A is a nonlinear resistor described by  $i = v^2 / 2$ , then the circuit is represented by

$$0.4 = \frac{v}{10} + \frac{v^2}{2}$$

Determine the values of  $v$  and  $i$ . In this case there are two solutions of the above equation. Nonlinear circuits exhibit more complicated behavior than linear circuits.

- (c) When element A is a nonlinear resistor described by  $i = 0.8 + \frac{v^2}{2}$ , then the circuit is

described by

$$0.4 = \frac{v}{10} + 0.8 + \frac{v^2}{2}$$

Show that this equation has no solution. This result usually indicates a modeling problem. At least one of the three elements in the circuit has not been modeled accurately.

### Solution:

(a)

$$0.4 = \frac{v}{10} + \frac{v}{40} = \frac{v}{8} \quad \Rightarrow \quad v = 3.2 \text{ V}$$

$$i = \frac{v}{40} = 0.08 \text{ A}$$

(b)

$$0.4 = \frac{v}{10} + \frac{v^2}{2} \quad \Rightarrow \quad v^2 + \frac{v}{5} - 0.8 = 0$$

Using the quadratic formula

$$v = \frac{-0.2 \pm 1.8}{2} = 0.8, -1.0 \text{ V}$$

When  $v = 0.8 \text{ V}$  then  $i = \frac{0.8^2}{2} = 0.32 \text{ A}$ . When  $v = -1.0 \text{ V}$  then  $i = \frac{(-1)^2}{2} = 0.5 \text{ A}$ .

(c)

$$0.4 = \frac{v}{10} + 0.8 + \frac{v^2}{2} \quad \Rightarrow \quad v^2 + \frac{v}{5} + 0.8 = 0$$

Using the quadratic formula  $v = \frac{-0.2 \pm \sqrt{0.04 - 3.2}}{2}$

So there is no real solution to the equation.