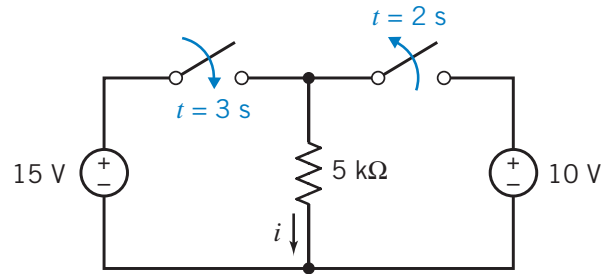



## Section 2-9 Switches

**P 2.9-1** Determine the current,  $i$ , at  $t = 1$  s and at  $t = 4$  s for the circuit of Figure P 2.9-1.



**Figure P 2.9-1**

**Solution:**

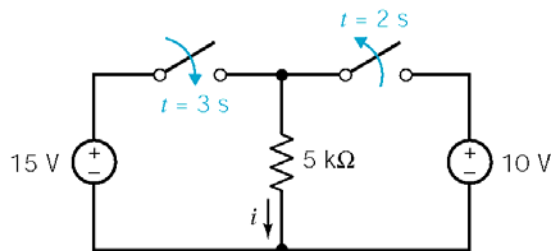


At  $t = 1$  s the left switch is open and the right switch is closed so the voltage across the resistor is 10 V.

$$i = \frac{v}{R} = \frac{10}{5 \times 10^3} = \underline{2 \text{ mA}}$$

At  $t = 4$  s the left switch is closed and the right switch is open so the voltage across the resistor is 15 V.

$$i = \frac{v}{R} = \frac{15}{5 \times 10^3} = \underline{3 \text{ mA}}$$

**P 2.9-2** Determine the voltage,  $v$ , at  $t = 1$  s and at  $t = 4$  s for the circuit shown in Figure P 2.9-2.

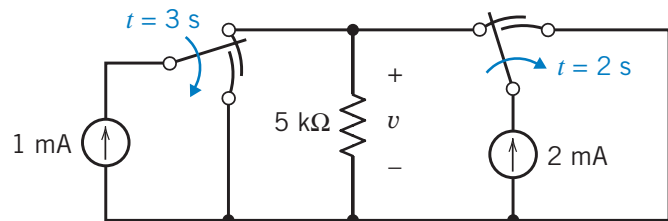



**Figure P 2.9-2**

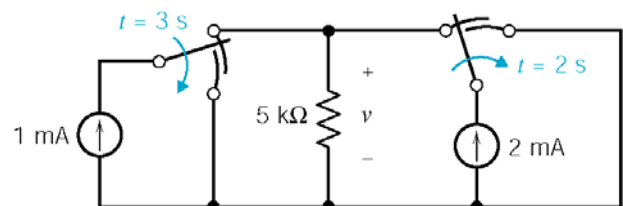**Solution:**

At  $t = 1$  s the current in the resistor is 3 mA so  $\underline{v = 15 \text{ V}}$ .

At  $t = 4$  s the current in the resistor is 0 A so  $\underline{v = 0 \text{ V}}$ .



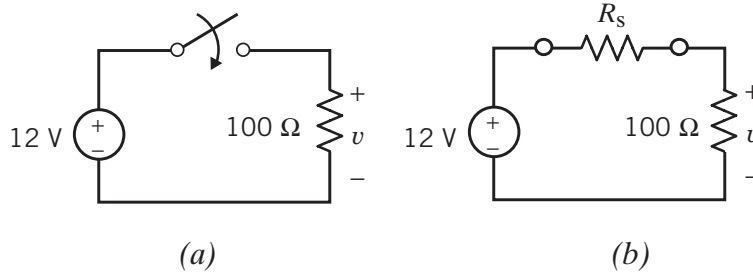

**Figure P 2.9-3**

**P 2.9-3** Ideally an open switch is modeled as an open circuit and a closed switch is modeled as a closed circuit. More realistically, an open switch is modeled as a large resistance and a closed switch is modeled as a small resistance.

Figure P 2.9-3a shows a circuit with a switch. In figure P 2.9-3b the switch has been replaced with a resistance. In figure P 2.9-3b the voltage  $v$  is given by

$$v = \left( \frac{100}{R_s + 100} \right) 12$$

Determine the value of  $v$  for each of the following cases.

- (a) The switch is closed and  $R_s = 0$  (a short circuit).
- (b) The switch is closed and  $R_s = 5 \, \Omega$ .
- (c) The switch is open and  $R_s = \infty$  (an open circuit).
- (d) The switch is open and  $R_s = 10 \, \text{k}\Omega$ .

**Solution:**

(a)  $v = 12 \, \text{V}$

(b)  $v = \left( \frac{100}{105} \right) 12 = 11.43 \, \text{V}$

(c)  $v = 0 \, \text{V}$

(d)  $v = \left( \frac{100}{10100} \right) 12 = 0.1188 \approx 0.12 \, \text{V}$