
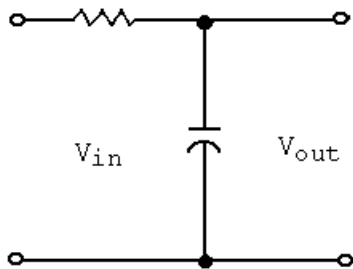


Chapter 1: The Decimal Number System

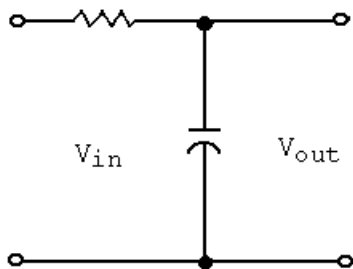1. In the circuit below, $V_{in} = 15\text{ V}$ and $R = 5\text{ k}\Omega$. What are V_O and X_C at f_{CO} ?
- a. $X_C = 7.07\text{ k}\Omega$, $V_O = 21.2\text{ V}$
 - b. $X_C = 7.07\text{ k}\Omega$, $V_O = 15\text{ V}$
 - c. $X_C = 5.05\text{ k}\Omega$, $V_O = 15\text{ V}$
 - d. $X_C = 5.00\text{ k}\Omega$, $V_O = 10.6\text{ V}$
 - e. $X_C = 3.5\text{ k}\Omega$, $V_O = 10.6\text{ V}$




2. In the circuit below, $V_{in} = 20\text{ V}$, $R = 12\text{ k}\Omega$, and $C = 0.003\text{ }\mu\text{F}$. Find f_{CO} .
- a. 2.8 KHz
 - b. 4.4 KHz
 - c. 8.3 KHz
 - d. 14 KHz
 - e. 84 KHz




Chapter 1: The Decimal Number System

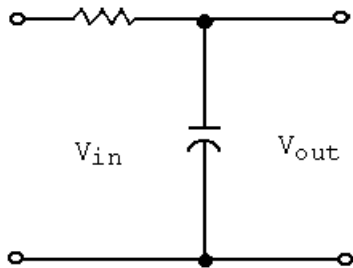3. In the circuit below, $V_{in} = 35 \text{ V}$, $R = 20 \text{ K}\hat{\Omega}$, and $f_{CO} = 23 \text{ KHz}$. Find V_O and C at f_{CO} .
- $V_O = 17.5 \text{ V}$, $C = 346 \text{ pF}$
 - $V_O = 17.5 \text{ V}$, $C = 230 \text{ pF}$
 - $V_O = 24.8 \text{ V}$, $C = 346 \text{ pF}$
 - $V_O = 24.8 \text{ V}$, $C = 200 \text{ pF}$
 - $V_O = 35.0 \text{ V}$, $C = 530 \text{ pF}$



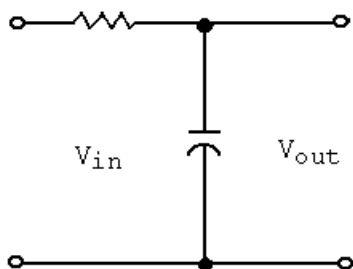
4. In the circuit below, $V_{in} = 35 \text{ V}$, $R = 20 \text{ K}\hat{\Omega}$, and $f_{CO} = 23 \text{ KHz}$. What is the circuit impedance and I_{max} for the circuit?
- $Z = 28.3 \text{ K}\hat{\Omega}$, $I = 1.24 \text{ mA}$
 - $Z = 40.0 \text{ K}\hat{\Omega}$, $I = 1.75 \text{ mA}$
 - $Z = 39.2 \text{ K}\hat{\Omega}$, $I = 3.50 \text{ mA}$
 - $Z = 28.3 \text{ K}\hat{\Omega}$, $I = 1.75 \text{ mA}$
 - $Z = 14.2 \text{ K}\hat{\Omega}$, $I = 1.24 \text{ mA}$




5. In a low pass filter, $V_{in} = 18.5 \text{ V}$ and $R = 4.5 \text{ K}\hat{\Omega}$. Find X_C , I_P and V_O at f_{CO} .
6. In a low pass filter, $V_{in} = 7 \text{ V}$, $R = 3.3 \text{ K}\hat{\Omega}$, $C = 180 \text{ nF}$. Find F_{CO} , and V_{out} at f_{CO} .

Chapter 1: The Decimal Number System

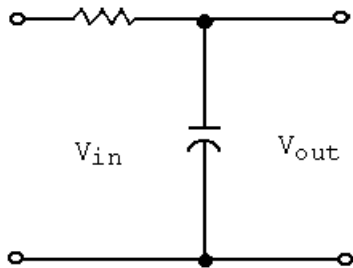7. Referring to the circuit below, the low pass filter has the following characteristic(s):
- The output voltage is equal to V_{in} at f_{CO}
 - The power output is 50% of max. at f_{CO}
 - The output decreases as frequency increases
 - The power output is 50% of max. at f_{CO} and the output decreases as frequency increases




8. Below is a circuit for a high pass filter. As the frequency increases, what happens to V_R and V_C ?
- V_R decreases, V_C increases.
 - V_R remains the same, V_C decreases.
 - V_R increases, V_C remains the same.
 - V_R increases, V_C decreases.
 - V_R increases, V_C increases.

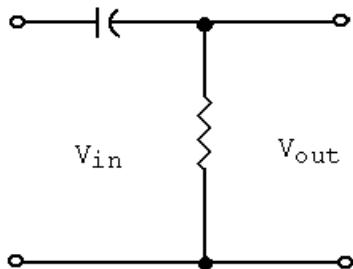


Chapter 1: The Decimal Number System

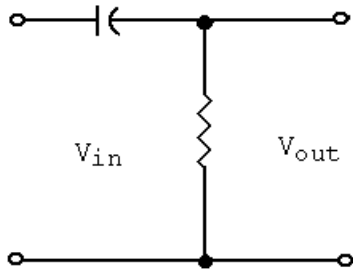9. In the circuit below, the frequency is increased from 100 Hz to a maximum value. At what frequency does V_O reach the cutoff frequency if $R = 100 \text{ } \Omega$ and $C = 0.01 \text{ } \mu\text{F}$?
- a. 2.53 KHz
 - b. 159.2 KHz
 - c. 8.11 KHz
 - d. 14.33 KHz
 - e. 11.93 KHz




10. If $R = 100 \text{ } \Omega$ and $C = 0.01 \text{ } \mu\text{F}$, what is the power dissipated in the circuit below at f_{CO} if $V_{in} = 20 \text{ V}$?
- a. 4.00 w
 - b. 2.82 w
 - c. 2.00 w
 - d. 1.41 w
 - e. 1.00 w

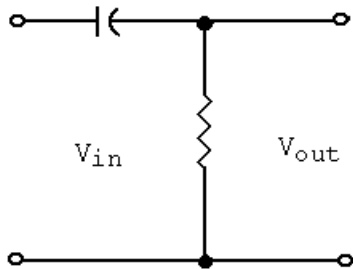


Chapter 1: The Decimal Number System

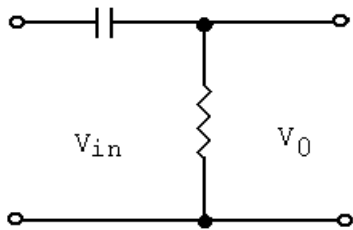11. In the circuit below, find f_{CO} and V_O if $V_{in} = 42 \text{ V}$, $R = 22 \text{ K}$, and $C = 0.00015 \text{ }\mu\text{F}$.
- $V_O = 29.7 \text{ V}$, $f_{CO} = 48.2 \text{ KHz}$
 - $V_O = 21.0 \text{ V}$, $f_{CO} = 48.2 \text{ KHz}$
 - $V_O = 21.0 \text{ V}$, $f_{CO} = 31.7 \text{ KHz}$
 - $V_O = 29.7 \text{ V}$, $f_{CO} = 31.7 \text{ KHz}$
 - $V_O = 21.0 \text{ V}$, $f_{CO} = 34.1 \text{ KHz}$




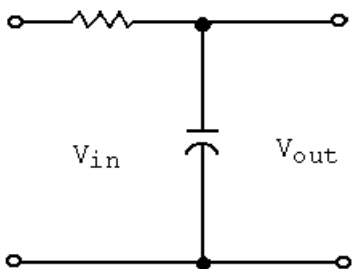12. What is the value of C required to cause a low pass filter to cutoff at 18 KHz if $R = 13.7 \text{ K}\Omega$?
- $0.00015 \text{ }\mu\text{F}$
 - 645 pF
 - $0.004 \text{ }\mu\text{F}$
 - 345 pF
 - $0.0006 \text{ }\mu\text{F}$
13. In the circuit below, $V_{in} = 18 \text{ V}$ and $R = 18 \text{ K}\Omega$ and $C = 0.001 \text{ }\mu\text{F}$. What is f_{CO} ?




14. Given a series RC circuit, what is the relationship of R and X_C at the frequency cutoff?

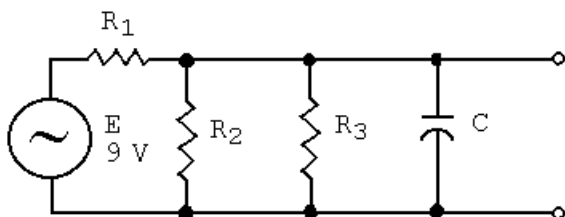
15. Using Thevenin's Theorem, find the equivalent circuit for a low pass filter when $R_1 = 5.6 \text{ K}\Omega$, $R_2 = 6.8 \text{ K}\Omega$, $R_3 = 10 \text{ K}\Omega$, and $C = 1200 \text{ pF}$.
- $R_{TH} = 13.1 \text{ K}\Omega$, $C = 1200 \text{ pF}$, output across R
 - $R_{TH} = 2.3 \text{ K}\Omega$, $C = 1200 \text{ pF}$, output across C
 - $R_{TH} = 11.2 \text{ K}\Omega$, $C = 1200 \text{ pF}$, output across C
 - $R_{TH} = 12.4 \text{ K}\Omega$, $C = 848 \text{ pF}$, output across R
 - $R_{TH} = 13.2 \text{ K}\Omega$, $C = 1200 \text{ pF}$, output across R



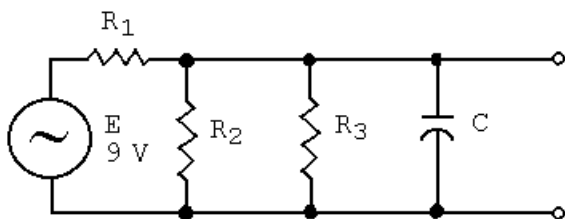16. Using Thevenin's Theorem, what is f_{CO} of an equivalent circuit for a lowpass filter when $R_1 = 5.6 \text{ K}\Omega$, $R_2 = 6.8 \text{ K}\Omega$, $R_3 = 10 \text{ K}\Omega$, and $C = 1200 \text{ pF}$.
- 15.1 KHz
 - 11.7 KHz
 - 56.4 KHz
 - 8.7 KHz
 - 6.2 KHz




17. In the circuit below, $R_1 = 3.3 \text{ K}\Omega$, $R_2 = 5.6 \text{ K}\Omega$, $R_3 = 4.7 \text{ K}\Omega$, and $C = 846 \text{ pF}$. Find V_O and R_N of an equivalent Norton circuit.
- $V_O = 15.0 \text{ V}$, $R_N = 4.7 \text{ K}\Omega$
 - $V_O = 8.5 \text{ V}$, $R_N = 5.86 \text{ K}\Omega$
 - $V_O = 7.5 \text{ V}$, $R_N = 2.56 \text{ K}\Omega$
 - $V_O = 6.5 \text{ V}$, $R_N = 3.3 \text{ K}\Omega$
 - $V_O = 3.9 \text{ V}$, $R_N = 1.4 \text{ K}\Omega$

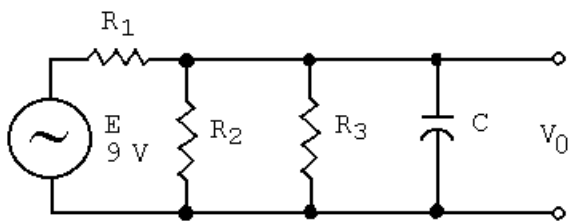

Chapter 1: The Decimal Number System


18. In the circuit below, $R_1 = 3.3 \text{ K}\Omega$, $R_2 = 5.6 \text{ K}\Omega$, $R_3 = 4.7 \text{ K}\Omega$, and $C = 846 \text{ pF}$. What is f_{CO} of an equivalent Norton circuit?

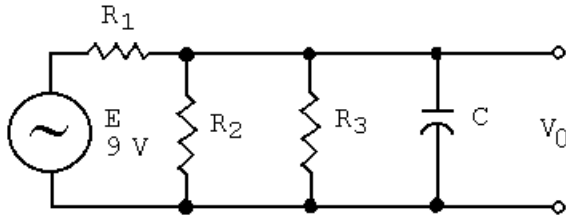- a. 843 KHz
- b. 521 KHz
- c. 470 KHz
- d. 213 KHz
- e. 131 KHz




19. In the circuit below, $R_1 = 3.3 \text{ K}\Omega$, $R_2 = 5.6 \text{ K}\Omega$, $R_3 = 4.7 \text{ K}\Omega$, and $C = 846 \text{ pF}$. What is I_C of an equivalent Norton circuit when $f = f_{CO}$?

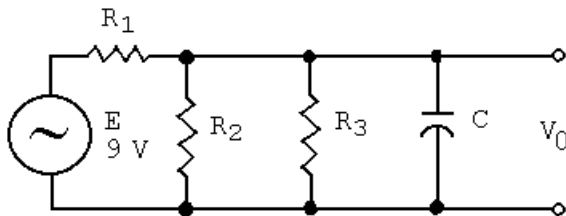- a. 4.5 mA
- b. 10.7 mA
- c. 1.9 mA
- d. 2.7 mA
- e. 1.8 mA




20. In the series resonant circuit below, $V_{in} = 8.0 \text{ V}$ and $R = 10 \text{ K}\Omega$. Find V_O .

- a. 3.3 V
- b. 4.0 V
- c. 5.6 V
- d. 6.6 V
- e. 8.0 V

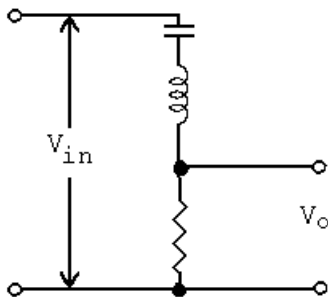


Chapter 1: The Decimal Number System

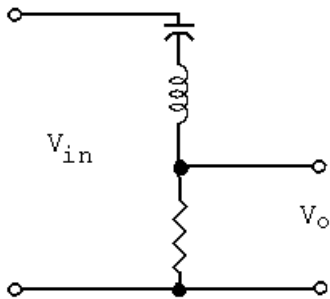21. In the circuit below, $V_{in} = 7 \text{ V}$, $R = 250 \hat{\epsilon}$, $x_C = 1000 \hat{\epsilon}$ at f_r , and $C = 90 \text{ pF}$. Find f_r and Q .
- $f_r = 3.1 \text{ MHz}$, $Q = 10$
 - $f_r = 1.8 \text{ MHz}$, $Q = 4$
 - $f_r = 1.8 \text{ MHz}$, $Q = 1.8$
 - $f_r = 1.2 \text{ MHz}$, $Q = 6$
 - $f_r = 1.0 \text{ MHz}$, $Q = 4$




22. In the circuit below, $V_{in} = 7 \text{ V}$, $R = 250 \hat{\epsilon}$, $x_C = 1000 \hat{\epsilon}$, and $C = 90 \text{ pF}$. Find the bandwidth.
- 310 KHz
 - 1000 KHz
 - 450 KHz
 - 200 KHz
 - 250 KHz

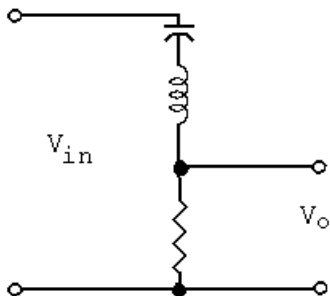

Chapter 1: The Decimal Number System

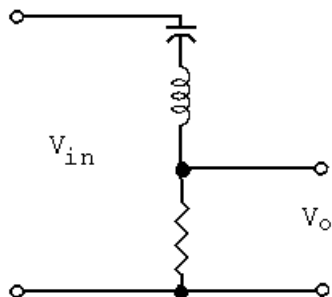
23. In the circuit below, $V_{in} = 7\text{ V}$, $R = 250\ \Omega$, $X_C = 1000\ \Omega$, and $C = 90\text{ pF}$. What are the values of V_O and I at f_1 ?
- $V_O = 4.95\text{ V}$, $I = 19.8\text{ mA}$
 - $V_O = 6.21\text{ V}$, $I = 19.8\text{ mA}$
 - $V_O = 7.00\text{ V}$, $I = 19.8\text{ mA}$
 - $V_O = 5.55\text{ V}$, $I = 22.2\text{ mA}$
 - $V_O = 7.00\text{ V}$, $I = 28.0\text{ mA}$




24. A series resonant circuit is used as a bandpass filter. What is Q if $BW = 3\text{ KHz}$ and $f_1 = 10\text{ KHz}$?
- 3.8
 - 3.3
 - 4.3
 - 6.3
 - 7.6
25. A series resonant circuit has $V_{in} = 9.0\text{ V}$, $Q = 6$, and $f_r = 150\text{ KHz}$. Find BW and V_O at f_1 .
- $BW = 25.0\text{ KHz}$, $V_O = 6.4\text{ V}$
 - $BW = 20.8\text{ KHz}$, $V_O = 9.0\text{ V}$
 - $BW = 29.2\text{ KHz}$, $V_O = 9.0\text{ V}$
 - $BW = 230\text{ KHz}$, $V_O = 6.4\text{ V}$
 - $BW = 277\text{ KHz}$, $V_O = 4.5\text{ V}$
26. A series resonant circuit has $V_{in} = 6.2\text{ V}$, $R = 500\ \Omega$, $f_r = 1.4\text{ kHz}$ and $Q = 15$. Find BW , f_1 , and f_2 .
27. For a low pass filter, $f_{CO} = 15\text{ KHz}$ and $V_{in} = 22\text{ V}$. What is V_O when the input frequency is 6.1 KHz ?
- 20.4 V
 - 11.0 V
 - 15.6 V
 - 31.1 V
 - 22.0 V

Chapter 1: The Decimal Number System

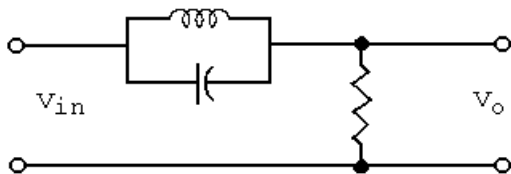28. Find the power dissipated at f_{CO} in a high pass RC filter circuit when $R = 4.7 \text{ K}\Omega$, $C = 500 \text{ pF}$, and $V_{in} = 30 \text{ V}$.
- 58.3 mW
 - 47.0 mW
 - 95.6 mW
 - 116.5 mW
 - 191.5 mW
29. A low pass filter has $R = 18 \text{ K}\Omega$, $C = 0.01 \text{ F}$, and $V_{in} = 10 \text{ V}$. Find V_O and I_C at f_{CO} .
- $I_C = 0.39 \text{ mA}$, $V_O = 10.0 \text{ V}$
 - $I_C = 1.82 \text{ mA}$, $V_O = 5.0 \text{ V}$
 - $I_C = 1.82 \text{ mA}$, $V_O = 7.1 \text{ V}$
 - $I_C = 0.39 \text{ mA}$, $V_O = 7.1 \text{ V}$
 - $I_C = 0.56 \text{ mA}$, $V_O = 10.0 \text{ V}$
30. The circuit shown below:
- Has maximum output at f_r
 - Has minimum output at f_r
 - Is a band reject filter
 - Has a maximum output at f_r and is a band reject filter
 - Has a minimum output at f_r and is a band reject filter




31. Find f_1 in the circuit below when $R_1 = 1 \text{ K}\Omega$, $R_2 = 4 \text{ K}\Omega$, $C_1 = 0.1 \text{ }\mu\text{F}$, $C_2 = 700 \text{ pF}$, and $E = 20 \text{ V}$.
- 1 KHz
 - 318 Hz
 - 4 KHz
 - 8 KHz
 - 16 KHz

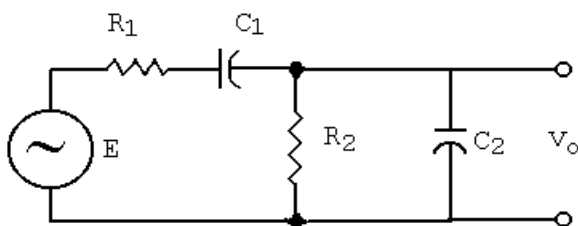


Chapter 1: The Decimal Number System

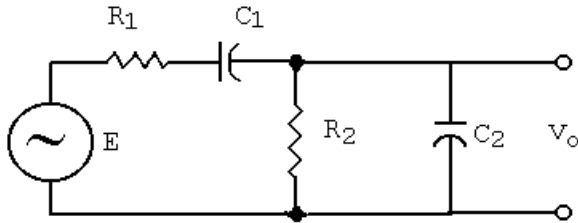32. What is f_2 in the circuit below when $R_1 = 1 \text{ K}\hat{\epsilon}$, $R_2 = 4 \text{ K}\hat{\epsilon}$, $C_1 = 0.1 \text{ }\mu\text{F}$, $C_2 = 700 \text{ pF}$, and $E = 20 \text{ V}$?
- 390 KHz
 - 284 KHz
 - 169 KHz
 - 71 KHz
 - 57 KHz



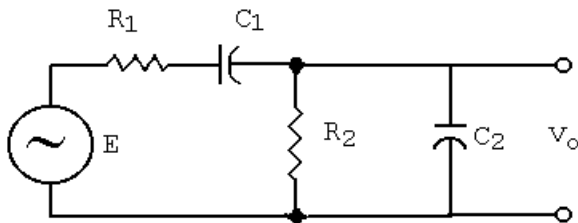33. Find the mid-frequency output voltage in the circuit below when $R_1 = 1 \text{ K}\hat{\epsilon}$, $R_2 = 4 \text{ K}\hat{\epsilon}$, $C_1 = 0.1 \text{ }\mu\text{F}$, $C_2 = 700 \text{ pF}$, and $E = 20 \text{ V}$.
- 4 V
 - 5 V
 - 10 V
 - 16 V
 - 20 V



34. In a bandpass filter, $f_1 = 45 \text{ KHz}$ and $f_2 = 60 \text{ KHz}$. Find f_m .
- 51.0 KHz
 - 52.0 KHz
 - 52.5 KHz
 - 54.2 KHz
 - 55.7 KHz
35. What is f_m for a bandpass filter when $f_1 = 20.0 \text{ MHz}$ and $f_2 = 28.9 \text{ MHz}$?

Chapter 1: The Decimal Number System

36. In a bandpass filter, the lower cut-off frequency, f_r , is best described by:

- a. C_N
 $\ddot{A}\ddot{A}\ddot{A}\ddot{A}$
 $2\hat{a}C_2$
- b. $\acute{U}\ddot{A}\ddot{A}\ddot{A}\ddot{A}\ddot{A}\ddot{A}$
 $\hat{u}f_1 \acute{u} f_2$
- c. 1
 $\ddot{A}\ddot{A}\ddot{A}\ddot{A}\ddot{A}\ddot{A}$
 $2\hat{a}R_{TH}C_1$

37. In a bandpass filter, Q is best described by:

- a. $\acute{U}\ddot{A}\ddot{A}$
 $2\hat{a}\hat{u}LC$
- b. BW
 $\ddot{A}\ddot{A}$
 2
- c. f_r
 $\ddot{A}\ddot{A}$
 BW
- d. $2\hat{a}fL$

1. d
2. b
3. c
4. a
5. $X_C = 4.5 \text{ K}\hat{\Omega}$
 $I = 2.91 \text{ mA}$
 $P = 38.03 \text{ mW}$
 $V_O = 13.08 \text{ V}$
6. $f_{CO} = 267.9 \text{ Hz}$
 $V_{out} = 4.95 \text{ V}$
7. d
8. d
9. b
10. c
11. a
12. b
13. $f_{CO} = 8.84 \text{ KHz}$
14. $X_C = R$
15. b
16. c
17. e
18. e
19. c
20. e
21. b
22. c
23. a
24. a
25. a
26. $BW = 93.3 \text{ Hz}$
 $f_1 = 1.35 \text{ kHz}$
 $f_2 = 1.45 \text{ kHz}$
27. a
28. c
29. d
30. e
31. b
32. b
33. d
34. b
35. $f_m = 24.04 \text{ MHz.}$
36. c
37. c