

Decide whether each of these statements is True (T) or False (F).

When a capacitor of $8\mu\text{F}$, which has been charged to 12 V , is connected across a $1\text{ M}\Omega$ resistor:

1

<https://selldocx.com/products/test-bank-engineering-science-5e-bolton>

(i) The circuit current is proportional to the rate of change of voltage across the capacitor.

(ii) 8 s after the connection, the circuit current has dropped to half its initial value.

(A) (i) T (ii) T

(B) (i) T (ii) F

Answer:

(B) (i) T (ii) F

(C) (i) F (ii) T

(D) (i) F (ii) F

Decide whether each of these statements is True (T) or False (F).

A 24 V supply is connected to a series arrangement of a $100\ \Omega$ resistor and a 50 mH inductor.

2

(i) The initial circuit current is 0.24 A .

(ii) After a time equal to the time constant, the circuit current has decreased to 36.8% of its initial value.

(A) (i) T (ii) T

(B) (i) T (ii) F

Answer:

(A) (i) T (ii) T

(C) (i) F (ii) T

(D) (i) F (ii) F